

Oct. 1980  
\$1.60\*NZ\$1.75



**ELECTRONICS  
TODAY  
INTERNATIONAL**

# FLASH TRIGGER

**Get great action shots using our project**


**Turn & hazard flasher for your vehicle**



**Project Gallileo  
Probe to land on Jupiter**

**HI-FI: Nakamichi 482 cassette deck — superb!  
Accuphase C7 MC headamp — how good?**
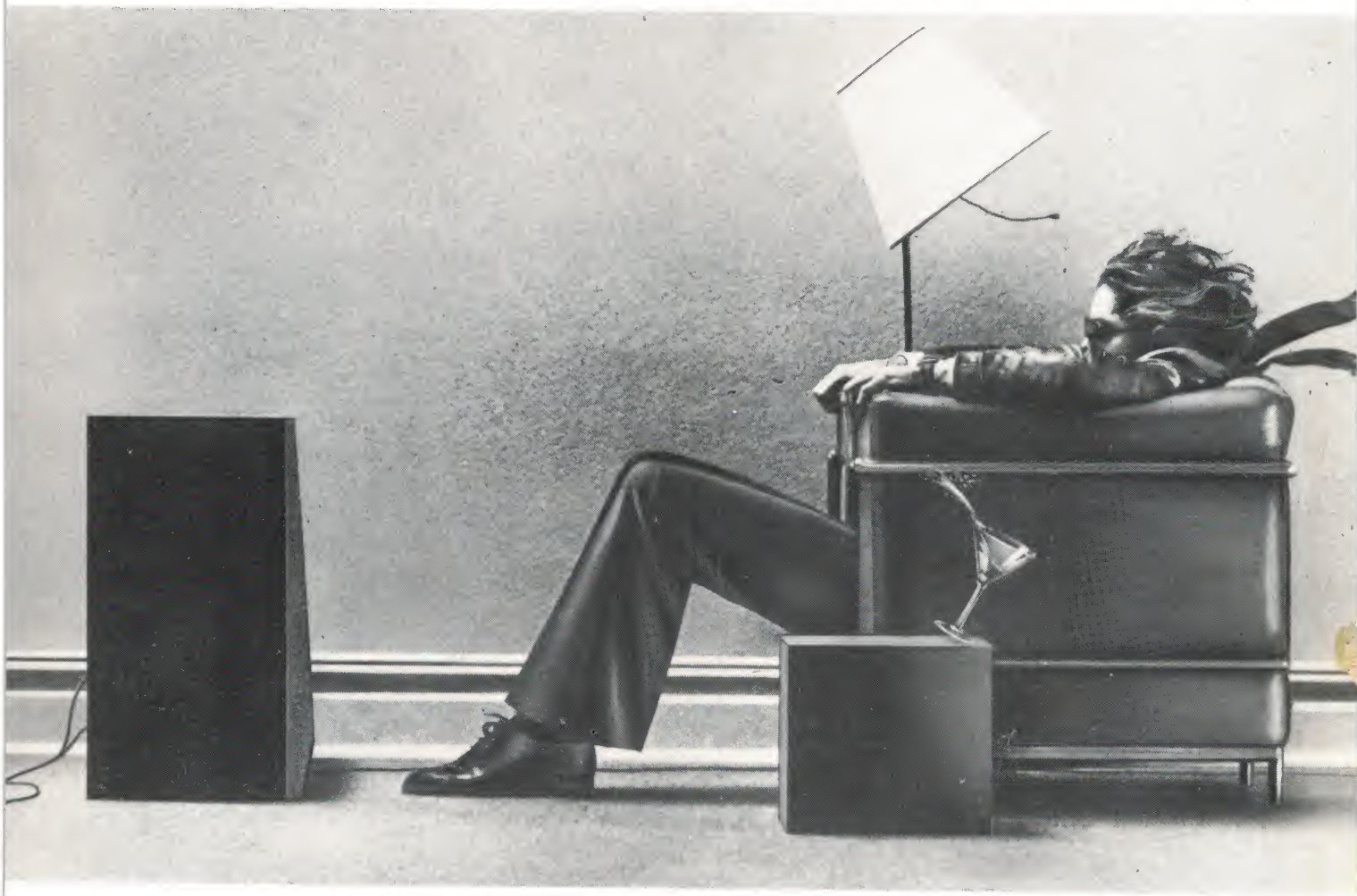
# AFTER 500 PLAYS OUR HIGH FIDELITY TAPE STILL DELIVERS HIGH FIDELITY.



If your old favourites don't sound as good as they used to, the problem could be your recording tape.

Some tapes show their age more than others. And when a tape ages prematurely, the music on it does too.

What can happen is, the oxide particles that are bound onto tape loosen and fall off, taking some of your music with them.

At Maxell, we've developed a binding process that helps to prevent this. When oxide particles are bound onto our tape, they stay put. And so does your music.

So even after a Maxell recording is 500 plays old, you'll swear it's not a play over five.

Distributed by  
**HAGEMEYER**

For further information on Maxell Tapes  
write to Maxell Advisory Service,  
P.O. Box 307, North Ryde, N.S.W. 2113



**maxell**®  
simply excellent

WT191/80



# ELECTRONICS TODAY INTERNATIONAL

Registered for posting as a publication —  
Category B

## QUICK INDEX

### FEATURES:

- 13** Project Galileo — Probe To Land On Jupiter
- 72** Micro Machine Has It All Sewn Up !
- 148** Radio Astronomy's Original Pioneer — Grote Reber
- 140** Special Offer on EMI Reel to Reel Tape
- 91** Floppy Disks — Special Reader Offer

### SOUND SECTION:

- 102** Sound News
- 122** Consumer Electronics Shows — Tale of Two Cities
- 110** Nakamichi 482 Cassette Deck Review
- 135** Accuphase C7 MC Headamp Review
- 98** Dindy High Energy Cassettes — Special Reader Offer

### PROJECT SECTION:

- 21** 568: Sound or Light Operated Flash Trigger
- 30** 147: Electronic Dummy Load
- 40** 327: Turn and Hazard Flasher
- 37** Short Circuits: Measuring Very Low Currents
- 47** Short Circuits: Brilliance Boost For Guitar
- 146** Short Circuits: Audio Noise Limiter
- 51** Lab Notes: The ETI-566 Metal Locator Revisited
- 60** Ideas For Experimenters
- 65** Shoparound
- 113** PC Board Patterns

IN GENERAL, Australia is slow to adopt technology from overseas until it is "fully proven". As a nation, we're technology followers, not leaders. There are a number of examples contrary to this, but the statement is generally true. However, when we do adopt a technology from overseas we do it with a rapidity and enthusiasm that is staggering.

Australia was almost the last Western country to commence monochrome television broadcasting. But, the growth of TV stations and sales of receivers reached 'saturation' level here faster than had been the case in any other country. The same story was repeated with colour television. It's the same in many fields. Take 'personal' computers for example. Sales growth here has proceeded much faster than in the United States. Indeed, some US companies have used Australia to test market new products in this line using consumers here virtually as a 'litmus' indicator.

Bearing this in mind, ponder a moment on what is likely to happen when 'robot' technology arrives here.

First generation robots were expensive and could only perform a limited number of tasks. Cost had to be recouped over quite a long period. Second generation robots are considerably more sophisticated, much less expensive, are more versatile and can pay their way inside a year. First generation robots have taken over unskilled, repetitive tasks whereas second generation robots will replace semi-skilled workers. Many Western nations, including the industrial giants USA and Japan, are making second generation robots *now*.

The Myers Report on the impact of technological change in Australia was released recently and we were interested in what it had to say about robots.

"Australia is slow to use robots", it says.

I think that should be qualified with: "At the moment". The Myers report doesn't explore many aspects of technology in any depth and I think a golden opportunity has been missed — or is it intended to reduce the effects of "future shock" by shying away from serious analysis of the impact of technology?




Roger Harrison  
Editor

## advertisers

Agfa Gevaert Ltd	103
A.P. Products	112
All Electronic Components	36
AWA	115
Ampec Electronics	49
Applied Technology	93
Audio Engineers	120
Aust. Guarantee Corp.	158
Aust. General Electric	56
Audio Reflex Aust.	138
AED	75
Auditec Aust. P/L	128
Audio Kits	118
Andrews Communications	47
Advanced Electronic Systems	62
Bose Aust	119
Barratt Lighting	126
BASF	134
Bell Instruments	142
Belle Lumiere P/L	11
Bib Hi Fi Aust.	130
Bright Star Crystals	147
Box Hill Tech	74
Computerland	20
C.I.S.A.	96
Consolidated Marketing	71
Chadwick Audio	116
Convoy	141
Comp-Soft Micro	92
Christie Rand	92
Computer Country	88
Cletrronics	147
Dicker Data Projects	68
Defense Force Recruiting	159
Dick Smith. 38,39,64,74,76,80,83,90,144,156	
Delsound	11
David East	44
Dynaudio	131
Daneva Control	88
Electronic Calculator Discounts	7
Ellistronics	54
Electro-Voice Aust. P/L	143
Electromedical Engineering	86
Electrocraft	131
Electronic Agencies	58
Emona Enterprises	58
Energy Control	74
Freedman Electronics	128
GFS Electronics	147
Hitachi (Sales) Aust.	100
Hagemeyer	2, 163
Hewlett Packard	61
Indeva	74
John F. Rose	28, 29
Jaycar	139
Kodak	101
Logic Shop	11
Looky Video	74
Magrath's P/L	18
Maruni Corp.	6
Micro-80	81
Maurice Chapman Group	133
Mensa Computers	84
McGill's Newsagency	132
Micro Pro Design	92
National Panasonic A/Asia	164
National Panasonic	109
Northpoint Hi Fi	136
Omni Computers	12
Parameters P/L	27
Pre Pak	46
Philips	124, 153
Plessey Components	44
Rod Irving	48, 66, 67
Radio Parts	58
Radio Despatch	62
Sansul	105
Sony	106
Stuart Alexander	108
Seeforth	34
S.M. Electronics	69, 97
S.I. Microcomputers	70
Systems Automation	44, 45
Spectrum Lighting	121
Speedy Communications	155
Sevien Lighting	132
Software Source	74
Tasman Electronics	61
VSI Electronics	50, 59
Vicom International	35
Warburton Frankl.	150
Woodland Audio	118
World Imports	118



**ELECTRONICS  
TODAY  
INTERNATIONAL**

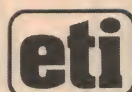

**ELECTRONICS  
TODAY  
INTERNATIONAL**

### FLASH TRIGGER

Get great action shots using our project

Turn & hazard flasher for your vehicle



Project Galileo  
Probe to land on Jupiter

HI-FI: Nakamichi 482 cassette deck—superb!  
Accuphase C7 MC headamp—how good?

### COVER

An artist's impression of the Project Galileo probe as it begins its descent into the atmosphere of Jupiter. Story on page 13.

## features



### PROJECT GALILEO

13

Early in 1982, NASA will launch a mission to investigate the planet Jupiter at close range and over an extended period.

### JANOME MEMORY 7 SEWING MACHINE

72

This microprocessor-controlled sewing machine makes embroidery child's play.

### GROTE REBER — PIONEER OF RADIO ASTRONOMY

148

Forty years ago, Grote Reber founded the science of radio astronomy. Today he still works with the antenna system he built many years ago in Tasmania.

## projects



### 568: SOUND OR LIGHT OPERATED FLASH TRIGGER

21

Some spectacular and intriguing events last only a fraction of a second. Our photo flash trigger helps you catch the action on film by triggering the flash at the right instant.

## news

### NEWS DIGEST

8

Communications in Arnhem Land; Satcom III post-mortem; Zinc chlorine batteries; VCR cleaner.

### PRINTOUT

77

Hand held computers; Z8000 support hardware; Speech recognition for TRS 80; HP85 disk drives; New TI speech synthesis chip etc.

### COMMUNICATIONS NEWS

145

Heard Island DX-pedition plans well advanced, etc.

### SHORTWAVE LOGGINGS

152

Radio Australia's Darwin transmitter to be revived; New Ecuador service; Iceland now possible.



**147: ELECTRONIC DUMMY LOAD** 30  
This general purpose dc load is convenient for testing power supplies etc. and incorporates multiple protection circuits.

**327: VEHICLE TURN AND HAZARD INDICATOR** 40  
Stable, reliable and powerful, this electronic flasher unit easily outperforms the standard electro-mechanical devices.

**THE ETI-566 METAL DETECTOR REVISITED** 51  
More about the metal detector we featured as a project in the April 1980 issue — alternative construction arrangements, coil details, etc.

**SHOPAROUND** 65

## sound

**SOUND NEWS** 102  
TEAC offer dbx; Single chip FM receiver; Distortion often goes unnoticed.



**CONSUMER ELECTRONICS SHOWS — A TALE OF TWO CITIES** 122  
This year's electronics shows in Perth and Sydney were both huge successes. Dennis Lingane reports on both and on the not-so-friendly rivalry between them.



**NAKAMICHI 482 CASSETTE RECORDER** 110  
The industry pacemakers continue their pursuit of perfection with this superb machine.

**ACCUPHASE C7 MOVING COIL CARTRIDGE HEAD AMPLIFIER** 135  
If you're thinking of upgrading to a moving coil cartridge and you don't want to replace your amplifier a head amp like this is just what you need.

**DINDY CASSETTE OFFER** 98  
High energy tapes at low, low prices.

**EMI RECORDING TAPE OFFER** 140  
Top reel to reel tapes at a discount.

## general

**SHORT CIRCUITS** 37  
Measuring very low currents  
Brilliance boost for guitar 47  
Noise limiter 146

**IDEAS FOR EXPERIMENTERS** 60  
SCR oscillator; Slave flash; Automatic turntable cutoff etc.

**IONOSPHERIC PREDICTIONS** 154

**LETTERS** 69

**FLOPPY DISK OFFER** 91

**MAIL ORDER BOOKS FROM ETI** 94  
Beginners' books, data books, circuit books etc.

**PC BOARDS** 113

**MINI MART** 157

**KITS FOR PROJECTS** 160

**ETI SERVICES** 161

**DREGS** 162

## next month



### SERIES 3000 'MINI' STEREO AMP

Since the success of the Series 4000 stereo amplifier (May, June, July issues, 1979) we've had an increasing number of requests for a 'compact' unit. This one should fill the bill — but we've not cut corners. It features low noise and distortion, delivers around 20 watts output, is simple to build and should cost around \$80!



### PINBALL WIZARDRY

Until quite recently, that seductive demon the pinball machine rattled and clattered its way through a five year life span totally unaided by modern technology. But . . . now the micro has taken over! Our correspondent takes you inside a modern monster.



### ELECTRONIC THERMOMETER

This simple project is suited to measuring air temperature over the range from  $-10^{\circ}\text{C}$  to  $+40^{\circ}\text{C}$  or  $-10^{\circ}\text{C}$  to  $+90^{\circ}\text{C}$  according to your fancy. It's great as an electronic thermometer or it can be used to check air conditioners, heating systems etc.

### BUILD A RADIO DIRECTION FINDER

This article describes how to make a direction finding antenna and how to use it with the popular Realistic DX160 receiver.

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.

**THE INCREDIBLE STUDIO 1000**



*N.B. MARUNI microphones take some beating too!!!*

**MARUNI**

SUPERLATIVE HEADPHONES AND MICROPHONES

THE **MARUNI** CORPORATION

297 WILLIAMSTOWN ROAD, PORT MELBOURNE, 3207 • TELEPHONE, 645 2079 • TELEX 32571

## EVERYBODY USES DIABLO PRINTERS — WHY NOT GO THE WHOLE WAY WITH A DIABLO COMPUTER SYSTEM?

Full integrated software — customised for each user,  
installed and fully supported.

Please contact us with your requirements and it will be  
our pleasure to submit a detailed proposal.



XEROX DIABLO 3200




XEROX  
DIABLO 3000

8" DISKS

## Hewlett-Packard HP's ONLY POST FREE!

- HP41C — over 400 steps, up to 64 data registers (continuous) \$374 (\$336)  
The 41C has 4 interface ports for:
- Card Reader \$273 (\$245)
- Printer/Plotter \$489 (\$439)
- Extra memory modules each with capacity of basic 41C \$56.40 (\$49.10)
- Plus 16 application pacs (plug-in modules) \$56.40 (\$49.10) each.
- And 24 solution books \$15.70 (\$13.60) each.
- Also HP67/97 software compatible.

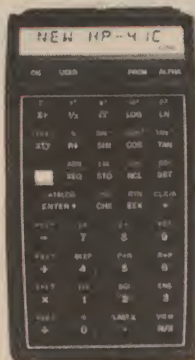

HP41C

- HP31E Scientific \$66.00 (\$59.00)
- HP32E Advanced Scientific Statistical \$91.50 (\$82.00)
- HP33E Advanced Scientific Programmable, 49 steps \$117 (\$105)
- HP29C Scientific Programmable 98 steps, continuous \$202.50 (\$182)
- HP97 Card Programmable, printing 224 steps \$913 (\$820)
- HP37E Business \$98 (\$88)
- HP38E Financial \$155 (\$139)
- HP92A "The Investor" Financial Printing \$530 (\$476)

### CONTINUOUS MEMORY

- HP34C Scientific Programmable, 210 steps \$192.50 (\$173)
- HP33C Scientific Programmable, 49 steps \$155 (\$139)

Price in brackets excluding sales tax.

## SUPERBRAIN™ BUSINESS SYSTEMS

Fully expandable — fixed disk,  
multi-user, terminals, printer  
options: IDS 440, TC810, Diablo  
Daisywheel.



### DEVELOPMENT SOFTWARE

Basic interpreter  
Basic compiler  
Cobol  
Fortran IV  
Data Base/query  
Pascal  
TTY communications  
IBM 2780/3780.

### BUSINESS SOFTWARE

Debtors  
Creditors  
General Ledger  
Invoicing, stock and order entry  
Wages and payroll  
Word processing  
Direct mail

## The CBM™ Computer Business System

3023 Friction Feed

### Tractor Feed Printer



3001-16/32



Authorised Dealer

### Dual Drive Floppy Disk



3040

Write or phone today for your  
coloured brochure and our  
unbeatable prices.

## FANTASTIC NEW PERIPHERALS COMING!

Continuous memory, larger  
monitors, colour controller, disk  
systems to 30 megabytes,  
low-cost intelligent modems, etc.  
Your CBM or PET computer will  
soon be able to talk, listen and  
draw.

## TEXAS PROGRAMMABLE SYSTEMS

### GREATEST PACKAGE DEAL EVER!!



TI59 and PC100C  
PRINTER

\$510 (\$450)

- TI58C \$149 (\$132)
- TI59 \$299.90 (\$265)
- PC100C \$237 (\$210)
- TI55 \$65.90 (\$58.50)
- Modules 58C/59 \$34.50 (\$30.50)
- Pakettes 58C/59 \$9.00 (\$8.00)
- 3 Rolls Therm Paper \$12.00 (\$10.50)
- 40 Mag Cards \$15.00 (\$13.50)

### A.P.F. LCD

#### School Calculators

- M5602, 40 functions \$23.00 (\$20.50)
- M8602, 60 functions \$29.30 (\$26.00)

Pack and post — all LCD models  
\$1.50 anywhere in Australia (except  
Caslo fx502p).  
Otherwise \$4.00 for registered post  
in NSW. \$5.50 elsewhere.

Copy and complete

Please debit my Bankcard \$ .....

No. .... Expiry Date. ....

Signature .....

Name .....

Address .....

## CALCULATOR AND COMPUTER DISTRIBUTORS

INCORPORATING EXCLUSIVE CALCULATORS & COMPUTERS  
and ELECTRONIC CALCULATOR DISCOUNTS

PHONE (02) 624-8849

MAIL ENQUIRIES:

PO BOX 106, BAULKHAM HILLS  
2153

## Keeping in touch in Kakadu

Ingenious frequency planning and the use of solar power are the key features of the communications system developed by Philips for the Kakadu National Park in the Northern Territory.

**The newly created park covers some 6000 square kilometres of tropical rain-forest in Arnhem Land. It is patrolled by rangers in a fleet of 24 vehicles, who need to be in constant radio contact with their bases, even when they are in the remotest reaches of the park.**

The rugged and inaccessible nature of the country, together with the hot and humid climate, meant that equipment with unusually high reliability and environmental stability had to be specified. Nor could the installations be allowed to detract from the outstanding beauty of the area, which in addition to its natural splendours is also the site of many sacred aboriginal burial grounds and rock paintings.


The complete communications system will cost about \$250 000 and will consist entirely of equipment designed and manufactured in Australia. It is expected to be finished in about two years and will be conducted in two phases. The first phase will involve the installation of a central control station at Jabiru, two base stations at the

existing campsites of Nourlangi Rock and East Alligator and two solar powered repeater stations (out of an eventual total of five) on mountain top sites.

Helicopter survey of the park has enabled the careful siting of equipment in rock crevices and other natural hiding places so as to leave the environment as undisturbed as possible. In the same spirit, the use of solar energy solves the power supply problems and keeps running costs down in the manner most consistent with the natural concept of the park.

Patrol vehicles will be fitted with specially ruggedised and weathersealed transceiving equipment designed to stand up to the harshest of driving conditions. In addition, each vehicle will carry a portable transceiver for use on foot patrols.

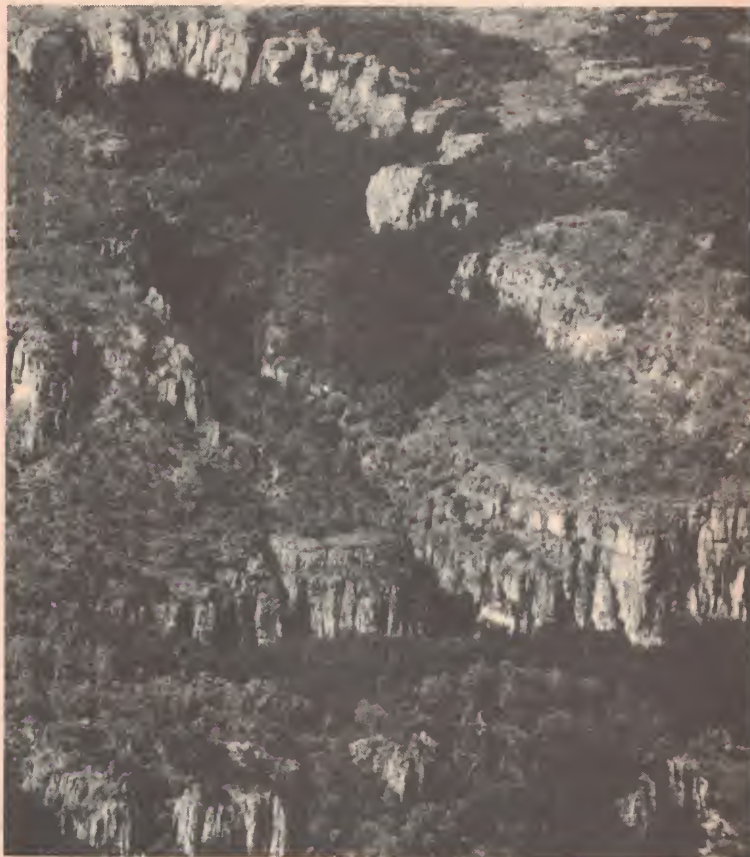So that radio contact can be maintained at all times, even on foot patrols, each vehicle's transceiver can be switched to a repeater mode when the driver leaves the vehicle. Philips' new approach to frequency planning, for which a patent is pending, means that this kind of



relaying can be achieved without the need to equip each vehicle with two separate radios and antennas. The consequent savings in installation costs and improvement in operating efficiency played a large part in winning the contract for Philips.

Another unique feature of the communications system is the automatic prevention of interference between two vehicles operating in close proximity to each other — a provision that could be very important in emergency situations.



## ... and in Brunei

**In the equally wild and remote jungle country of Brunei, Philips are to supply solar powered telephone equipment.**

The company will provide thirty single channel remote subscriber radio-telephone systems to extend the telephone service to some of the most inaccessible regions of the Sultanate. Solar arrays will supply the power in areas not covered by the national electricity grid.

And the Royal Brunei Police

Force have recently taken delivery of more than 100 two-way VHF radios for use in fixed and mobile operational situations. The model FM828 radios are the same that will be used in the Arnhem Land patrol vehicles (see story above) and for the same reasons. Few places in the world are as hot and steamy as the Brunei jungles.

## Satcom III — where are you ?

**The mysterious disappearance of RCA's US\$48 million Satcom III communications satellite late last year caused quite a stir — but they think they know what happened, now.**

A recently concluded study suggested two possibilities. The most likely scenario is as follows: as the apogee kick motor starts (to boost the satellite from the transfer orbit to geostationary orbit), the exhaust cone breaks, letting the hot gases melt the rear portion of the satellite resulting in loss of the communications equipment.

The second scenario suggests that the kick motor ignites normally but the solar arrays deploy prematurely. Owing to the satellite's spinning and kick motor thrust, the arrays suffer rapid structural damage, leading to total failure of the on-board power system.

All communications from the satellite ceased 14.5 seconds into the 28-second kick motor

burn. At the same time, exhaust temperature sensors indicated overheating. It is this that led the review board to prefer the first scenario.

Apart from the cost of the launch and satellite hardware, RCA stand to lose a further US\$20 million in revenue. Insurance cover was for a total of US\$77 million so it seems they won't be out of pocket.

To fill the gap, RCA has leased 11 pre-emptable transponders on AT&T's Comstar D-2 satellite. Instead of charging customers the US\$70 000 cost for the Comstar D-2 transponders, RCA will only charge the US\$40 000 per transponder it was to charge for Satcom III usage. RCA will launch a replacement satellite next June.

## Business radio saves fuel

**The use of two-way business radio is saving the community at least 225 million litres of motor fuel a year and would be much greater with more encouragement of mobile radio by the authorities.**

So says the first issue of "ABIRA Voice", newsletter of the recently formed Australian Business & Industrial Radio Association (ABIRA), representing business, industrial and professional users of mobile two-way radio.

ABIRA Voice said research among radio manufacturers and suppliers had shown that four vehicles fitted with two-way radio do the work of five without. Applied to the existing estimated 180,000 two-way radios in service in Australia, this is saving in total at least 225 million litres of fuel, valued around \$70m, a year.

The newsletter noted that the Federal Government had recently reduced licence fees for two-way radio users, but said

the reductions did not go far enough.

ABIRA has asked the Minister for Post and Telecommunications, Mr A.A. Staley, to change the licence fee structure to widen the differential between small and large users next financial year.

This would promote efficiency, particularly among small business, and further reduce fuel consumption.

The newsletter added that to save administrative costs, licence fees should be payable five-yearly instead of yearly, and licences should expire on set quarterly dates.

For further information about ABIRA, contact Terry Winters on (03) 561-3555, or Rick Melgaard on (02) 428-5197.

## Briefs

**Microwave room heating could save fuel by only warming people, not objects, suggests R.V. Pound of Harvard Uni. The idea is to use a wavelength of 30 mm, which would only penetrate about 1 mm into a person's skin, avoiding heat damage to internal organs. But there are a few drawbacks. Wood and paper would absorb the waves, but metal objects would not, so on freezing cold days anything metallic would be untouchable. Pot plants and cut flowers would probably get very hot and bothered (because their leaves and petals are thin) and in any case prolonged exposure to microwave radiation is not now thought to be very healthy for human beings.**

Funeral parlours in California are now selling the Memorial Audio Reproduction System, a solar powered tape recorder that fits snugly into your tombstone and will repeat a message to your descendants for many generations to come. The makers are planning to follow this up with a solar powered tombstone-mounted colour TV. Weird, huh?

**Toronto will be the venue for the 1981 International Electrical, Electronics Conference and Exposition, which will be held from October 5th to 7th. This will be the 25th anniversary of the biennial conference, which is an international scientific marketplace for all aspects of electronics, with particular emphasis on telecommunications. Over a hundred technical papers will be presented and a call for these will be issued shortly. Enquiries to Southex Exhibitions, 1450 Don Mills, Ontario, Canada M3B 2X7.**

Intel have issued a seven page application note detailing how their 5 volt EPROMs can be used with microcomputer systems. The note explains EPROM pinout evolution and philosophy, leading on to a

discussion of system architecture. Particular emphasis is laid on eliminating system bus contentions and on the microprocessor/program store memory interface. Copies of application note AP-72 can be had free from A.J.F. Systems and Components, 310 Queen St, Melbourne 3000.

**The United States is aiming to protect its lead in the semiconductor industry against increasing foreign competition. The Department of Commerce proposes a co-operative effort to concentrate research and development in university based 'centres of excellence' or in a central national lab. The US semi-conductor industry apparently feels that taxation policies, over-stringent application of environmental restrictions and interference by government and other institutions are hampering its progress. It sees the removal of these impediments as a priority for any semiconductor development programme.**

Meanwhile, at least one communist country is beginning to rival the Americans in the quality of their integrated circuits (thereby threatening the balance of power, eroding US complacency, precipitating World War Three, etc!). Officials of the US National Bureau of Standards, who visited IC factories in Czechoslovakia, reported that the quality of the devices produced was apparently equal to that of Western devices, although the scale of production and the level of automation are not yet equal to US producers.

**A new power MOSFET has been developed by Siemens. Known as SIPMOS, it's made by an ion implantation process that's said to give higher production yields and a better control of channel widths. SIPMOS also has a low threshold voltage — only 2 V.**

## Zinc/chlorine batteries are current favourites

**Institutions in the United States are looking very favourably on the new zinc/chlorine storage batteries being developed by Gulf and Western.**

The Department of Energy last year gave US\$11.5 million to build 100 of the batteries for tests in power stations, where it is hoped they can be used to store excess energy generated at off-peak times. Now the Electric Power Research Institute has just donated another US\$14 million to Gulf and Western's research programme on top of the US\$13 million it already has invested.

Electric road vehicles are likely to prove the most lucrative application of the new batteries. A prototype has been used to

drive a small car a distance of 240 kilometres at 90 km/hour, which is a considerable improvement on the 160 km that can be achieved in the same car by a nickel/zinc battery and much better than the 80 km range of advanced lead-acid batteries. Zinc/chlorine batteries wear better too—they last six or seven times as long as other types.

Despite complex engineering problems which have yet to be completely mastered, Gulf and Western's President predicts that electric car engines will be selling for US\$3000 by 1984.



## Audio auto-analyser

**Microprocessor control allows a new audio analyser from Hewlett-Packard to be set with a single keystroke to measure frequency response over the entire audio spectrum.**

The 8903A combines a low distortion audio source and an analyser in one instrument which measures dc volts, ac volts, distortion, signal-to-noise, signal-to-noise-and-distortion (SINAD), hum and noise, gain and power output.

The audio source section gives 0.6 mV to 6V open circuit from 20 Hz to 100 kHz and can be set for log sweeps as well as incremental changes. Distortion can be measured to around 0.003% (-90dB) in the audio range and ac level accuracy is specified at  $\pm 0.5\%$ .

Digital displays resolve frequency to five digits and

amplitudes to four. Amplitudes can be displayed in dB or percentage terms relative to a previous measurement or a keyed-in value.

The 8903A source can also be used in transceiver testing to modulate the test transmitter while the analyser section of the same instrument measures the demodulated output of a companion 8901A Modulation Analyser for distortion and frequency response.

More details from Hewlett-Packard (Australia) Pty. Ltd., 31-41 Joseph St, Blackburn, Vic 3130. Phone (03) 89-6351.



## Unique VCR cleaner

**A unique video recorder cleaning cassette has been produced by Allsop, makers of the famous 'Allsop 3' audio cassette deck cleaning cassette.**

The device incorporates a chamois cleaning tape inside a standard VCR cassette assembly and, like the Allsop audio cleaning tape, the whole cleaning action is driven by the machine itself.

The Allsop 3 Video Cassette Recorder Cleaner is placed in the machine and the play button operated. The machine's mechanism then draws the cleaning chamois tape out of the cassette and drives it around the video and audio heads, removing any foreign particles but not abrading the heads, according to Allsop. A judiciously located felt pad presses on the capstan and pinch roller and cleans these two components as well. The cassette shuts off the recorder after the cleaning action is completed. A specially-formulated cleaning fluid is used on the chamois and felt pad.

We had an associate try out one of these units on a VCR that had not been previously cleaned. The number of drop-outs was reduced by a factor of four after the first use and reduced to negligible proportions following two further cleanings. Allsop recommend three 'playings' for a thorough clean.

The assembly in the cassette containing the chamois and felt pad is replaceable.

The Allsop 3 Video Cassette Recorder Cleaner, model 60800, suits VHS machines and is available at reputable video outlets for around \$35. The replacement cleaning cartridge, model 61800, costs around \$10.

More information from the sole importer, Communications Power Inc., P.O. Box 246, Double Bay NSW 2028. (02)357-2022.

# Now you can breathe easier!

## NEGATIVE IONS.

For more than 20 years Medical research has been demonstrating the amazing benefits of negative air ions. They clear the air of smoke and dust, reduce fatigue and increase alertness, reduce up to 75% of airborne bacteria and much more.

In natural surroundings they are abundant but in stale or polluted air they quickly become depleted. Now an inexpensive device to alleviate this condition is being manufactured in Australia.

The "Aironic" negative ion generator electrically produces safe, natural levels of negative ions. Stale odours and smoke are removed from the room and the air becomes fresh and invigorating once more.



**Aironic**  
NEGATIVE ION GENERATOR

See your health food shop or natural therapist or post coupon to:

## BELLE LUMIERE PTY. LTD.

SYDNEY: P.O. BOX 216, Lane Cove, NSW. 2066. Tel: (02) 428 1334  
MELBOURNE: 5/47 Fitzroy St., St. Kilda. Vic. 3182. Tel: (03) 534 7493  
BRISBANE: P.O. BOX 184, Toowong. Qld. 4066. Tel: (07) 371 3645

- ☐ Home/office model. \$85 each.  
☐ Deluxe wood casing. \$95 each.

Add \$2.00 for postage and packing.  
I enclose cheque/money order for .....

NAME .....

ADDRESS .....

POSTCODE .....

Bankcard Mail Orders Welcome.

Expiry Date .....

Signature .....

☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐

Send SAE for further literature on negative ions.

## DEL SOUND — PTY. LTD — BRISBANE

### NEW PRODUCTS

#### TOGGLE SWITCHES

1. 250V 10A
  2. AC 1500V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- R6-7A S.P.D.T. 0.99 each  
R6-7D D.P.S.T. 1.49 each  
R6-7E D.P.D.T. 1.76 each  
R6-7F D.P.D.T. 3 position 1.82 each



#### TOGGLE AND LEVER SWITCHES

1. 120V 5A & 240V 3A
  2. AC 1000V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- R6-8B S.P.D.T. 0.88 each  
R6-8C S.P.D.T. 3 position 1.09 each  
R6-8E D.P.D.T. 0.99 each  
R6-8F D.P.D.T. 3 position 1.09 each



#### TOGGLE AND LEVER SWITCHES

1. 120V 5A & 240V 3A
  2. AC 1000V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- R6-8H S.P.D.T. 0.76 each  
R6-8I D.P.D.T. 0.82 each

#### PUSHBUTTON SWITCHES

1. 250V 3A
  2. AC 1500V
  3. More than 100M  $\Omega$  at DC 500V
  4. Less than 50m  $\Omega$
  5. More than 20,000 times
- A-push "ON" and push "OFF"  
B-push "ON"  
R7-3A Push on push off. 0.80 each  
R7-3B Push on 0.63 each



#### A TYPE FUSE HOLDER

- 6.4  $\phi$  x 30mm  
Net weight: 12.5gr.  
R1-2A 3AG type 0.40 each  
R1-2App 3AG approved 1.50 each



#### PLUGS, JACKS AND CLIPS

- Diamond Type Colour Lamp  
Net Weight: 16.4gr.  
M, E, S, Multi facet bezel red 0.45 each



#### I.C. TEST CLIPS

- Gold plated, 3 models  
14-16, 26-28 and 40 way  
from \$6.00 each



#### LED VU METER

- Power supply 12-15V DC  
Current 40 mA  
Frequency response 20Hz to 100 KHz  
Sensitivity 770mV = 0dB  
Rise & Decay Adjust  
1mFD to 10mFD \$24.00 each

Above shows only part of our huge range, customers special requirements our speciality.

All prices plus tax. Prices and availability subject to deliveries, stocks and fluctuations.

For further information, local agents and wholesale prices, write to the Australian Importers:

## DELSOUND PTY. LTD.

1 Wickham Tce. (Cnr. Wharf St.)  
Brisbane. Phone 229-6155.  
Wholesale and Retail suppliers of  
Electronic Hardware and  
Components.

## \$ THE LOGIC SHOP PTY. LTD.

DISCOUNT SHOPPING for your professional Microcomputer and terminal requirements.



### COMPUCOLOR II

ex stock

Features: • up to 32K user RAM  
• Eight colour display • 32 lines of 64 characters • 5" Mini disk drive • 40 tracks, 48 TPI



### TELEVIDEO TVI 912B DISPLAY UNIT

ex stock

Features: • 24 lines at 80 characters per line • Transmission rates 75 — 19,200 Bd. • 96 character ASCII upper and lower case • 12 inch monitor.



### MICROLINE 80 PRINTER

ex stock

Features: • 80 char/sec • 80 and 132 char/line • 9 x 7 dot matrix • Character or graphics printing • Plug compatible to TRS-80. ® Rgd. Tm. Tandy Corp.

### SPECIAL

5 1/4 Diskettes — \$3.95 ea. Inc. tax.

## \$ THE LOGIC SHOP PTY. LTD.

212 High St., PRAHRAN, VIC. 3181. Tel: 51-1950.  
91 Regent St, CHIPPENDALE NSW. 2008  
Tel: 699-4910

TRS-80 ® is a registered trade mark of Tandy Electronics.

# Omni COMPUTER SHOP

## Omni Business Computer System

The Omni small business computer system has been designed to incorporate the most advanced hardware available in the eight bit micro computer field.

The computer consists of 4MHz processor, 64K bytes of 200ns RAM, ROM resident diagnostics and monitor, is capable of running up to four user terminals, each with it's own 4MHz processor and 64K bytes of RAM. The system comes with up to 2MB's on line.

**TOTAL SYSTEM WITH DATAROYAL PRINTER AND SANYO CRX VDU,**

**COSTS FROM \$11,500.00 plus 15% sales tax.**



### **SANYO CRX 1000 VDU**

- High-resolution display of up to 1920 (8 x 12 dot) characters, 80 per line in 24 lines, on a 12" screen.
- ASCII keyboard with typewriter-style shift and shift-lock keys for capital letters and block-type arrangement for easy operation.
- Teletypewriter key format for alphanumerics, separate numeric pad.
- External interface employs EIA RS-232C interface and 20mA current loop.
- Hard copy interface on RS-232C AUX port output enables print-out of data from host computer.

Control system Microprocessor control

Display screen 12" diagonal, non-glare display P1 Green. 8 x 12 dot Matrix (numerical character and alphabetic character with lower-case letters in 5x9 dot matrix display and other special characters in 8x12 dot matrix display).

Capacity 80 characters x 24 lines

Display editing Insert character, delete character, delete sentence, insert sentence, erase sentence.

Cursor editing Left, right, up, down, home direct addressing



**\$1495** plus 15 percent s/t


Interface Either RS-232C or 20mA current loop

Transmission Half or full duplex  
Visual Reverse video, underline and blinking (Centronics interface optional).
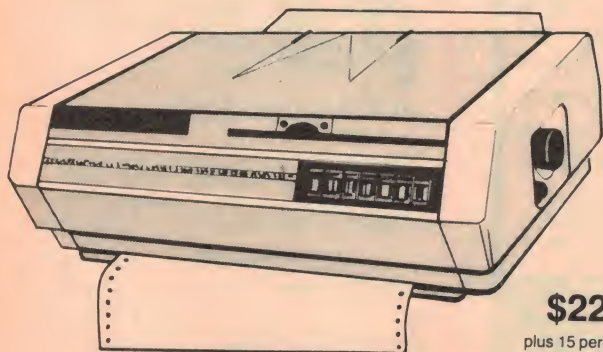
### **DATAROYAL 5000**

Paper Up to 6 ply  
Ribbon Cartridge type  
Format 9 x 9 dot matrix, lower case descenders and underline capacity

Printer Rate 150 CPS, bidirectional  
Interface Parallel (8 bit)  
(Other printers optional, including daisy wheel)



**\$2250**

plus 15 percent s/t

All prices F.O.B. North Sydney, are subject to change without notice. S.T.C. service contract available.

**1st Floor, 127 Walker Street, North Sydney, NSW, 2060. Tel (02) 922-5948.**

# Project Galileo

Brian Dance

In our January issue, Brian Dance reported on Voyager 2's visit to Jupiter. Now he looks ahead to the next US mission to the giant planet.

JUPITER has fascinated men ever since Galileo first observed four of its moons in 1610. This huge gaseous planet has 50 times the mass of all the other planets put together and probably has a composition similar to that of the sun.

Two Voyager missions flew past Jupiter within a few months of each other last year and greatly extended our knowledge of the region. They discovered the planet's rings and the peculiar weather patterns around the great red spot, and revealed that the satellite Io is the scene of intense volcanic activity.


Scientists are now eager to gather more information at closer range and over a longer period, so NASA has planned a spacecraft which will orbit Jupiter and return data more or less continuously for at least 20 months. In

addition, a probe carried with this spacecraft will be released before the craft reaches Jupiter and sink deep into the atmosphere to gather and transmit data.

This project was originally known as the Jupiter Orbiter Probe, but it has


since been renamed Project Galileo after the famous astronomer. According to current plans, the Galileo spacecraft will be launched in January 1982 and arrive in the vicinity of Jupiter in July 1985. The project will be managed by the Jet Propulsion Laboratory of California and NASA's Ames Research Center will be responsible for the development of the probe. Data from the spacecraft will be received by the huge Deep Space Network antennae at Goldstone (California), Tidbinbilla (near Canberra) and Madrid in Spain.

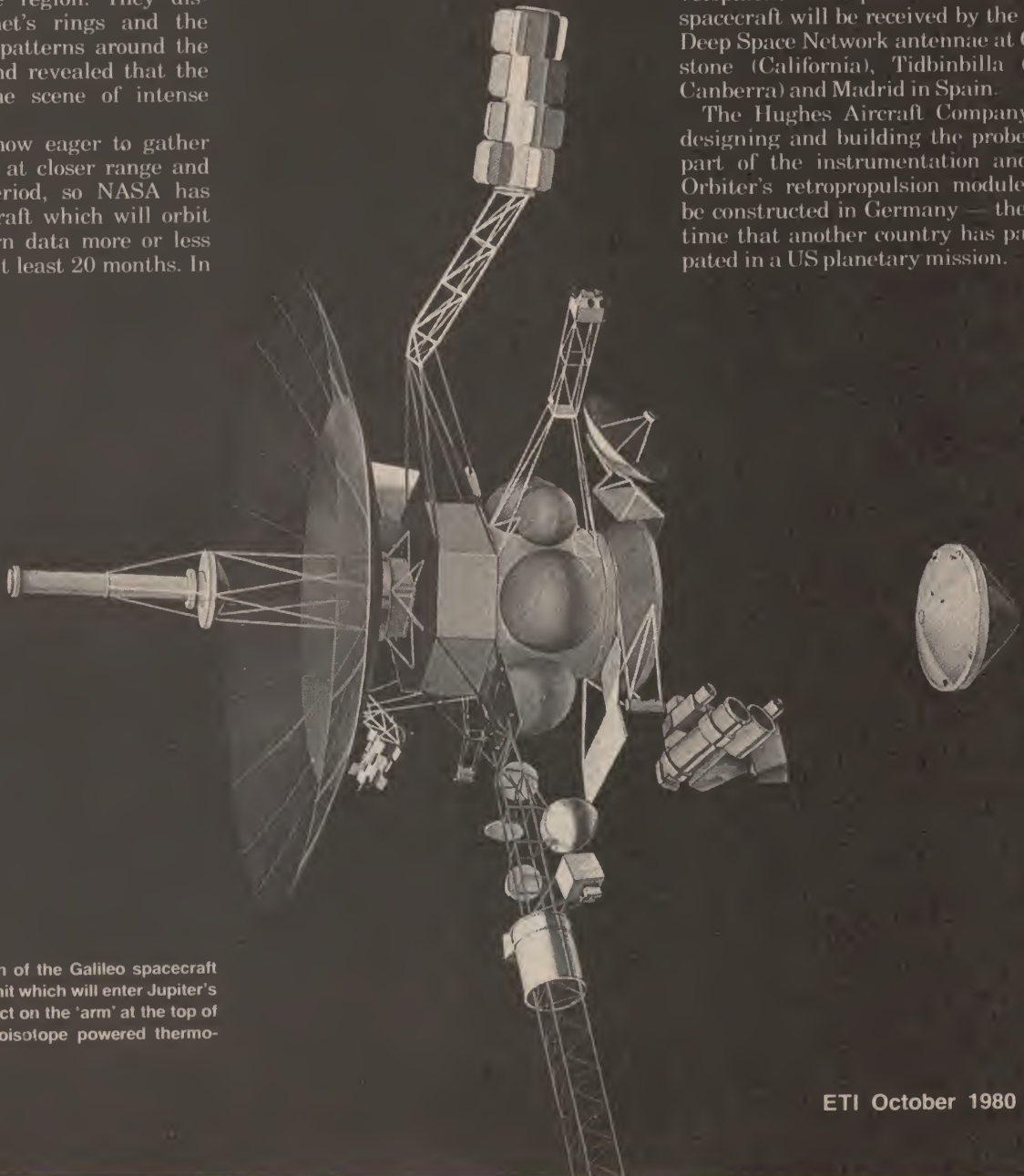The Hughes Aircraft Company are designing and building the probe, but part of the instrumentation and the Orbiter's retropropulsion module will be constructed in Germany — the first time that another country has participated in a US planetary mission. ►



An artist's impression of the Galileo spacecraft releasing the Probe unit which will enter Jupiter's atmosphere. The object on the 'arm' at the top of the picture is a radioisotope powered thermoelectric generator.

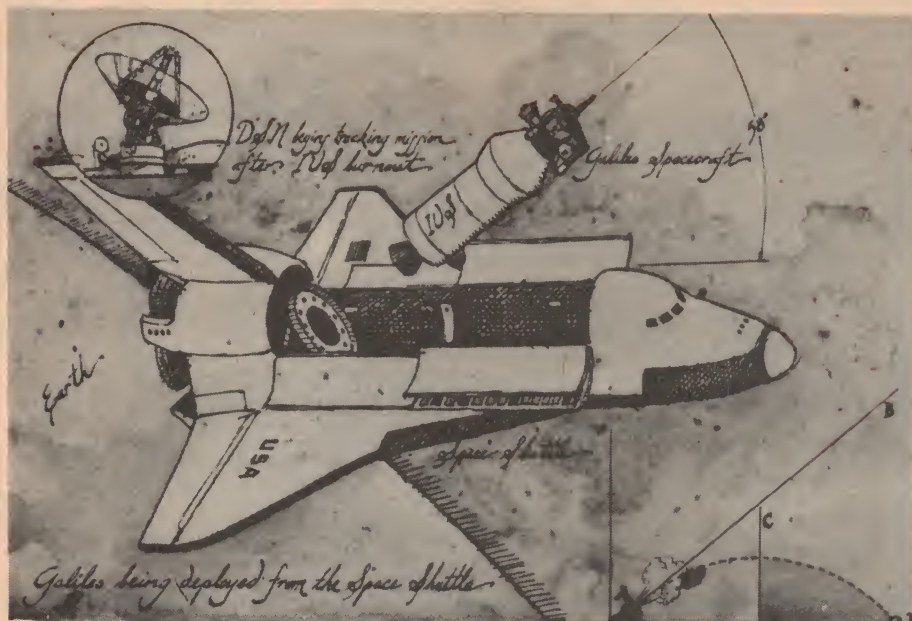An artist's impression of the Galileo spacecraft and inertial upper stage leaving the space shuttle.



## Entry and descent

The probe will be aimed at the light coloured equatorial zone of Jupiter between 1.0 and 5.5 degrees north or south latitude, so as to enter through the highest cloud regions and hopefully make diagnostic measurements of all the important cloud layers. Time of entry will be late afternoon on the Jovian clock.

Let us follow the sequence of events as the probe approaches the giant planet. It will decelerate rapidly from its approach velocity of some 48 km per second (over 100 000 miles per hour), thereby encountering a force of 400 times Earth gravity, and atmospheric friction will cause its heat shield to glow brightly.

Shortly after entry the probe's parachute will open, the heat shield will be jettisoned and the package of instruments will descend more slowly. During its descent it will send data continuously to the Orbiter, which will relay the information to Earth.

After about 40 minutes the probe will have sunk to a depth in the atmosphere at which the pressure is about ten times that at sea level on Earth. The lowest of Jupiter's cloud regions are expected to be in this region, nearly 90 km below the uppermost cloud layer. Temperatures of about 73°C are anticipated.

## Launch and trajectory



Project Galileo will take advantage of the best Jupiter launch opportunity for the rest of this century to send a large amount of scientific equipment to Jupiter and will be the first mission to use the Space Shuttle as an interplanetary launch vehicle, always assuming that the present problems with the Shuttle are solved in time.

An Inertial Upper Stage will be released from the Shuttle in Earth orbit and aligned for the first stage rocket to be fired. Three rocket motors will fire in sequence and the Galileo craft will be sent speeding towards Mars. About 100 days after launch the craft will fly past Mars, using the red planet's gravity to assist it on its way to Jupiter.
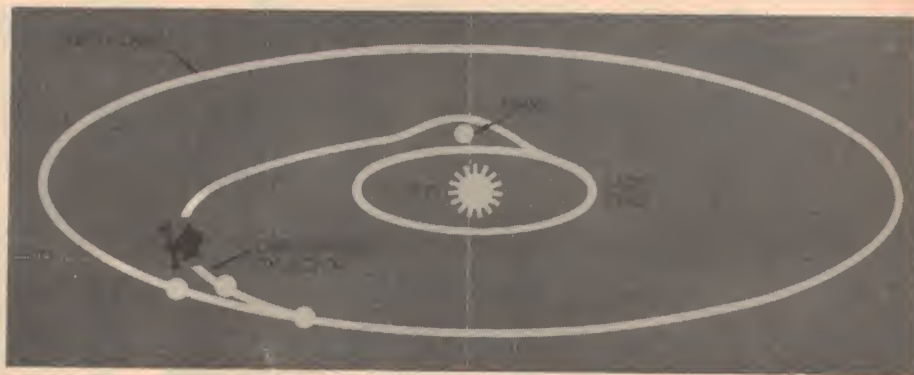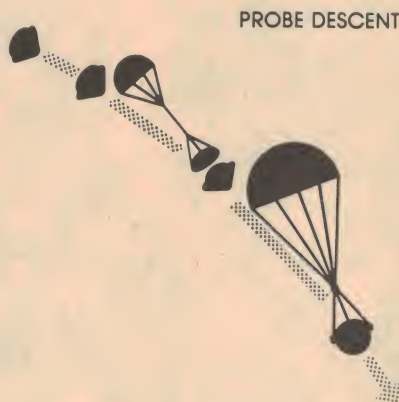
## Probe separation

Near the end of its long journey, about 150 days before it reaches Jupiter, the probe will be separated from the Orbiter vehicle. The trajectory of the craft before probe separation is critical. It is essential that the probe strikes the atmosphere of Jupiter at a shallow angle, since the heat generated by a steep descent would burn it up like a meteor. But the angle must not be too shallow or the probe will bounce off the top of the atmosphere into space, like a stone skimming the surface of a lake. Once the probe has left the Orbiter its path cannot be changed.

After probe separation, the rocket motor of the Orbiter will ignite to deflect it away from the atmosphere. The Orbiter will receive radio signals from the probe during atmospheric entry and relay this data immediately to Earth, as well as storing it on magnetic tape for retransmission later if necessary.




Path of the Galileo craft on its flight to Jupiter.

ABOVE: The red-hot heat shield separates from the descent module which is slowed by parachute. (Picture courtesy of the Jet Propulsion Laboratory).

The probe will continue to sink through the atmosphere, but its mission will be complete after about 60 minutes. By this time it will have reached a depth below the top cloud layers of some 130 km where the pressure is about 20 earth atmospheres and radio signals to the Orbiter will be severely attenuated. Also the higher temperature will have made its circuitry unreliable or inoperative in any case. ►

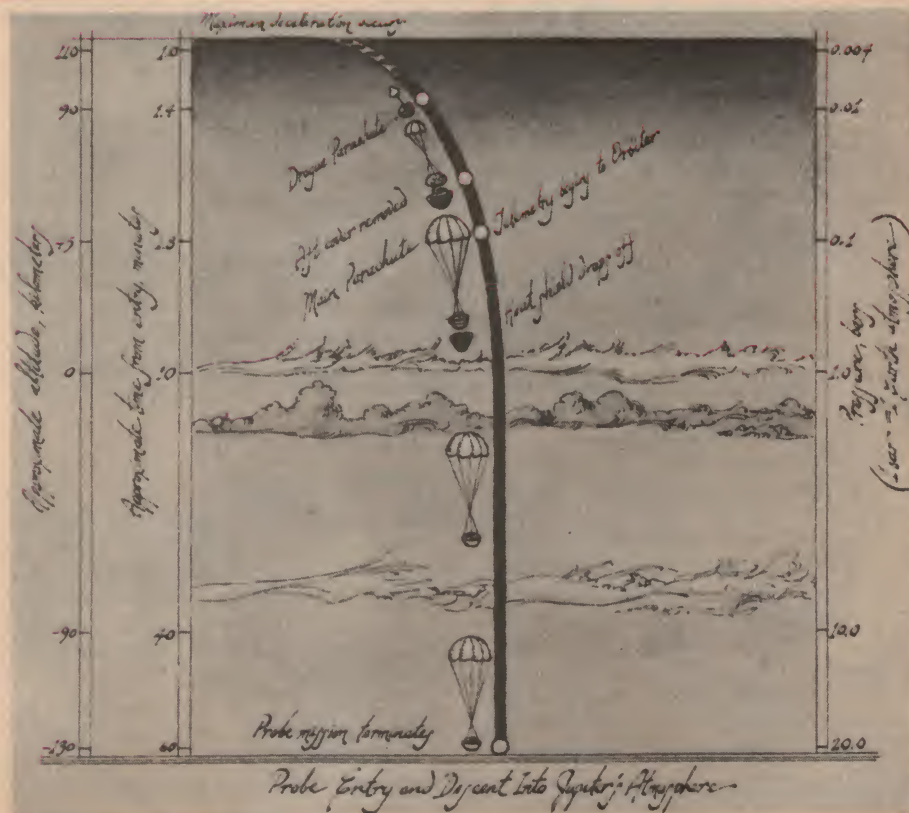An artist's impression of the Probe's descent into the Jovian atmosphere showing the heat shield being jettisoned and the parachute opening.





The series of elliptical orbits for observing the Jovian system

## The Orbiter's mission

The main rocket motor of the Orbiter will burn for nearly 50 minutes after the end of the probe's mission, so that the Orbiter enters an elongated elliptical orbit around Jupiter. About this time it will fly past Io, the innermost of the four Galilean satellites and will use Io's gravitational field to reduce the amount of fuel it requires to enter the desired orbit around Jupiter. The firing of the rocket will take the Orbiter outwards from a distance of about 358 000 km (five Jupiter radii) to a distance of some 19.5 million km.

After 100 days, at a point of greatest distance in its elliptical orbit from Jupiter, the craft's large rocket will be fired for the third and last time. This will change its orbit to one that makes closest approach about 900 000 km above the planet's cloud tops.

Each time the Orbiter passes near to the satellite Ganymede it will use the latter's gravitational field to alter orbit slightly. This technique will save fuel and provide at least 11 near encounters with Jupiter and 11 close passes by Ganymede and Callisto — the two outer Galilean satellites. Some of the encounters will be very close, within one tenth of the radius of the satellites, and details as small as 30 to 50 metres on the surface will be resolved. This is 10 to 100 times better resolution than that obtained by the Voyager craft.

It is planned that Galileo will spend 20 months orbiting Jupiter in ellipses with periods of 200 days (initially), 94 days and 42 days. It is expected to be still functioning at the end of this time, in which case it may be used to look at the dawn regions of the planet and to study the moons in more detail.

The craft will also be used to explore the general environment of the huge planet. During at least one of its orbits Galileo will study the 'magnetotail' of Jupiter — the magnetic fields in a direction opposite to that of the sun. This involves measurements at distances out to 150 times the radius of Jupiter, some 10.74 million km. This type of work cannot be undertaken with fly-by missions, since their trajectories are too near the planet and too strongly deflected to reach the desired region of space behind it.

## Orbiter design

Like all planetary craft, the Galileo Orbiter and its probe will carry a variety of scientific instruments, all designed for minimum mass and volume. When it is launched from the Inertial Upper Stage of the Shuttle the mass of the complete system will be over 1500 kg. Much of this will be rocket fuel and the supporting structure. The Orbiter payload will be only a little over 60 kg, and that of the probe 30 kg.

One interesting new feature is that,

because of the conflicting requirements of different sets of experiments, one part of the Orbiter vehicle is to be spin stabilised and the other part is three-axis stabilised. During the passage to Jupiter, the two parts of the craft will be allowed to spin together. When a command signal is sent from Earth, the part of the craft containing the imaging camera systems will be de-spun to provide a stable platform. The on-board instruments can then be pointed accurately at Jupiter and its satellites to provide high quality, stable images. The instruments for observing Jupiter's magnetosphere, on the other hand, require a platform which spins several times a minute, so they are situated in the other part of the craft.

A large, 4.8 metre diameter deployable antenna on the Orbiter will transmit signals to the Earth stations of the Deep Space Network in the S band (4 GHz) and the X band (8 GHz). This antenna will be folded during the launch and extended rather like an umbrella with its supporting ribs when the craft is on its trajectory towards Jupiter. A much smaller dish antenna will be used to receive signals from the probe. Radio signals to and from the Earth stations will take about 40 minutes to travel the 700 million km between Jupiter and Earth.

The very low intensity of sunlight at such enormous distances from the sun means that solar cells cannot be used to

power the transmitters and other electrical systems. Radioisotope thermoelectric generators are the only source of continuous long term power light enough to be carried on deep space missions. Two such generators will be mounted on short arms on each side of the Galileo Orbiter, behind the main antenna.

## Probe design

The probe to be carried with Galileo is basically similar in principle to the large probe of the Pioneer Orbiter vehicle (see ETI June 1978 and May 1979). It consists of a deceleration module and a descent module. As it is of vital importance that this long and expensive mission shall not fail, a heat shield of very conservative design will be incorporated in the craft — indeed,



Descent module of the Probe.



Descent module (top) and heat shield.



The complete Probe in its heat shield with aft cover.  
(All above pics courtesy of Hughes Aircraft Co.)



The probe will transmit data to the Orbiter craft which will then relay the data to Earth.

44% of the weight of the probe assembly is taken up by the heat shield. The problem of designing this shield is made more difficult by the fact that we can only guess at the conditions which are present beneath the uppermost cloud layers of Jupiter.

If the descent module had to withstand the very high pressure of the lower Jovian atmosphere, it would need to be extraordinarily massive. For this reason a vented design has been chosen, which allows the pressures inside and outside the module to be equal all the time.

The probe requires electrical power only during its relatively short descent through the Jovian atmosphere. This power will therefore be provided by a lithium battery which lies unused throughout the interplanetary flight to Jupiter. Lithium cells are well known for their long shelf life, but an extra special design has doubtless been selected for the Galileo probe. This battery will power all the probe systems during the descent and also provide the radio

transmitter power to communicate with the Orbiter vehicle. But the probe will not be able to transmit directly to Earth.

Special antennae mounted on the rear of the probe have been designed for data transmission to the Orbiter for the longest possible time under the difficult conditions prevailing deep in the Jovian atmosphere. The probe will not receive any command or other signals from the Orbiter, but merely send data.


A timer and a g-switch (gravitational acceleration switch) in the probe will initiate heat shield separation and the parachute deployment sequence. The electronic systems will be turned on by another timer about five hours before entry into the atmosphere and shortly afterwards the probe will start gathering data about the lightning and radio emissions from the planet. This data will be stored in the probe memory until a g-switch turns on the probe radio transmitter after the heat shield has been jettisoned. The stored data and the real time data will then be sent to the Orbiter.

# MAGRATHS



IN THE HEART OF MELBOURNE

## SOANAR CAPACITORS

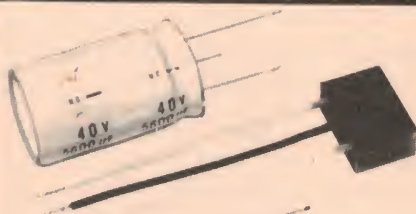

### Electrolytic

#### PCB Can

2,500 — 5,600  $\mu$ F  
35V — 80V DCW

#### Radial

47 — 2,500  $\mu$ F  
6.3V — 450V DCW

#### Axial

47 — 4,700  $\mu$ F  
6.3V — 500V DCW

#### Lug Terminal


90 — 8000  $\mu$ F  
15V — 450V DCW

#### Bi-Polar

47 — 1000  $\mu$ F  
50V DCW

#### Computer Grade

2,900 — 100,000  $\mu$ F  
16V — 40V DCW

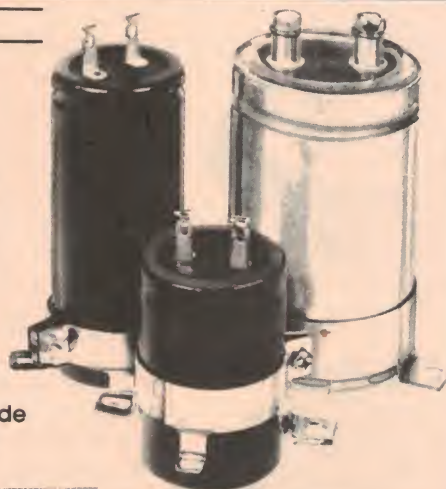

### Film

Polypropylene  
Polystyrene  
Polyester

### Ceramic

### Tantalum




### NEW!

RBLL Low Leakage  
Electrolytics

.1 — 100  $\mu$ F  
25V — 50V DCW

FOR ALL YOUR ELECTRONIC COMPONENTS

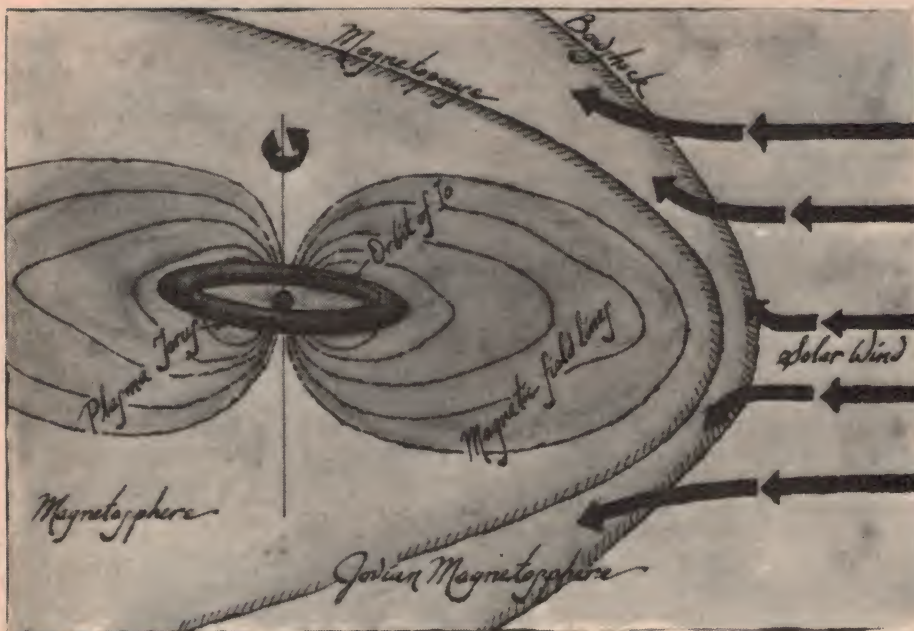

Jupiter's magnetosphere extends for a considerable distance from the planet

## Orbiter instrumentation

Previous planetary missions have used conventional vidicon tubes in their TV camera systems, but the Galileo Orbiter will use a new Charge Coupled Device (CCD) camera with a 1.5 m focal length, which will have a broader spectral response and better resolution. This and other remote sensing instruments will be carried on a short arm at the rear of the craft.

Another instrument in the de-spun section of the craft is the near infrared mapping spectrometer which will provide spectral images in many different wavelength ranges, measuring reflected sunlight and thermal emission from Jupiter's atmosphere and from its satellites. This will allow scientists to study the atmospheric composition, cloud structure and temperature, and to identify materials on the surface of satellites. An ultraviolet spectrometer will also be used to study the composition of the planet's upper atmosphere and the rare atmospheres of the satellites.

A photopolarimeter/radiometer in the de-spun section will measure temperatures at various heights in Jupiter's atmosphere and on the surfaces of the satellites. Cloud characteristics will also be investigated with this instrument.

Turning now to the spinning section of the Orbiter, we find a magnetometer which measures the magnitude and spatial variation of the magnetic fields around Jupiter and its satellites. Because electric currents and magnetic materials on board can disturb the field near the Orbiter, the magnetometer will be attached to a long boom to hold it

well away from the body of the craft.

Plasma instruments will gather information on low energy particles and clouds of ionised gases in the magnetosphere (more about this later), so that scientists can study their resonances and the effects on them of the magnetic and electric fields near Jupiter.

A particle detector in the spinning section will provide data on the composition, distribution and energy spectra of high energy particles trapped in the Jovian magnetic fields, which cause radiation belts like the Van Allen belts around the earth. A dust measurement instrument will determine the size, speed and charge of micrometeorites and other small objects.

Also in the non-spinning part of the Orbiter will be radio propagation experiments to investigate the structure of the atmospheres and ionospheres of Jupiter and its satellites using radio waves. Celestial mechanics experiments will also be performed to detect any gravity anomalies which may be caused by concentrations of mass in the planet or its satellites.

## Probe instrumentation

An atmospheric pressure instrument in the descent module will provide further information on the temperature, density, pressure and molecular weight of the atmospheric gases, while a neutral mass spectrometer will measure their composition at different levels.

A helium abundance interferometer will measure the ratio of hydrogen to helium with extremely high accuracy. This measurement is of great importance to cosmologists, since it should provide evidence for or against the 'big

bang' theory of the origin of the universe.

A nephelometer will determine the size of cloud particles and the location of the cloud layers in the Jovian atmosphere. A net flux radiometer will measure the energy radiated and received by the planet at different levels. At present it looks as if Jupiter radiates  $2\frac{1}{2}$  times as much energy as it receives from the sun.

Lightning and radio detection equipment will measure the electromagnetic radiation generated by lightning flashes in the atmosphere. An energetic particle detector will determine the energies of electrons and protons in the inner regions of the radiation belts and their distributions near the edges of the belts.

## The magnetosphere

As long ago as 1955 when radio astronomers first detected signals from Jupiter, they were certain that the planet must have a large magnetic field which could trap particles and generate radio waves. This region of magnetic field and trapped particles is known as the magnetosphere and it will be one of the main objects studied by the Galileo project.

Jupiter's magnetic field is 20 to 30 times stronger than Earth's, which makes its magnetosphere very large. If the Jovian magnetosphere emitted enough light to make it visible from Earth, it would appear about the same size as the moon in our sky!

There are three distinct regions. The innermost is doughnut-shaped and similar to the magnetosphere of the earth, but larger and more intense. It contains several shells where charged particles of extremely high energy can be concentrated. A middle region consists of a sheath of charged particles driven around by Jupiter's rotating magnetic field. In the outermost region, streams of electrons and protons from the sun interact with the magnetic fields in constantly changing patterns. Some leak into the magnetosphere, while others may be deflected across the solar system as far away as Mercury.

A study of these regions may not only provide us with a much better understanding of astronomical phenomena, but could be very useful in other fields. Nuclear fusion researchers for example will welcome a better knowledge of the ways in which high-temperature plasmas may be contained by magnetic fields.

The writer acknowledges the assistance of the Hughes Aircraft Company, NASA's Ames Research Center, California and the Jet Propulsion Laboratory in preparing this article. ●

# archives

*the price breakthrough in  
performance business computers.*

Success in today's business world demands efficiency and financial accuracy. But the ever-increasing cost and complexities of doing business are forcing you to find new ways to cut labour cost as well as gain tighter control over your business.

The ARCHIVES BUSINESS COMPUTER can give you the control you need to be successful, all in one economical desk-top cabinet.

The ARCHIVES BUSINESS COMPUTER can do your daily business functions such as accounts receivables and payables, general ledger and inventory control. It can keep track of stock on hand, stock on order, and supplies to be ordered. As a Word Processor the ARCHIVES BUSINESS COMPUTER can do your correspondence, text editing of manuals, contracts and proposals. The ARCHIVES BUSINESS COMPUTER can do virtually any information handling or record keeping operation you are presently doing plus many desirable operations that cannot economically be performed by manual methods.

The Archives disk storage can reduce entire filing cabinets to convenient 5¼ inch disks and instantly retrieve any information that you may need when you need it.

Sound incredible? The ARCHIVES BUSINESS COMPUTER is that and more!

It's a business assistant. One that never forgets, never loses reports, makes efficient use of its time and is completely trustworthy.

The ARCHIVES BUSINESS COMPUTER is also easy to work with. So easy in fact, it's no more difficult to operate than any other office machine. While the ARCHIVES BUSINESS COMPUTER is handling the extra work load, you can have more time to develop new business in the field.

There is no question that the major area restricting your business growth is in the office. This is one place where employee efficiency is still in the dark ages - requiring the handling of paper, forms and files. What you really need is not the physical presence of obsolete forms and letters, but the information and data they contain. You need the Archives Business Computer.

The Archives Business Computer offers you an economical way to individualised computing power. You can take it anywhere there's work to be done. Plug it in, turn it on, and it's working for you giving you instant access to the information you need.

Designed especially for a small business or single department in a large corporation, the Archives Business Computer is a system you can understand and use with a high degree of efficiency without being a computer specialist.

Incorporating quality and reliability the Archives Business Computer provides you with today's and tomorrow's best value in a computer system. The Archives Business Computer is a system to help your business grow.

The Archives Business Computer is backed by competent and qualified technical support for both equipment maintenance and software aid as well as continuing personalised service.

One of the best investments you can make in this inflationary economy is the Archives Business Computer. In fact, virtually every business enterprise can benefit in some practical way from business computing.

A full scale demonstration of the Archives Business Computer will help you draw positive conclusions about how your business can improve its cash flow, reduce costs and risks, improve customer service, increase sales, and improve your employee productivity.

It's time to make a move for the future.  
It's time to contact Computerland  
Melbourne your Archives dealer.

## FEATURES

- Z80 4MHz Processor**
- 64 K RAM Standard**
- 744K Bytes Storage (Standard)**
- 1½ Megabytes Storage (Optional)**
- 12" Green Phosphor Monitor**
- 25 Lines x 80 Display**
- CP/M Operating System**
- Selectric Style Keyboard**
- \$100 Expansion Inbuilt Microprocessor Keyboard**
- 240 x 100 Graphics Format**
- Numeric Keypad and Function Keys.**



## SOFTWARE

- Microsoft Fortran**
- Microsoft Basic**
- Microsoft Cobol**
- General Ledger**
- Stock Control**
- Mail List**
- CBasic 2**
- Accounts Payable**
- Accounts Receivable**
- Property Management**
- Word Processing System**
- Microsoft Basic Compiler**

# ComputerLand® in Melbourne

555 Collins St. • Melbourne, Vic. • Australia 3000 Phone 62 5581 • 62 6737 • Telex AA37007




# Sound or light operated flash trigger has many features

**Phil Wait**  
**Simon Campbell**

You too can take spectacular action shots just like those shown in these pages. This project is simple to build, suits any flash unit and can be triggered in a number of ways.



# Project 568

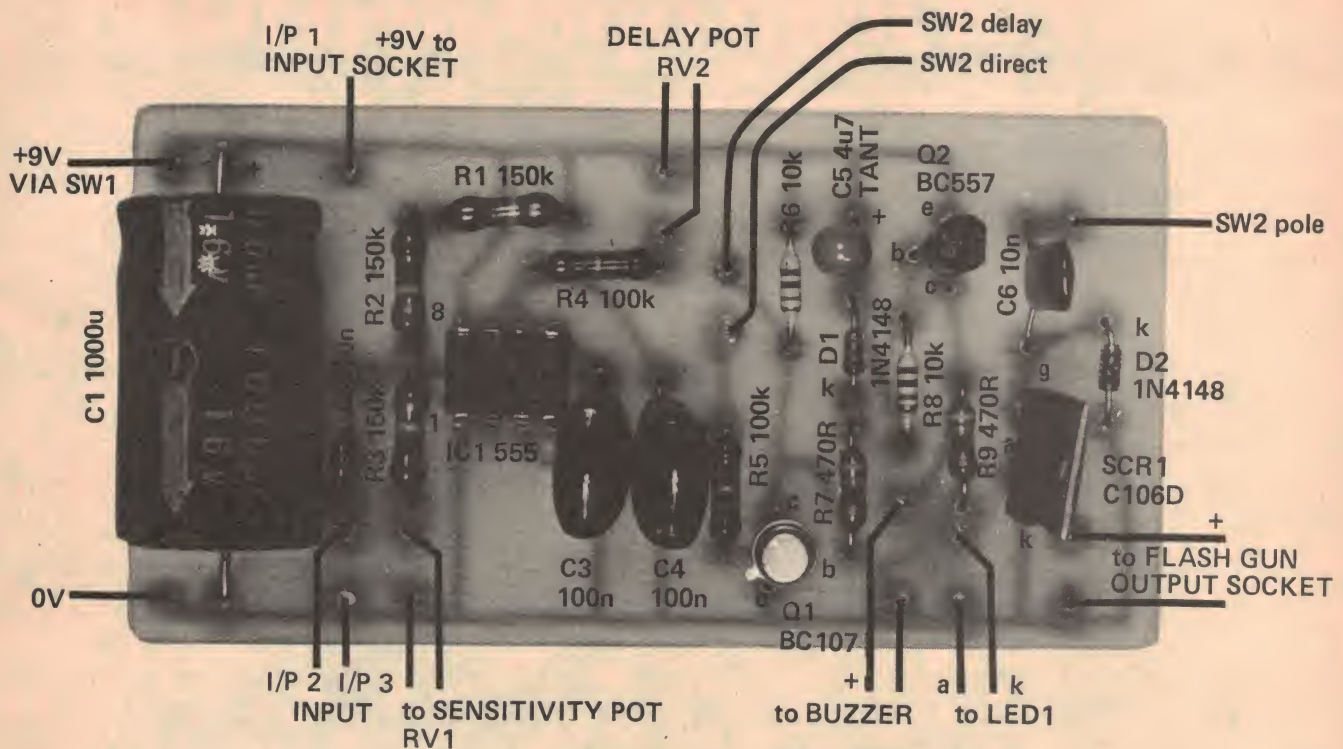

NOTE: Printed circuit board artwork is on page 113.

PHOTOGRAPHICALLY 'freezing' an action while it is in progress is an extraordinarily difficult task unless you can accurately time the flash to 'fire' at a particular instant during the event. This project does exactly that. You can trigger your flash from a sound, such as that produced by a bouncing ball, or by light — by having an object break a beam of light for example. You can arrange to trigger the flash by a light source turning on, or turning off. In addition, this unit permits you to *delay* the triggering of the flash by a preset amount, allowing you to 'catch' the action at differing periods after the triggering event.

The attraction of this unit is that you need no fancy equipment to take good pictures like those you see on these pages. You don't have to have a fancy SLR camera — just a simple model on which the shutter can be locked open. We haven't tried it, but with a powerful flash gun even a pinhole camera should work!

## The circuit

A 555 timer IC (surprise, surprise!) is employed to provide a trigger pulse from a suitable input sensor. This can be an inexpensive crystal microphone or a phototransistor connected to trigger the

555 from a light source turning on or a light source turning off. Obviously, the unit can be used as a slave flash trigger also.

The 555 is operated in the *monostable* mode. That is, when triggered by the input signal detector it provides a single pulse output, the width of this pulse being predetermined by a preset control. The pulse output of the 555 is arranged to turn on an SCR which is connected in series with the flash gun's power supply via an interconnecting cable.

To provide a variable delay, the SCR is triggered from the *trailing* edge of the pulse output from the 555. The width of the pulse can be varied with a potentiometer control. A minimum delay of about 10 milliseconds and a maximum delay in excess of 200 milliseconds can be obtained. If you require a shorter delay, the value of R4 may be reduced, but do not use a value less than 1k.

When setting up a shot, one needs some indication that the trigger unit is being correctly fired by the action, without having the flash gun 'popping' numerous times. For this reason we have included a LED on the front panel and a piezo buzzer to provide both a visual and an audible indication. The piezo buzzer is optional, but we found it

handy as you can't always be involved in the action and watch the LED at the same time.





For 'rehearsals', the flash gun cable is disconnected. With everything set to go the sensitivity control on the trigger unit is set at some arbitrarily chosen level and the action initiated. If all is well, the LED will light and/or the buzzer will sound.

The whole unit is powered by a single 9V battery. A No. 216 transistor radio battery does the job nicely and should give long life.

## Construction

We constructed our unit using a pc board to mount all the minor components. We recommend you use the pc board as it simplifies construction and avoids the more common wiring errors. The whole unit was assembled into a convenient 'jiffy' box measuring 160 mm long by 95 mm wide by 50 mm deep. All the major components were mounted on the aluminium front panel and wired to the pc board with hookup wire. We used a five-pin standard DIN socket for the input connector and a two-pin socket, usually used as a speaker connector, as a connector for the flash gun cable. The sensors generally need to be placed in a convenient position re-

# flash trigger

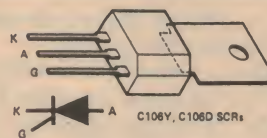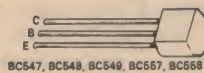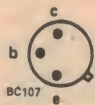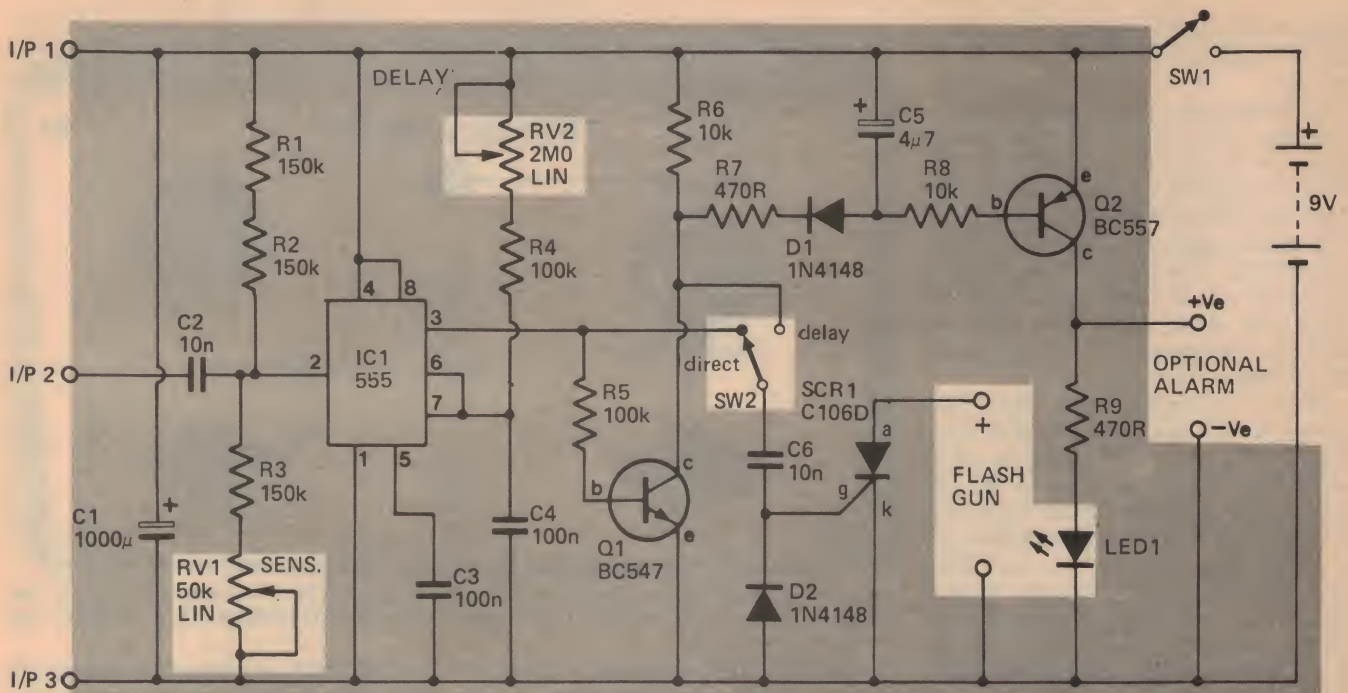


TANTALUM  
CAPACITOR



This sensor triggers  
when light source  
turns on

This sensor triggers  
when light source  
turns off

Sound trigger

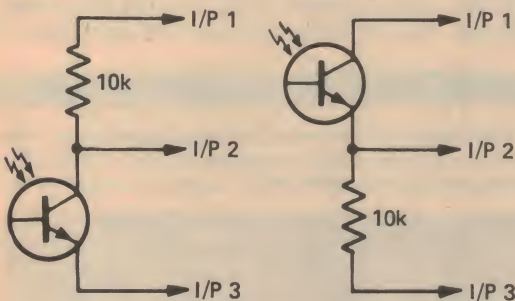

Use phototransistors, type FPT100 or TIL78 or similar

## HOW IT WORKS — ETI 568

IC1 is a 555 timer connected in the monostable mode. The timing period is determined by RV2, R4, C4 and is adjustable between 11ms and 230ms with the values shown. The trigger input of the chip is held just above its firing potential of one third supply voltage by adjustment of RV1 which acts as a sensitivity control. A negative-going signal is coupled to the input by capacitor C2. Note that the values of R1, 2, 3, RV1 provide a medium input impedance and screened cable may be required when the sensor must be separated from the unit.

When IC1 is 'fired', its output (pin 3) goes high for the monostable period. With SW1 switched to 'direct', this positive going pulse will fire the SCR and discharge the flash enabling the unit to be used as a slave flash.

There will be a finite delay owing to rise time of phototransistor response, propagation delay within IC1 and rise time of its output. However, this will be measurable in microseconds and should be negligible.

When used in the 'delay' mode, the output pulse is inverted by Q1 causing the flash to fire on the trailing edge of the monostable pulse. To avoid repeated use of the flash when setting up the unit, indicator LED1 is provided. Each negative excursion of Q1 collector causes C5 to charge via R7, D1 effectively stretching the monostable pulse and providing a clearly visible flash.

An optional alarm, for example a solid-state buzzer, can be connected into the circuit providing audible indication of triggering.

Capacitor C1 provides overall decoupling. Supply current is about 10 mA.

## PARTS LIST — ETI 568

Resistors all 1/4W, 5%

R1,2,3 ..... 150k  
R4,5 ..... 100k  
R6,8 ..... 10k  
R7,9 ..... 470R

Potentiometers

RV1 ..... 50k lin  
RV2 ..... 2M lin

Capacitors

C1 ..... 1000u electrolytic  
C2,6 ..... 10n polyester  
C3,4 ..... 100n polyester  
C5 ..... 4u7 tantalum

Semiconductors

IC1 ..... 555  
Q1 ..... BC547, BC107 etc  
Q2 ..... BC557, BC177 etc  
SCR1 ..... C106D or similar  
D1,2 ..... 1N4148 or 1N914  
LED1 ..... any LED

Miscellaneous

SW ..... SP DT toggle switch  
SW2 ..... SP DT toggle switch  
ETI-568 pc board; flash gun connector, crystal microphone with plug and socket (if used); 9V battery and battery clip; box to suit; buzzer (if required).

Additional Components for Light Operation:

Phototransistor FPT 100, TIL78 etc.  
10k resistor.


# Project 568

mote to the trigger unit and we made up several cables for each of the different sensors.

Construction is best commenced by loading the components into the pc board. It is usually convenient to start with the resistors and capacitors. Take care with the orientation of the  $4.7\ \mu\text{F}$  tantalum capacitor and the  $1000\ \mu\text{F}$  electrolytic. The semiconductors can be mounted on the board next. Here too, take care to get them the right way around. Particularly watch the orientation of the IC and the two diodes.

Some mechanical work comes next. Mark out the front panel carefully and drill all the holes. Temporarily mount each individual component on the panel, just to make sure that they all fit without problems. We used a Scotchcal front panel to dress up the unit. If you are doing likewise, now's the time to attach it to the panel of the jiffy box. Having done that, finally mount the two pots, the two sockets, the switches, the LED and the buzzer (if you've elected to use one).

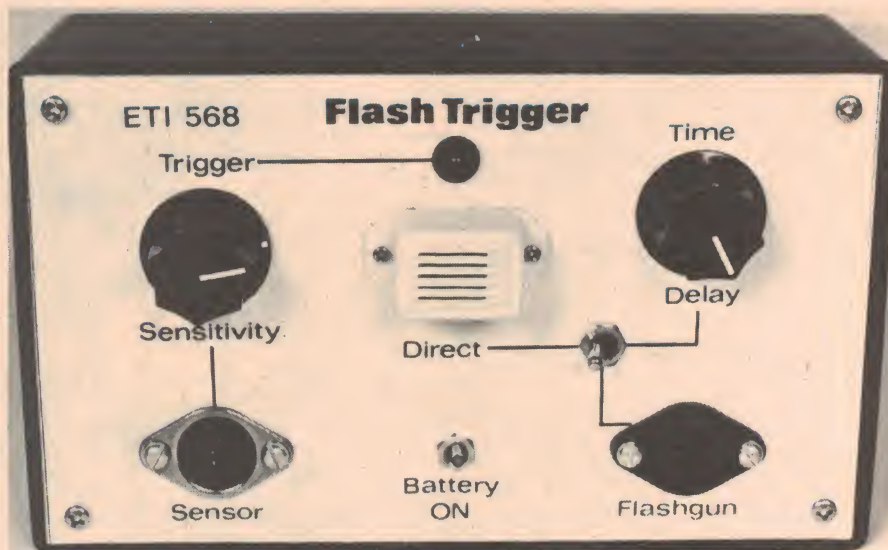Now you can install the wiring between the pc board and the components on the front panel. Note that pin 1 of the input socket is wired to the pc board via a short length of shielded cable. This is to avoid pickup of stray signals, such as hum, which may cause triggering difficulties. Be careful with the connections



The prototype was housed in a 'jiffy' box measuring 160 mm long by 95 mm wide by 50 mm deep. The front panel was dressed up with a Scotchcal transfer. These should be available through suppliers — see Shoparound on page 65.

to the LED and the two pots. The component overlay and wiring diagram should make this stage of the construction fairly clear.

You don't have to use a DIN socket for the input connector as we have, indeed a tip-ring-and-sleeve jack socket could equally well be used. Any sort of socket having three connections will do the job. Similarly, we used a two-pin socket for the flash gun connector as we had it on

hand. Both these connectors are readily available and this was the main consideration in our choice.


You will have to make up a suitable lead to go between the trigger unit's output connector and the flash gun's remote trigger connector. Use the appropriate connectors at each end.

Polarity is important as the trigger unit employs an SCR for the triggering 'switch' device. One way of determining

This series of pictures shows how the variable time delay facility can be used to capture the effect of a ball bouncing in a container of fluid (milk here). The shots were sound-activated and the time delay was set for delays between



## flash trigger

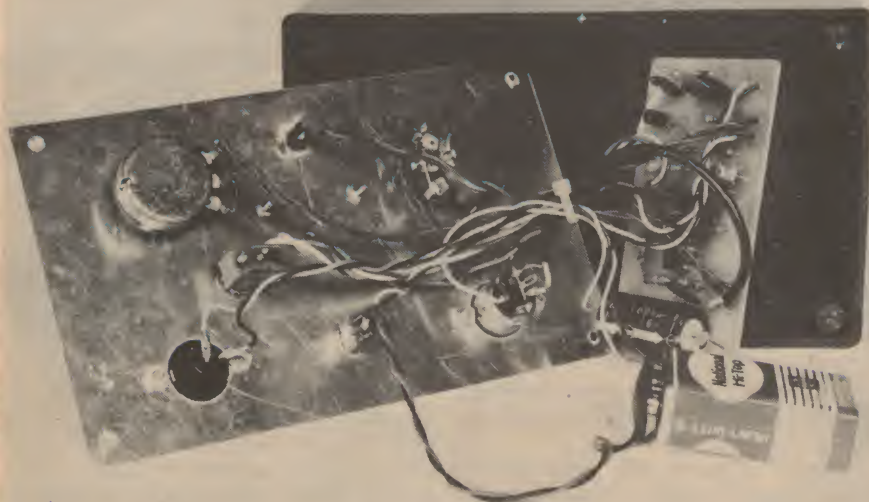

Internal view of the completed prototype. Note that wiring between I/P2 and the panel-mounted input socket is via shielded cable. Sensors should be wired with shielded leads also.

the polarity of the flash gun is to measure the voltage present at its trigger socket with a multimeter.

### Sensors

Before you can try out the unit, you will need to assemble some suitable sensors. The simplest is just a crystal microphone. We used an inexpensive 'lapel' mic and obtained excellent results. A crystal mic is recommended as it has

quite a high output level. You can give the unit a 'dry run' at this stage. Set the Direct/Delay switch to Direct and the Sensitivity control to mid range and turn on. Clap your hands once and, if all is well, the LED will light and the buzzer will sound for a brief period. Set the unit to Delay and the Time control fully clockwise. Clap once more and again the LED will light following a brief delay. Experiment a little with the

sensitivity control so that you get some idea of how it affects the operation.

There are two ways the unit can be triggered from a light source, as we said before — by a light source turning on, or a light source turning off. The different sensor circuit configurations are given in the accompanying circuits. An inexpensive, readily available phototransistor is employed — either a Fairchild FPT100 or a TIL78 from Texas Instruments. There are many similar devices available and no difficulty should be experienced here.

The phototransistor can simply be 'hung' from the leads at the end of a cable, the other end being terminated in the input plug (which suits the input socket used). The 10k resistor may be mounted in the input plug housing. There is plenty of room in a DIN plug. If you want something a little more salubrious, the phototransistor could be inserted in a small diameter plastic tube (say, 12 mm dia.) with the 'business' end of the device flush with the end of the tube. The tube can then be filled with epoxy resin. It's advisable to have the phototransistor attached to the cable before you do this!

Microphones usually come in their own housing, so there's no need to go to any trouble with them. The lapel mics come with a handy clip, so they can be attached to any convenient support. ►

50 milliseconds and 200 milliseconds. Similar shots could be light activated by arranging the ball to break a beam of light.



# Project 568

Another sensor to try out is a silicon solar cell. To use one as a sensor with this unit, you will need to obtain one of those small 'transistor radio audio transformers' — the type having a "1000 ohm" primary and an "8 ohm" secondary, or similar. It is used 'back to front' in this application. Connect the solar cell directly across the transformer's low impedance winding and connect the high impedance winding between I/P2 and I/P3. It's simple, but it's sensitive. Suitable solar cells, or solar cell pieces, are obtainable from David Reid Electronics stores, Dick Smith Electronics stores, Ellistronics, Electronic Agencies, Radio Despatch Service (all advertisers in ETI) or Amtex Electronics of P.O. Box 285, Chatswood NSW 2067.



Above, a ball on the bounce. Top right, breaking a light bulb.

## Using the trigger

You'll probably need a fair bit of practice before you get properly used to working with our flash trigger, but persevere — the results will be well worth it.

First of all, position the microphone or light sensor near the object to be photographed, taking care to keep it out of the camera's field of view. The sensitivity of the trigger is quite high, so it should be possible to place the sensor quite remote from the action. For scenes involving explosions or splashing liquids this is certainly advisable!

Set up your camera for the shot you want and then do a dry run of the action with the camera shutter closed and the flash gun disconnected. The purpose of this is to make sure that the trigger is being reliably fired by the action. If all



is working well, the front panel LED will light and the buzzer (if one is fitted) will sound. If not, adjust the sensitivity control or move the sensor.

Once you're happy with the operation of the trigger, you're ready to start shooting in earnest. Connect the flash gun to the trigger unit and set your camera aperture according to the exposure guide table supplied with the flash gun. Remember that the aperture setting given in the guide relates to the distance from the object being photographed to the *flash gun*, not to the camera. Take another look through the viewfinder, just to check that all the action will be in frame and neither the flash gun nor the sensor is visible.

The camera shutter cannot be triggered by the flash, so it must be set to the 'time exposure' or 'B' position. Before you open the camera shutter, make sure the room is in TOTAL darkness. Try not to trip over any of the equipment in the dark!

Open the camera shutter and set off the action, releasing the shutter button when the flash has fired. You may find a cable shutter release very useful if you don't have a friend helping you to set up the shots.

You should now have a picture, but at this stage you won't know whether or not you've captured the exact instant of the action you wanted. So set the trigger unit to give a different delay and shoot again. If your trigger is sound operated, you can get very fine control over the delay by taking advantage of the relatively slow speed of sound. Sound waves move at about 330 metres per second, so for every metre change in the object-to-microphone distance there's a 3 millisecond change in the triggering delay.

By this time you'll have spent quite a lot of time and trouble (and some money) in constructing and setting up your flash trigger, so don't be mean with film. Shoot a whole roll if necessary, to make sure of getting the one or two shots that you really want.

The ability of the flash trigger to freeze very fast action such as explosions or collisions will depend on the speed of your flash. Most camera flashes have a flash period around one millisecond which may produce a blurred picture in some circumstances. If you find your picture is blurred you will have to use a faster flash or strobe unit.

## Calibrating the delay

If you wish you can use an oscilloscope to calibrate your delay control.

If you have a dual-trace oscilloscope, connect one vertical input to the sensor output and the other to the gate of the SCR. Set the oscilloscope to trigger from a positive going edge on the sensor output and the time base to 10ms per division. Switch the flash trigger to the delay mode and activate the sensor. Looking at the CRO you should see a delay between the first negative edge of the sensor output and the gate pulse. You should be able to vary the gate pulse, by rotating the delay control, from about 10 ms to 200 ms. As the trace will only sweep once for each trigger pulse, it may be difficult to see. Retriggering the sensor quickly with a flashing light will improve the visibility of the trace. Alternatively the sensor can be replaced with a low frequency pulse generator, but be careful not to have a pulse period shorter than the delay you are trying to measure. Measure the delay for each 20 degrees or so of the delay potentiometer and calibrate your scale. Our unit measured close to 11 ms minimum delay to a little over 200 ms at maximum.

The procedure for using a single trace oscilloscope is similar, except that the sensor output is fed to the external trigger input on the oscilloscope, and the trigger control set to trigger from a negative going edge. The vertical input is connected to the gate of the SCR and the sensor activated. The delay is then measured from the left hand edge of the trace to the gate pulse.

**"The bright clear trace makes the Trio CS1560AII easy for operators to use..."** says John Shillabeer, Head of Test Equipment Engineering at S.T.C.



**TRIO**

John Shillabeer's department is involved in the maintenance, calibration and servicing of all test equipment used within S.T.C. We asked him why S.T.C. used Trio CS1560A scopes.

"My department gets involved with all test gear purchases. As a general purpose scope we've found that the Trio provides excellent performance for its price. Being easy to trigger we find staff can readily get it up and going. On the production

line, the bright clear trace makes it an easy scope for operators to use.

"Over the past three or four years, S.T.C. has bought 8 Trio 1560s and we've had virtually no trouble from them. Any minor services have been easy to carry out. As you can see we even use one in our department in the development of our own digital test equipment."

15MHz Trio CS1560AII Dual Trace



30MHz Trio CS1577 Dual Trace



**PARAMETERS<sup>PTY</sup> LTD**

**"Perfection in Measurement"**

Sydney 439 3288 Melbourne 90 7444

Available from selected dealers

N.S.W. Sydney Dick Smith Stores 888 3200; George Brown & Co 519 5855; Radio Despatch Service 211 0191. Newcastle D.G.E. Systems 69 1625; Elektron 2000 26 2644. Wollongong Hundell Engineering 74 0278; Macelec 29 1455; A.C.T. Canberra Electronic Components 80 4654. QLD Brisbane Audiotronics 44 7566; L.E. Boughen 36 1277; N.S. Electronics 36 5061. VIC Melbourne Browntronic 419 3986; Douglas Radio 211 1698; J.H. Magrath 663 3731; Radio Parts 329 7888; Tech Rentals 267 5877; G.B. Teleparts 328 4301. Geelong Teleparts 21 7288. S.A. Adelaide K.D. Fisher & Co 269 2544; Gerard & Goodman 223 2222; Trio Electrix 51 6718. W.A. Perth Hinc Engineering 381 4477; W.J. Montcrieff 325 5722; Rablec Engineering 381 2866. TAS Hobart Imbros Surpath Systems 23 2892. Launceston W & G Genders 31 2511.

# JOHN F. ROSE

## COMPUTER SERVICES PTY. LTD.

33-35 ATCHISON STREET, ST LEONARDS, N S W 2065, AUSTRALIA

### OPAL 1000

The OPAL 1000 is an 8 slot S-100 system conforming to the new IEEE standards. A Delta Products Z80a 4Mhz CPU card with 2 RS232c serial and 3x8 bit parallel ports is used in conjunction with the Delta Products Disk Controller. One serial and one parallel (Centronics interface) port have been initialised as printer ports.

Memory is provided by a 4Mhz 64k dynamic RAM Board by Measurement Systems and Control. The memory board is fully bank selectable and is designed for upgrading to a multi-user system.

Disk drives are 2x8" Shugart SA801R running at double density (480k/drive) and fitted with our exclusive Disk Saver which prolongs the life of the drives and floppy disks by turning off the AC power to the drives 14 seconds after the last drive select and thus reduces routine maintenance. The Disk Saver also reduces the risk of data loss due to power failures.

The system is mounted in an attractive pressed Aluminium housing with a cast front panel fitted with reset button and key operated on/off switch.

The operating system software is CP/M version 2.2 with Delta Product's utilities which include DTEST (for testing drives and floppy disks) and M2 (a comprehensive memory test program). The Delta PROM monitor enables fault finding to be carried out independently of the Disk Drives.

**PRICE** \$4,174.00 + 15% sales tax.

### OPAL 1004

The OPAL 1004 is an upwards compatible version of the OPAL 1000. The OPAL 1004 is based on an upgraded CPU card with a real time clock. The system is supplied with 1 x Shugart SA801R disk drive (operating at single density) and 1 x Shugart SA1004 10 Megabyte hard disk drive. The operating system is CP/M 2.2.

**PRICE** \$7,700.00

### OPAL 10004 Multi-User

The multi-user version of the OPAL 1004 features 128k RAM and Digital Research's MP/M operating system. The system is fully implemented for connection to 2 serial terminals and a NDK S-2000 or S-4000 printer.

**PRICE** \$9,345.00

### OPAL 5 + 5

Any OPAL system can use an AMPEX 5 + 5 (5 fixed Megabytes and 5 removable megabytes - top loading cartridge) hard disk drive. The AMPEX 5 + 5 is housed in an attractive timber case together with the controller unit. The unit is supplied with the S-100 interface card and all necessary cabling. The CP/M 2.2 and MP/M operating systems are supplied fully implemented for use with the OPAL system. Up to 4 AMPEX 5 + 5 drives can be daisy chained together.

**PRICE (excluding OPAL)** \$8,500 plus 15% sales tax.

John F. Rose Computer Services Pty Ltd can also supply the new AMPEX 16 + 16 hard disk.

### OPAL SMD

An industry standard SMD interface is available for the OPAL range. This allows the OPAL to control up to 600 Megabytes of on-line hard disk storage.

**PRICE** \$3,000.00 plus 15% sales tax.

### TELEVIDEO 920c

The TVI 920 by Televideo includes editing capabilities, protected fields, addressable cursor, micro-processor control, line and character insert/delete, upper and lower case and tabbing. Options include a second 1920 second page character display memory. General features are:

- Standard 96 ASCII Character set displayable
- 1920 character display
- 24 lines x 80 characters
- 10 transmission rates from 75 to 19,200 baud
- 14 key numeric pad, 6 cursor control keys, 11 special function keys, two transmission keys.
- Dynamic control of conversation/block mode
- Single key edit operations
- Page field or line edit
- Blinking, blank and underline fields
- Dual intensity and reverse video
- Field tab/backtab, typewriter tabs, storage tabs.
- Protect and self test modes
- Cursor addressing and cursor read
- 15 CPS repeat. Typamatic keyboard
- Standard RS232, point to point 20ma current loop.

# SEND \$1.00 FOR YOUR COMPREHENSIVE 130 PAGE CATALOGUE

TELEPHONE (02) 439 1220    TELEX AA 27901

- Non-glare etched screen
- 115/230 VAC 50/60 Hz Refresh
- Serial port for hard copy (OPTIONAL)
- Functionally equivalent to the ADM-31 terminal.

**PRICE     \$1,305.00**

## MPI 88T Serial/Parallel Printer

### Specification:

PRINTING TYPE	Impact bidirectional, 7 x 7 dot matrix.
PRINT RATE	100 characters per second (maximum).
THRUPUT	80 characters per second (maximum).
CHARACTER SET	Full upper and lower case 96 character ASCII set, software selectable single or double wide character fonts.
CHARACTER HT.	0.1 in. (0.25 cm)
PRINT FORMAT	8.0 in. (20.3 cm) line length, 80 characters per line at 10 CPI, 96 characters per line at 12 CPI, 132 characters per line at 16.5 CPI.
PAPER FEED	10 lines per second, stepper motor controlled. User selectable pressure roller or tractor feed.
LINE SPACING	6 or 8 lines per inch, user selectable.
MEDIA	Roll paper: 8.5 in. (21.6 cm) wide by 5 in. (12.7 cm) diameter single ply or pressure sensitive multiple copy paper, 0.012 in. (3 mm) maximum thickness. Fan fold paper: 1 in. to 9.5 in. sprocket (including sprocket margins), 0.012 in. maximum thickness. Cut Sheet paper: Maximum width 9.5 in.
RIBBON	Continuous loop cartridge, 20 yds x 0.5 in. width blk ribbon, 5 million character life.
INPUT POWER	115/230 V + or - 10%, 50/60 Hz.
TEMPERATURE	10 - 40 deg. C operating; 0 - 70 deg. C Storage.
HUMIDITY	20% - 90% operating (non-condensing); 5% - 95% storage (non-condensing).
DATA INPUT	Parallel: Centronics compatible 7-bit ASCII, TTL levels with strobe, acknowledge returned to indicate data was received. Serial: RS232C or 20 ma Current loop with BUSY handshake, 10 or 11 bits; 110, 150, 300, 600 or 1200 baud rate.
DATA BUFFER	Two lines standard; optional 1k and 2k buffers available.
FORMS CONTROL	Top of form (8 selectable forms lengths), skip over perforations.
OP. CONTROLS	Power On/Off; Top of form set; select/deselect; forms feed.
DIMENSIONS	41.3 cm wide x 27.3 cm deep x 15.9 cm high. Dimensions exclude paper and paper holder. Weight is less than 6.75 kg.
WARRANTY	30 days.

**PRINTER     \$935.00**

## NDK S-4000


### MATHEMATICS SAMPLE USING STANDARD CHARACTERS

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{\text{rms}} = \sqrt{4KTR(f_2 - f_1)}$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

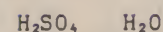

$$W_{xy}(f) = \int_{-\infty}^{\infty} \psi_{xy}(\tau) e^{-j2\pi f\tau} d\tau$$

$$L = \int_0^x \sqrt{\left(\frac{dx_1}{d\theta}\right)^2 + \left(\frac{dy_1}{d\theta}\right)^2} d\theta$$

$$\psi_{xy}(f) = \tan^{-1} \left[ \frac{P_{xy}(f)}{C_{xy}(f)} \right]$$

$$\left. \begin{array}{l} a_1x + b_1y = c_1 \\ a_2x + b_2y = c_2 \end{array} \right\}$$

$$x = \begin{vmatrix} c_1 & b_1 \\ c_2 & b_2 \end{vmatrix} \div \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix} = \frac{c_1b_2 - c_2b_1}{a_1b_2 - a_2b_1}$$

$$S = \sum_{j=1}^n X_j$$

$$\Delta f_{\text{max}} \tau_{\text{max}} \leq 0.3$$

$$|W_{xy}(f)| = \sqrt{C_{xy}^2(f) + Q_{xy}^2(f)}$$

$$\Psi_{xy}(\tau) = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T f_x(t) f_y(t+\tau) dt$$

**\$3,105.00 Plus sales tax.**

# Electronic dummy load

Jonathan Scott

With this unit you can test power supplies at currents up to 15 amps and voltages up to 60 volts. It can 'sink' up to 200 watts on a static test and you can modulate the load to perform dynamic tests.

THIS PROJECT is fundamentally a test instrument — but an unusual one. It is intended primarily for testing and 'setting up' power supplies of all varieties — from ordinary transformer-rectifier supplies to sophisticated regulated supplies. It can even be used to plot the discharge characteristics of storage batteries.

The unit employs four high power transistors connected as constant current 'sinks'. These dissipate power from the source to which the unit is connected. The characteristics of the load are controlled by controlling the base drive to these transistors. Self-destruction is avoided by the addition of protection circuitry which 'shuts down' the load if the rated current or power is exceeded. In addition, a relay will disconnect the unit if more than a safe voltage is applied.

The load can be *modulated* to vary the load current by means of an externally-applied signal. It can be modulated at frequencies up to 70 kHz. The resultant load current waveform can be monitored on an oscilloscope connected to the *current output* socket. The specifications of the unit are given in the accompanying box. We have also drawn up a graph showing the *operating area* of the unit.

## Applications

Regulated power supplies have a finite 'reaction time' following the application of a load or variation in load current. This project can be used to test the transient response, the reaction time, of a power supply as the load can be modulated. A low frequency square wave applied to the unit's *modulation input* will effectively vary the load resistance. The rise and fall times of the power supply under test can then be ascertained from an oscilloscope connected to the *current output*. Varying the level of the signal applied to the modulation input will vary the 'depth' of modulation. The load can be 'swung' from full current to zero current, or over a lesser range, and a good idea of how the supply reacts to this test can be gained.

The same technique can be used to check a power supply's regulation and to set the internal impedance.

## Construction

We chose to use one of the larger Horwood rectangular boxes to house the



# dummy load

project. The layout is not particularly critical and the unit could be assembled in a number of different ways. We chose the Horwood box as it proved convenient and inexpensive. It's convenient as the assembly is dominated by the 220 mm long heatsinks which have to be mounted vertically, and that's how we used the box — a little unconventional, but entirely practical. The box is designated type 34/9/DS and measures 240 mm x 100 mm x 70 mm. It comes in four pieces — the rectangular 'tube' is in two pieces and there are two end pieces. The heatsinks are mounted off the sides of the case on standoff pillars. This allows a free air flow around the vertically mounted heatsinks, ensuring good cooling efficiency.

There are several sources for suitable heatsink sections. Dick Smith Electronics stocks a 225 mm length, catalogue number H-3426. Rod Irving Electronics stocks a suitable style of



Side view showing Q9, Q10 and D2 mounted on the heatsink.

heatsink, manufactured locally, but you may have to ask for a length to suit.

First thing to do is tackle the metalwork. Carefully mark out and drill the heatsinks. One heatsink has two of the transistors mounted on it plus the BYX200R/21L diode, D2. This is a stud-mounting diode that is meant to 'press-fit' into a suitable hole in the heatsink. However, it is easier for home construction if you buy a bolt-on mount for it. These should be available from the supplier from whom you bought the diode. The transistors should be mounted well away from each other, but not too close to the ends of the heatsinks.

Having drilled all the holes in each heatsink, remove any burrs as these in-

terfere with good thermal contact. Bolt all the semiconductors to the heatsinks using thermal compound (such as Bevaloid GS13). No insulating washers are necessary, but solder lugs should be inserted under each of the transistor mounting bolts. Although all the transistor collectors are connected directly to the case, separate wires are run from each to the pc board so as not to rely on the mechanical connection and so that the unit may be tested or serviced with the case disassembled. The anodising on the heatsinks is actually a good insulator, and whilst toothed washers may be used where necessary to provide an electrical connection, we felt it better to provide a direct wire to the pc board. It's certainly more reliable.

Two standoff pillars, about 10 - 15 mm long, are used to support each end of each heatsink, as can be seen from the photographs.

Next, drill the case. Front panel layout is not critical and you can arrange it


to suit yourself.

Mount relay behind the front panel using a small clamp fashioned from a scrap of aluminium. You can glue it on if you wish! It should be mounted quite close to the positive terminal so that a very short, heavy lead can run from the terminal to the relay contact pins.

The pc board is mounted on standoff pillars on the panel of the case opposite the front panel. It can be mounted in any convenient position. The panels on which the heatsinks mount have a large diameter hole (9 - 13 mm) drilled in them through which the wiring to the heatsink-mounted components passes. These holes should be grommeted to prevent possible shorts to the case. Transistor Q8, a TIP31 flatpack, is mounted on the case panel adjacent to the pc board. It is insulated from the case using an insulating washer and insulated mounting bush.

All the components that mount on the front panel can be assembled next. If

— text continues page 34. ►

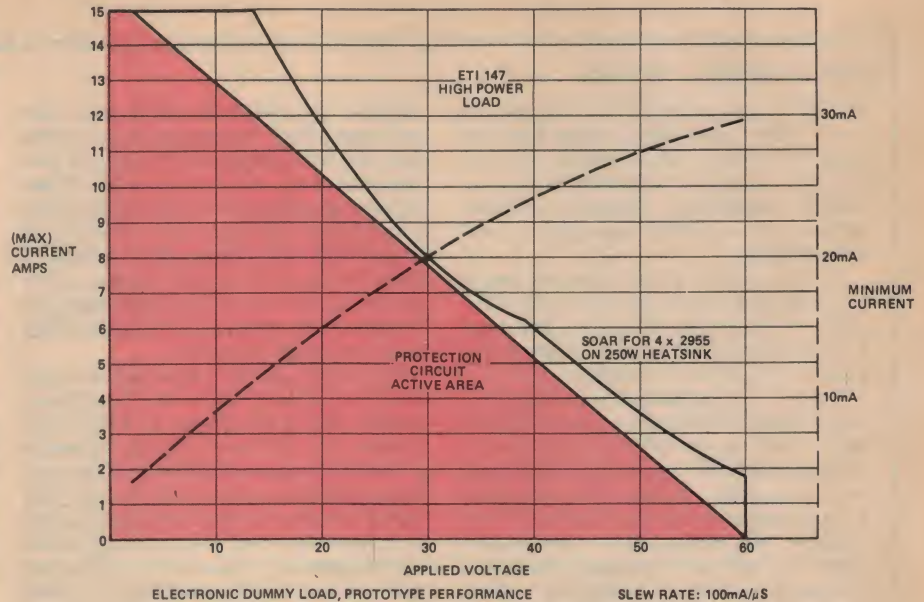

## SPECIFICATIONS ETI-147 ELECTRONIC LOAD

Maximum dissipation	200 watts (see graph)
Maximum voltage	60 volts
Maximum current	15 amps
Minimum voltage	2 volts
Minimum current	3 mA
Modulation range	0 to full current
Modulation sensitivity	1 V p-p or better
Mod. frequency response	1kHz - 70 kHz
Protection	see graph

# Project 147

## HOW IT WORKS — ETI 147

The ETI 147 dummy load is a passive constant current 'sink' which draws power from the supply to which it is connected. The load includes circuitry for protection from over-voltage, overcurrent, overpower, reverse voltage and secondary breakdown of the power devices.

For convenience of explanation, the circuit can be divided into five sections — the main power dissipator and drivers, the reference circuit, the reference comparison circuit, the protector circuit and the indication circuit.

The power is dissipated in transistors Q9 - Q12. MJ2955 transistors have been chosen because, as they are PNP, their collectors can be connected to the heatsink without the need for an insulating washer. This decreases thermal resistance from the transistors to the heatsink. The resistors R24 - R27 ensure correct current sharing between the power transistors as well as forming the current sensing resistance for the protection circuit.

An internal reference is provided by passing a constant current — generated by ZD1, Q3 and Q4 — through R6 and RV1. Using a constant current generator allows the unit to operate over a very wide range of supply

voltages, yet deliver a stable, low value reference voltage. The transistor Q6 compares the reference voltage from RV1 with the voltages across the resistors R24 to R27. These voltages are proportional to the current in the output devices and appear at the emitter of Q6 through R18 to R21. Q6 supplies current to the driver transistors, Q7 and Q8. The output transistors are turned on sufficiently to cause the voltage on the emitter of Q6 to be about 0.6 V above the voltage on its base.


The current sensing voltages appear on the base of Q5 through R14 to R17. R10 proportionally adds a component of the terminal voltage. Should either the current, the voltage or their sum exceed safe limits, Q5 turns on, tripping SCR2 and turning off the load. This 'sum-of-volts-and-current' circuit protects the unit from overcurrent, overpower and secondary breakdown. Because shutting down the load will not provide protection from over-voltage a relay is provided which operates when SCR1 conducts. SCR1 has been arranged to cut in if the current shutdown looks like being inadequate, i.e: if there is considerable voltage present. If the device protects only by current shutdown, turning

RV1 to minimum will reset the circuit. If, however, the relay is operated it will be necessary to remove power to the unit before it will reset. Reverse polarity protection is provided by D2 and FS1.

The current through the load is monitored by M1 which senses the voltage at the emitter of Q6. The meter is calibrated by RV2. A LED indicating that the unit is operating is driven from a constant current source comprised of ZD1, Q1 and Q2. When the voltage is sufficient to operate the load the LED will light, giving an 'adequate voltage' indication. The LED will also extinguish if the relay drops out, indicating the need to remove power.

Finally, in order to make dynamic measurements, C1 provides the option of modulating the reference, and thus the current drawn, from anywhere between zero and full load. The actual current may be viewed with an oscilloscope connected to the output at C2. Capacitors are used here to avoid grounding these points, which would interfere with the operation of the unit. There is no reason why the dc voltage appearing on the meter could not be made available if so desired.

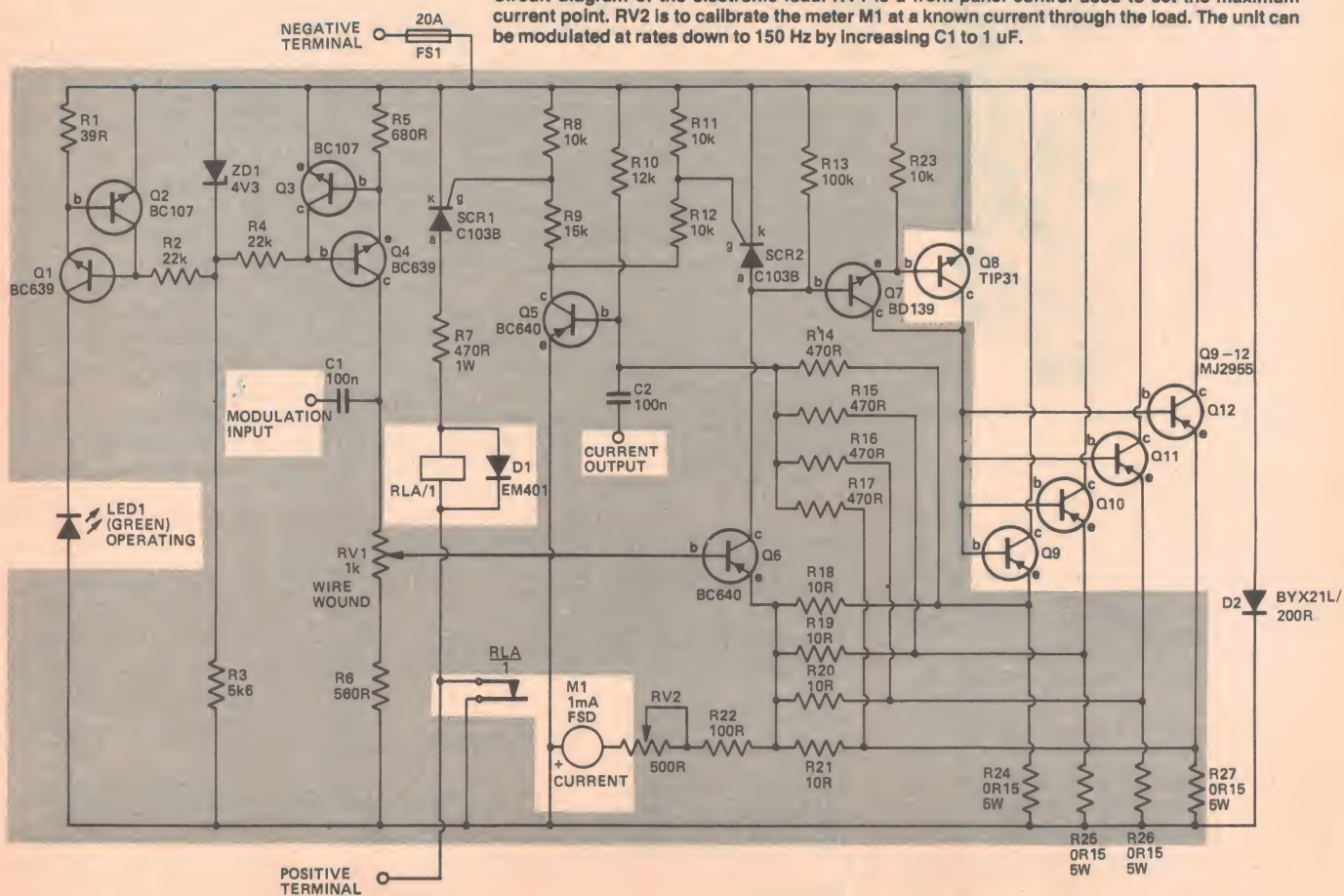Circuit diagram of the electronic load. RV1 is a front panel control used to set the maximum current point. RV2 is to calibrate the meter M1 at a known current through the load. The unit can be modulated at rates down to 150 Hz by increasing C1 to 1  $\mu$ F.



## PARTS LIST — ETI 147

### Resistors all 1/4W, 5% unless marked

R1	39R
R2, R4	22k
R3	5k6
R5, R6	680R
R7	470R, 1W
R8, R11, R12, R23	10k
R9	15k
R10	12k
R13	100k
R14 - R17	470R
R18 - R21	10R
R22	100R
R24 - R27	0.15 ohm, 5W

### Potentiometers

RV1	1k wire wound
RV2	500R trimpot

### Capacitors

C1, C2	100n greencap
--------	---------------

### Semiconductors



D1	EM401 or similar
D2	BYX21L/200R or similar 25A diode

ZD1	4V3, 400mV zener diode
LED1	Green LED, TIL220G or similar
SCR1, SCR2	C103B or similar SCR
Q1, Q4	BFY50, TT801, BC639*
Q2, Q3	BC107, BC547 or similar
Q5, Q6	TT800, BC640*
Q7	BD139
Q8	TIP31
Q9 - Q12	MJ2955

### Miscellaneous

M1	1 mA FSD meter, University TD48 or Minipa MU45 or similar
RL1	24 V relay with 15 A contacts, see Shoparound on p.65

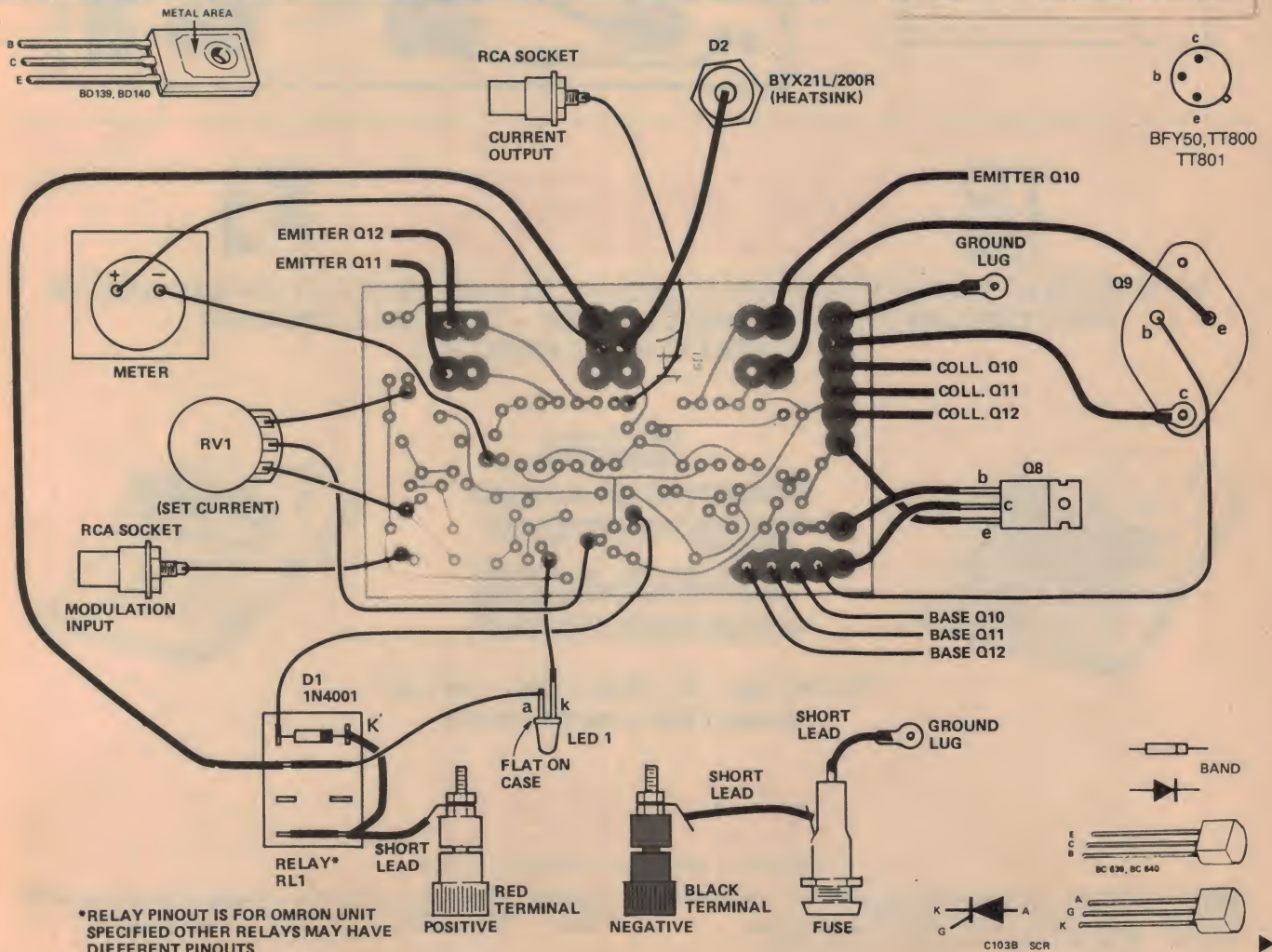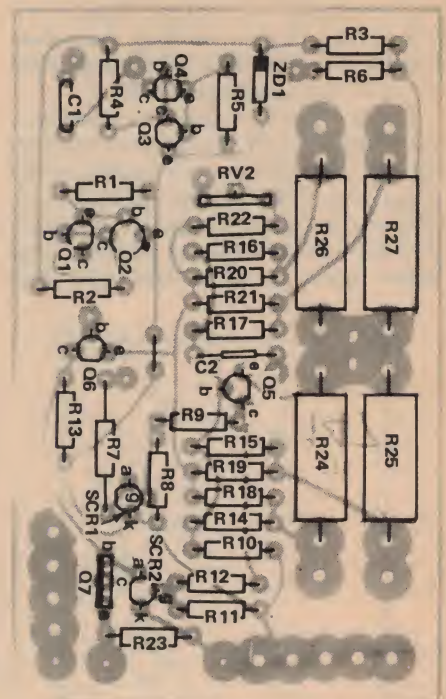ETI-147 pc board; fuse holder with 20 A fuse; two RCA sockets; two screw terminals; 10 x 12 mm standoffs; two lengths 225 mm-long flat-sided heatsink (see Shoparound, p.65); Horwood box, type 34/9/DS; 15 A hookup wire.





you are using a Scotchcal label, don't forget that it goes on first. Suppliers should have Scotchcal labels available — see Shoparound on page 65.

The pc board should be assembled next. Refer to the component overlay, taking care with the orientation of the transistor. If BC639 and BC640 transistors are used for Q1 and Q4, note that they have quite different pinouts to the other types, *so be careful*. The four

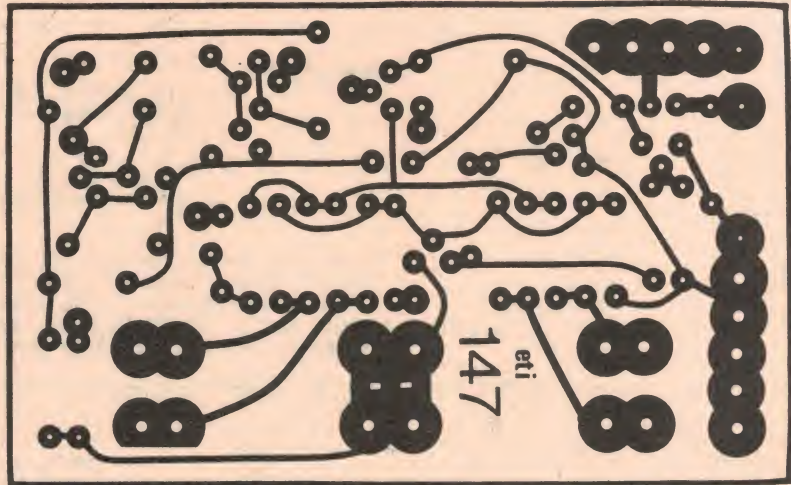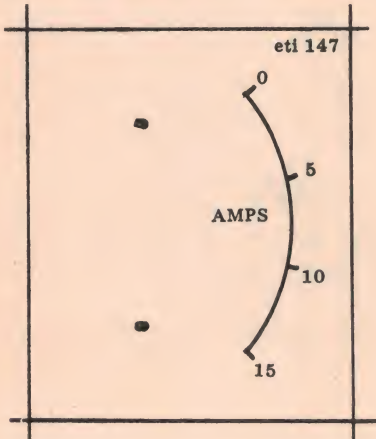0.15 ohm, 5W resistors should be mounted 5 - 6 mm off the pc board to allow free circulation of air.

Check the pc board before wiring it to the case mounted components. Heavy duty, multi-strand hookup wire should be used to wire all high current carrying connections. This includes the collector and emitter leads to Q9, Q10, Q11 and Q12, the lead to the cathode of D2, the


lead from the pc board 'ground' connection to the 'ground' lug on the case, wiring to the fuse and input terminals and to the relay contacts. Heavy lines on the wiring diagram indicate where to use heavy wiring leads. We suggest 32 x 0.2 mm cable as a minimum, preferably something heavier. Remember that it may have to carry as much as 15 amps.


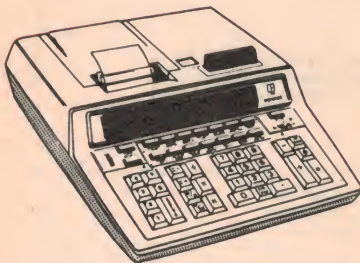
## MONROE




WITH THEIR 67 YEARS OF MANUFACTURING AND MARKETING EXPERTISE BELIEVE THAT THEY DO NOT SELL CALCULATORS — THEY SELL ANSWERS TO COMPUTATIONAL PROBLEMS



WHEN YOU CONSULT WITH YOUR MONROE REPRESENTATIVE YOU GET

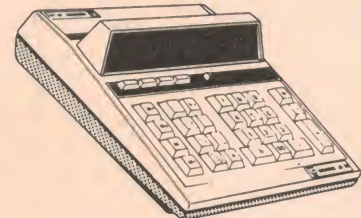- AN HONEST EVALUATION OF THE CALCULATOR MOST SUITED TO YOUR SPECIFIC APPLICATIONS.
- IN-HOUSE TRAINING OF YOUR OPERATORS TO ENSURE CORRECT AND TOTAL USE OF YOUR CALCULATOR.
- TRAINING ON RHYTHMIC TOUCH OPERATION (WITH A CERTIFICATE OF PROFICIENCY) WHICH ENSURES A MANY TIMES SPEEDIER OPERATION.
- 12 MONTHS UNCONDITIONAL WARRANTY AND FULL SERVICE AND SUPPLIES AVAILABILITY.



FOR THE SAKE OF A PHONE CALL WHY NOT CONSULT THE PROFESSIONALS.

## SEEFORTH

SEEFORTH COMPUTER SYSTEMS PTY. LTD

MELBOURNE 437 St. Kilda Road, Melbourne 3004. Phone (03) 26 3341, 267 5371, 267 2269.  
 SYDNEY 1 Angel Place, Sydney 2000. Phone (02) 233 1302.  
 BRISBANE 555 Old Cleveland Road, Camp Hill 4152. Phone (07) 398 8855.  
 ADELAIDE 300 Glen Osmond Road, Fullarton 5063. Phone (08) 79 2275.

CANBERRA Shop 2, Waramanga Shopping Centre, Waramanga 2611. Phone (062) 88 2000.  
 PERTH Suite 5, 12 Davallia Road, Carine Glades 6020. Phone (09) 447 4430.  
 HOBART 106 New Town Road, New Town 7007. Phone (002) 28 5500.

# Get real satisfaction. Build a JostyKit!


(Just arrived from Denmark)

There's a quality of design and innovation in JostyKits that instantly identifies them as Scandinavian in origin. They're created by qualified electronic engineers. They utilise state-of-the-art electronics. Each kit comes with a comprehensive instruction booklet.

For novices and experienced builders alike, JostyKits offer a complete range of electronic gear to give you hours of satisfaction in construction and performance!
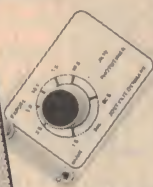
## JK10 AC mains timer unit

Thyristor controlled mains timer. Operates from 2-60 secs. Complete with over-ride switch. Especially useful as photo-timer



**\$25**

## NT 400 lab power supply

For the advanced enthusiast or professional user. 0-40 v. DC. 2-4 amp. series regulated design provides constant, smooth output.



**\$158**

HF65 FM Transmitter 11.00  
M1360 Multivibrator sig gen 500-3000Hz 6.00  
SY340 37W Stereo system 289.00  
SY310 15W Stereo system 230.00

## JK08 light sensitive switch

Great as an automatic Home Sentinel. Switches lights on at sundown-off at dawn. Keeps thieves at bay when you're away!



**\$22**

JostyKits are available now from:

### Sydney:

Custom Communications.  
6 Orchardleigh  
St. Yennora. Ph: 631 3544  
Radio Despatch Service  
869 George St.  
Sydney. Ph: 211 0816.

**Melbourne:** Eastern Communications. 898 Riversdale Rd. Camberwell. Ph: 836 8635.  
Magrath J. H.  
208 Lt Lonsdale  
St. Melbourne.  
Ph: 663 3731

**Adelaide:** Hamtronics.  
Goodwood Rd. Kingspark.  
Ph: 272 8417. Port Adelaide  
International Communications Systems. 75-77 Dale St.  
Port Adelaide. Ph: 47 3688.

**Brisbane:** Delsound. 1 Wickham Tce. Ph: 229 6155.  
**Launceston:** Advanced Electronics. 5A Quadrant.  
Ph: 31 7075. Tasmanian Hi-Fi Company. 87A Brisbane St. Ph: 31 5815.

## Josty Kits

JK01	General Purpose Amp .0.5W	20.00
JK02	Microphone Amplifier	18.00
JK03	Sine Generator 20-20KHz	32.00
JK04	FM Tuner 87MHz to 108MHz	30.00
JK05	27MHz Receiver ch 19	29.00
JK06	27MHz Transmitter & Mod Ch 19	29.00
JK06A	Aerial Hit for JK-06	12.00
JK07	Dual Tone Recorder ro RD Control	29.00
JK08	Light Right for 240-VAC	22.00
JK09	Siren Incl Loudspeaker	18.00
JK10	Photographic timer 240-VAC	25.00
JK101	Burglar Alarm	42.00
JK105	VHF FM Scanner	77.00
AE1	100 mW Amplifier	6.00
AE2	Preamplifier	4.00
AE5	Test Generator	4.00
AF25	Audio Mixer	12.00
AF30	Preamplifier	13.00
AF300	3W Audio Amplifier	25.00
AF310	15W Audio Amplifier	25.00
AF340	40W Audio Amplifier	36.00
AF350	Preamplifier	123.00

AF360	60W Audio Amplifier	66.00
AF380	2W General Purpose Amp	14.00
AT320	AC/DC relay timer	44.00
AT350	2 Amp Triac dimmer	13.00
AT356	6 Amp AC dimmer	28.00
AT357	Touch Dimmer	34.00
AT465	3 Channel Light Show	65.00
AT468	4 Channel Light Show	76.00
B606P	Box for AT-468	29.00
HF305	Converter 175-105MHz to 105 MHz	29.00
HF310	FM Tuner	51.00
HF325	Quality FM Tuner	79.00
HF330	Stereo decoder	25.00
HF385	VHF/UHF Preamplifier	32.00
HF395	Antenna Preamplifier	8.00
HF61	MW Receiver	20.00

# VICOM

Vicom International Pty. Ltd.

68 Eastern Road,  
South Melbourne, VIC 3205.  
Phone 699-6700.

339 Pacific Highway,  
Crows Nest, NSW 2065.  
Phone 436-2766.

Gold Coast 32-2644 Adelaide 43-7981, 272-8417 Perth 321-7609, 446-3232 Cairns 54-1035  
Brisbane 341-5377, 38-4480 Hobart 28-1500 Launceston 44-3882 Wellington (NZ) 69-7625

# ALL ELECTRONIC COMPONENTS

## That's our name . . . that's our game!!!

MAJOR STOCKISTS OF ALL GENERAL RADIO AND ELECTRONIC COMPONENTS

Only "recognised brands" and top-quality components stocked. Resistors (incl. large industrial types) capacitors, semi-conductor devices, switches, meters, valves, metalwork, front panels, plugs, sockets, cable connectors, transformers, speakers, etc. Prompt and efficient attention through our mail order department. Major stockist of all ETI & EA kits — you name it — we will quote.

**ETI AND EA KITSET SPECIALISTS — TOP QUALITY, LOW PRICES**  
**LEARN WHILE YOU BUILD**

### STEREO UNITS

- S1 ETI 484 Compressor Expander
- S2 ETI 482 50 watt per channel Amplifier
- S3 ETI 482A Preamp Board
- S4 ETI 482B Tone Control Board
- S5 ETI 485 Graphic Equalizer
- S6 ETI 480 50 watt Amplifier less H/S
- S7 ETI 480 100 watt Amplifier less H/S
- S8 ETI 480 Power Supply for above
- S9 ETI 443 Expander Compressor
- S10 ETI 444 Five Watt Stereo
- S11 ETI 422B Booster Amplifier including metalwork
- S12 ETI 438 Audio Level Meter
- S13 ETI 440 25 watt Stereo Amplifier including metalwork
- S17 ETI 422 50 watt per channel Amplifier \*
- S18 ETI 426 Rumble Filter
- S19 ETI 429 Simple Stereo Amplifier
- S21 ETI 417 Over led Distortion Monitor
- S22 ETI 410 Super Stereo Sound Source Width Control
- S24 ETI 427 Graphic Equalizer \*
- S25 E.A. Playmaster 10 + 10
- S26 E.A. Playmaster 128 40 watt
- S27 E.A. Playmaster 132 40 watt
- S28 E.A. Playmaster 136 13 watt
- S29 E.A. Playmaster 137 3 watt
- S30 E.A. Playmaster 143 12.5 watt
- S32 E.A. Musicolor 11 1000 w/ch
- S33 E.A. Musicolor 111 1000 w/ch
- S34 E.A. Stereo Dynamic Noise Filter
- S35 ETI 470 60 watt audio amplifier module
- S36 ETI 4000 Series 60 watt stereo amplifier
- S37 ETI 451 Hum Filter for Hi-Fi systems
- S38 E.A. Stereo Infrared Remote Switch
- S39 ETI 455 Stereo Loudspeaker Protector
- S40 E.A. Super-Bass Filter Less Power Pack

### PRE-AMPLIFIERS AND MIXERS

- P1 ETI 445 Stereo Pre-amplifier
- P2 ETI 449 Balance Mic Pre-amplifier
- P3 ETI 414 Master Mixer 8 channel
- P6 ETI 419 Mixer Pre-amplifier - 4 ch. Mixer Pre-amplifier - 2 ch.
- P7 ETI 401 F.E.T. 4 Input Mixer
- P9 E.A. Simple Mixer for Pickup and Microphone
- P10 E.A. Playmaster 145 Mixer
- P11 ETI 446 Audio Limiter
- P12 ETI 471 High Performance Stereo Pre-Amplifier
- P13 ETI 477 Moving Coil Cartridge Preamp
- P14 ETI 474 High to Low Impedance Interface

### RECEIVERS/TRANSMITTERS

- R1 ETI 711 Remote Control Transmitter Switch
- R2 ETI 711R Remote Control Receiver
- R3 ETI 711D Remote Control Decoder
- R4 ETI 711B Single Control
- R5 ETI 711C Double Control
- R6 ETI 711P Power Supply
- R7 ETI 707A 144 MHz Converter
- R8 ETI 707B 52 MHz Converter
- R9 ETI 708 Active Antenna
- R10 ETI 710 R.F. Power Amplifier
- R11 ETI 780 Noise Transmitter
- R12 ETI 703 Antenna Matching Unit
- R14 E.A. 240 Communications Receiver
- R15 E.A. 110 Communications Receiver
- R16 E.A. 160 Communications Receiver
- R17 E.A. 130 Communications Receiver
- R18 E.A. All Wave 1/C2
- R20 E.A. Fremodyne 4 Complete Kit
- R21 E.A. Fremodyne RF Section
- R23 E.A. Mos Fet 52 MHz Converter
- R29 E.A. Short Wave Converter for 27 MHz
- R30 E.A. Simple S.W.R. Meter
- R31 E.A. 27 MHz Pre-Amp
- R32 E.A. 10-30 MHz Pre-Amp
- R33 ETI 718 Shortwave Radio
- R34 ETI 490 Audio Compressor
- R35 ETI 721 Aircraft Band Converter (less XTALs)
- R36 ETI 726 6 or 10 meter Power Amp

### MODEL TRAIN UNITS

- MT1 ETI 541 Model Train Control
- MT2 E.A. 1974 Model Train Control
- MT3 E.A. 1971 S.C.R. P.U.T. Control Unit
- MT4 E.A. Electronic Steam Whistle
- MT5 E.A. Electronic Chuffer
- MT6 E.A. 1978 Train Control

### TEST EQUIPMENT

- TE1 ETI 134 True RMS Voltmeter
- TE2 ETI 135 Phase Meter
- TE3 ETI 533C Digital Display
- TE4 ETI 129 R.F. Signal Generator
- TE5 ETI 130 Temperature Meter
- TE6 ETI 706 Marker Generator
- TE7 ETI 709 R.R. Alternator
- TE8 ETI 122 Logic Tester
- TE9 ETI 124 Tone Burst Generator
- TE10 ETI 123 C Mos Test
- TE11 ETI 116 Impedance Meter
- TE12 ETI 533 Digital Display
- TE13 ETI 117 Digital Voltmeter 1975 Display
- TE14 ETI 117 Digital Voltmeter 1976 Display
- TE15 ETI 704 Cross Hatch Dot Generator
- TE16 ETI 120 Logic Probe
- TE17 ETI 121 Logic Pulser
- TE18 ETI 118 Digital Frequency Meter 1975 Display
- TE19 ETI 118 Digital Frequency Meter 1976 Display
- TE20 ETI 222 Transistor Tester
- TE21 ETI 113.7 Input Thermocouple Meter
- TE22 ETI 107 Wide Range Voltmeter
- TE23 ETI 108 Decade Resistance Box
- TE25 E.A. SWR Reflectometer
- TE26 E.A. R.F. Impedance Meter
- TE27 E.A. Antenna Noise Bridge
- TE28 E.A. 1968 Transistor Test Set
- TE29 E.A. 1971 Transistor (F.E.T.) Tester
- TE30 E.A. 1977 Digital Logic Trainer
- TE31 E.A. 2 1/2 Digit Volt Ohm Meter
- TE32 E.A. Simple Function Generator
- TE33 E.A. Direct Reading Capacitance Meter
- TE34 ETI 487 Real Time Audio Analyser
- TE35 ETI 483 Sound Level Meter
- TE36 ETI 489 Real Time Audio Analyser
- TE37 ETI 717 Cross Hatch Generator
- TE38 E.A. 3 MHz Frequency Counter
- TE40 E.A. Direct Reading Ohm Meter
- TE41 E.A. Function Generator
- TE42 E.A. Transistor Tester incl. Bipolar & F.E.T.S.
- TE43 ETI 591 Up Down Pre-settable Counter
- TE44 ETI 550 Digital Dial (less case) includes ETI 591
- TE45 ETI 144 Expanded Scale R.M.S. Voltmeter
- TE46 ETI 148 Versatile Logic Probe
- TE47 ETI 724 Microwave Oven Leak Detector
- TE48 ETI 150 Simple Analog Frequency Meter
- TE49 ETI 151 Linear Scale Ohm Meter
- TE50 ETI 152 Linear Scale Capacitance Meter
- TE51 E.A. Digital Capacitance Meter
- TE52 ETI 589 Digital Temp. Meter
- TE53 E.A. TV C.R.O. Adapter
- TE54 E.A. Zero Voltage x.s. Heat Controller
- TE55 E.A. XTAL Locked TV Pattern Generator
- TE56 E.A. Decade Resistance Box
- TE57 E.A. Decade Capacitance Box
- TE58 E.A. Capacitor Substitution Box
- TE59 E.A. Tantalum Cap Sub Box

### POWER SUPPLIES

- PS1 ETI 132 Experimenters Power Supply
- PS2 ETI 581 Dual Power Supply (High Powered Version)
- PS3 ETI 712 CB Power Supply
- PS4 ETI 131 Power Supply
- PS5 ETI 119 5 volt switching regulator supply
- PS6 ETI 105 Laboratory Power Supply
- PS7 ETI 111 1 C Power Supply
- PS8 E.A. D.C. Voltage Reference
- PS9 E.A. 1976 Regulated Power Supply
- PS10 E.A. Dual 30-2 0-30V + 2A or 0-60V + 2A or Dual Pos and Neg 30V + 2A
- PS11 E.A. C.B. Power Supply (fully protected)
- PS12 ETI 142 Power Supply 0-30 V 0-15 A
- PS13 ETI 472 Power Supply
- PS14 E.A. Power Supply for Dream 6800
- PS15 ETI 577 Dual 12V supply

### AUDIO TEST UNITS

- AT1 ETI 441 Audio Noise Generator
- AT2 ETI 128 Audio Millivolt Meter
- AT3 ETI 112 Audio Attenuator
- AT4 ETI 102 Audio Signal Generator
- AT5 E.A. A.F. Tone Burst Generator
- AT6 E.A. Laboratory Solid State A.F. Generator
- AT7 ETI 137 Audio Oscillator
- AT8 ETI 138 Audio Power Meter

### MISCELLANEOUS KITS

- M1 ETI 604 Accentuated Beat Metronome
- M2 ETI 546 G.S.R. Monitor (less probes)
- M3 ETI 549 Induction Balance Metal Detector includes wire for search Head
- M4 ETI 547 Telephone Bell Extender
- M5 ETI 602 Mini Organ (less case)
- M6 ETI 544 Heart Rate Monitor
- M7 ETI 544 Two Tone Doorbell
- M8 ETI 043 Heads and Tails
- M9 ETI 068 L.E.D. Dice Circuit
- M10 ETI 539 Touch Switch
- M11 ETI 529 Electronic Poker Machine
- M12 ETI 236 Code Practice Oscillator
- M13 ETI 218 Monophonic Organ
- M14 ETI 701 Masthead Amplifier
- M15 E.A. 1 C Volume Compressor
- M18 E.A. 240 volt Lamp Flasher
- M19 E.A. A/C Line Filter
- M20 E.A. Bongo Drums
- M21 E.A. Keyless Organ
- M22 E.A. Auto Drums
- M23 E.A. Electronic Roulette Wheel
- M25 E.A. Digital Metronome
- M26 E.A. Voice Operator Relay
- M27 E.A. Gas Detector Car Boat
- M28 E.A. Led Chaser
- M29 E.A. Sound Effects Generator \* see below
- M30 ETI 551 Light Chaser 3 channel 1000 watt/ch.
- M31 E.A. Electronic Poker Machine
- M32 E.A. Remote TV Headphone
- M34 ETI 650 STAC Timer
- M35 ETI Wheel of Fortune
- M36 ETI 557 Reaction Timer
- M37 ETI 249 Combination Lock (less lock)
- M38 ETI 814 Dinky Die
- M39 E.A. Electronic Combination lock (including lock)
- M40 E.A. Mast Head Amplifier
- M41 ETI 576 Electromogram
- M42 E.A. Prospector Metal Locator including Headphone
- M43 ETI 561 Metal Locator Less dowel & tubing potplant stand

\*Set as for Steam Train and Prop Plane noise

### VOLTAGE/CURRENT CONTROLS

- V1 ETI 481 12 volt to  $\pm 400$  D.C. 100 watt Inverter
- V2 ETI 525 Drill Speed Controller
- V3 E.A. S.C.R. Speed Controller
- V4 E.A. Stage (etc.) Auto Dimmer 2 K.W.
- V5 E.A. Stage (etc.) Auto Dimmer 4 K.W. & 6 K.W. add on for above
- V6 E.A. 1976 Speed Control
- V7 ETI 592 Light Show Controller (3 ch.) (1000 w/ch)
- V8 E.A. Inverter 12V D/C Input 230V 50Hz 300VA output
- V9 ETI 593 Colour Sequencer (for use with ETI 592)

### PHOTOGRAPHIC

- PH1 ETI 586 Shutter Speed Timer
- PH2 ETI 548 Photographic Strobe (less reflector)
- PH3 ETI 514B Sound Light Flash Trigger
- PH4 ETI 532 Photo Timer
- PH6 ETI 505 High Powered Strobe (less reflector)
- PH7 ETI 513 Tape Slide Synchronizer
- PH8 ETI 512 Photographic Process Timer
- PH9 ETI 515 Slave Flash
- PH10 ETI 540 Universal Timer
- PH11 E.A. 1970 Stroboscope Unit (less reflector)
- PH12 E.A. Syn-a-Slide
- PH13 E.A. Auto Trigger for Time Lapse Movies
- PH14 ETI 558 Mast Head Strobe
- PH15 ETI 553 Tape Slide Synchronizer
- PH16 E.A. Digital Photo Timer
- PH17 ETI 594 Development Timer

### TUNERS

- T1 ETI 062 A.M. Tuner
- T2 ETI 740 F.M. Tuner \*
- T4 E.A. Playmaster 146 AM-FM Tuner \* Wooden Cabinet not included

### AUTOMOTIVE UNITS

- A1 ETI 317 Rev. Monitor
- A2 ETI 081 Tachometer
- A3 ETI 316 Transistor Assisted Ignition
- A4 ETI 240 High Power Emergency Flasher
- A5 ETI 239 Break Down Beacon
- A6 ETI 312 Electronic Ignition System
- A7 ETI 301 Vari-Wiper
- A8 ETI 502 Emergency Flasher
- A10 ETI 303 Brake Light Indicator
- A11 ETI 309 Battery Charger
- A12 E.A. 1970 C.D.I. Capacitor Discharge Ignition
- A13 E.A. High Efficiency Flasher
- A14 E.A. Dwell Meter
- A15 E.A. Variwiper
- A16 E.A. Tacho for Tune-ups
- A17 E.A. Ignition Analyser and Tachometer
- A18 E.A. Strobe Adaptor for Ignition Analyser
- A19 E.A. 1975 C.D.I. Capacitor Discharge Ignition
- A20 E.A. Mains Supply for Car Cassettes
- A21 E.A. Automatic Heavy Duty Battery Charger
- A22 ETI 318 Digital Car Tachometer (less Metalwork)
- A23 ETI 319A Variwiper Mk. 2 (no dynamic braking)
- A24 ETI 319B Variwiper Mk. 2 (for dynamic braking)
- A25 ETI 555 Light Activated Tacho
- A26 ETI 320 Battery Condition Indicator
- A27 E.A. Transistor Assisted Ignition

### GUITAR UNITS

- G1 ETI 447 Audio Phaser
- G2 ETI 413 2 x 100 watt Bridge Amplifier
- G4 ETI 408 Reverberation Unit
- G5 ETI 413 100 watt Guitar Amplifier
- G6 ETI 410 A.D.U. for your Guitar
- G7 E.A. PM 125 50 watt Guitar Amplifier
- G8 E.A. PM 134 21 watt Guitar Amplifier
- G9 E.A. PM 138 20 watt Guitar Amplifier
- G10 E.A. Waa Waa Unit
- G11 E.A. Fuzz Box
- G12 E.A. Sustain Unit
- G13 E.A. PM 135 12 watt Guitar Amplifier
- G14 ETI 452 Guitar Practice Amplifier
- G15 ETI 466 300 watt Amp module - less H/S & Transformer

### COMPUTER AND DIGITAL UNITS

- C1 ETI 633 Video Synchron Board \*
- C2 ETI 632M Part 1 Memory Board V.D.U. \*
- C3 ETI 632P Part 1 Power Supply V.D.U. \*
- C4 ETI 632A Part 2 Control Logic V.D.U. \*
- C5 ETI 632B Part 2 Control Logic V.D.U. \*
- C6 ETI 632C Part 2 Character Generator V.D.U. \*
- C7 ETI 632 Mother Board including P.S. \*
- C8 ETI 632 U.A.R.T. Board \*
- C9 ETI 631-2 Keyboard Encoder \*
- C10 ETI 631 A/Sch. Keyboard Encoder (less keyboard) \*
- C11 ETI 630 Hex Display
- C12 E.A. Educ-8 Computer
- C13 E.A. Cassette Tape Interface
- C14 ETI 638 Epron Programmer
- C15 ETI 637 Cuts Cassette Interface
- C16 ETI 651 Binary to Hex Number Converter
- C17 ETI 730 Getting Going On Radio Tele Type
- C18 E.A. Dream 6800 Computer for Beginners less keyboard and cover

### WARNING SYSTEMS

- WS1 ETI 583 Gas Alarm
- WS2 ETI 066 Temperature Alarm
- WS3 ETI 528 Home Burglar Alarm
- WS4 ETI 702 Radar Intruder Alarm
- WS5 ETI 220 Warning Siren
- WS6 ETI 219 Hee Haw Siren
- WS7 ETI 313 Car Alarm
- WS9 ETI 503 Electronic Thief Trap
- WS10 ETI 506 Infra Red Intruder Alarm
- WS11 ETI 305 Automatic Car Alarm System
- WS12 ETI 582 House Alarm
- WS13 E.A. Electric Siren
- WS14 E.A. 1976 Car Alarm
- WS15 E.A. 10 Ghz Radar Alarm

E. D. & E. (SALES) PTY. LTD., NOW

# ALL ELECTRONIC COMPONENTS

118 LONSDALE STREET, MELBOURNE, VIC. 3000. TEL: 662-3506.

## Measuring very low currents


IT IS NOT POSSIBLE to accurately measure currents of a few microamps or less using an ordinary panel meter or multimeter. In order to make such measurements it is necessary to use an active circuit such as the one shown here. It can be built as a self-contained unit or used as part of an instrument requiring a highly sensitive current range.

This instrument will measure from 100 nanoamps ( $10^{-7}$  amps) to 10 mA full scale, in six ranges. The higher ranges are included so that the instrument may be accurately calibrated and they generally overlap with the lower current ranges on many multimeters.

The meter, M1, is a  $100\ \mu\text{A}$  movement connected as a voltmeter having 1 V full scale deflection. Resistors R10 and R11 (a trimpot) are the 'multiplier' resistors. The trimpot is a calibration control, adjusted to give full scale meter deflection on the 10 mA or 1 mA ranges.

IC1 is an op-amp connected in the non-inverting mode and having a dc voltage gain of about 100 times (set by the feedback network R8 and R1). C2 reduces the ac gain to about unity to improve stability and immunity to stray pick-up. The non-inverting input of IC1 is biased to the 0 V rail by whichever of the range resistors (R2-R7) is selected by SW1. In theory, this gives zero output voltage and no meter deflection, but in practice it is necessary to compensate for small offset voltages using the offset null control, RV1.

Current in the circuit being measured flows into the instrument's input terminals. A voltage will be developed across the selected input resistor, one of R2 to R7. This voltage will be amplified by IC1 and will produce a positive meter deflection. Say the 10 mA range has been selected. The input current will flow through R2. If the input current is 5 mA, say, from Ohm's law, 5 mV will be developed across R2.

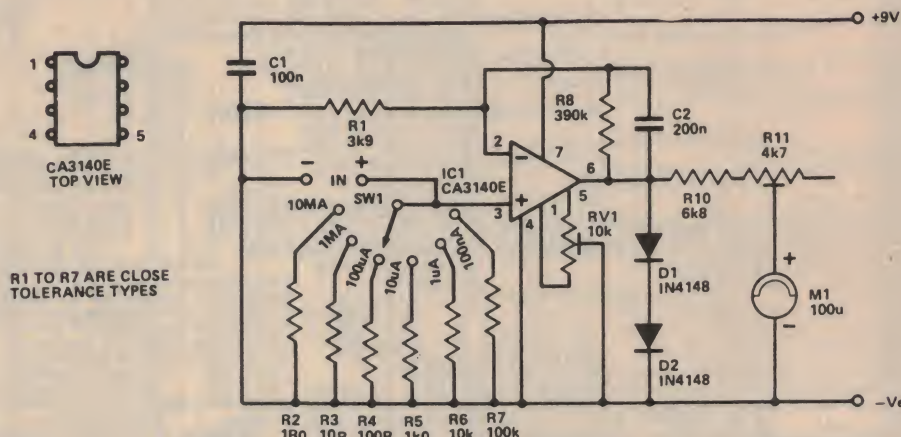

R1 TO R7 ARE CLOSE TOLERANCE TYPES

$$E = I.R$$

$$= 5 \times 10^{-3} \times 1$$

$$= 5 \text{ mV}$$

Now, IC1 has a gain of 100, as

$$\text{Gain} = \frac{R8}{R1}$$

$$= \frac{390 \times 10^3}{3900}$$

$$= 100$$

The voltage at pin 6 of IC1, with 5 mA flowing in the input, will be 500 mV, or half a volt. The meter will thus indicate half scale, giving a reading of 5 mA.

Successive ranges increase the sensitivity of the instrument by a factor of 10.

This arrangement relies on the fact that IC1 (a 3140) has a very high input impedance so that it does not 'load' the input resistor selected and affect the accuracy of the reading by drawing a significant amount of input current itself. The 3140 is a FET-input op-amp having a typical input impedance of 1.5 million megohms. Note that, to achieve reasonable accuracy, the input resistors R2 to R7 and the op-amp feedback resistors should all have a tolerance of 2 % or better.

Meter protection is provided by D1 and D2. Should the input current exceed the maximum for the range, the output of IC1 will rise higher than 1 V. If it exceeds about 1.2 V, the two diodes con-

duct, preventing any further rise in the output of IC1 and protecting the meter from any overload exceeding 20% of the rated input.

When adjusting the offset null control (RV1), start with its slider positioned at the end connected to pin 5 of IC1. The meter should show a strong deflection. Back off RV1 just far enough to zero the meter and no further.

The unit may be calibrated by a number of methods. A simple way is to obtain a variable power supply that will provide 10 V and a 10k 1% or 2% resistor. You will also need either a good mirror-scale multimeter or a digital multimeter.

Connect the resistor and the low current meter in series and connect across the output of the power supply. Also connect the multimeter across the output of the power supply (observe polarities). Select the 1 mA range on the low current meter and a suitable range on the multimeter. Turn the output of the power supply down and switch it on. Set the power supply to give a reading of 10 V on the multimeter. Do this carefully for best accuracy. Now, adjust R11 for full scale deflection. Your low current meter should now be calibrated. If you substitute a 1k, 1% or 2% resistor for the 10k resistor, you can check the calibration on the 10 mA range.

## PARTS FOR NEW KITS

If a kit you want to build is not listed, the parts may be available anyway. Check the Dick Smith Catalogue or call in to your nearest Dick Smith store.

**ACOUSTIC COUPLER** (See EA September)  
Complete kit, including metalwork, etc. Cat K-3605 \$75.00  
Printed Circuit Board only Cat H-8380 \$4.00

**EXPANDED SCALE AUTOMOTIVE VOLTMETER** (See ETI Sept.)  
Printed Circuit Board Cat H-8630 \$1.50  
LM3914 IC Cat Z-6295 \$4.25  
Choose round or rectangular, large or small LEDs to suit your particular application.

**CHASER** (See EA August)  
Complete kit, including front panel Cat K-3145 \$69.50  
PCB only Cat H-8379 \$6.95

**NASA POWER CHOPPER** (See EA August)  
Short form kit (All components & PCB) Cat K-3325 \$16.50  
PCB only Cat H-8378 \$3.00

**LEDS AND LADDERS GAME** (See EA August)  
Complete kit inc. printed panel Cat K-3390 \$15.75  
PCB only Cat H-8378 \$3.00

**LED TACHO** (see ETI August)  
Short Form Kit (includes PCB components etc, but no case - build it into your dash board) Cat K-3240 \$24.50  
PCB only Cat H-8627 \$3.00

**FAST NICAD CHARGER** (See ETI August)  
(All other components in this kit are normal stock lines)  
GUITAR/PA PREAMP (See ETI August)  
Short form kit PCB & components, no transformer or case Cat K-3035 \$29.50

**300 WATT AMPLIFIER** (See EA June)  
Printed Circuit Board only Cat H-8376 \$9.95  
(Most other components are normal stock lines)  
TV CRO ADAPTOR (See EA May)  
Complete Kit Cat K-3080 \$29.95  
Printed Circuit board Cat H-8375 \$3.75

## IT'S A DIALLER! IT'S A CALCULATOR! AND IT'S A CLOCK!

Great for busy executives, secretaries, or even in the home! It remembers 32 numbers for you, and dials them at the push of a button. But it's more than that. It is also a comprehensive memory calculator, and a clock: great for timing those STD & ISD calls!  
Note: although this fits perfectly onto our phone system, present regulations do not permit them to be used in this way.

Cat. X-1176

**\$179<sup>00</sup>**



## ANOTHER TWO NEW STORES NOW OPEN!

We're still expanding! A new store in up-town Sydney (near the Tech & Institute of Technology). And one in the heart of the Northern Beaches. Call in and compare our prices with others in the area!

**818 GEORGE ST  
BROADWAY  
Ph 211 3777**

**531 PITTWATER RD  
BROOKVALE  
Ph 93 0441**



## MAJOR DICK SMITH RE-SELLERS:

**ATHERTON, QLD:** Tabland Radio Service

2 Jack Street, Phone 812 017

**BAIRNSDALE, VIC:** Odyssey Electronics

101 Main Street, Phone 525 262

**BENIOGO, VIC:** Summer Electronics

86 Mitchell Street, Phone 431 877

**BLACKHEATH, NSW:** Goodwin Electronics

123 Station Street, Phone 878 378

**BROKEN HILL, NSW:** Crystal TV Rentals

80 Crystal Street, Phone 6887

**COFFS HARBOUR, NSW:** Coffs Harbour Electronics

3 Coffs Harbour Plaza, Park Ave, Phone 525 684

**DARWIN, NT:** Kent Electronics

42 Stuart Highway, Phone 814 740

**FAIRY MEADOW, NSW:** Trilogy Wholesale Elect.

40 Prince Hwy, Phone 831 218

**GEELONG, VIC:** Electrolux

133 Melop Street, Phone 87 827

**GERALDTON, WA:** KB Electronics & Marine

301 Main Terrace, Phone 212 176

**GOSFORD, NSW:** Tomorrow's Electronics & Hi Fi

80 William Street, Phone 247 246

**HOBART, TAS:** Aero Electronics

123a Bathurst Street, Phone 348 232

**KINGSTON, TAS:** Kingston Electronics & Records

Chemical Court, Phone 298 802

**LAUNCESTON, TAS:** Advanced Electronics

5 The Quadrant, Phone 317 675

**LISMORE, NSW:** Dacre Electric

Cor Magellan St & Brunner Hwy, Phone 214 137

**MACKAY, QLD:** Stevens Electronics

42 Victoria Street, Phone 511 723

**MARYBOROUGH, QLD:** Kallier Electronics

218 Adelaide Street, Phone 214 558

**MORUYA, NSW:** Coastal Electronics

43 Vulcan Street, Phone 742 545

**MT GAMBIER, SA:** Hutcheon's Communications

5 Elizabeth Street, Phone 258 404

**MUSWELLBROOK, NSW:** Silicon Chip Electronics

Suite 3, 88 Bridge Street, Phone 43 1086

**NAMBOUR, QLD:** Nambour Electronic Shop

Shop 4, Lowan House, Ann St, Phone 411 604

**NEWCASTLE, NSW:** Elektron 2000

181 Wharf Road, Phone 282 844

**NOWRA, NSW:** Lyrebird Electronics

50 Barry Street, Phone 25 526

**ORANGE, NSW:** M&W Electronics

48 McNamara Street, Phone 826 481

**ROCKHAMPTON, QLD:** Purely Electronics

15 East Street, Phone 21 058

**SOUTHPORT, QLD:** Amateurs' Paradise

121 Norong Street, Phone 322 844

**SURFERS PARADISE, QLD:** Viking Electronics

3108 Gold Coast Hwy, Phone 322 844

**TAMWORTH, NSW:** Sound Components

78 Brisbane Street, Phone 861 363

**TOOWOOMBA, QLD:** Hunts Electronics

10 Neil Street, Phone 329 844

**TRARALGON, VIC:** Power'n'Sound

16 Franklin Street, Phone 743 838

**VINCENT, QLD:** Tropical TV

240 Fulham Road, Phone 781 421

**WAGGA, NSW:** Wagga Wholesale Electronics

82 Forsyth Street, Phone 454 784

**WALGETT, NSW:** P.J. O'Brien Electronics

82 Woe Woe Street, Phone 243

**WINOSOR, NSW:** Hawkesbury Electronic Centre

111 George Street, Phone 773 411

**WOONGA, VIC:** A & M Electronics

78a High Street, Phone 244 508

**WYALLA NORRIE, SA:** Moller Enterprises

Shop 2, Forsyth Street, Phone 454 784

## DON'T FORGET: ONLY 11 WEEKS TO CHRISTMAS!!!

Need a few ideas for someone into electronics? Go no further than your nearest Dick Smith store!

## LOWEST PRICE EVER!

### 16K MEMORY UPGRADE KIT SUITS ALL COMPUTERS!!!

Fast (256Kb) 4116 memory IC's for updating any microcomputer to 16K (or to 32K or 48K)

Complete with instructions for fitting - a huge saving over our previous price!

**WAS \$149 ONLY 12 MONTHS AGO!!**

**\$59<sup>95</sup>!!!**

Cat X-1186

### BE QUICK FOR THIS



**FM TOO!**

**\$149 \$129**

Cat. A-6480

Update your car sound - and save! This superb FM/AM/Car cassette is now \$20 off: you reap the benefit of Dick's bulk buying! Easy to fit (fits in standard dash opening). Here's your chance to own a superb car sound system at a bargain price! (Speakers extra).

### GREAT GIFT IDEA...

It's the greatest teaching aid since the book! Children not only learn to say the words, they learn to spell them as well! Amazing microcomputer technology actually creates the sounds: no tapes! And with the plug-in modules (optional) the range of the speak-and-spell is greatly increased!

**\$79<sup>50</sup>**

### NEON TEST S DRIVER

You've often wondered if a circuit is live... Find out with this neon test screwdriver. If it has mains voltage applied to the tip, the neon lights. The rest of the time it's a handy screwdriver!

**ONLY \$1<sup>00</sup>!!**

Cat T-4005



### NEED A SAFE AC SUPPLY FOR YOUR PROJECTS?

Now about 12 volts at 500mA!!!



**\$9<sup>50</sup>**

Cat M-9555

Most plug-packs give you around 200mA. This one gives 500mA! The reason: it's ALL transformer. You put the rectifiers, capacitors, etc. in the project; and plug in the AC supply. It's a great space saver!

### WAVE A FLAG

What's an electronic stars selling flag for, you ask? Dick couldn't buy one himself, so he thought 'I'll fix that!' Show your Aussie spirit and fly your own flag. 1 metre long.



**\$9<sup>95</sup>**

Cat X-1001

### OUR PIECE DE RESISTANCE

YES! We now have good stocks in all values of our famous 1% metal film high quality resistors. These used to sell for around 35c each: look at our price!

They're great for all close-tolerance uses, and we have sufficient quantities to suit the OEM as well as the design lab, the technician and the hobbyist!

**5c**

(per 100 up of some value)

## Playmaster Graphic Equaliser

A Playmaster Graphic equaliser in your hi-fi system will make so much difference you won't believe it! The graphic equaliser can boost or cut various bands of frequencies over the entire audio spectrum, allowing you to adjust the sound to make up for system deficiencies; or to make the sound the way YOU like it. If you want deep bass, you've got it. If you want high highs, you've got it! A graphic equaliser in your system can make it sound like one costing twice as much!

The kit is very easy to build, and perfectly suits practically all hi fi amplifiers.



**\$99<sup>50</sup>**

Cat K-3800

THE PERFECT ADD-ON TO ANY HI-FI SYSTEM!

TIMBER SLEEVE SHOWN IS OPTIONAL. (Cat H-3113 @ \$8.50)

DON'T WANT TO MAKE THE KIT? SEE THE BUILT-UP MODEL AT RIGHT!

## Playmaster Graphic Analyser

• ALSO DOUBLES AS A PEAK LEVEL METER!



**\$99<sup>50</sup>**

Cat K-3510

GET THE MOST FROM YOUR SOUND SYSTEM!

TIMBER SLEEVE SHOWN IS OPTIONAL. (Cat H-3113 @ \$8.50)

Like the horse needing the cart, the graphic analyser needs a graphic analyser. This remarkable piece of equipment allows you to obtain the maximum performance from your graphic equaliser by setting the system up to suit the room and furniture exactly. You've probably noticed if you move your speakers around the room they sound different: the graphic equaliser can take care of this, but the graphic analyser tells the equaliser what to do! And when you've set up your system, the graphic analyser isn't wasted: flick a switch, and it becomes a superb peak level reading meter - a mini light display playing along with your music!

## DICKSMITH ELECTRONICS

### BUYING BY MAIL?

**ORDER VALUE:**  
\$5 (min) to \$9.99 \$1.00  
\$10.00 to \$24.99 \$2.00  
\$25.00 to \$49.99 \$3.00  
\$50.00 to \$99.99 \$4.00  
\$100 or more \$5.00

NOTE: These charges apply to goods sent by post in Australia only. Large and bulky items cannot be sent by post.

If you prefer, we will dispatch your order by Comet Road freight to anywhere in Australia for only \$5.00 - that's below what it costs us! Large and bulky items are normally sent by Comet unless you specify differently (eg by rail or air - you pay freight on delivery).



399 Lonsdale Street  
Ph (03) 87 9834



656 Bridge Road  
Ph (03) 428 1614



168 Logan Road  
Ph (07) 391 8233



842 Gympie Road  
Ph (07) 59 6255



98 Gladstone Street  
Ph (082) 80 4944



60 Wright Street  
Ph (08) 212 1962



414 William Street  
Ph (09) 328 6944

## DICK SMITH'S GUIDE TO SORCERER BASIC & SYSTEM 80 BASIC

**NEW!**

**\$9.95 EACH**

Yes - you asked for them, so here they are. Written in language anyone can understand, and they start at the basics (like how to turn it on). Now there are two books, similar in content, but each written specifically for its own computer system. The first is for the superb Exidy Sorcerer, the second is for the incredibly popular Dick Smith System 80 (but it also applies to the TRS-80). If you don't know what a computer is help about, then these books will help you understand.



## TOO NOO COMPOOTER YEARBOOKS

From Elect. Aust. MICROPROCESSORS & PERSONAL COMPUTERS  
112 pages of data on computers, allied equipment, etc. plus background info.

**\$5.00**

From Elect. Today Int. Computers and Computing Yearbook  
154 pages, with system reviews, projects to build etc. plus glossary, technical tips, market guides, etc.

**\$4.95**

**HUGE RANGE OF OTHER COMPUTER BOOKS IN STOCK. JUST ASK!**

## PROGRAMMERS

**WANTED:** Free-lance programmers familiar with TRS-80 level II BASIC to write customised software packages for us.

If you are a Uni. student, tutor, lecturer, computer programmer, professional person or a microcomputer buff and you own a System 80 or TRS-80 and enjoy programming in BASIC, why not take this opportunity to make some extra money in your spare time by writing various software for us?

Give us a call: you have nothing to lose, but plenty to gain.

Call Mark Sim. on (02) 888 3200

## CAN YOU BELIEVE IT?

A 3 channel, digital proportional radio control system, complete with servos, and it's less than \$100!

That's right: compare this little beauty with similar models elsewhere. You get the transmitter, receiver, battery pack and three servos, as shown, for less than \$100!! We've never seen these for less than \$150.00 before! It's the ideal system for model planes, boats, cars, etc. etc.: each channel is individually proportional controlled and has a preset position on the transmitter to allow for trimming, mechanical wear, etc. Our initial shipment is limited, so hurry in for this if you're at all interested in radio control (or would like to be!)

**AND THE PRICE? JUST \$99.00!!!!**

## COMPUTER MAINS FILTER

Don't lose that important program through mains spikes. This filter effectively smooths the mains supply, resulting in less 'crashes'. A must for all serious computer users; businesses, etc.

**\$75**

## More of Dick's BONZA BULK BUY BARGAINS: BEWDY!


We admit it: we blew it! A mistake on our order has left us with rad faces: and a couple of thousand wrong switches! We can't send them back, so we've slaughtered the price just to get rid of them! They're five position, single pole switches, which can also be used as two, three or four position: just ignore the extra positions. They would normally sell for around \$1.50: look at the price now! Thousands of hobbyist users - buy now while stocks last!

**\$55c!**

## A 15MHz DUAL BEAM CRO FOR ONLY \$638?

Yes! This superb Hitachi 15MHz CRO offers dual beam capability, high (1mV/div) sensitivity, X-Y operation, trace rotation, Z-axis input, 10x sweep magnifier, and five modes of vertical deflection operation! It's a superb piece of craftsmanship; way ahead of its opposition!

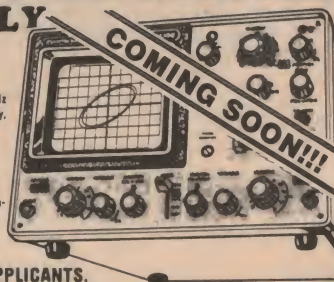**TERMS AVAILABLE TO APPROVED APPLICANTS.**



## NEW RANGE OF SOUND CARE EQUIPMENT JUST ARRIVED!

You asked for it: so here it is! Economy sound care equipment that will do a really professional job on your records and cassettes. Something for everyone, at a bargain price!

Cassette winders, labels and reel locks. Cat. C-7088  
Cassette head care kit. Cat. C-7088  
Cassette head demagnetiser and cleaning fluid. Cat. C-7080  
Deluxe record cleaner. Cat. C-7082  
Deluxe record cleaning arm and brush. Cat. C-7084

**\$2.95 \$2.95 \$4.50 \$3.95 \$4.95**

## WOTTA BARGAIN!

We've just bought a HUGE shipment of these incredibly popular push button telephone dials in - as our cart has dropped. You reap the benefit of Dick's huge bulk buying power! Simply substitute for any rotary dial. Although these units fit perfectly into standard Aust. phones (no soldering required) current regulations do not allow you to use them for this purpose.

**NOW: \$39.50**

**\$49.50**

How's this for a bargain: a superbly made 4PDT relay with 12 volt (185 ohm) coil at near half price! Yes, hundreds of uses for the professional, the hobbyist and the experimenter. And for 10 or more, the price drops to just \$2.50 - incredible! Cat. S-7000

**\$2.90**

Unbelievable price: Famous quality Memorex reel-to-reel tape at pre-1974 prices! Yes, 2400 ft Memorex tape on 7" reel, in box, for around 1/3 off current price - making it ideal for bench work or the toolbox. While stocks last. **\$9.95!**

Cat. C-3406

## BIG PRICE CUT ON 5 1/4 IN DISKS

High quality 5 1/4 inch (sorry, Matric conversion board!) diskettes for all disk drives at a new low bargain price. Both hard and soft sector; with huge savings for quantity buyers, too! And they're now in stock: so hurry before you miss out! Hard Sector: Cat. X-3505 (Suit Microp. type) Soft Sector: Cat. X-3510 (Suit Partec type)

**WERE \$5.95 EACH - NOW: 1 TO 10: \$4.95! 10 TO 100: \$3.95! OVER 100: \$3.50!!!**

## INCREDIBLE QUALITY SOUND from such a tiny speaker!

You'll find it hard to believe that such good sound can come from such a small speaker! They're ideal for cars, vans, boats etc. and, of course, for extension speakers around the pool, in the rumpus room, etc. etc. They're made of heavy aluminium, with a tweeter and a woofer in each enclosure. Yet the size is only 120 x 120 x 190mm! They come complete with mounting brackets and spring-loaded connecting terminals. Check them out soon!

**\$99.50 pair**

Cat. A-2375

## Dear Customers,

Quite often, the products we advertise are so popular they run out within a few days. Or unforeseen circumstances might hold up goods so that advertised lines are not in the stores by the time the advert appears. Please don't blame the store manager or staff: they cannot solve a dock strike on the other side of the world, or even locate a shipment that has gone astray. What we are trying to say is that, if you're about to drive across town to pick up a particular line at a Dick Smith Store, why not give the store a ring first (addresses and phone numbers below) ... just in case! Thanks.

**Dick Smith and Staff**

## TOP VALUE MAINS IRON

Dick's own 240V fully approved mains soldering iron. Supplied with free solder sample, great value for hobbyist & technician alike. 25W rating.

**COMPARE OTHERS AT \$14 AND MORE!!! OURS: \$9.75**

**\$9.75**

T-1300

## DICK'S ZIPPYS ARE BEST

Dick Smith Zippy Boxes are unique: they're the ones with slotted sides allowing for easy mounting of pcb's, etc. Inset on them!

**COMPARE OTHERS AT \$14 AND MORE!!! OURS: \$9.75**

**\$9.75**

T-1300

## GRAPHIC EQUALIZER WITH LED LEVEL DISPLAYS

Music sound a little dead? Listen it up with a graphic equalizer. Also has twin LED VU meters for a superb effect! You really won't believe the difference a graphic equalizer can make to your sound system until you try it out!

**\$169.00**

**LIKE TO BUILD YOUR OWN? SEE OPPOSITE PAGE!**

## DIRECT DRIVE TURNTABLE: UNDER \$200.00!!!

Incredible! A true direct-drive turntable offering outstanding performance: complete with a Shure magnetic cartridge and housed in a deluxe plinth with clear acrylic cover - and it's less than \$200!!! Records are getting very expensive these days: they deserve the best treatment. Give it to them with a direct drive turntable: you won't be disappointed!

**\$199.00**



Cat. A-1850



Cat. A-3078

## PLAY IT SAFE: INSTALL AN ALARM!

This two sector alarm control module gives you an edge over the crooks; and these days, you need one! Easy to install, extremely reliable in operation. Accepts all standard detecting and sensing devices (reed switches, trap switches, fire detectors, motion detectors, etc. etc.). Why wait until you have been burgled? Fit an alarm now and beat the burglar! Cat. L-5055

**\$49.50**

**LARGE RANGE OF ALARM SENSORS ALWAYS IN STOCK: DESIGN YOUR OWN SYSTEM!**

**\$49.50**

## THE BARGAIN OF THE CENTURY! dbx BOOM BOX:



**LESS THAN HALF PRICE!**

**NOW ONLY \$125.00!!!!**

**(STRICTLY LIMITED STOCK)**

First question: What is a 'Boom Box'? The Boom Box is aptly named: it is a sub-harmonic synthesizer which connects to your stereo system. It electronically synthesises another octave below the lowest notes in the music, resulting in a base note you've got to feel to believe! It adds a whole new dimension to your hi fi sound!

The bad news was that these remarkable devices sold for well over \$300.00 each!

Now for the good news: Dick Smith has made a scoop purchase of manufacturer's distress stock! You can save \$200 on the normal retail price ...

**NOW ONLY \$125.00!!!!**

**(STRICTLY LIMITED STOCK)**

Cat. A-1750

Please note: If you don't know whether or not you want a Boom Box at this crazy price, please don't buy one! There are so many people who definitely will want them, we won't have enough to go around!

## NEW! AF & RF WIDEBAND SIGNAL GENERATOR

Here's a great new test instrument for the hobbyist and the professional. It's a wideband AF & RF signal generator offering sine and square wave capability from 10Hz to 200MHz in 6 ranges (AF 10Hz to 220kHz; RF 100kHz to 50MHz in fundamental, 50 to 200MHz in harmonics). It is solid state for reliability and light weight (240V operated) - making it ideal for bench work or the toolbox. Another Dick Smith quality import. Cat. C-1305

**ALL THIS FOR ONLY \$149.50**

**WOULD YOU LIKE TO WORK WITH US?**

Dick Smith Electronics is expanding - if you've been watching your local press you'll probably have noticed this already! Opening new stores requires new staff. Good staff. Electronics enthusiasts who can be trained to become professional sales people and managers.

If you're talented and enthusiastic, we offer good wages and conditions. If you're above average, promotion can be very rapid. (One of our salesmen became general manager three years later!)

No matter what area you live in, if you'd like to work with us, drop us a line. When we open a store in your area, we'll be in touch ...

Send your application to: The Personnel Manager, Dick Smith Electronics Pty Ltd PO Box 321, North Ryde, NSW 2113

# DICK SMITH ELECTRONICS


<b>SYDNEY</b>  125 York Street Ph (02) 290 3377	<b>GORE HILL</b>  162 Pacific Hwy Ph (02) 439 5311	<b>CHULLORA</b>  147 Hume Hwy Ph (02) 842 8922	<b>PARRAMATTA</b>  30 Grove Street Ph (02) 683 1133	<b>BLAKEHURST</b>  613 Princes Hwy Ph (02) 546 7744	<b>WOLLONGONG</b>  263 Keira Street Ph (042) 28 3800	<b>MAIL ORDER AND SERVICE CENTRES:</b> Cnr Lane Cove & Waterloo Rds, North Ryde NSW 2113 (Monday to Friday, 9AM to 5PM only) SHOPS OPEN: 9AM TO 5.30PM MON. TO FRI. 12 NOON SATURDAY (Brisbane 1/2 hour earlier)
--	---	---	--	--	---	---



# Turn and hazard indicator for your vehicle
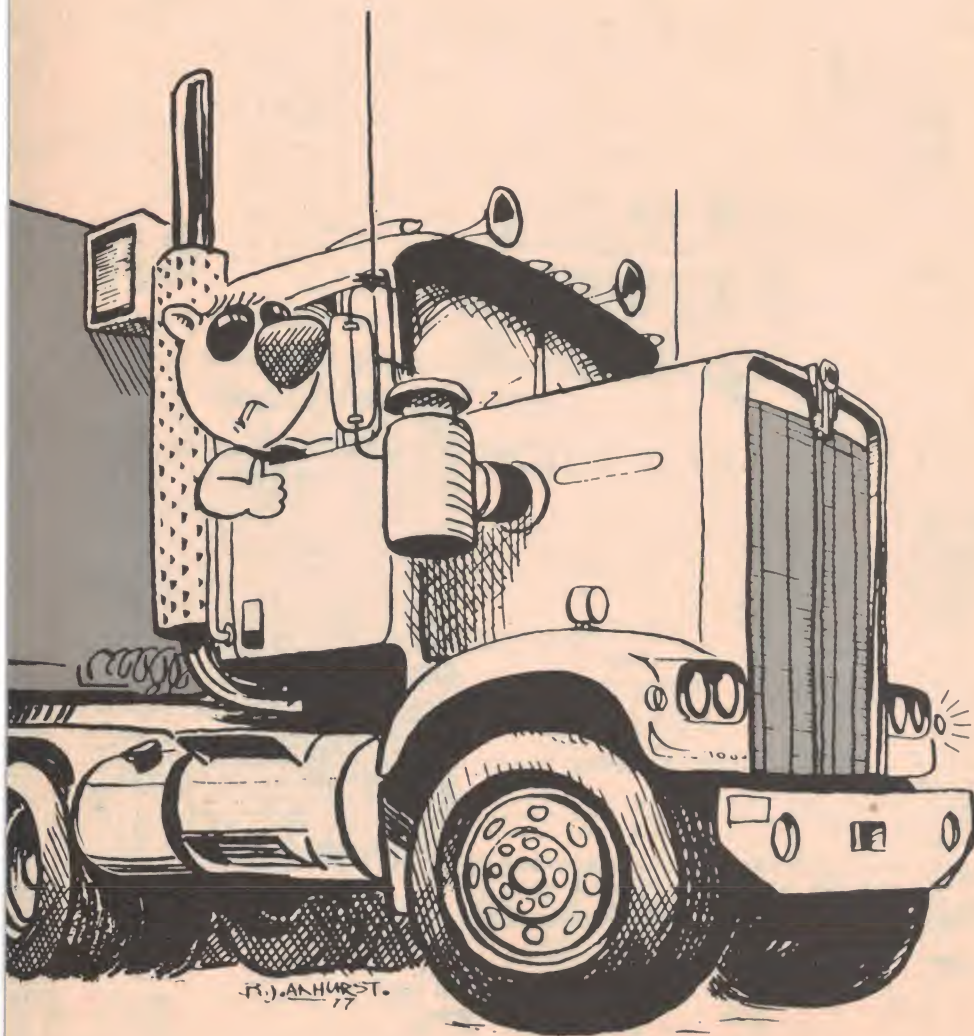
## Staff

This 'electronic flasher' is a great improvement on the electromechanical flashers fitted as standard equipment on most cars. It features a stable flash rate, high reliability and the ability to drive up to 144 watts worth of indicator lamps!




IF YOUR CAR was made before 1960 it probably doesn't have any kind of indicators, but all cars built after that date are fitted with turn indicators of some sort and post-1970 models have hazard flashers too. However, the conventional bimetallic strip flashers fitted to nearly all cars have a few shortcomings which we have attempted to overcome with our new solid state unit.

The bimetal flashers give only a weak sound indication, which can easily be drowned out by general vehicle noise. They are especially difficult to hear if the ravages of time (or uproarious living, or overindulgence in very loud music etc.) have left you with less than perfect hearing. Another disadvantage of conventional units is that they cannot cope with the extra power drained by the turn/hazard indicators on a trailer or caravan. Also the flash rate of bimetallic units is preset by the manufacturer and cannot be adjusted to compensate for drift caused by battery voltage variations and ageing of the metal strip.

Our solid state flasher connects easily to the car's wiring and is designed to completely replace the existing bimetal unit. It can handle up to 12 amps, which allows it to drive a substantial load (up to 144 W at 12 V). The flash rate will remain substantially the same through-

# turn/hazard flasher

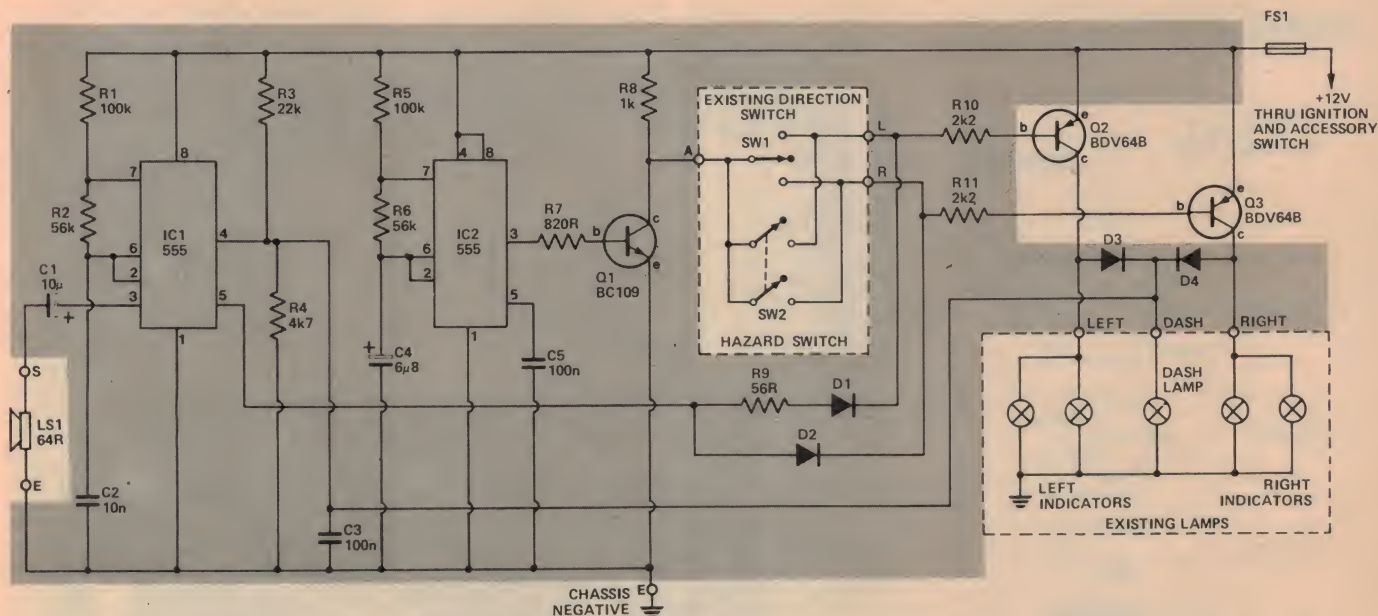

## HOW IT WORKS — ETI 327

The flasher consists of a low frequency oscillator, IC2, producing a pulse at about one Hertz, driving either or both of two Darlington output transistors, Q2 and Q3. These switch the vehicle's battery to the turn indicators and dash light. An audio oscillator, IC1, gives an audio tone through the speaker at a different frequency for left, right and hazard.

The output of IC2 (a 555) gives the flash frequency. The frequency and duty cycle (on to off time) are set by the values of R5 and R6 and can be made variable by substituting trim pots for these two resistors.

The pulses from IC2 are fed to an inverter, Q1, and then to the vehicle's turn and hazard switches. If the vehicle doesn't have a hazard switch, one can be added. Transistors Q2 and Q3 are Darlington output transistors used here for their very high current gain. Darlington transistors have two transistors in the one package in a gain multiplication configuration.

The pulses are fed to either of the Darlington transistors for turn indication, or to both for the hazard indication. The transistors switch the battery to the appropriate indicator lights on the vehicle.

The dash light is illuminated through D3 and D4 whenever either of the Darlington transistors are turned on.


IC1 is an audio oscillator with a variable frequency controlled by the voltage on its control input, pin 5. This pin is tied to the bases of Q2 and Q3 through D1, D2 and R9 in such a way that the oscillator gives a different tone for left, right, and hazard. The oscillator is enabled by the voltage on pin 4 which is normally held low through the dash light. When the dash light turns on pin 4 goes high and the oscillator starts, beeping in time with the flash of the indicators.

out the life of the unit. A special feature is that it provides an audio tone whose pitch is different for each of the three modes — 'left turn', 'right turn' and 'hazard'. If you want to alter the flash rate, two of the fixed resistors can be replaced by trimpots to allow variation of the frequency and duty cycle.

The flash rate is determined by a 555 timer IC, whose output is routed through the car's turn indicator switch on the steering column and turns one of two Darlington power transistors on and off. These transistors are actually



two transistors connected in the same package in such a way as to provide a very high current gain. This allows them to be operated with a low base drive current to switch quite high currents, making them ideal for this application.

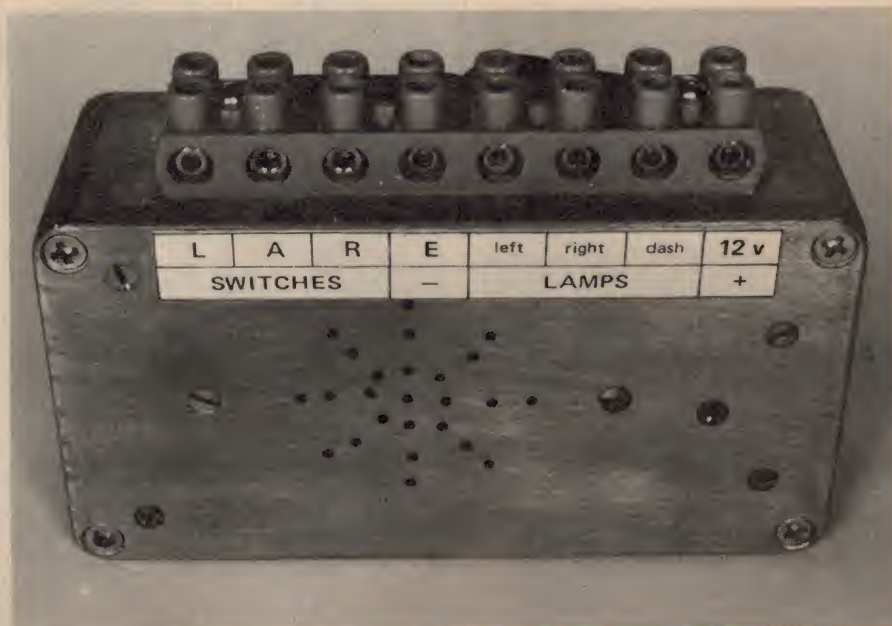A second 555 IC is used as an audio oscillator to drive a small loudspeaker. This oscillator is held off until one of the Darlington transistors is turned on and then turns on and off in time with the Darlington, producing a beeping sound which is synchronised to the flashes. ▶



# Project 327

## COMPONENT PINOUTS

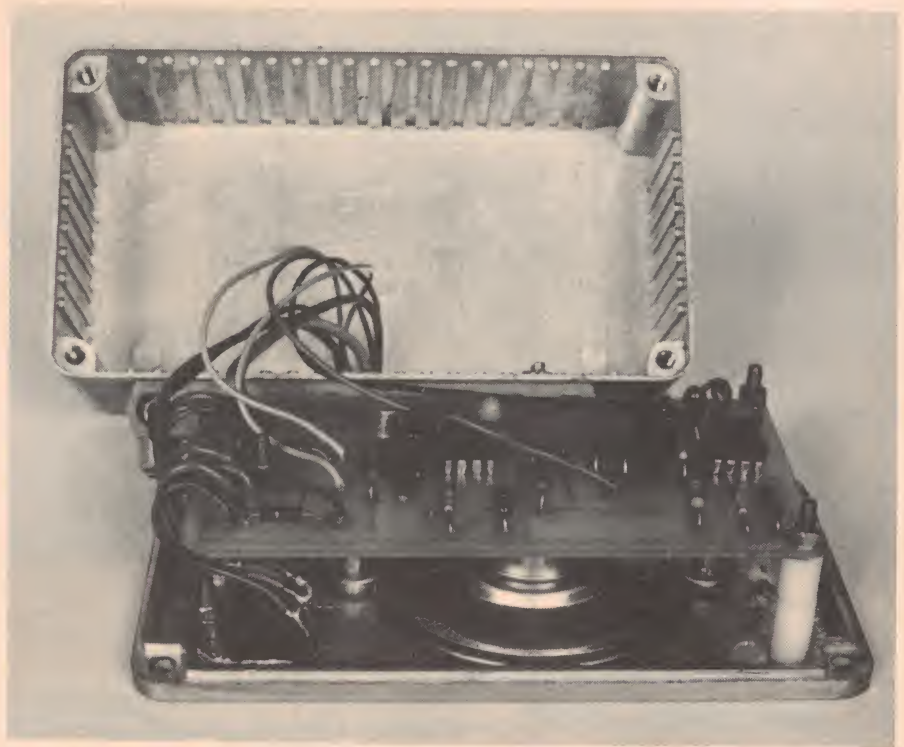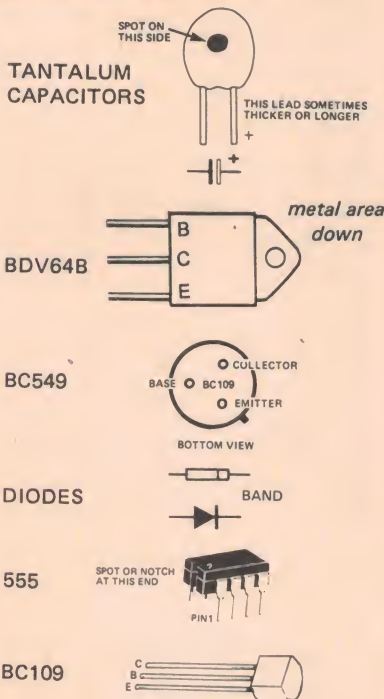

Our unit was assembled into a diecast box using standoff pillars to support the pc board. If you use an 8 ohm or 16 ohm speaker with a series resistor, the value of the resistor may be varied to alter the speaker volume. With a high impedance speaker, a suitable value resistor may be inserted in series to lower the volume. Try 100 ohms as a start.

## Construction


Since the unit is designed to operate inside a car it should be made as rugged as possible. Our prototype was constructed in a diecast aluminium box which doubled as a heatsink for the switching transistors.

Connection to the vehicle's wiring is made via a terminal strip mounted along the outside of the box. The speaker and the pc board are mounted inside the lid of the box to facilitate wiring.

Start by mounting the resistors and non-polarised capacitors on the pc board. Next mount the two tantalum capacitors, the diodes, the ICs and the transistor, paying particular attention to their orientation.

If you wish to vary the flash rate and the duty cycle, the two timing resistors R5 and R6 can be replaced by trimpots as the pc board has been designed to accommodate either trimpots or fixed resistors. Drill holes in the lid of the box for the pc board, the Darlington transistors and the speaker. We drilled a series of small holes in front of the speaker but this may not be necessary in some circumstances because the sound from the speaker is quite loud.

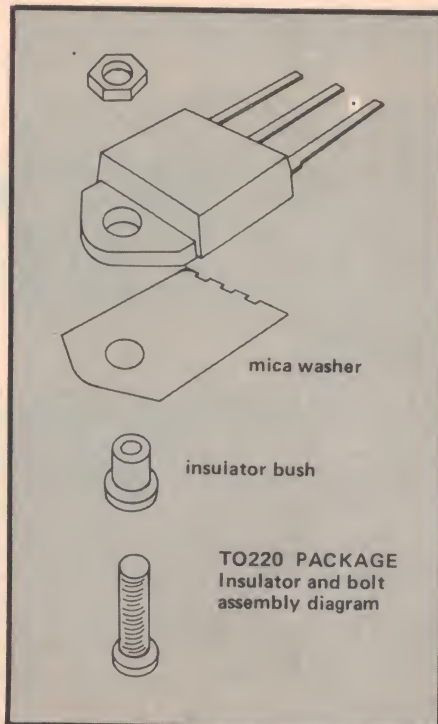The two Darlington switching transistors are mounted on the lid of the box




as shown in the photo of the prototype. The cases of these transistors are connected to the collectors and must therefore be insulated from the diecast lid. Mount the transistors using a mica or plastic insulator and plastic sleeves as shown in the diagram. Use an ohmmeter to check that there is an open circuit between the collectors and the diecast lid after the transistors are mounted.

Mount the loudspeaker on the lid, using nuts and bolts with two large washers clamping the edge of the speaker against the lid. If you have an eight ohm speaker you can use that instead, if a 47 ohm, ½ watt resistor is connected in series with one of the speaker leads.

Solder all the connecting wiring from the pc boards and Darlington transistors, using heavy gauge wire to the emitters and collectors of the transistors. Then mount the pc board on 20 mm standoffs above the speaker and transistors. Connections to the car's electrical system are made via a length of screw terminal strip with the wires to the pc board run through a grommet in the side of the box.

# turn/hazard flasher

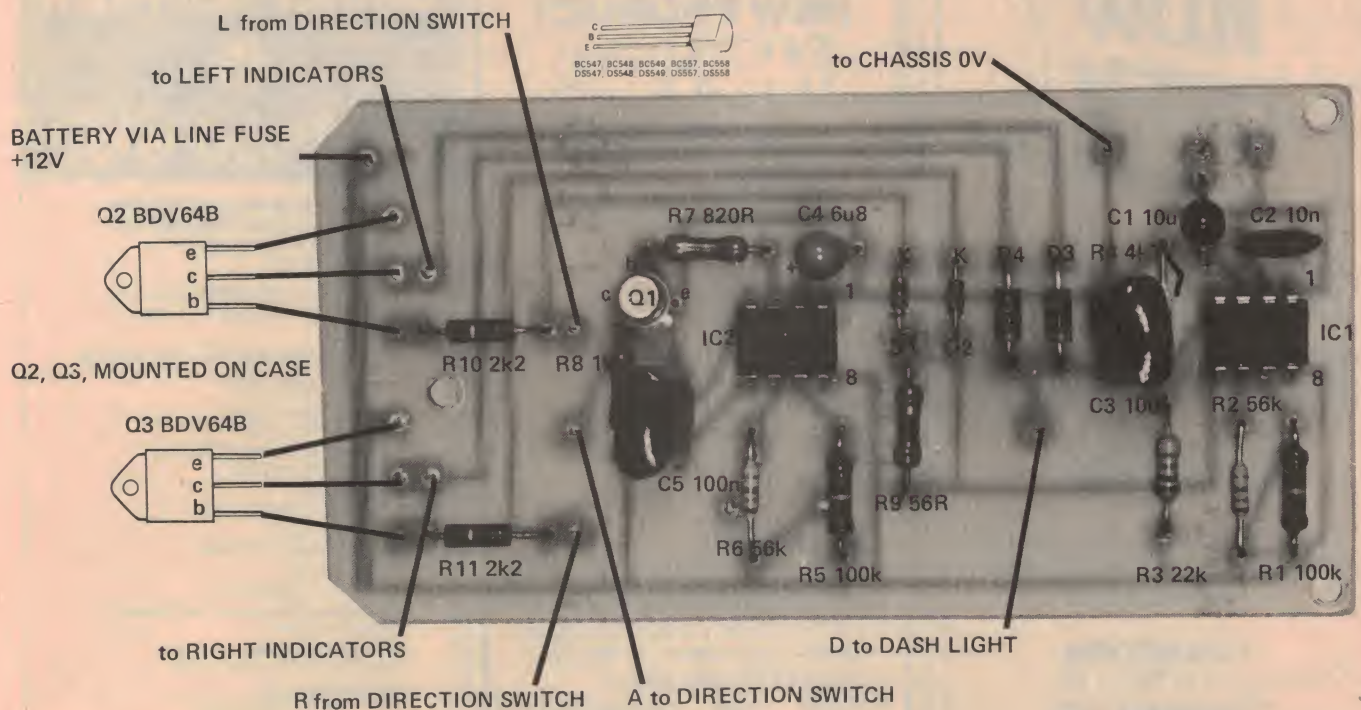

Component overlay and external component connections.

NOTE: The printed circuit board artwork is reproduced on page 113.

## Installation

The flasher unit can be installed in any convenient position under the dash within earshot of the driver. However, it is not a good idea to mount it near the output pipe of the heater as it could get quite hot there. The connection to the battery can be taken from the battery terminal through a 10 A line fuse, or from the accessories position on the ignition switch. This way the hazard flasher can still be used with the engine turned off.

If your car is too old to have turn indicators you can mount a double pole switch on the steering column and run

wires under the dash to the unit. You can buy switches with long lever extensions which are ideal for the purpose. The hazard switch should be a push-off/pull-on type (to avoid accidentally knocking it on) and can be mounted in any convenient position on the dash with the dash turn indicator.

External lights are easily mounted and are available from motor accessory stores. Make sure the connection from the light to the chassis is good. If in doubt, run a wire from the light case chassis connection to a good chassis contact point on the vehicle or direct to the battery negative terminal.

## Flashers and the Law

Flashing turn and hazard indicators fitted to motor vehicles must comply with Australian Design Rule No. 6 (ADR 6), whose provisions are summarised below.

- Colour: Rear and side flashers must be amber or orange.  
Front flashers on Australian-made vehicles must be orange; on imported vehicles they may be orange or white.
- Flash Rate: Not less than 60 and not more than 120 flashes per minute.
- Duty Cycle: Not specified.

## PARTS LIST — ETI 327

Resistors	all ½W, 5%
R1	100k
R2	56k
R3	22k
R4	4k7
R5	100k or 250k min. trimpot.
R6	56k or 100k min. trimpot.
R7	820R
R8	1k
R9	56R
R10,R11	2k2

### Capacitors

C1	10u/25V tantalum
C2	10n greencap
C3,C5	100n greencap
C4	6u8/25V tantalum

### Semiconductors

D1,D2	1N914, 1N4148 etc.
D3,D4	1N4001, A14A etc.
Q1	BC549, BC109 etc.
Q2,Q3	BDV64B Darlington transistor

### Miscellaneous

SW2	DPDT toggle switch
LS1	small, high impedance speaker (48-80 ohms) or eight ohm speaker with 47R series resistor.

ETI-327 pc board; line fuse with 10 amp fuse; diecast box to suit (65mm x 120mm x 40mm); eight-connector barrier strip.

# NOW OPEN

## DAVID EAST COMPONENT CENTRE

33A Regent Street, Kogarah NSW  
(Opposite Kogarah High School)  
Phone 588-5172

### RESISTORS

1/4W — 5c. 1 W — 8c. PW5's — 45c.

### TRANSISTORS

BC 107, 108, 557, 558 — 33c. BC 559 — 30c. BC 547, 548 — 25c. BC 549 — 27c. BC 109 — 36c. BD 139, 140 — 95c. BC 639, 640 — 75c. 2N3055 (Motorola type) — \$1.30.

### SEMICONDUCTORS

4001, 4011 — 40c. 4016 — \$1. 4017 — \$1.75. 7400, 7402 — 45c. 7490 — \$1. 74C00, C02 — 50c.

### DIODES

IN914 — 5c. IN4004 — 8c. IN4007 — 18c.

### REGULATORS

7805, 12, 15 — \$1.25. 7905, 12, 15 — \$1.75.

### SCR's

C103B (200V, 800 mA) — \$1.16. C106DI (400V, 4A) — \$1.08. C106YI (30V, 4A) — 70c. C122E (500V, 8A) — \$2.56.

### TRIACS

SC14ID — \$1.28

### DIACS

ST2 — 38c.

### BRIDGE RECTIFIERS

All 400V, 1.5 amp to 30 amp.

### POTS

Single gang log and linear: 500R-1M — 75c. Trim-pots — 39c. Cermet, Vert & Horiz — 42c.

### LED's

5 mm Clear and Diffused Sankin Type. Red — 22c. Green and Amber — 31c.

Also a large range of capacitors, Electrolytics, Greencaps, Tag Tantalums.

All first quality components  
at prices you CAN afford.



## PLESSEY COMPONENTS NEW PRODUCT

# NOVOL


NON VOLATILE  
LOGIC  
256 BIT MEMORY  
(64 x 4)

### MN9210

- Electrically alterable
- Non-volatile memory
- MNDS technology (not NMDS)
- plus 5 V minus 12 supply
- Low current programming supply minus 39 V
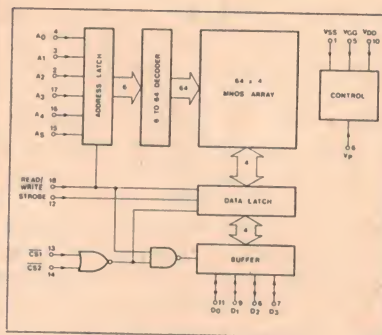
### FEATURES

- Guaranteed data retention of one year in the absence of applied power.
- Latching data and address inputs.
- Three-state outputs on data lines.
- TTL/CMDS compatibility.
- Single word preprogramming facilities.
- Temperature range minus 40 degrees C plus 70 degrees C.
- 18-pin dual-in-line package.



This is a new addition to our existing range of Novol.

MN9102 — 4 bit data latch  
MN9105 — 4 decade BCD counter  
MN9106 — 6 decade UP counter  
MN9107 — Counter to 100 hours  
MN9108 — Counter to 10,000 hours.



## PLESSEY COMPONENTS

PO BOX 2, VILLAWOOD,  
NSW 2163.  
PHONE: (02) 72-0133.

# Ohio Scientific dealer network is Australia-wide

For more information and advice  
call on your local dealer to help  
you select the best system  
for your needs

AUSTRALIAN DISTRIBUTOR-TCG,  
31 Hume Street, Crows Nest, N.S.W.  
2065

### AUTHORISED AUSTRALIAN AGENTS

#### NEW SOUTH WALES

Bambach Electronics  
NEWCASTLE 2-4996  
Compuserve Newcastle Pty. Ltd.  
HAMILTON 61-2579

Hi-Fi Gallery  
TAMWORTH 66-2525

Macalec Pty. Ltd.  
WOLLONGONG 29-1455

Micro Visions  
KINGSFORD 662-4063  
Shoalhaven Communication Services  
NOWRA 24-444

J.G. Pearce Systems  
DOVER HEIGHTS 789-4300

Unique Electronics  
MERRYLANDS 682 3325

#### VICTORIA

Ellison Hawker Education Pty. Ltd.  
HAMPTON 598-9141

Cypher Data Systems  
MELBOURNE 86-22122

Comprocessing Pty. Limited  
SALE 44-3399

#### QUEENSLAND

Dialog Pty. Ltd.  
BRISBANE 221-4898

#### SOUTH AUSTRALIA

Applied Data Control  
FULLARTON 79-9211

K Tronics  
ADELAIDE 212-5505

#### WESTERN AUSTRALIA

Datas Computer Accounting Services  
SUBIACO 381-3648

Micro Data Pty. Ltd.  
EAST PERTH 328-1179

Micro Solutions  
SUBIACO 328-8372

#### TASMANIA

Eastside Computers  
EAST DEVONPORT 27-8121

J. Walsh & Company  
HOBART 34-7511

#### AUSTRALIAN CAPITAL TERRITORY

Minicomputer & Electronic Services  
PHILLIP 82-1774

#### NEW ZEALAND DISTRIBUTOR

Computer Consultants,  
3 Wolfe St., Auckland N.Z.  
Phone: 79-8345

Computer Consultants  
Queens Rd., Lower Hutt, N.Z.  
Phone: 69-4979




TOMORROWS TECHNOLOGY TODAY

# OHIO SCIENTIFIC
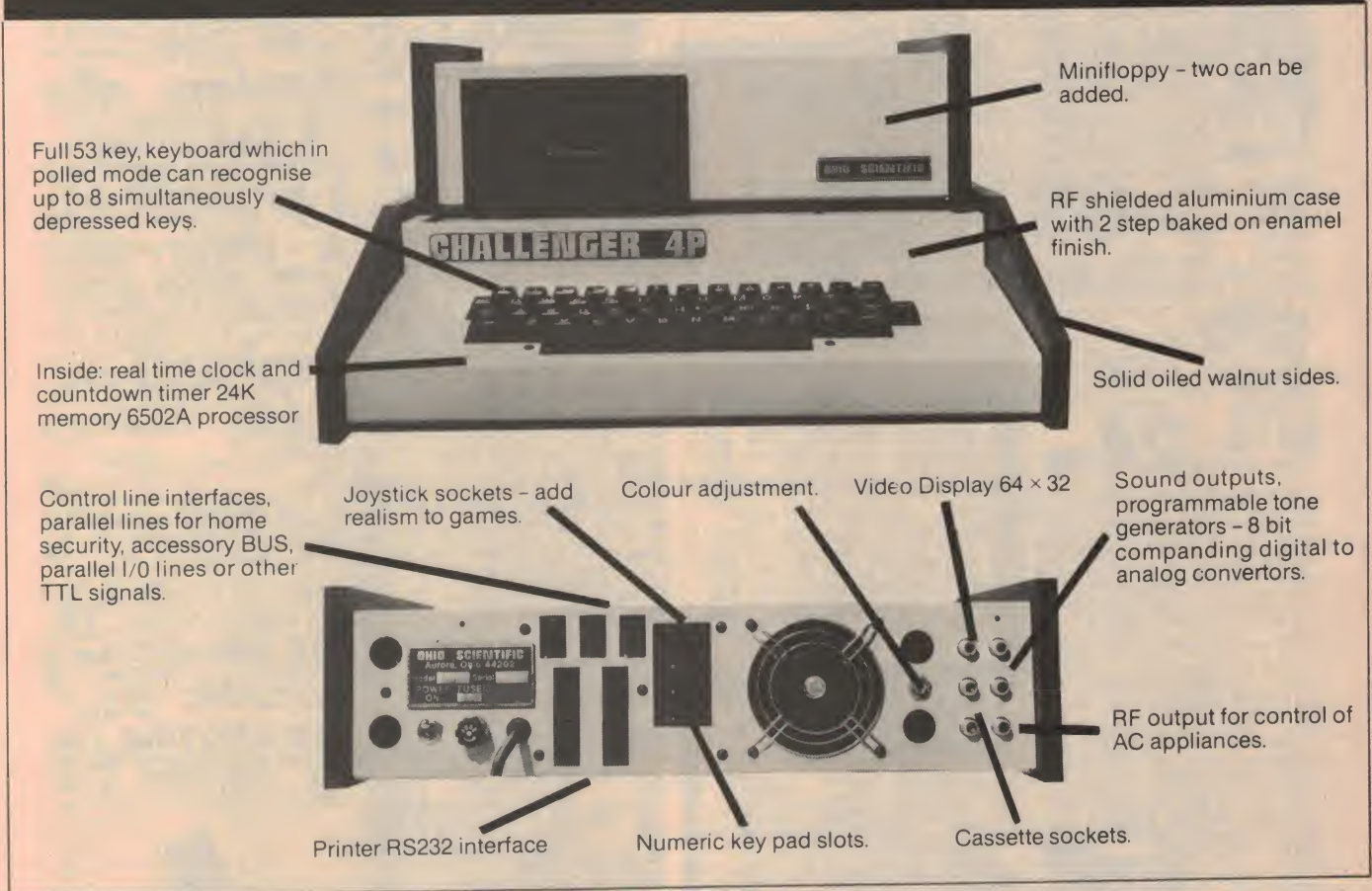
# The Challenger 4

Whichever way you look at it, no other computer offers so much for so little, and in colour!



You'd have to go a long way to get better value in a computer. It has execution speed that really separates the computers from the toys. We think the Challenger 4 is way ahead of anything you've seen so far, for a wide variety of uses including business, personal, educational and games, as well as a real-time operating system, word processor and a data base management system.

The Challenger 4 has a 2MHz 6502 processor, and if that's not fast enough we can supply the GT option with the 6502C processor, and 120 nanosecond memory which averages over one million instructions per second.

A real time clock and count down timer, a 64 x 32 display in 16 colours, including 8K memory in the cassette version, 24K for the minifloppy. A BUS structure allows easy plug in of extra memory or many more OHIO boards. The BUS means modularity. If you bought your vintage C2-4 in 1977 we can change the boards at a much lower cost than a new computer.

For the best surprise of all ask our opposition if they can provide all these facilities. When they can't, ask us!

For the complete list of dealers, please refer to listing on opposite page.

**OHIO SCIENTIFIC**  
TOMORROWS TECHNOLOGY TODAY

TCG Ohio Scientific Pty. Ltd.

31 Hume Street, Crows Nest, N.S.W. 2065

Phone: 439-6477

**SAVE TODAY**

**25W**  
RMS

**8 inch 3 way 8Ω**

**SPEAKER KIT SALE!**

WALNUT finish, ready-made boxes, black speaker cloth.

8 WOOFER + 5 MID-RANGE + 3 TWEETER + X'OVERS + wire and Innerbond + screws!

**PER PAIR \$69**

Can be finished in 2 hours!  
Great sound!  
Great OR price!

**ASSEMBLED & TESTED PAIR \$109**

# Loads more for your money.

## \*NEW BIG POWER Speaker Systems

**ETI 4000/2 KITS 150 W**

JUNE ETI p-51 5 WAY INCLUDING Kits are all complete with screws, wire, and crossover networks are wound, ready to install. Cabinets are assembled and ready to fit speakers.

**\$360 PR. \$498 PR.**

**do-it-yourself**

**3-13L PLAYMASTER SPEAKER KITS**

**80W \$175**

E.A. SPEAKERS \$115 PR DEC '79 BOXES ONLY \$75 PR

**ETI 4000/1 KITS 156W RMS**

FEBRUARY ETI 4 WAY SPEAKERS INCLUDING X'OVERS CABINETS

**\$460 PR. \$698 PR.**

**SPECIAL OCTOBER OFFER FREE!** MAIL ORDERS FREIGHT Sorry, does not include Bankcard Sales

## BULK SPECIALS

any 5w w.w. RESISTORS 10 for \$2  
Range: 0-51, 0-68, 0-75, 1-2, 1-5, 1-8, 2-2, 2-7, 3-9, 4-7, 27, 47, 56, 68, 82, 91, 470, 100, 910Ω

500 mixed 1/2w RESISTORS \$2  
200 mixed 1w RESISTORS \$2

any Single Gang POTS 8 for \$2  
Range: 500K, 1K, 20K, 25K, 50K, 250K, 500K, 1M, 2M, 5M

20 Lucky-Dip POTS asst. \$2  
40 Assorted KNOBS only \$2

any SWITCH-POTS 4 for \$2  
Range: 5K, 10K, 25K, 50K, 250K, 500K, 1M, 2M, 5M

2x1RPM MOTORS 110vac \$2  
90 Lucky-Dip ELECTROs \$2

any Tag Tant. CAPS 10 for \$2  
Range: 0-4755, 0-6855, 155, 1-5, 25, 2-25, 4-75, 47-5, take your pick

12x 0-1uF 630v Poly CAPS a.c. \$2  
any 400v Poly CAPS 20 for \$2  
Range: 0-0022, 0-0033, 0-0047, 0-0068, 0-012, 0-033, 0-047, 0-082, 0-15 mFD

10 Lucky-Dip SWITCHES asst \$2  
30 Metres HOOK-UP WIRE 25c \$2  
6 Metres 3 Core Mains Cable \$2  
8 Metres Fig 8 Shielded Cable \$2

**THIS MONTH'S SPECIAL OFFER**

**741** 10 for \$2 or 30¢ ea.

**BUY AND SELL**

• ALL TEST GEAR  
• Elect. Parts BULK STOCKS  
• Elect. MAGAZINES BACK ISSUES 1970 ON  
• 24, 27, 31, 35 Heat months available, also English, American mags!  
Wanted to buy same for cash, any quantity!

**5 METRES 5m Speaker Cables**

**ONLY \$50** COLOUR-CODED TOO!

**Speakers**

2 1/2" 33, 4" 15, 5" 35, 5 1/2" 15, 6 1/2" 15, 8" 15, 10" 15, 12" 15, 15" 15, 18" 15, 20" 15, 24" 15, 28" 15, 4368" 15, 4372"

## "Brilliance boost" for guitar

A TREBLE BOOSTER circuit can be used with a guitar, and other electronic musical instruments, to boost a range of the higher order harmonics and give a more "brilliant" sound. A circuit to achieve this has a fairly flat response at the bass and across most of the middle frequencies while the upper middle and most of the treble frequencies are given a substantial gain boost.


The circuit is basically just an op-amp (IC1) used in the non-inverting amplifier mode. The non-inverting input is biased by R4 and R5 via a decoupling network which is comprised of R3 and C3. C4 and C5 give dc blocking at the input and output respectively. With SW1 open there is virtually 100% negative feedback through R1, R2 and C1, giving the circuit unity gain and a flat response. Closing SW1 brings C2 into circuit, and this decouples some of the feedback through R1 and R2 at frequencies of more than a few hundred Hz, giving the required rising response.

Feedback through C1 at high treble frequencies causes the response to fall away above about 5.5 kHz, and


prevents the very high frequency harmonics from being excessively emphasised.

As the unit has unity gain at frequencies where boost is not applied it can simply be connected between the instrument and the amplifier.

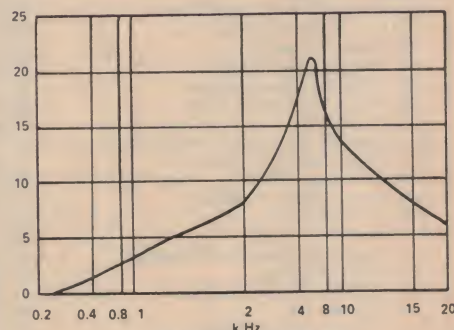It is normal to give only a modest amount of emphasis to the upper-treble in order to get good stability and a low noise level. This also prevents the output from sounding too harsh. The frequency response of this treble booster is shown in the accompanying graph.



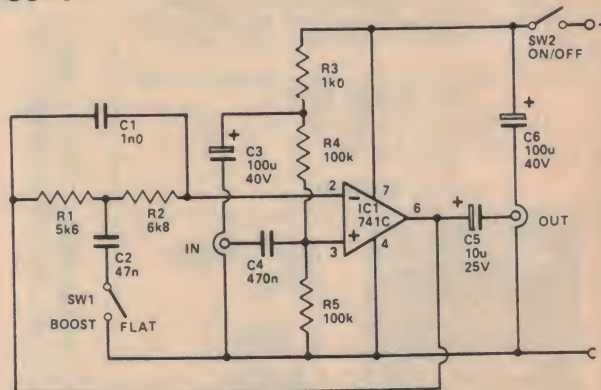THE FREQUENCY RESPONSE OF THE TREBLE BOOSTER



## Andrews Communications Systems

IMPORTERS OF QUALITY COMMUNICATIONS EQUIPMENT — Ph. (02) 349.5792/344.7880

★ Bearcat ★ Regency ★ Redco ★ DSI ★ RF linear amplifiers ★ RF power transistors

### Bearcat® 220 FB scanner



our price  
**\$475**  
20ch.  
(RRP \$637)

All VHF/UHF commercial bands inc. Australian Low Band plus Aircraft band. Searches and Scans. AM/FM modes.

★ BC210 .....\$350 ★ Thinscans from \$179

### Regency M100E2 scanner



First  
release in  
Australia  
**\$395**  
10ch.

Searches and scans Australian Low Band, High Band and UHF to 512MHz. Touch tone frequency programming.

★ M400E2 30ch Scanner.....\$445

### REDCO FREQUENCY COUNTERS

FM.60 displays to 60MHz .....\$149  
FM.600 displays to 600MHz .....\$225  
FM. 600T (TCXO) to 600MHz .....\$295

### NEW KENWOOD R1000 receiver



our price  
**\$450**  
(RRP \$510)

★ KENWOOD TS-130S Transceiver only .....\$745

★ YAESU FT-707 Transceiver only.....\$725

SHOP 7, GARDEN ST., MAROUBRA JUNCTION, N.S.W./P.O. BOX 33, KENSINGTON, 2033.

# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE VICTORIA.

## SCOTCHCAL

### FRONT PANELS FOR ETI AND EA PROJECTS


ETI 452 Guitar Practice Amp	\$4.80
Series 4000 Any colour	\$12.50
Moving Coil Pre Amp	\$2.00
577 Power Supply	\$2.00
455 Loudspeaker Protector	\$2.70
Variable Power Supply	\$2.70
Linear Ohmmeter	\$2.50
Muscle Activity Meter Scale	\$1.40
ETI 576 Electromyogram	\$2.80
561 Metal Detector	\$2.50
EA Capacitance Meter	\$3.50
EA Flash Exposure Meter	\$4.25
EA Sound Triggered Flash	\$3.50
EA Slave Flash	\$1.20
EA Playmaster Graphic Analyser	\$8.50
EA Metal Detector 79md9	\$3.90
EA Pulse Generator	\$4.80
EA Square Wave Oscillator	\$2.50
EA RF Z Bridge	\$3.25
EA Thyristor Tester	\$2.40
EA Quartz Frequency Reference	\$2.70
EA Multi Monitor	\$1.90
EA Experimentors Supply	\$2.80
EA Quiz Master	\$3.70
EA Variable Wiper Delay	\$1.10
EA Playmate Stereo Amplifier	\$4.50

All front panels available from day of release of magazines. When ordering front panels, specify colour of lettering first, then colour of background.

### 10 TURN POTS

1/4" SHAFT. VALUES: 100, 500, 1K, 2K, 5K, 10K, 20K, 50K, 1M.

Inc. tax **\$8.50** ea.

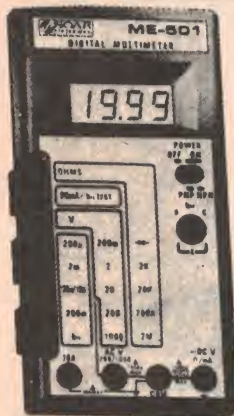

**Soar Model 501A**

**4 digit  
LARGE  
LCD  
DISPLAY**

Send for specs.

**\$77.00**

Add \$3 P&P and certified mail.

### INTERSIL LCD 3 1/2 DIGIT PANEL METER KITS

**INTERSIL ICL7106 \$32.50**

Build a working DPM in 1/2 hour with these complete evaluation kits.

Test these new parts for yourself with Intersil's low-cost prototyping kits, complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter. ICL7106EV (LCD)

## KITS & CIRCUIT BOARDS



(Kits of parts including quality fibreglass boards)

### ETI SERIES 4000 AMP

- Complete Kit, woodgrain slides \$179.00
- Rack Mounting..... \$185.00
- Quality front panel to suit above...\$9.99
- ETI 470 kit of parts.....19.90
- ETI 480 kit of parts 100w (incl. bracket).....19.75
- ETI 470 PS kit of parts.....19.50 (Includes relay, not transformer)
- Transformer to suit.....22.90
- ETI 471 pre-amp.....45.50
- ETI 585R ultra sonic RX.....15.95
- ETI 585T ultra sonic TX.....8.95
- EA 79 SF9 sound flash trigger.....15.00
- All parts available for DREAM computer project.
- P.C.B.'S (all quality fibreglass boards)
- ETI 574 disco strobe.....2.80
- ETI 549A metal detector.....2.75
- DREAM circuit board.....10.90

### Project Boards (Fibreglass)

ETI 043.....1.40	ETI 450B.....1.90	EA 78N6.....3.20
ETI 044.....1.30	ETI 480.....2.40	EA 78NG4.....2.50
ETI 047.....1.50	ETI 480PS.....2.40	EA 78UT4.....3.90
ETI 061.....1.40	ETI 481M.....2.00	EA 78T3.....4.20
ETI 062.....1.80	ETI 481PS.....3.50	EA 78C5.....3.90
ETI 063.....1.70	ETI 483.....2.20	ETI 470.....\$2.90
ETI 064.....1.70	ETI 484.....3.90	ETI 471.....\$9.90
ETI 065.....1.70	ETI 485.....2.90	ETI 472.....\$2.90
ETI 067.....1.80	ETI 486.....2.90	ETI 476.....\$4.90
ETI 068.....1.40	ETI 489A.....2.50	ETI 474.....\$2.80
ETI 071.....1.40	ETI 499.....1.90	ETI 473.....\$4.50
ETI 072.....1.80	ETI 528.....2.20	ETI 573.....\$2.90
ETI 081.....1.50	ETI 541.....2.20	ETI 577.....\$2.90
ETI 083.....1.80	ETI 547.....2.20	ETI 111B.....\$2.30
ETI 084.....1.70	ETI 581.....2.20	ETI 150S2.60 ETI
ETI 085.....1.30	ETI 583.....2.20	260.....\$1.90
ETI 130.....1.90	ETI 585R.....1.60	ETI 261.....\$1.90
ETI 134.....1.90	ETI 585T.....1.40	ETI 262.....\$1.80
ETI 135.....1.90	ETI 586.....2.30	ETI 263.....\$2.20
ETI 136.....1.80	ETI 603.....2.50	ETI 606.....\$2.90
ETI 137A.....2.90	ETI 604.....1.60	79se3.....\$3.90
ETI 137B.....2.90	ETI 635.....2.90	Dream 6800.....10.90
ETI 139.....1.90	ETI 638A.....3.90	79sf10.....\$1.90
ETI 245.....1.60	ETI 708.....1.90	79md9.....\$2.60
ETI 417.....1.80	ETI 713.....3.90	79pg9.....\$2.90
ETI 445.....1.50	ETI 714.....1.90	79ps11.....\$2.90
ETI 446.....1.90	ETI 717.....2.90	79T111.....\$2.75
ETI 449.....1.50	EA 78A06.....2.90	79PC12.....\$2.20
ETI 450A.....1.90	EA 78TMB.....2.00	79EB12.....\$2.90

### NEW PROJECT BOARDS

EA 801pg9.....	\$3.20
EA 80ch7.....	\$4.90
80 pp7A.....	\$4.80
80 pp7B.....	\$2.20
80 pc7.....	\$2.90
80 M07.....	\$3.90
80 B7.....	\$2.50
ETI 564.....	\$5.90
ETI 262.....	\$2.90
ETI 324.....	\$2.90
ETI 250.....	\$2.50
EA 80tr9.....	\$4.90
EA 80LL7.....	\$2.90
EA 80dm9.....	\$5.90
ETI 326.....	\$2.20
ETI 475.....	\$4.50

## NEW PRODUCTS



**HEX KEY PAD \$24.90**

**63-key Keyboard \$55.00**

### RIE are now distributors for 3M Products, including SCOTCHCAL RANGE

8016	Blue on White Plastic	\$4.10
8018	Green on White Plastic	\$4.10
8011	Red on White Plastic	\$4.60
8012	Black on transparent Plastic	\$4.10
8013	Black on Yellow Plastic	\$4.10
8015	Black on White Plastic	\$4.10
8009	Light blue on aluminium	\$4.10
8001	Red on aluminium	\$4.10
8005	Black on aluminium	\$4.60
8007	Reversing film	\$3.75
NOTE: ALL ABOVE SHEETS 10" x 12"		
8500	Photosensitive Developer	\$6.40
3900	Clear Coating (Glossy Finish)	\$9.30
3930	Clear Coating (Matte Finish)	\$9.30
ML-3	Applicator block	\$3.90
ML-4	Developer pads	\$8.90
8002KA	Evaluation Kit	\$55.00

### Attention Sorcerer and TRS 80 owners -

### MEMORY EXPANSION KITS AVAILABLE

We also offer full service on the popular computer projects and systems.

### SPECIAL 4116 RAM OFFER

8 of prime spec 4116 IC's	\$64.00
16 of prime spec 4116 IC's	\$120.00
32 of prime spec 4116 IC's	\$220.00

### STATIC RAM KIT 16K S-100

Kit form	\$249.00
Ass & tested	\$279.00



**Bankcard  
Mail Orders  
Welcome**

Please debit my Bankcard.

Bankcard No. ....

Expiry Date .....

Name .....

Signature .....

All prices current only until 7th November, 1980.


GENERAL ENQUIRIES (03) 489-8131, MAIL ORDER ENQUIRIES (03) 481-1436, RITRONICS WHOLESALE (03) 489-7099.

HEAVIER ITEMS ADD ADDITIONAL POSTAGE, EXTRA HEAVY ITEMS SENT COMET FREIGHT ON.

PRICES SUBJECT TO CHANGE WITHOUT NOTICE. SEND 60c & SAE FOR FREE CATALOGUES.

MAIL ORDERS: PO BOX 235, NORTHCOTE, VICTORIA 3070. MINIMUM PACK and POST \$1.00

# Coming! PERSONAL D.M.M.-AGE

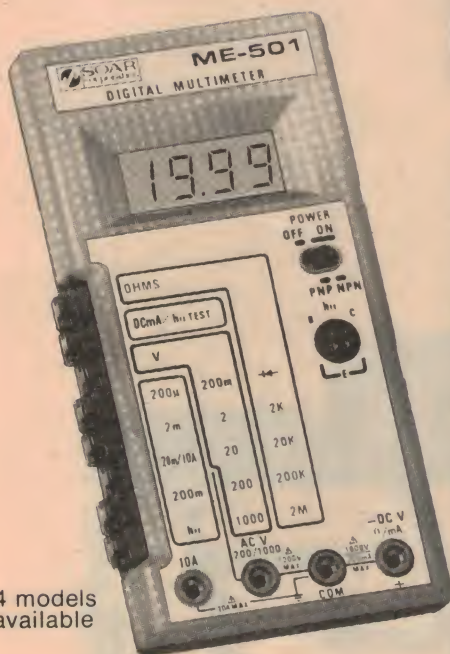

4 models available

SPECIALISTS IN TESTING AND MEASURING INSTRUMENTATION



## ME-501A SPECIFICATIONS

### DC Voltage

Ranges: 200 mV, 2V, 20V, 200V, 1000V  
Input R: 10 M Ohm  
Accuracy: 1 (0.8 percent of rdg plus 1 dgt)  
Overload protection: 100V dc/peak

### AC Voltage

Range: 1000V  
Input R: 10 M Ohm  
Accuracy: 1 (1 percent of rdg plus 5 dgt)  
Overload protection: 1200 Vrms

### DCmA:

Ranges: 200 uA, 2mA, 200 mA, 10A  
Voltage Burden: 250mV maximum at F.S.  
except 10A range, 5.00 mV  
Accuracy: 1 (1.2 percent of rdg plus 2 dgt)  
Overload protection: 0.5A/250V Fuse

### Resistance:

Ranges: 2k, 20k, 200k, 2M, Diode test  
Accuracy: 1 (1 percent of rdg plus 2 dgt)  
Overload protection: 250 Vdc/rms

### Transistor Hfe Checker:

Range: 0 — 100 (IB 10 mA)  
Accuracy: 1 (10 percent of rdg plus 2 dgt)

## RELIABLE SOAR DIGITAL MULTIMETERS


### PROFESSIONAL RANGE

### ME-522

General Specifications  
Display: Liquid Crystal Display.  
Maximum indication: 1999 or -1999.  
Measuring mode: DC V, AC V, DC mA, AC mA, OHMS.  
Measuring range: 5-range change-over in each mode.  
Polarity: Automatic, negative polarity indication.  
Zero adjustment: Automatic.  
Overrange indication: The top of digit position of (1) or (-1) is displayed.  
Sampling time: 300 mSec.  
Battery voltage indication: the "BATT" mark lights on the display panel.  
Power source: Single 9V transistor battery. (NEDA 1604 or S-006P)  
Power consumption: Approximately 15mW.
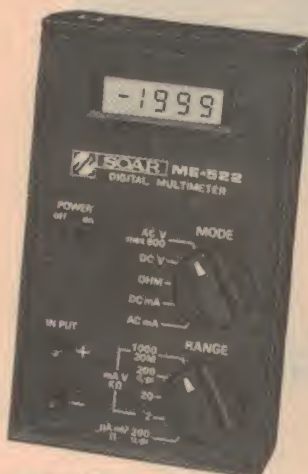
### ME-523

General Specifications  
Display: Liquid crystal display.  
Maximum indication: 1999 or -1999.  
Measuring mode: DC V, AC V, DC mA, AC mA, and OHMS.  
Measuring range: 5-range change-over in each mode.  
Polarity: Automatic, negative polarity indication.  
Zero adjustment: Automatic.  
Overrange indication: the top of digit position of (1) or (-1) is displayed.  
Sampling time: 300mSec.  
Battery voltage indication: When the voltage drops below the operating voltage, the (BATT) lights on and the decimal point (not yet used) lights on.  
Power source: Single 9V transistor battery. (NEDA 1604 or S-006P)  
Power consumption: Approximately 15 mW.



**ME-522**  
3 1/2 DIGIT LCD DISPLAY




**ME-523**  
3 1/2 DIGIT 3/4" HIGH LCD  
WITH MODE DISPLAY

Digital Multimeter at an Analog price! Send for detailed specifications and compare before buying.
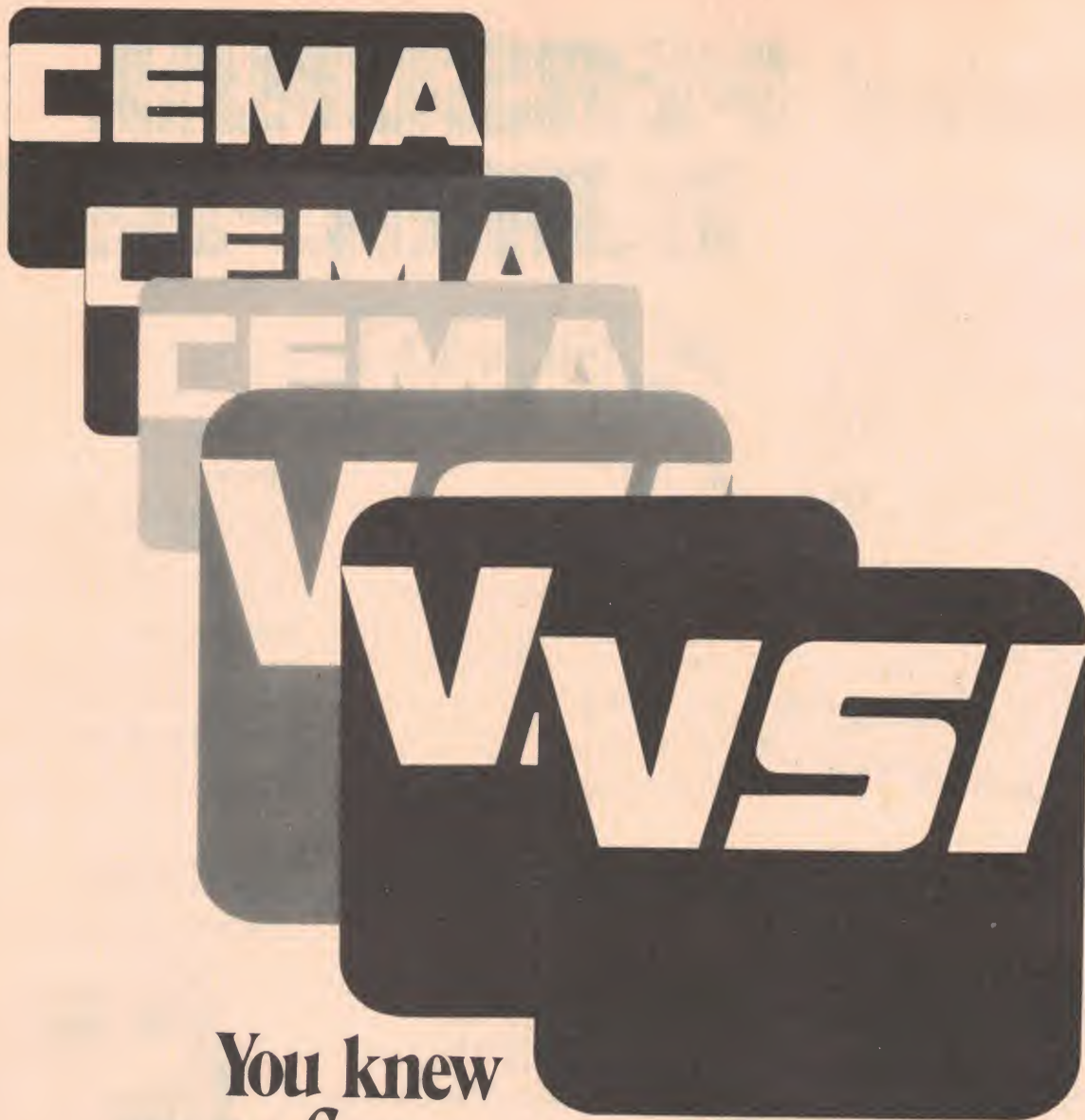
## AMPEC ELECTRONICS PTY. LTD.

1 Wellington St, Rozelle, 2039. PO Box 132, Rozelle 2039. Ph (02) 818-1166.

Available from: **NSW** David Reid Electronics, 29-6601. Radio Despatch Service, 211-0191. Electronics (Distributors), 636-6052. Martin De Launay, 29-5834, Applied Technology, 487-2711. **VIC**: Stewart Electronics, 534-3733. Ellistronics, 602-3282. John Pearce, 528-5240. **QLD**: N.S. Electronics, 36-5061. **SA**: Protronics, 212-3111. **WA**: Reserve Electronics, 275-2377. Taimac, 328-1988.



**You knew  
us as Cema  
We're now called  
VSI Electronics Australia**



**VSI  
ELECTRONICS  
(AUSTRALIA)  
PTY LTD**

**SYDNEY 439 8622 MELBOURNE 877 5311 ADELAIDE 516 483 BRISBANE 52 4261 PERTH 328 8091**

# Lab Notes

## The ETI-566 Metal Detector Revisited

This project, published in the April 1980 issue, has proven to be pretty popular amongst experimenters who have clamoured for more complete construction details. Your patience is herewith rewarded!



IT SEEMS from correspondence that this project has been popular amongst experimenters. We have been asked to give more details on the unit and/or alternative construction etc. There have also been problems with component supply, particularly the coils. This Lab Notes gives details, for the experimenter, of alternative construction arrangements, coil details and suggestions on different configurations to make the unit more sensitive to small objects.

This provides the minimum induction of the signal from the transmitter loop into the receiver loop as there is minimum magnetic coupling between the two. To permit accurate alignment, the receiver antenna loop can be varied over a small angle.

The transmitter puts out a pulsed signal at 20 kHz. The pulsing is principally to provide a modulated signal for the receiver that may be demodulated and put through a speaker or headphones for the convenience of the operator. The

transmitter is deliberately designed to have a considerable harmonic content in its output. The inductive coupling between the antenna loops is greater at the third harmonic than it is at the fundamental frequency, but ground penetration is better at 20 kHz than 60 kHz as the ground resistivity increases with frequency. The transmitter antenna loop is oriented vertically to give maximum ground penetration of the transmitted signal and maximum induction into buried metal objects.

With the instrument near the ground, the effect of the ground on the field patterns of the two antennas will result in some distortion of their fields but this can be compensated for by realigning the receiver antenna for a null (minimum signal).

When a buried metal object is encountered, eddy currents induced in the object will cause a distortion in the field pattern of the transmitter antenna. As the antenna is tightly coupled to the oscillator, this will also bring about a distortion in the field pattern of the antenna at the harmonic frequencies. This will increase the coupling between the transmitter and receiver antenna loops and a signal will be heard in the receiver.

Metal objects buried close to the surface will affect the field pattern of both antennas, but deeply buried objects will primarily influence the transmitter antenna field.

The 'depth sensitivity' of the instrument is dependent on a number of ►

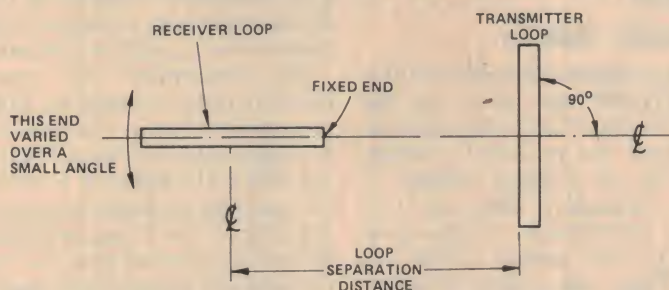


Figure 1. The 'Induction Balance' principle employed in the ETI-566

### Notes on the principle of operation

First of all, to be able to experiment with the construction of the instrument, it is useful to know something of the principle of operation. As explained in the original article, the unit employs an *induction balance* technique. As illustrated in Figure 1, the transmitter antenna loop and the receiver antenna loop are located with their planes at right angles and a small distance apart.

pulse repetition frequency may be set to some convenient pitch in the audio range between about 200 Hz and 1.5 kHz.


The alignment of the antennas is adjusted such that, with no metal object within the field of the instrument, there is minimum (or no) received signal.

The receiver is tuned to the *third* harmonic of the transmitter, i.e.: 60 kHz. This provides better sensitivity than if it were tuned to the transmitter at 20 kHz. It seems to work like this: the

# Lab Notes



**LEFT:** General use of the Instrument. With the receiver correctly adjusted for a null, proceed along a line, or parallel lines, until an indication is received. For accurate location, cross the indication point from each side and mark with your heel where the indication is strongest. The location of the buried object is between the two marks.

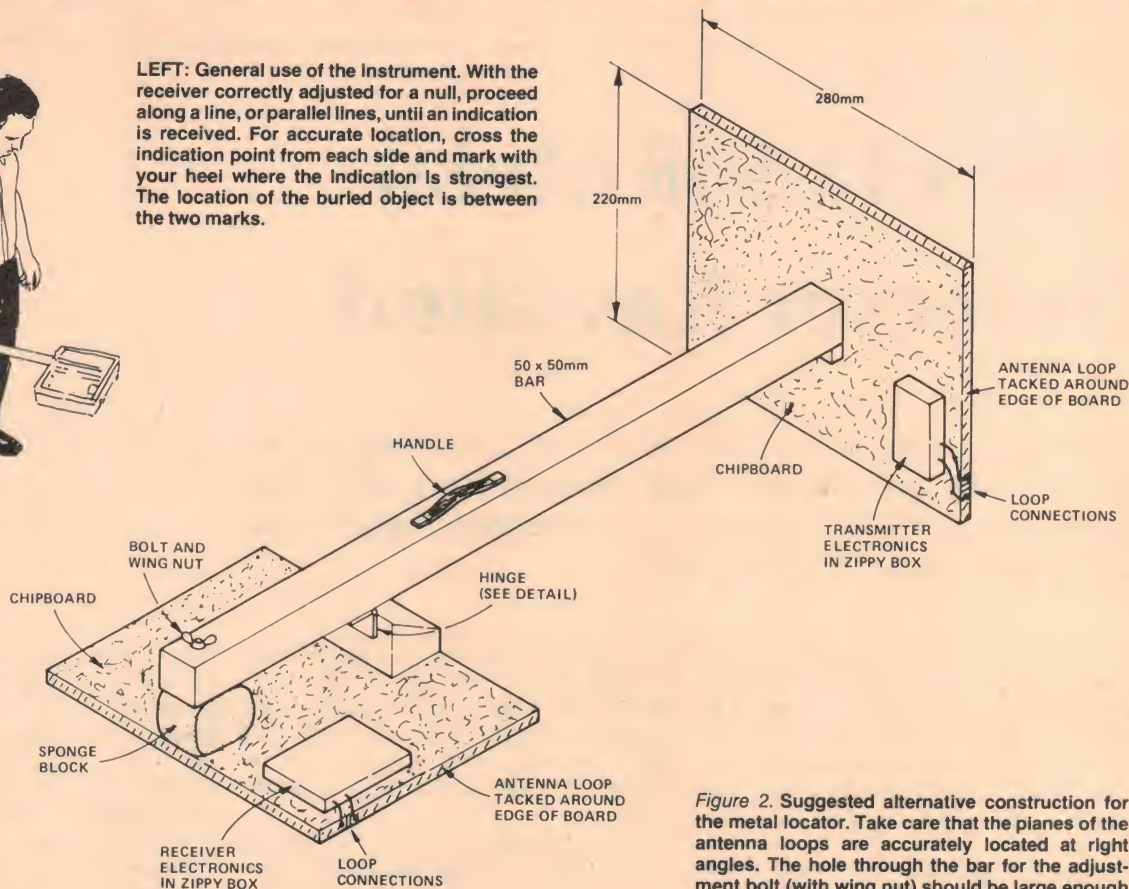

**Figure 2.** Suggested alternative construction for the metal locator. Take care that the planes of the antenna loops are accurately located at right angles. The hole through the bar for the adjustment bolt (with wing nut) should be large enough to clear the bolt when the receiver baseboard is fully angled towards the bar.

factors — primarily the 'loop separation distance' (see Figure 1), the size of the antenna loops, the power of the transmitter and the sensitivity of the receiver. Ground mineralisation also affects sensitivity and penetration.

The ability of the instrument to detect small objects depends largely on the loop separation distance and the size of the loops. Smaller loops and closer spacing improve the unit's sensitivity to small objects, but at the expense of penetration.

Constructed to the dimensions illustrated, a football-sized object can be detected at depths as great as two to five metres, depending on ground mineralisation and how long it has been buried. Small diameter pipes can be readily detected at depths of one metre below ground level.

As a matter of interest, the principle of operation is some 50 years old! Following the April article a reader sent us a clipping from a popular electronics magazine, describing a similar instrument, published in the 1930s!

## Alternative construction details

Full details of alternative coils suitable for the ETI-566 are given in the accompanying box. Pin connections can be taken from the pc board overlays published in the original article. A suggested alternative form for the mechanical construction is shown in Figure 2. It ain't pretty — but it's practical! There are plenty of possibilities — which we'll leave to your ingenuity — but keep the basic principles in mind.

Two pieces of chipboard, 15 - 19 mm thick, serve as bases to mount the antenna loops. The latter are made from aluminium (or copper — if you can afford it!), as shown in Figure 3, and tacked around the edge of each board. The connections to the loops should be as good as you can make them to ensure low resistance contact. Solder lugs pop-riveted to the edge of the loops at the 'break' make good connection, or you could use pk screws and solder lugs —

with shakeproof washers on both sides of the solder lugs to ensure a good 'bite' into the metal and a secure connection.

The transmitter and receiver pc boards can be mounted in 'zippy' boxes of convenient sizes — the receiver board is amply accommodated in one measuring 196 x 113 x 60 mm or thereabouts, the transmitter board in a box measuring 130 x 68 x 41 mm, or similar. They should be mounted near the 'breaks' in the antenna loops to keep lead length to the loops as short as possible. Twist the leads.

The wooden bar which holds the two chipboard antenna bases could be a length of 50 x 50 mm dressed western red cedar (to minimise warping). Alternatively, you could use a length of square-section aluminium tubing. Overall length of the bar should be about one metre for best depth penetration with this arrangement (the original project used a handle measuring 1120 mm). However, there is plenty of room to experiment. All wooden parts should be sealed and painted or given

several coats of 'Estapol' or similar clear lacquer finish to preserve them from the effects of the weather. Do this prior to final assembly.

The hingeing arrangements for the receiver antenna baseboard are shown in Figures 2 and 3. An 80 mm length of 50 x 50 mm dressed timber is chamfered as indicated and fixed to an edge of the receiver baseboard, in the centre. A hole is drilled in the middle of the opposite side, just smaller than the outside diameter of a 1/4" Whitworth nut. The nut is forced into this hole. A corresponding hole is drilled in the bar. A 1/4" Whitworth bolt, 6" (150 mm) long, with a wing nut screwed up to the head, is passed through the bar and into the nut in the receiver baseboard. A block of

sponge rubber serves as a 'spring'. The diagram in Figure 2 makes it all clear.

A brass hinge is fixed to the chamfered block and the underside of the bar, as illustrated in Figure 3.

The transmitter baseboard is mounted flush on the end of the bar. Note that this end must be cut as square as possible. The underside of the bar is 60 mm above the horizontal centre line of the baseboard. Fix the baseboard to the bar with a single long wood screw. This allows you to rotate the transmitter antenna to achieve correct alignment. The small block shown under the bar, against the transmitter baseboard, is glued in place after the antenna is aligned.

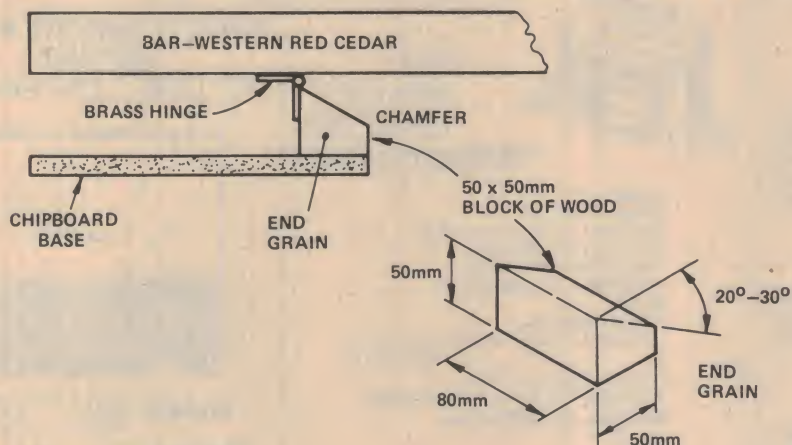


Figure 3. Hingeing arrangement for the receiver antenna baseboard.


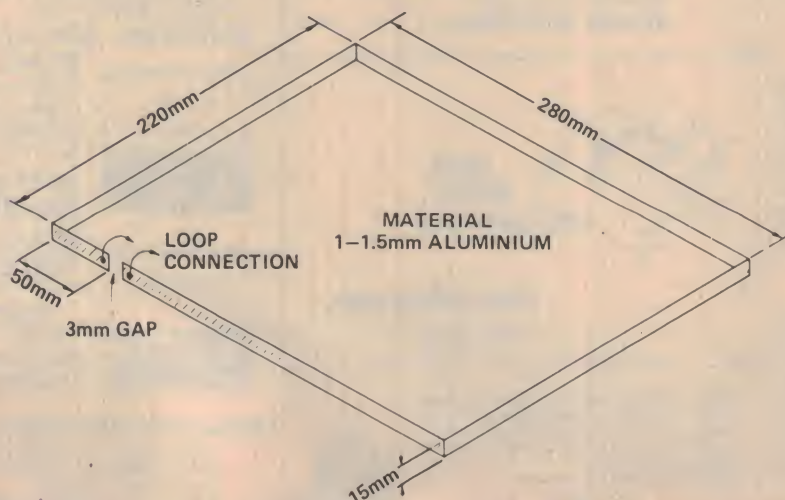


Figure 4. Dimensions of the antenna loops. The 'break' for the loop connections need not necessarily be as indicated here, but could be located at a corner or midway along one side.

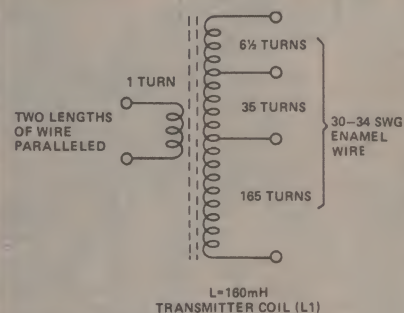


#### ETI-566A (Tx) — L1

Inductance — 160 mH. Wound on pot core assembly, primary and secondary turns and tapings as illustrated above. Pot core is Philips type P18/11, 3H1 material, ungapped with two-section bobbin, can and tag plate.

##### Part Numbers

Pot core —	4322 020 2150
Bobbin —	4322 021 30280
Can —	4322 021 30530
Tag plate —	4322 021 30450

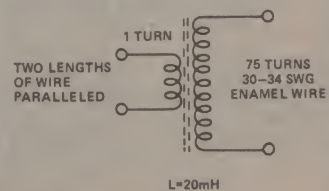


#### ETI-566B (Rx) — L1

Inductance — 20 mH. Wound on pot core assembly, turns of primary and secondary as illustrated above. Pot core, Philips type, P18/11, 3H1 material, ungapped with two-section bobbin. This assembly is bolted to the pc board through the central hole.

##### Part numbers

Pot core —	4322 020 2150
Bobbin —	4322 021 30280

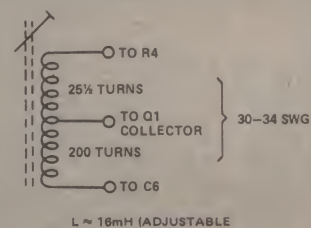

#### ETI-566B (Rx) — L2

Inductance — approx. 16 mH, adjustable. Wound on pot core assembly, turns and tapings as illustrated above. Pot core, Philips type, P18/11, 3H1 material ( $\mu_e = 150$ ), with single-section bobbin, adjuster (colour-coded white), can and tag plate.

##### Part numbers

Pot core —	4322 022 24270
Adjuster —	4322 021 32130
Bobbin —	4322 021 30270
Can —	4322 021 30530
Tag plate —	4322 021 30450



289 LATROBE ST. MELBOURNE. 3000  
PHONE (03) 602-3282, 602-3836. TELEX AA37758 LSTRON.

Ellistronics now stock in excess of 2000 different types of semiconductors plus computer components and systems. Altogether we have over 8000 various electronic components. The largest range available in Melbourne



**YES! WE ACCEPT BANKCARD.** All prices valid month of issue. Heavy items sent Comet freight forward. Minimum post \$3.00.

### SUPER SPECIALS

2114 450Ns	\$3.10 ea.
2716.5v Single Supply	\$16.75 ea.
4116	\$6.95 ea.
2114 300Ns	\$3.75 ea.
2708	\$6.50 ea.

### FLOPPY DISC CONTROLLERS

FD 1771	\$37.00 ea.
FD 1791	\$62.00 ea.
FD 1793	\$62.00 ea.

### MEMORIES

2758 1k x 8 5v Supply	\$12.50 ea.
2716 200ns 5v Supply	\$22.00 ea.
2732	\$66.00 ea.
MB 8414 (2114 CMOS 250ns)	\$21.00 ea.
65 x 08 1k x 8 CMOS	\$9.00 ea.

### 8 BIT MPU'S

6802	\$11.80 ea.
6808	\$10.50 ea.
6809	\$46.77 ea.
6821	\$5.10 ea.
6840	\$7.84 ea.
6845	\$38.94 ea.
6847	\$28.00 ea.
6850	\$4.40 ea.
6852 (\$5.50)	\$5.50 ea.

### RAM

Expansion Kit for TRS80	\$64.00 ea.
Z80	\$14.82 ea.
Z80A	\$17.40 ea.
Z80CTC	\$9.49 ea.
Z80A CTC	\$11.44 ea.
Z80 PIO	\$9.49
Z80A PIO	\$11.44
4116 200ns	\$8.26

ABOVE PRICES PLUS 15 PERCENT SALES TAX IF APPLICABLE.



### TOP QUALITY LOW COST TRANSFORMERS

**R-2150**  
Primary: 240V AC.  
Secondary Voltage: 12.6 volts CT.  
Secondary Current: 150mA.  
Termination: Flying leads.  
**\$3.80 ea. 10 up \$3.34 ea.**

**R-2155**  
Primary: 240V AC.  
Tapped Secondary Voltages: 6.3, 7.5, 8.5, 9.5, 12.6, 15.  
Secondary Current: 1 amp.  
Termination: Solder lugs on transformer.  
**\$5.75 ea. 10 up \$5.06 ea.**

**R-6672**  
Primary: 240V AC.  
Tapped Secondary Voltages: 15, 17.5, 20, 24, 27.5, 30.  
Secondary Current: 1 amp.  
Termination: Solder lugs.  
**\$7.48 ea. 10 up \$6.44 ea.**



### DIAL DESK TELEPHONE

Only \$8.50 each.  
2 for \$16.

**S2000 8"** (200mm) wide range general purpose. Includes transformer, mounting holes for P.A. and background use. Very smooth over-all response 45 Hz-12 KHz. Fitted to a 1.9 cubic ft vented enclosure they sound unbelievable.  
8 Ohm 8 Watt RMS 5.6 oz magnet.  
**\$6.00 TRADE, \$6.95 inc. tax**



### DIRECT IMPORT PANEL METERS AT LOW, LOW PRICES



**MU-65** 1MA — 120 ohms  
100uA — 1400 ohms

Dimensions: Overall — 100mm(W) x 82mm(H)  
Scale — 100mm(W) x 50mm(H)  
Mounting: Hole required — 63mm  
Bolts centres — 80mm(W) x 64mm(H)  
Nuts and washers provided

**\$10.18 ea. plus \$1.52 tax**



**MU-45**  
O-1MA-120 ohms  
O-50UA-1400 ohms  
O-5ADC-3 Shunt  
O-20VDC-100 ohms

**\$6.91 ea. plus \$1.04 tax**




**MU-45 VU METER**  
VU (OdB equals 1mW into 600ohms)  
— 1,000ohm

**\$7.93 ea. plus \$1.11 tax**

### MU-45 DIMENSIONS

Overall — 58mm(W) x 52mm(H)  
Scale — 58mm(W) x 31mm(H)  
Hole required — 44mm  
Bolt centres — 38mm(W) x 38mm(H)  
Nuts and washers provided  
10 or more less 10 percent

# Lab Notes

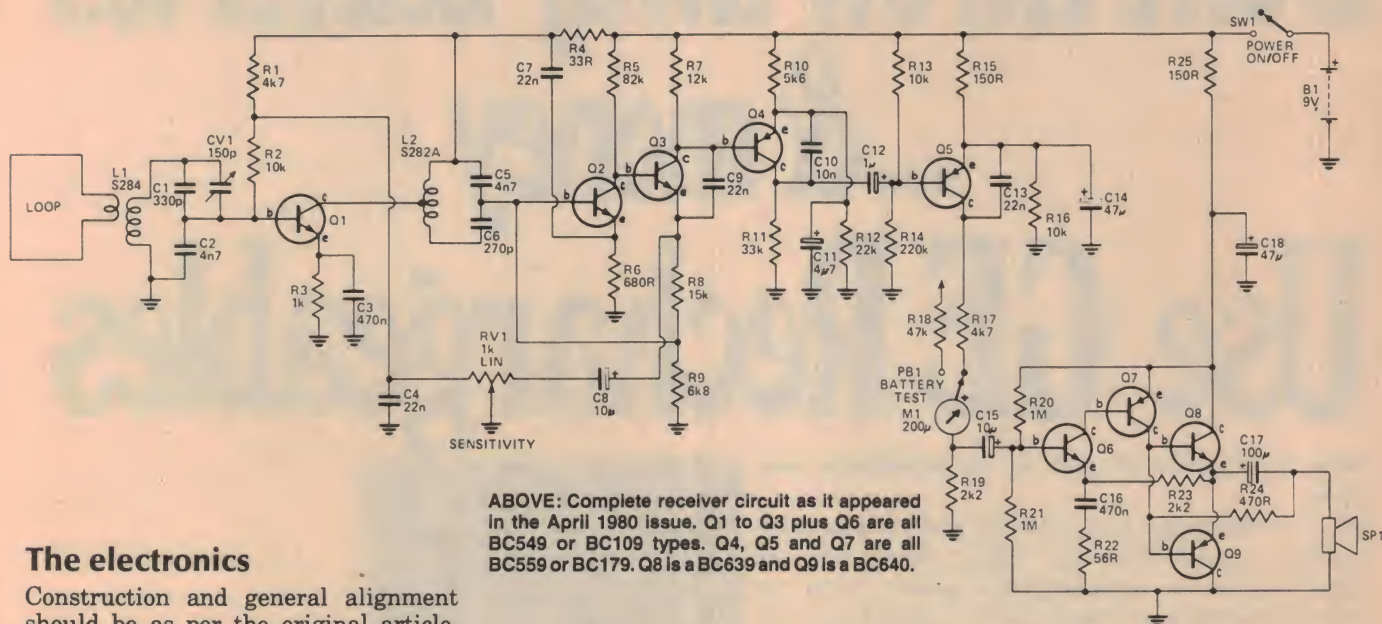

ABOVE: Complete receiver circuit as it appeared in the April 1980 issue. Q1 to Q3 plus Q6 are all BC549 or BC109 types. Q4, Q5 and Q7 are all BC559 or BC179. Q8 is a BC639 and Q9 is a BC640.

## The electronics

Construction and general alignment should be as per the original article. NOTE: Q6 in the receiver was left out of the original parts list — it is a BC549 or BC109. Coil details are given in the box on page 53. Note that, as these coils are jumble wound on the formers they will have greater self-capacitance than those specified for the original instrument. This will result in some variation in the tuning but there should be sufficient adjustment in the trimmer capacitors in the transmitter and receiver and the core adjuster in L2 in the receiver. If any difficulty is experienced, C4 in the transmitter and C1 in the receiver could be reduced to 270 pF each. In addition, C6 in the receiver could be reduced to 220 pF.

The trimpot (RV1) in the transmitter should be set at mid-point resistance prior to alignment and adjusted to produce a suitable pitch in the receiver after the initial alignment.

As for batteries, a No. 2362 or 2364 9V battery may be used in the receiver with the size box suggested, while a No. 2362 battery will fit in the box suggested for the transmitter. Alternatively, 'No. 216 size 9V batteries may be used, but they won't last too long with prolonged use. (Alkaline types in this size might be ok, though).

## Antenna alignment


Following initial alignment of the electronics, the antenna baseboards can be attached to the bar and the transmitter antenna aligned. Standing well clear of metal objects (at least 5 - 6 metres) align the receiver baseboard such that it is

parallel with the bar. Turn on both units and adjust the receiver sensitivity to obtain a convenient indication on the meter. Rotate the transmitter baseboard to get minimum received signal, adjusting the sensitivity if necessary. Tighten the screw securing the transmitter baseboard. Check that you can get a good null with the receiver baseboard adjusting screw; the receiver sensitivity should be advanced at least 3/4 at the point of minimum signal. If so, glue a small block of wood in place, as per Figure 2, on the underside of the bar where it meets the transmitter baseboard.

That's it. Happy hunting!
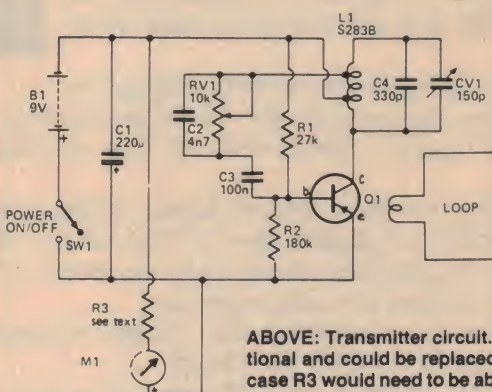
## Experimentation

The following details are suggestions for the dyed-in-the-wool experimenter.



ABOVE: Transmitter circuit. The meter, M1, is optional and could be replaced with a LED, in which case R3 would need to be about 270 or 330 ohms.

The instrument can be constructed to improve sensitivity to small objects by decreasing the 'loop separation distance' (see Figure 1). We tried a bar only 600 mm long and found the unit would detect a small bunch of keys at about 300 - 400 mm. However, the alignment of the receiver antenna is much more critical.

Smaller antenna loops will improve sensitivity to small objects, at the expense of penetration, as discussed earlier. This, combined with closer spacing, should provide a good starting point for further experimentation. Indeed, a number of units could quite easily be constructed, sharing a common bar perhaps, with different antenna loop dimensions. Incidentally, the loops need not be square or rectangular, but could be circular.

With close-spaced loops, the receiver ►

# Don't throw away batteries ...& money Use GE Rechargeables

From the frontiers of space to the products in your home.

When reliable batteries were needed for missions to the Moon and Mars, General Electric was a leading supplier. Now GE's Nickel Cadmium battery leadership has pioneered a low cost system for you that can recharge all of GE's popular battery sizes (AA, C, D and 9 volt) up to 1000 times, with a single low-cost charger.

If you're tired of buying batteries, it's time for GE Rechargeables.

Rechargeable batteries make sense in today's value-conscious market. GE's proven efficiency and dependable system is rapidly attracting more and more consumers to the advantages of GE Rechargeables.

**Convenience:** Charge overnight or keep extra batteries charging, fresh and ready to use.

**Longlife:** GE Batteries are rechargeable up to 1000 times and they will last for years.

**Performance:** GE Rechargeables maintain voltage for the life of the charge to keep your products operating with steady performance.

**Warranty:** Guaranteed not to leak, with resultant damage to your product, plus all GE battery products have a full one year warranty.

**Economy:** One GE Rechargeable outlives 100 or more throwaways — even the long-life alkaline kind.

**Tests show that one GE Rechargeable Battery outlasts:**

350 Alkaline AA size batteries in a photo flash.

140 Alkaline C size batteries in a cassette recorder.

250 Carbon-Zinc D size batteries in a torch.

100 Alkaline D size batteries in a motor-driven toy.

150 Alkaline 9-Volt batteries in a calculator.

Available from leading retailers.

**Trade enquiries:**

Australian General Electric (Sales) Limited,  
86-90 Bay Street,

Ultimo, New South Wales 2007.

Rank-General Electric Housewares Pty. Ltd.

296 Ferntree Gully Road,  
Notting Hill, Victoria 3168.

plus regional offices in Capital City areas.

C. G. E. Marketing Services,  
117 Burnley Street,  
Richmond, Victoria. 3121.

Products from the Wonderful World of General Electric

**GENERAL  ELECTRIC\***

\*Trademark General Electric Company  
U.S.A. World's Largest Electrical  
Enterprise.



**Batteries that last for years!**

# Lab Notes

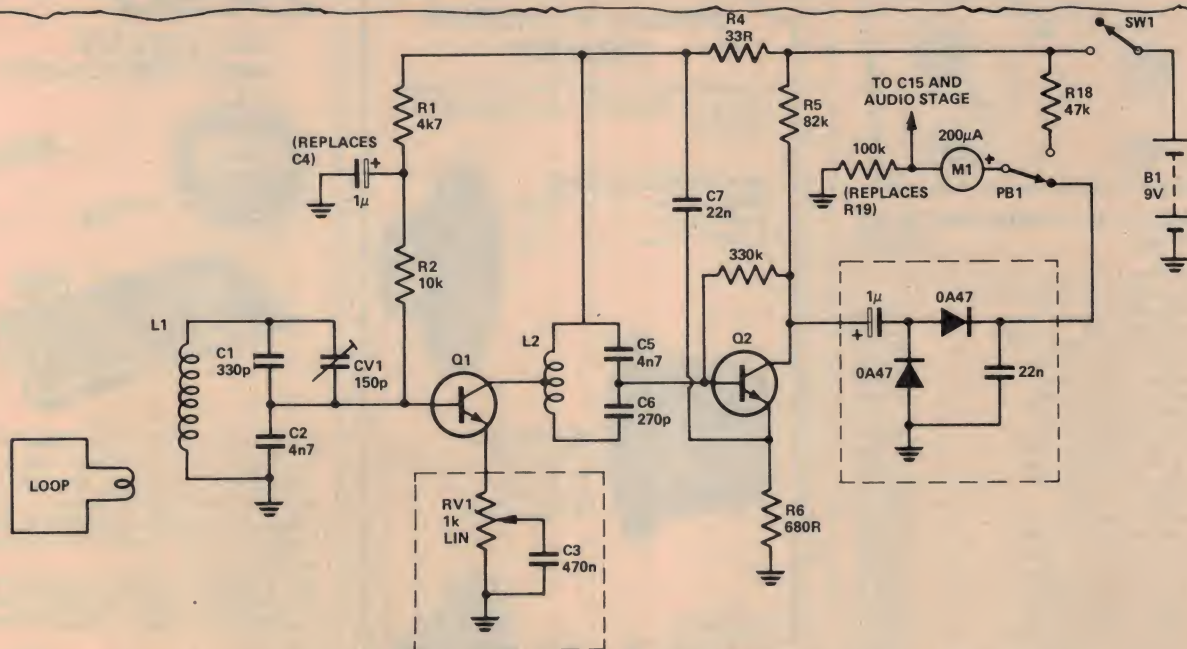


Figure 5. Suggested alternative for a simpler, lower gain receiver. This may prove a better proposition where small, close-spaced antenna loops are used. The original pc board may be used, the unnecessary components being removed. Major changes are shown inside the dashed squares. A voltage doubler diode detector is coupled directly from the collector of Q2, its output being taken to the pushbutton PB1. R19 is replaced with a 100k

resistor; the original audio stage is retained. If you only want to use headphones, the audio stage could be removed also and the phones (Hi-Z) capacitively coupled to the 100k resistor. The construction should be arranged so that there is only a short lead between the gain pot (RV1) and the emitter of Q1. Mount C3 on the pot. Note that C4 is replaced with a 1uF tantalum capacitor.

may be over sensitive. A modified circuit is suggested in Figure 5. The original pc board may be used but only the first two stages involving Q1 and Q2 are necessary, along with some of the original components. Major changes are shown in the dotted lines. The gain control is shifted to the emitter of Q1 and provides various amounts of degeneration as the bypass capacitor, C3, is connected across a greater or lesser part of the emitter resistance of Q1, formed by RV1. Greatest gain is provided when C3 is connected across the whole of RV1.

A simple half-wave voltage doubler diode detector is coupled from the collector of Q2. A 330k bias resistor is connected between base and collector in this circuit as Q2 in the original circuit had the base bootstrapped to the emitter circuit of Q3 (now removed).

This circuit should provide a stable receiver of adequate sensitivity for close-spaced antenna loops.

As suggested in the original article, lowering the unit closer to the ground from the natural carrying position at arm's length improves penetration. However, it upsets the alignment of the receiver antenna a little and you have to stoop down and re-adjust it. Carrying the instrument in this position is a pain in the ... whatever ... so if you can devise some method of carrying it such that the antennas are placed closer to

the ground, results can be improved. A strap for this purpose was shown with the original unit and is certainly effective, though it's "fiddly" to adjust the receiver antenna alignment. An extra attachment could be fashioned to perform the same task. We'll leave that to your ingenuity, once again — *but it*

*must not be metal.*


When using the unit close to the ground, it is generally most effective if the bar is not horizontal, but tilted forward slightly so that the receiver antenna is angled towards the ground.

From here on in, it's up to you. Good luck!

## CONDENSED INSTRUCTIONS

- 1) Set receiver angle adjustment fully clockwise so that the front of the receiver is close to the bar. Keep away from cars, fences and metal objects when setting up the instrument.
- 2) Turn on receiver and set the gain to about 3/4 range.
- 3) Turn on transmitter. A loud tone should be heard in the receiver.
- 4) To adjust the instrument, hold it level at normal arm length beside your body. Adjust the receiver angle until no tone is heard and/or no meter reading is obtained. Continue adjusting the receiver angle in the right direction until a slight indication is obtained. The instrument is now ready for use.
- 5) If a correct 'null' cannot be obtained, check you aren't near a metal object and then reduce the sensitivity control.
- 6) To locate metal objects, proceed along a series of parallel lines until an indication is received. To accurately locate the object, cross this indication point from each direction along your line and mark, each time, with your heel where the indication is strongest. The object will be midway beneath the two marks.

## SOUND AND LIGHT OPERATED FLASH

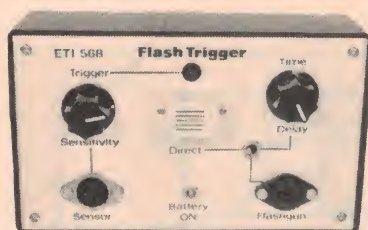

Complete kit of this exceptional design by ETI only .....\$26.95

Below is a list of our electronic project kits. Possibly the largest range of kits in Australia.

2020 CAR ALARM ETI KIT.....	\$12.50
2025 IND. BAL. MET. DET. KIT.....	\$32.50
2030 TV MASTHD. AMPL. KIT.....	\$28.50
2035 TRAN. ASST. IGNT. KIT.....	\$32.50
2050 300 WATT ETI AM KIT.....	\$63.50
2055 MINICOLOUR C/ORG KIT.....	\$49.90
2060 ETI578 N/CD. CH KIT.....	\$39.00
2065 DIG. CAP. METER KIT.....	\$59.00
2070 TV CRO. ADAPTOR KIT.....	\$29.40
2075 LIGHT CHASER EA KIT.....	\$65.00
2080 LED TACHO. ETI KIT.....	\$29.95
2085 INTERSIL LCD KIT.....	\$42.50
2090 140W VALVE AMP. KIT.....	\$220.00
2095 300W MODULE EA KIT.....	\$75.00
2096 300W SPK. PRT. EA KIT.....	\$12.95
2097 300W P/SUP. EA. KIT.....	\$52.95
2098 300W CH. PART. EA KIT.....	\$8.25
2110 300W MODULE ETI KIT.....	\$63.50
2117 4000 NO. BOX. TRF KIT.....	\$139.00
2119 60W A/MOD. ETI470 KIT.....	\$29.90
2122 P/SUP. 472. NOTRF KIT.....	\$32.50
2125 PRE-AMP. ETI471 KIT.....	\$47.90
2127 4000 CHAS. PARTS KIT.....	\$25.00
2135 240/plus, minus 15V.P/S KIT.....	\$9.50
2150 AUD. LEV. MTR. 438 KIT.....	\$11.95
2152 LED LEVEL METER KIT.....	\$14.50
2155 4 INPUT GT. P/AMP KIT.....	\$29.50
2297 MIKE PREAMP. SML KIT.....	\$9.50
2300 SIMP. PRE. AMP. KIT.....	\$9.75
2302 BUZZ BOARD KIT.....	\$3.90
2303 2 TONE DRBELL KIT.....	\$4.50
2304 HEADS AND TAILS KIT.....	\$3.50
2305 TEMP. ALARM KIT.....	\$4.90
2306 2 OCTAVE ORGAN KIT.....	\$8.50
2307 MORSE PRACT KIT.....	\$3.50
2308 BASIC AMP KIT.....	\$5.50
2310 ELECTR. SIREN.....	\$5.50
2311 LED DICE KIT.....	\$5.90
2312 BATTERY SAVER.....	\$3.90
2313 CONTINUITY TESTER KIT.....	\$3.00
2314 SING LOIST MET. KIT.....	\$4.90
2315 500 SEC. TIMER KIT.....	\$4.50
2316 AM TUNER ETI KIT.....	\$6.50
2317 ELECTR. BONGOS KIT.....	\$5.00
2320 DS PROJECT 1-10 KIT.....	\$6.90
2325 DS PROJECT 11-20 KIT.....	\$7.50
2360 2-INP. GUIT. PRAM KIT.....	\$12.50
2365 100W MOD. ETI 480 KIT.....	\$25.00
2370 50W MOD. ETI 480 KIT.....	\$19.50
2373 CAR BOOSTER AMP KIT.....	\$29.50
2375 12V. 6 CIG. CLOCK KIT.....	\$19.75
2380 LCD CLOCK MOD. KIT.....	\$17.50
2394 CALCUL. KEYBOARD KIT.....	\$3.75
2398 DRILL SPEED CTR KIT.....	\$13.50
2401 AUTOCHIME KIT.....	\$29.75
2402 P/M 40 plus 40 AMP KIT.....	\$129.00
2404 P/M AM/FM TUNER KIT.....	\$129.00
2406 P/M. GRAPHIC EQ. KIT.....	\$99.50
2408 P/M. GRAPH. ANALY. KIT.....	\$99.50
2410 RADAR INTRUD. AL KIT.....	\$69.00
2415 R-L-C BRIDGE.....	\$36.50
2420 40MHz. FREQ. MET. KIT.....	\$99.50
2425 AUDIO OSCILLAT. KIT.....	\$36.50
2430 TRANSISTOR TEST KIT.....	\$19.75
2435 MINI ORGAN ETI KIT.....	\$29.50
2450 DISCO STROBE KIT.....	\$34.50
2455 MUSICOLOUR MK3 KIT.....	\$69.50

### Bill Edge's ELECTRONIC AGENCIES

115-117 Parramatta Road, Concord 2137  
(Cnr Parramatta Rd and Lloyd George Ave)

Trading Hours: 9am-5.30 pm Mon-Fri  
9am-Noon Saturday • 10am-2pm Sunday  
Phone (02) 745-3077

Please send me..... Kits at \$.....  
plus \$..... P&P.  
Cheque, M.O., B' card No. (with signature enclosed).  
Please send more information on..... Kit.  
(Give name and address)

NEW

## RPG HI-FI & MUSICAL INSTRUMENT SPEAKERS

Manufactured to Radio Parts Group specifications by the world's largest speaker manufacturer.

### HIGH EFFICIENCY TWEETERS

H66AP45-01F 6w.....	\$5.14
E66CP45-01F 8w.....	\$5.14
B45DP70-01F 10w.....	\$8.95



### HI-FI MID RANGE

B11EC80-02F 30w.....	\$15.79
(can back) 4 1/2 inch	
A11DP60-02F 15w.....	\$7.37
(sealed back) 4 1/2 inch	



### WIDE RANGE

4 1/2" B11EC80-01F 15w.....	\$13.49
6" A16DC61-01FW 12w.....	\$8.44
6" C16E70-01FW 15w.....	\$13.23
8" A20EP80-03FW 20w.....	\$15.04
8" A20EC70-03FW 30w.....	\$14.35



### WOOFERS

8" A20EU75-01F 30w.....	\$15.29
10" A25EP65-02F 20w.....	\$15.41
10" C25FU90-03F 50w.....	\$31.47
12" A30EU80-01F 35w.....	\$29.44
12" A30FU20-01F 65w.....	\$42.09



### MUSICAL INSTRUMENT

8" B20HP14-01F 50w.....	\$23.54
12" A30GC40-01F 100w.....	\$57.92



RPG Speakers are only available from:



562 Spencer Street, West Melbourne.  
Phone (03) 329-7888.  
1103 Dandenong Road, East Malvern.  
Phone (03) 211-8122.

## Sinclair ZX80

Australia's first  
under \$300 computer

**\$295**  
INCL. ZX80 BASIC  
MANUAL



With Sinclair ZX80, for just \$295 you get everything you need including leads for direct connection to your own cassette recorder and television. The ZX80 really is a complete, powerful full-facility computer matching or surpassing other personal computers costing much more.

Two unique and valuable components of the Sinclair ZX80: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC manual.

The ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer because the ZX80's brilliant design packs the RAM so much more tightly. (Key words occupy just a single byte). You can add to the memory via the expansion port, giving a maximum potential of 16K.

Now available from:

**EMONA ENTERPRISES PTY. LTD.**  
CBC Bank Bldg., 661 George Street,  
Haymarket, Sydney. (02) 212-4815.

**EMTRONICS**

649 George Street, Sydney.

**Order Form:** Emona Enterprises P/L,  
PO Box 188, Coogee, NSW, 2034.

Ready-assembled Sinclair ZX80 Personal Computer, excl. mains adaptor.....	\$295.00
Mains Adaptor.....	\$9.50
Memory Expansion Board(s) takes up to 3K bytes.....	\$28.50
RAM Memory chips — standard 1K bytes capacity.....	\$10.00
TOTAL.....	\$

Please send further information and prices:

Sinclair Measuring Instruments ☐

SEW Multitestors/panel meters ☐

National Semiconductors — new  
range of calculators ☐

Consumer products: electronic kits, childrens metal detectors, radios/clock radios, walkie talkies, intercoms, mics, h/phones, car sound equipment, dictating and business machines, etc. ☐

I enclose cheque/Bankcard. Total \$.....

\_\_\_\_\_

Name.....

Address.....P' code.....

# Call VSI's 'HOT LINE'



for **PHILIPS**  
Transistors • Diodes • Integrated Circuits  
Capacitors • Resistors • Connectors  
and Ferrites

Call VSI's 'Hot Line'

**SYDNEY**  
**438 3960**

**MELBOURNE**  
**877 5822**



VSI  
ELECTRONICS  
(AUSTRALIA)  
PTY LTD

formerly




CEMA  
ELECTRONICS  
PTY LTD

Adelaide 51 6483    Brisbane 52 4261    Perth 328 8091
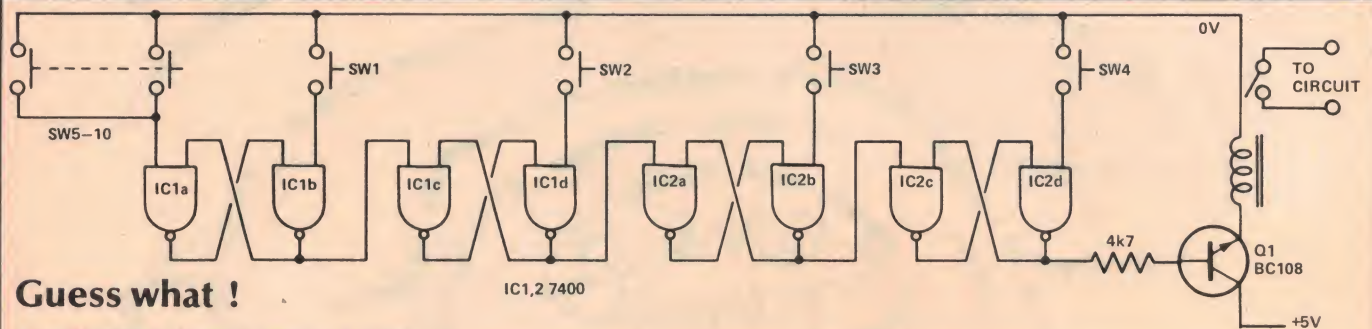
# Ideas for Experimenters


These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.



## Guess what !

ANOTHER COMBINATION LOCK we hear you say! This one, from **Denis Dowling of Mulwala, NSW**, only operates the relay when the switches are pressed in the correct order. The unit provides a large number of combinations to foil the would-be thief. By the way, the correct order for this circuit is SW1, SW2, SW3, SW4, but of course, when you build the unit these switches can be mounted in any order. If any of the switches SW5 - SW10 are pressed the circuit will reset. The ten switches should be mounted in a matrix and wired in the combination order you wish.

## Slave Flash

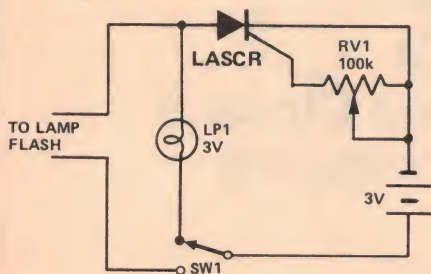

This is a simple but effective slave flash unit for use with the fusible type of flash bulb (magnesium filament). The firing is done using an LASCR which is an SCR which is triggered by light. When the master flash gun fires the LASCR is switched on, allowing current to flow to the flash bulb. The bulb blows and the LASCR turns off (as the supply is then not connected).


To set the sensitivity, switch the output over to the light bulb LP1, and adjust RV1 for reliable triggering from the master flash. A simple, but effective idea from **Michael Saleeba of Croydon, Vic.**

## SCR oscillator

An SCR can be made to oscillate when connected in the circuit as shown. The component values specified give 100  $\mu$ s pulses at intervals of 28 mS. The output voltage with a 10 V supply is about three volts.

The current through the bias resistors, R3 and R4, must be high enough to allow adequate gate current for reliable switching. The charging resistor, R2 and the supply voltage are chosen so the current through the SCR is below its minimum holding current.

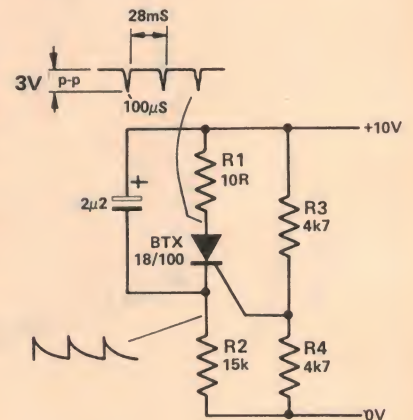
The frequency is determined by the gate voltage and the value of the capacitor. The output voltage is largely dependent on the voltage on the capacitor when the SCR fires. Pulse width is determined by the value of R1 and the capacitor.




The circuit can be voltage controlled by altering the gate voltage, but this will also alter the output voltage. Another cunning circuit from **Phillip Denniss of Chippendale, NSW**.
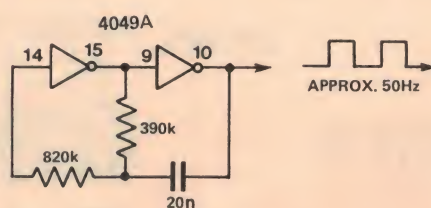
## Signal injector for logic probe

**Ian Shearer of Darwin, NT**, added a signal injector to his ETI-148 logic probe using two inverters and a two-pole, three-position switch. The centre position is a test function, which, when the oscillator and probe are working correctly, should light all LEDs on the probe.



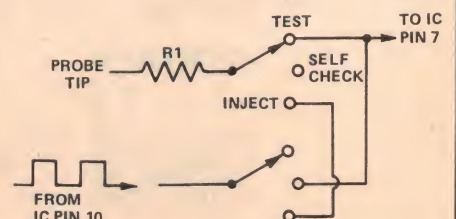The oscillator circuit uses two inverters in a 4049 IC and oscillates at about 50 Hz. The frequency can be varied by changing the values of the capacitor and the two resistors.



# TASMAN ELECTRONICS

12 Victoria Street,  
Coburg 3058.  
Phone (03) 354-5062.

## DIODES.

AAY30.....	40c
BA102.....	70c
BA244.....	22c
BP104.....	\$2.80
BYX71.....	\$1.20
HP5082.....	\$2.50
OA47.....	40c
OA90.....	20c
OA91.....	20c
OA202.....	80c
OA636.....	70c
P600G.....	90c
1N3493.....	\$1.70
1N3493R.....	\$1.70
1N4001.....	08c
1N4002.....	10c
1N4004.....	10c
1N4007.....	20c
1N4148.....	06c
1N5404.....	40c
1N5408.....	80c

## ZENERS

400mW.....	
3V3-33V.....	19c
1 WATT.....	
3V3-33V.....	30c
2½ WATT.....	
8V2-18V.....	65c
5 WATT.....	
5V1,12,15V.....	\$1.20

## LINEAR IC

301.....	50c
307.....	70c
308.....	\$1.20c
310.....	\$2.60
311.....	70c
318.....	\$3.20
319.....	\$3.50
324.....	\$1.00
339.....	90c
358.....	70c
377.....	\$2.70
378.....	\$4.20
379S.....	\$6.90
380N14.....	\$1.50
381.....	\$2.30
381AN.....	\$3.96
382.....	\$2.00
383.....	\$3.20
387.....	\$1.80
388.....	\$1.38
555.....	35c
556.....	\$1.20
565CH.....	\$3.30
566.....	\$3.10
567CH.....	\$3.00
709.....	80c
710.....	80c
711.....	80c
725.....	\$4.20
739.....	\$2.80
741.....	30c

747.....	\$1.00
748.....	60c
1458.....	60c
1558.....	\$1.90
1830.....	\$2.80
2917.....	\$3.20
3089.....	\$4.20
3360P.....	\$1.40
3911.....	\$1.60
3914.....	\$4.50
3915.....	\$4.50
3916.....	\$4.50
7392.....	\$3.30
13600.....	\$2.20
CA3046.....	\$1.65
CA3080.....	\$1.90
CA3086.....	65c
CA3130.....	\$1.50
CA3140.....	\$1.50
CA3302.....	70c
CA3401.....	80c
LF356.....	\$1.10
NE571.....	\$7.50
MC1494L.....	\$6.65
OM350.....	\$7.90
RC4136.....	\$1.45
SAK140.....	\$2.64
TBA641.....	\$2.40
UAF771.....	50c
UAF772.....	98c
UAF774.....	\$1.70

## DISPLAYS

FND350.....	\$1.98
FND357.....	\$1.40
FND500.....	\$1.40
DL747.....	\$3.50
MV57164.....	\$3.80

## SCR's

C103YY.....	80c
C106Y.....	65c
C106D.....	90c
C106E.....	70c
C122D.....	\$1.30
S4015L.....	\$1.90
S2025H.....	\$3.75

## TRIAC's


SC141D.....	\$1.30
Q4015L5.....	\$2.80
BT139-600.....	\$2.80

## TRIM CAPS

1P4-5P5.....	30c
2P-22P.....	40c
5P-65P.....	30c
5P5-40P.....	40c

MAIL ORDERS — \$1.00  
min. post & pack please.

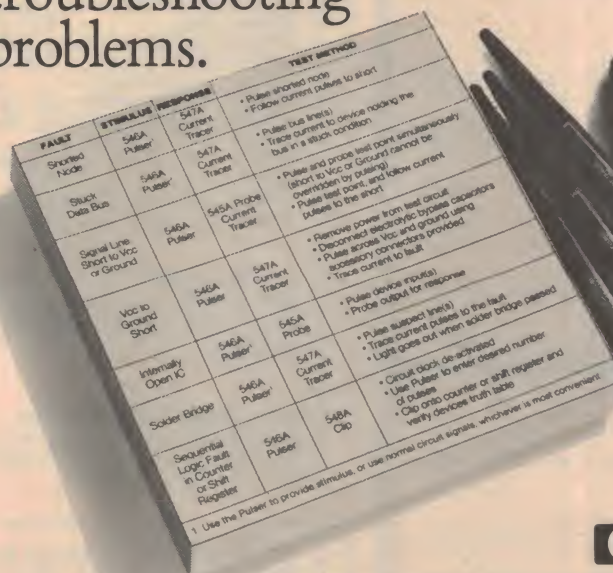**MAIL US THIS AD**  
and we'll help you  
discover simple, effective  
solutions to difficult  
troubleshooting  
problems.



**Logic Pulser** stimulates IC's in-circuit for testing. Automatically drives the circuit to its opposite state. No unsoldering components or trace cutting. \$125-\$190.

**Logic Probe** shows pulse activity: HIGH, LOW or bad level; single pulses or pulse trains. More convenient than a scope. \$100-\$150.

**Logic Clip** displays state of up to 16 IC pins at once. Automatic operation, overload-protected. \$125.

**Current Tracer** inductively senses and displays current pulses, finds shorts and stuck nodes. Uses in-circuit current or pulses from logic pulser. \$380.


I want to discover easy solutions to difficult troubleshooting problems. Please rush me a free copy of HP's 20-page IC Troubleshooters Catalogue. Prices subject to change, duty & sales tax.

Name: \_\_\_\_\_

Company: \_\_\_\_\_

Address: \_\_\_\_\_

P/Code: \_\_\_\_\_ Phone: \_\_\_\_\_

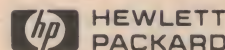


Adelaide 272 5911/ Auckland 68 7159/ Brisbane 229 1544/ Canberra 80 4244/ Melbourne 89 6351  
Perth 386 5455/ Sydney 449 6566/ Wellington 87 7199

ENTER THE 80's NOW WITH

# UNI-BOARD

THE "UNIVERSAL" CIRCUIT BOARD

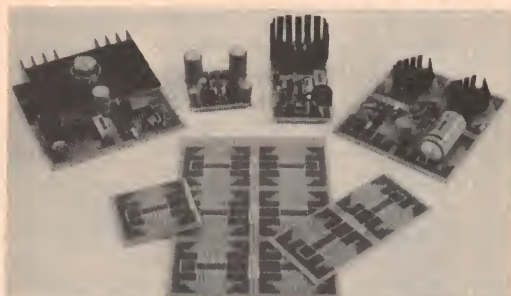

## BUILD ALMOST ANY CIRCUIT

- AMPLIFIERS
- REGULATED POWER SUPPLIES
- LINEAR IC CIRCUITS
- DIGITAL IC CIRCUITS
- PRE-AMPS, TONE CONTROLS
- STANDARD 6 PACK UNI-BOARD (41" x 6 1/2") HAS SOME 2,800 HOLES SO IT CAN EASILY ACCOMMODATE EVEN 40 PIN IC's
- MANY, MANY MORE!

## ECONOMY PLUS!

UNIBOARD WILL SAVE YOU MONEY.

- NO WASTE — SURPLUS BOARD CAN BE USED ON ANOTHER PROJECT
- USE AGAIN & AGAIN
- LOW COST "BREAD BOARDING"
- PROTOTYPE LAYOUTS CAN ALSO BE USED FOR YOUR "UNI-BOARD" PRODUCTION RUN
- BOARD EASILY CUT OR TRIMMED TO SUIT THE SIZE OF YOUR PROJECT.

### PRICE LIST

UNI-BOARD SINGLE MODULE PACK (STANDARD GRADE) .....	\$2.20
UNI-BOARD SINGLE MODULE PACK (PROFESSIONAL GRADE — F/GLASS) .....	\$2.60
UNI-BOARD TWIN PACK (STANDARD GRADE) .....	\$3.20
UNI-BOARD TWIN PACK (PROFESSIONAL GRADE — F/GLASS) .....	\$3.80
UNI-BOARD SIX PACK (STANDARD GRADE) .....	\$7.97
UNI-BOARD SIX PACK (PROFESSIONAL GRADE — F/GLASS) .....	\$9.90

TO: ADVANCED ELECTRONIC SYSTEMS PTY LTD  
3 STANILAND GROVE, ELSTERNWICK 3185

PLEASE SUPPLY ..... UNI-BOARDS AT \$.....EA.  
I ALSO ENCLOSE 70c P&P.

NAME.....

ADDRESS.....

POSTCODE.....

# RADIO DESPATCH SERVICE

869 George Street,  
Sydney, NSW. 2000.  
(Near Harris Street)  
Phone 211-0816, 211-0191.

## HITACHI OSCILLOSCOPES



	Excl. tax	Incl. tax
V 152 15 MHz Dual Trace ....	\$560.00	\$644.00
V 302 30 MHz Dual Trace ....	\$880.00	\$1021.00
V 550 50 MHz Dual Trace ....	\$1670	\$1920.50
2 types of probes extra \$20.00 and \$35.00 plus sales tax.		

### Texas Calculators

TI. 1750 .....	\$16.40	\$18.15
TI/B.A. II .....	\$40.97	\$45.35
TI.50 .....	\$36.40	\$40.30
TI.55 .....	\$53.35	\$59.00
TI. Programmable 58C .....	\$132.00	\$149.00
TI. Programmable 59 .....	\$265.00	\$299.90
PC100 C Printer .....	\$210.00	\$237.00
Speciality Pakettes .....	\$8.30	\$9.10
Library Modules .....	\$33.32	\$36.90
ELI Attractor De-soldering Tool .....		\$12.60
"ISO-TIP" Portable Cordless Soldering Iron .....		\$33.00
CC 250 Universal Current/Polarity Checker .....		\$6.25
"ARLEC-TPI" Thermo Plug .....		\$15.52
RE-501K ROSS Electronic Cassette Head Demagnetiser .....		\$20.15
5DH-7D Raimar Stereo Headphone Sets .....		\$11.07
S2010 Altronic Horn Speaker 8ohm 5 watt .....		\$8.90

We specialize in P.C. Boards for ETI and E.A. projects. Scotchcal front panels for recent ETI and E.A. projects

### MAIL ORDER CUSTOMERS

\$1.00 packing plus 5 percent of order value up to \$80.00, thence a flat \$4.00 for postal items. Carrier — freight on.

OPEN: Mon-Fri 8 am to 5.30 pm.  
Thursday night late shopping till 8.30 pm. Saturday 8 am to 11.45 am.


# Ideas for Experimenters

## SWR trimmer for homebrew halfwave

Max Soul of Weipa, WA, uses a half wave dipole from his location just 400 metres from Albatross Bay. His antenna is made from aluminium window box section with tuning rods attached to each end for fine adjustment of SWR.

The brass insert from an electrical connector is filed down to a tight fit inside the box section at the top of the antenna. Two holes are drilled through the box section to align with the holes in the connector. The screws hold the brass insert in place and also clamp a length of 4 mm welding rod. The SWR is adjusted by moving the welding rod in and out while using an SWR meter. When the correct position is found, the rod is clamped tightly in place with the two screws.

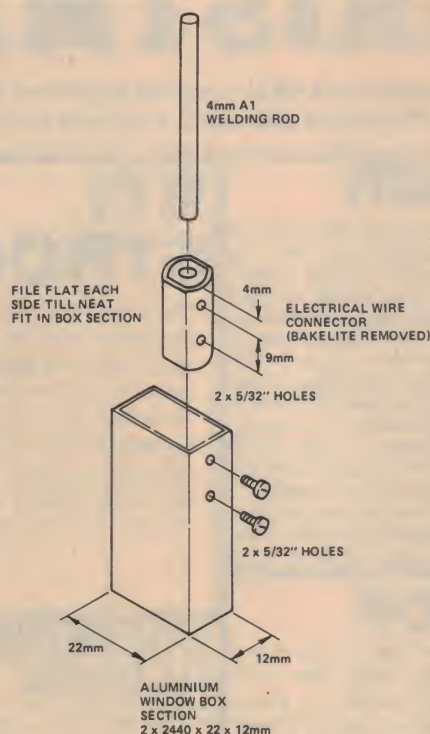Max has achieved SWR readings as low as 1.1/1 using this system, though his location near the sea requires him to clean the contact surfaces twice yearly.




## Automatic cutoff for a manual turntable

Mr. T. Threlfall of West Perth, WA, built this unit into a manual turntable to prevent the record being carved up, or more likely, to prevent stylus wear if he forgot to take the tone arm off after the record had finished.

A neon tube is mounted in the end of a black plastic tube and an LDR is on the other end. A slot is cut across the tube so the light beam can be interrupted by a small plastic flag connected to the tone arm shaft. The flag must be light, to

allow proper operation of the tone arm, and positioned so the light is interrupted when the tone arm is at the end of the record.

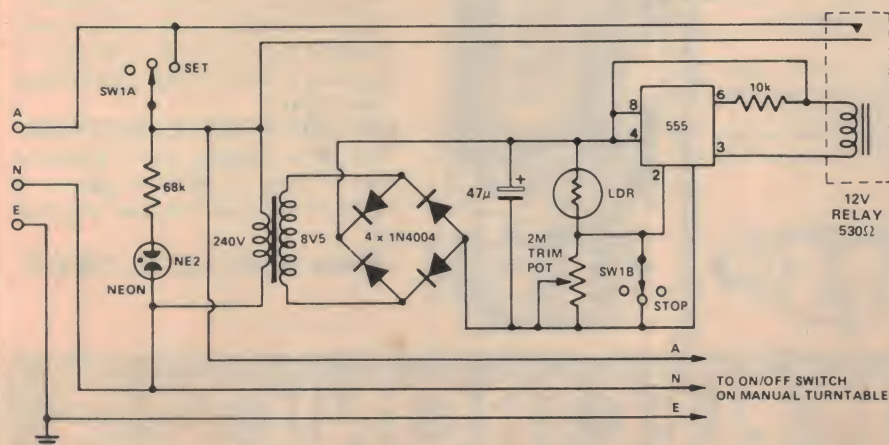The 555 latches when the voltage on pin 2 rises, operating the relay and starting the turntable. When the beam is broken the voltage on pin 2 falls, the relay drops out and the turntable stops. The potentiometer is adjusted for correct operation.




## Keyboard modification

Len Henson of Dural, NSW, submitted this modification for the KBO4 keyboard used with the 5740 decoder to give a lower case keyboard function.

The copper track is cut between pin 31 of the UART (D6) and pin 10 of the 7407 and the circuit modified as shown.

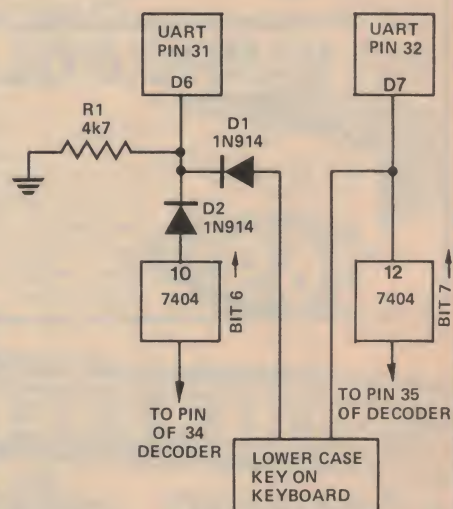With the key depressed, HEX 00 — 3F are unaffected, HEX 40 — 5F are raised to HEX 60 — 7F, giving lower case. As the KBO4 is easy to expand (keywise) the modification is a junkbox project which, since no special lower case routine is necessary, saves memory space. A flip flop could be added between the key switch and the diode D1 if required.



## Any ideas ?

Have you had a bright idea lately, or discovered an interesting circuit modification? We are always looking for items for these pages so naturally, we'd like to hear from you.

We pay between \$5 and \$10 per item — depending on how much work we have to do on it before we publish it.

The sort of items we are seeking, and the ones which other readers would like to see, are novel applications of existing devices, new ways of tackling old problems, hints and tips.

# BUILD NOW FOR CHRISTMAS!



Get ready for the Christmas festivities and save \$\$\$! You'll be surprised at how easy a Dick Smith Kit is to build; and your Christmas bill won't cost you a fortune!!!

## NEW EA CHASER



**\$69<sup>50</sup>**

Cat. K-3145

What a way to add life to your next Christmas party with this incredible Light Chaser.

Features include reverse/forward chasing, variable flash rate control plus an invert/normal switch. This switch can make two lights appear to move instead of one at a time. The versatility is increased with 'auto reverse' & 'auto invert' functions. When either control is switched on, the unit will automatically invert or reverse the display at any set rate. All this makes it a worthwhile project that will save \$\$\$ and give hours of entertainment.

## ETI STROBE



**\$34<sup>50</sup>**

Cat. K-3152

Get your Christmas party swinging with this superb Disco Strobe. This popular kit contains up-to-date circuitry and comes complete with photographic type reflector, perspex safety guard and instructions. Vary the flash rate to the beat of your music.

## EA MUSIC COLOR



**\$69<sup>50</sup>**

K-3140

Turn your music into a light show. This unit will accept an audio input from almost any amplifier and uses the information to control 3 channels of colour. The ideal unit for your Christmas or New Year's party, disco, bands etc etc. Also makes an ideal present.

## COLOURED GLOBES

Ideal for discos, parties etc. Use with your Musicolor. Available in 4 colours: yellow, red, blue, & green.

**\$7<sup>95</sup>ea**

Cat. S-3850/52/54/56



SWIVEL BASE Globe Holder attaches to wall or ceiling.

**\$3<sup>50</sup>**

Cat. P-5620

## HOLD IT!

Line socket for bayonet mount lamps makes it ideal for running wander light leads for loft & outside. Ideal for holding standard colour globes for parties, Xmas decorations outside etc.



P-5510

**95¢**

## OTHER EXCITING DICK SMITH KITS...


### ACOUSTIC COUPLER

We've lost count of the number of customers who have asked for this project: well here it is! This acoustic coupler acts like a modem without any physical connection to the phone lines. It uses your standard telephone handset, placed over a small microphone & speaker in the coupler case, & transfers the information from your computer by sound. Hence the name, acoustic coupler. Now you can have your computer talk to another across the street, across the town - even across the country (or further!) It is a must for all serious computer users, and we hope to release the kit soon.

**A must for everyone with a computer**

**\$75<sup>00</sup>**

Cat. K-3605

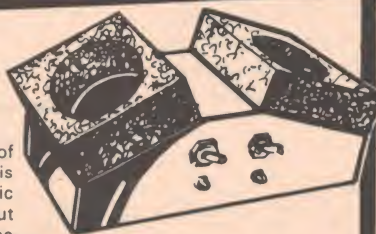

### LEDS & LADDERS GAME



**NOW ONLY**

**\$15<sup>75</sup>**

One of our most popular kits of the past was the intriguing 'LEDS & LADDERS' game described in EA in 1975. Now EA have come up with a new version of the game which is not only easier to build, it is also easier to play! Can you climb out of the well without being plummeted down again?

**AND NOW FOR THE BEST NEWS:** This kit is actually \$1.00 cheaper than it was in 1976 - despite 4 years of inflation! Makes an ideal gift.

**Was \$16.75 in 1976**

Cat. K-3390

# DICK SMITH ELECTRONICS



SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS

# Shoparound

THIS PAGE is to assist readers in the continual search for components, kits and printed circuit boards for ETI projects. If you are looking for a particular component or project — check with our advertisers if it is not mentioned here. Also, for a list of suppliers who stock the ETI projects published over the last few years, our "Kits for Projects" page may generally be found on the page immediately before the DREGS page (inside the back cover).

Readers should have little difficulty obtaining parts for this month's projects.

For the **Electronic Dummy Load, ETI-147**, the relay we used is an Omron type LY2. We paralleled the contacts for greater current carrying capacity. Other types may be used and almost any 24 V relay with contacts rated at 15 A, or pairs of contacts rated at 10 A each, will do the job. It won't be called on to switch full load very often and it will only be switching dc on a resistive load, so little trouble should be experienced.

The heatsinks for this project we obtained from Dick Smith and they are listed as catalogue number H-3426. They measure 225 mm long by 105 mm wide. Rod Irving Electronics stock a similar heatsink, with a slightly better thermal capacity, but the nearest standard length is 300 mm. They can have it cut to size we are informed, so you might ask.

## Front panels, meter faces etc

Scotchcal front panels, meter scales and labels for our projects are available from a number of suppliers. In Sydney, Radio Despatch Service, 869 George St, Broadway, stock a small supply for our projects from 1979 onwards. If they don't have what you want in stock, then they'll make it up on order. Electronic Agencies also stock a supply of front panels and meter scales for our recent projects. They're at 115 Parramatta Rd, Concord.

In Melbourne, Rod Irving Electronics of 425 High St, Northcote stock front panels, labels and meter faces for our projects from 1979 onwards and generally have stocks available for current issue projects shortly after the issue goes on sale. All Electronic Components stock panels and meter faces from way back and generally have

stocks for current issue projects shortly after we go on sale also. They're at 118 Lonsdale St, right in the heart of Melbourne.

## The 3080 again !

Last month we omitted to mention an important supplier of this useful device. The CA3080, by RCA, is distributed here by AWA. You can buy the IC direct from the AWA Micro-electronics division at 554 Parramatta Rd, Ashfield 2131. Many thanks to the reader (an avid 3080 fan!) who drew our attention to this omission.

## 'Universal' circuit board

Every month — nay, every day! — the post brings a swag of 'press releases' about the products of various companies. Every (and we mean *every*) press release extolls the virtues of the product about which it is written. Many weird and wonderful products are drawn to our attention, plus the usual 'run-of-the-mill' range of new products which are updates on familiar items. However, every now and then, a product comes to our attention that sets itself apart from the rest. We refer to "Uni-board".

We ran a small item on the product under *Briefs* in August *News Digest* (page 9). We rang the supplier, Advanced Electronic Systems, for more information and some weeks later their Director arrived on our doorstep with

samples, photographs ... and more information.

The product struck us as a good idea well done. Uni-board is a printed circuit board with rows of holes at 2.5 mm intervals. The pc tracks are arranged in a carefully thought-out pattern to accommodate ICs from eight to forty pins, along with discrete components in a convenient grouping. Uni-board is useful for either prototyping, experimenting or for complete projects and can accommodate power transistors, including heatsinks, trim pots, power resistors etc and even bridge rectifiers. Apart from that, the product has several unique — and very useful — features. To assist in arranging the component layout, all the circuit trackwork is reproduced on the 'top' side of the board in a colour-coded pattern. A brilliant innovation. All the pc tracks are solder coated to assist assembly. We understand Uni-board is available in single and double board packs as well as six board packs. A multi-board pack is economical to use and can be trimmed to suit the size of your project or prototype.

Uni-board is Australian designed and manufactured. You can obtain an 'introductory kit' from Advanced Electronic Systems Pty Ltd at 3 Staniland Grove, Elsternwick Vic 3185, for \$9.95 including post and packaging. In this kit you get a Uni-board twin pack and a six pack, plus an applications manual.

## Project price estimates

This information is published as a guide and a variety of factors may affect the actual price of a project, whether obtained as separate components or as a kit.

ETI-568 Flash Trigger	\$27 - \$33
ETI-147 Electronic Load	\$68 - \$75
ETI-327 Turn/Hazard Unit	\$18 - \$22



Uni-board is a "universal" prototyping and construction pc board for electronic projects. It can be obtained with fibreglass or phenolic base material and in packs containing single, twin and six modules.

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. PH (03) 489-8131

**425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. PH (03) 489-8131.  
RITRONICS WHOLESALE PH (03) 489-7099, MAIL ORDERS PH (03) 481-1436**

# ELECTRONIC COMPONENT SUPPLIERS DESIGNERS AND MANUFACTURERS.

7106	12.90	220uf	.20	1.1, 2.1, 5	1.00	OPTOCOUPERS	ETI 152	\$2.00	ETI 561	\$2.75	79md9	\$2.20	(Redesigned board with notes to eliminate 6875 clock chip.) Please note boards are figerglass 1 oz copper precision drilled.
7107	15.00	330uf	.25	1.8uf	1.00	MCT2	ETI 261	\$1.50	ETI 573	\$2.90	80au3	\$2.90	
7210	13.20	470uf	.35	2.2uf	1.20	MCT6	ETI 264	\$1.50	ETI 576	\$4.50	80cm3A	\$2.40	
LS7220	6.00	1000uf	.50	3.3uf	2.00	MCT275	ETI 321	\$3.90	ETI 577	\$2.70	80cm3B	\$3.50	
280 CPU	14.00	2200uf	.90	4.7uf	3.40	MCC671	ETI 322	\$2.75	ETI 606	\$2.30			
280A CPU	16.00	35V				4N28	ETI 452	\$5.90	ETI 726	\$3.30			
280 P10	13.80	2u2/3u3	.10			4N33	ETI 466	\$6.50	80sa3	\$3.90	DREAM 6800	\$10.90	
280A P10	16.50	10uf	.15			4N26	ETI 474	\$2.20	79FE11	\$2.50	DREAM 6802	\$11.90	
280 CTC	13.80	100uf	.20				ETI 470	\$2.70	79UPS6	\$2.90			
280A CTC	16.50	220uf	.30				ETI 471	\$9.90	79T111	\$2.20			
280 DMA	40.70	1000uf	.70				ETI 472	\$2.70	79SF9	\$2.60			
280 S10/0	56.90	2000uf	.90				ETI 541	\$2.60	79PS11	\$2.90			
280 S10/1	56.90	2200uf	1.10				ETI 549A	\$2.50	79se3	\$3.90			
280 S10/2	56.90	50V											
280A S10/0	63.00	0.47uf	.08										
280A S10/1	63.00	1u2u2	.08										
280A S10/2	63.00	3.3uf	.15										
8035	27.00	4.7uf	.15										
INS8050	15.00	10uf	.15										
INS8080	8.00	22u33u	.20										
P8085	25.00	47u/100u	.20										
8155	22.00	220uf	.50										
8165	22.00	470uf	.60										
8205	5.00	63V											
P8212	4.00	0.47uf	.10										
8214	8.00	1u2u2	.10										
8216	5.90	3u3/4u7	.10										
8224N	5.50	10u25u	.15										
8224	7.50	47uf	.20										
8226	5.90	100uf	.25										
8228	9.50	63V											
8238	8.00	220uf	.40										
8243	8.00	330uf	.45										
8251	14.00	470uf	.80										
INS8251	6.50	160V											
8253	19.50	2.2uf	.20										
8255A	8.60	10uf	.30										
8257	99.00	22uf	.50										
8259	99.00	250V											
8275	99.00	2.2uf	.25										
8278	99.00	350V											
8295	25.00	1uf	.20										
DM8578	3.50												
Ay-5-2376	19.56	35V											
MM5104N	10.00	2500uf	1.95										
MM55106N	10.00	40V											
MM57160	7.50	5600uf	1.90										
8748A	99.00	50V											
8755A	99.50	6800uf	4.50										
MCT2	.80	63V											
MCT6	3.30	2500uf	3.25										
MCT275	1.50	75V											
MCC671	3.00	3300uf	5.90										
4N28	.85												
4N33	1.20												
4N26	.85												
MM80C95	.90	3u3/4u7	.30										
80C96	.90	10u22uf	.40										
MM80C97	.90	33uf	.69										
80C98	.90	47uf	.80										
CAPACITORS		100uf											
16V		125V											
33uf	.15	100pf to	.45										
330uf	.40	10,000pf to	.55										
25V		10,000pf											
100uf	.25												
330uf	.45												
2500uf	1.00												
50V													
2500uf	2.15												
63V													
10uf	.16												
47uf	.30												
100uf	.40												
220uf	.55												
470uf	.75												
1000uf	1.65												
RB. (PCB)													
6.3V													
470uf	.20												
1000uf	.30												
10V													
4.7uf	.10												
100uf	.10												
16V													
10uf	.08												
22uf	.10												
33/47uf	.10												
100uf	.15												
220uf	.20												
470uf	.25												
640uf	.45												
1000uf	.40												
2500uf	.65												
25V													
2u2/3u3	.10												
4u7/10u	.10												
25u33u	.12												
47uf	.13												
100uf	.15												

All prices current only until 15th November, 1980.

For heavier items add additional postage. Extra heavy items sent Comet freight on. Prices subject to change without notice. Send 60c and SAE for free catalogues. Minimum pack and post \$1.00. Bankcard Mail Orders welcome.

## Economy Sized Computers™ don't stunt your growth.



A lot of small business computers are like our ads—they start out small and stay that way.

But Vector's Economy Sized Computers grow as you grow. Whenever you need to, you can have up to 4 more terminals, more power, more memory.

With Economy Sized Computers, you get data and word processing capabilities you only expect from much larger computers. All for the price of a new copying machine—

See the Vector Economy Sized Computers at your nearest computer dealer.

Because no matter how small they may look, their performance grows on you.

**VECTOR**  
VECTOR GRAPHIC INC.

Dicker Data Projects P/L

31 Cawarra Road, Caringbah, 2229.

Ph: (02) 524-5639, 525-4707. Telex: 70182.

NSW: Chatswood (02) 911-1892, Quakers Hill (02) 626-9874, Albury (060) 21-3926, Coffs Harbour (066) 52-4077, Newcastle (049) 26-2644. QLD: Brisbane (04) 229-4710, Cairns (070) 51-3632. VIC: Melbourne (03) 878-1255. WA: Perth (09) 321-9232, Bentley (09) 362-1745. TAS: Hobart (002) 34-9018.

# LETTERS

Dear Sir,

Have you ever published a design for a receiver antenna suitable for use on HF, VHF and UHF bands, 30 MHz to 514 MHz? If you haven't published such a design, could you recommend a commercially available antenna construction book?

**L. Jones  
Subiaco, W.A.**

Unfortunately, we have not published the design of such an antenna, I doubt if anyone has published a single antenna design to do the job you ask.

Theoretically speaking, the "discone" antenna is capable of doing the job, but in practice, there are difficulties. The nearest thing to your requirements that we have described as a project is the ETI-714 Log-Periodic Antenna. This was published in the February and March issues, 1978. It covers 40 MHz to 250 MHz.

For books on the subject, you might look at "The Radio Amateur Antenna Handbook" by Orr and Cowan; the "ARRL Antenna Handbook" by The American Radio Relay League or perhaps "The Radio Handbook" by Orr. Most libraries will have copies or can obtain them on inter-library loan. Many technical book specialists also carry them, as do Dick Smith Electronics.

Dear Sir,

I am very interested in electronics and would like to learn about radio and hi-fi systems. I know very little about these fields and would like to learn. Could you please tell me where to get information on the basics of radio and hi-fi.

The article in your July issue about "Good Car Sound" was much appreciated. Sealing the cavity in the doors and boot made a big difference to my modest system!

**Stephen Sutcliffe  
Parramatta, NSW**

It is very difficult for us to suggest a book that covers the basics of hi-fi. Quite a number are available pitched at "the layman" but it seems you want something more technical. Unfortunately, we've seen nothing recently that covers the technical basics of the subject.

The same is not true for radio, though.

"A Course in Radio Fundamentals" by George Grammer, published by The American Radio Relay League, covers the subject very thoroughly. Most technical book specialists stock it. A series of books, published by Hayden, called "Electronics One", "Electronics Two" etc also covers the subject, but in a more descriptive manner. These are distributed here by Butterworths Pty Ltd, 586 Pacific Highway, Chatswood NSW 2067.

Dear Sir,

People these days are becoming increasingly interested in CB radios. Would it be possible for you to design a "compact" walkie-talkie which would include such features as good sensitivity, low current drain, reasonable working range (5 - 10 miles), squelch, beeper, a range of channels (say three or four of the most used ones, including ch. 14) and incorporating "chips".

It may sound a lot, but if you are able to do this in the near future (say two issues) I think it would be worthwhile. Price should be less than \$30, if possible.

**Chris Muller  
Bellington, NSW**

It not only "sounds a lot" — it's quite a tall order! For certain, we could design such a project, but unfortunately it is not practical. Firstly, a licence would have to be obtained by any person wishing to use the completed equipment. For you to obtain the licence, the equipment would need to be 'type approved' by the P & T Department. As performance would be subject to variations in construction — including possible modification — we doubt type approval would be forthcoming. It's not that we couldn't design a unit to meet the appropriate specifications, it's that actual performance is completely in the hands of the constructor.


Getting onto the technical problems, a reasonable working range of "5 - 10 miles" with a walkie-talkie requires power. This precludes low current drain — except perhaps in the receiver. In any case, the range will depend greatly on terrain and antenna efficiency — and antennas suitable for handheld transceivers are generally inefficient. Lastly, I doubt if such a project would cost "less than \$30".

It seems like a good idea . . . at first.

**Sm ELECTRONICS**  
MELBOURNE  
Ph (03) 842-3666

Trading Hours: 10am-6pm Mon to Fri.


## S-100 I/O PORT BOARD

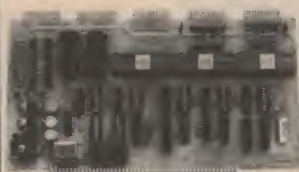

Now with dual serial ports


**DUAL SERIAL I/O CARD** Features:- dual independently controlled serial ports with TTY and RS232 outputs and inputs. Nine programmable parallel ports, crystal controlled baud rates fully buffered and address decoded. Plated through holes & solder resist mask.  
Price: Kit \$189. Ass. \$225.

## UV EPROM ERASER

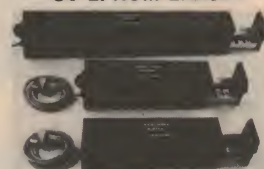

New product range. Model LEE/T 15W tube, 120 min timer, up to 40 EPROMs will erase in 10/15 mins. Model MEE/T 8W tube 120 min timer, up to 10 EPROMs will erase in 20/30 mins. Model MEE is same as MEE/T but with no timer. All erasers are fully assembled and have a safety switch.  
LEE/T \$125. MEE/T \$105. MEE \$85.

## S-100 EXTENDER/TERMINATOR

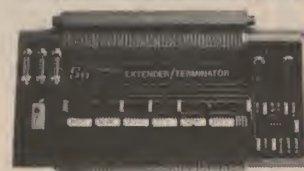

**EXTENDER TERMINATOR CARD** — features:- true active termination of the bus with inbuilt extender connector on top of board, fused rails to extended board. Test points numbered, solder resist, plated through. Price: Kit \$80. Ass. \$110.

## LA34 DECWRITER PRINTER/ TERMINAL

Desk Top printer, full 128 ASCII character set, switchable 110 and 300 baud rates, 30 cps speed, adjustable character widths, adjustable line spacing, 9 x 7 dot matrix printing. Price \$1,595 ex stock.

## TELEVIDEO TV1-912B TERMINAL

80 x 24 display, upper and lower case, 110 to 9600 baud rate, dual intensity, numeric pad, cursor controls, XY addressable cursor, block mode, self test, microprocessor controlled. Price \$1,295.

**SME  
SYSTEMS**

1096 Doncaster Rd, Doncaster East, Vic 3109.  
PO Box 19, Doncaster East, 3109. Telex AA37213.  
DEALER: Canberra — 81-5011, Sydney — 661-9237.

Send 66c in stamps for COMPUTER PRINTOUT CATALOGUE for more details.

ALL PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST).  
DEALER ENQUIRIES WELCOME.  
Prices and specs. subject to change without notice.

All prices tax free, for retail prices add 15 percent.

# Micro Computers From INDUSTRIAL MICRO SYSTEMS



**IMS SERIES 8000**



**IMS SERIES 5000**



**THE NEW MODEL 16  
HARD DISK SUBSYSTEM**

**WINCHESTER TECHNOLOGY  
WITH BUILT-IN BACKUP**

A chain is only as strong as its weakest link, and any system is only as good as its individual components. Because of the way they have been developed, you won't find any weak links in the systems made by Industrial Micro Systems. They have evolved. Evolution means survival of only the fittest components. From the popular and reliable static RAM boards to the floppy disk sub-systems, Industrial Micro Systems quality components have been used for years in thousands of systems by many well known companies around the world. With the development of the Z80 CPU, I/O cards and DMA double density floppy disk controllers, Industrial Micro Systems components have evolved into Microcomputer Systems. Thus the systems have inherited the Industrial Micro Systems quality and field proven reliability of their components.

If you are looking for only the best in Microcomputer Systems you cannot ignore the Industrial Micro Systems family of Computers and component sub-systems. Aside from their mechanical strength and reliability, the systems feature incredible versatility in regard to expansion of both hardware and software. The size of the system that you will purchase initially does not place any restriction on the ultimate size of system to which you can expand.

There are a host of other reasons why we think that these systems are the best available. Give us a call, write or drop in and see us. We will be at the 8th World Computer Exhibition in Melbourne this month so why not pay us a visit at STAND 42.

You can also see the systems in Tasmania — call Bruce Lipscombe in Computer World at 98 Main Rd, Moonah (28-6288).

## BASIC SPECIFICATIONS:-

CPU: Z80A operating at 4 MHz.

BUS: S-100 with 12 slot Motherboard.

18A at 5 Volts available.

MEMORY: 8-bit Static or 8-bit plus parity Dynamic RAM from 32K to 256K Byte using 16K, 32K, 64K memory boards.

DISKS: 8 inch: DMA, IBM format compatible, single/double density controller. 8" drives, single or double sided (500 Kb storage per side).

5 inch: DMA, soft sector, double density controller (150Kb per side).

Hard Disk (Sub-system 16) option provides 32, 64, or 96 Megabytes of storage. Subsystem 16 includes a 16 Megabyte removable SMD Technology Disk Pack for ease of data backup and archival storage and a 16, 48, or 80 Megabyte fixed media that employs Winchester 3340 technology. It also includes the Model 490 hard disk controller, credenza enclosure, cabling and disk pack for the most complete and attractive large storage capability available. Data transfer is by DMA or PIO, your choice. Transfer rate is 1.2 Megabyte/sec !

I/O: The Systems are provided with 2 RS232C serial inter-faces with software controlled baud rates up to 1920Bd. Terminal port defaults at 9600Bd, second port at 300 baud for Modems or slow printer. Plus three parallel I/O ports, all as standard. Amongst other refinements, (too numerous to mention them all), there is a real time clock provided for each user as well.

# S.I. MICROCOMPUTER PRODUCTS PTY LTD

Formerly Sigma International Pty. Ltd.

GPO BOX 72 SYDNEY 2001 92 PITT ST SYDNEY (02) 2314091 232 6804

# Australia's first under \$300 COMPUTER...

**\$295**  
INCL. ZX80 BASIC  
MANUAL

Remember — all prices shown include sales tax, postage and packing.  
N.B. Your Sinclair ZX80 may qualify as a business expense.

## Sinclair ZX80 -British made.

Until now, building your own computer could cost you around \$600 — and still leave you with only a bare board for your trouble. The Sinclair ZX80 changes all that. For just \$295 you get **everything** you need including leads for direct connection to your own cassette recorder and television. The ZX80 really is a complete, powerful full-facility computer matching or surpassing other personal computers costing much more. The ZX80 is programmed in BASIC and you could use it for anything from chess to running a power station.

Two unique and valuable components of the Sinclair ZX80: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC manual. The unique Sinclair BASIC interpreter: offers remarkable programming advantages — unique 'one touch' key word entry. The ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST etc) have their own


single key entry. Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately, preventing entry of long and complicated programs with faults only to discover them when you run.

Excellent string handling capability — takes up to 26 string variables of any length. All strings can undergo all rational tests (e.g. comparison). The ZX80 also has string input to request a line of text; strings do **not** need to be dimensioned. Up to 26 single dimension arrays. FOR/NEXT loops nested up to 26. **Variable names** of any length. BASIC language also handles full Boolean arithmetic, conditional expressions, etc.

Exceptionally powerful edit facilities, allows modification of existing program lines. **Randomise** function, useful for games and secret codes. **Timer** under program control. **PEEK** and

**POKE** enable entry of machine code instructions, **USR** causes jump to a user's machine language sub-routine. **High resolution graphics** with 22 standard graphic symbols. The Sinclair teach-yourself-BASIC manual 96 page book free with every kit.

Fewer chips, compact design, volume production means **MORE POWER FOR YOUR DOLLAR!** The ZX80 owes its low price to its remarkable design; the whole system is packed onto fewer, newer more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer because the ZX80's brilliant design packs the RAM so much more tightly. (Key words occupy just a single byte). You can add to the memory via the expansion port, giving a maximum potential of 16K.

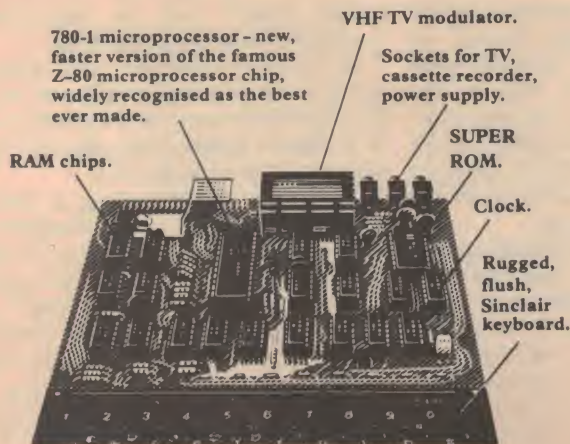

### ORDER FORM:

SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD.  
308 High St., Kew 3101, Vic. Tel. 861 6224.

Quantity	Item	Item Price	Total
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price incl. ZX80 BASIC manual, excl. mains adaptor.	\$295.00	
	Mains Adaptor(s) (600Ma at 9V DC nominal unregulated).	\$ 16.00	
	Memory Expansion Board(s) takes up to 3K bytes.	\$ 28.50	
	RAM Memory chips — standard 1K bytes capacity.	\$ 10.00	
	Sinclair ZX80 Manual(s) free with every ZX80 computer.	\$ 15.00	
TOTAL			

I enclose cheque/Bankcard/ Diners Club/Amex

☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐

Name \_\_\_\_\_ ETI

Address \_\_\_\_\_ Postcode \_\_\_\_\_



# Micro machine has it all sewn up !

**William Fisher**

Employing modern microprocessor technology and precision stepping motor drives, this machine is several 'quantum leaps' from Thimonnier's wooden wonders of 1830.

THE microprocessor-controlled sewing machine just released by Janome applies modern technology to a craft that has persisted virtually unchanged since the dawn of civilisation — embroidery.

The pace and impatience of modern lifestyles and the changing patterns of education have led to a steady decline in the popularity of decorative needlework. Few people nowadays have enough skill, patience or time to embroider by hand and although sewing machines have been able to execute fancy stitches for years, the results are generally recognisable as inferior to work done by hand.

Janome's Memory 7 sewing machine is flexible and versatile enough to match the quality and variety of hand stitching and does not require any special expertise from its operator. Thirty-one different stitch patterns are preprogrammed in its memory and each of these patterns can be varied in length and width over a wide range.

Stitches are selected by touch buttons and the machine can be programmed to run through any combination of up to seven different stitches in sequence, sewing the sequences repeatedly in rows or freehand. So for example, complex hem decoration lines can be sewn in a single pass or freestanding multi-

stitch motifs can be embroidered without resetting the machine.

A 'mirror' program will laterally invert a programmed sequence, so that a row of stitches can be matched to a row of reversed stitches, for example down either side of a blouse front.

Automatic buttonholing is nothing new, inasmuch as many machines already on the market can be set to sew a run of buttonhole stitches, but getting the buttonholes the right length has previously involved either guesswork or inserting pins at the 'stop' points (which involves some risk of breaking the needle if it strikes the pin). Janome have made the whole thing a lot easier

by building a program into the Memory 7 that allows the user simply to preset the width and length of a buttonhole. Similar buttonholes can then be repeatedly sewn without any resetting, so that all the buttonholes on a garment can be exactly matched with no trouble.


Apart from its decorating capabilities, the Memory 7 has a number of features that assist plain sewing. At the end of straight seams, it automatically sews four, on-the-spot locking off stitches to give a neat and secure finish. When the machine is stopped it automatically returns the needle to its 'up' position, clear of the workpiece, to avoid cotton jamming.

A comprehensive range of attachments allows the Memory 7 to perform overlocking, insertion of zips, scalloping, pleating, pintucking and other dressmaking operations.


We obtained a Memory 7 from Janome and gave it to staff member Elaine Ray to try out for us. Among her many other talents, Elaine is an expert seamstress, so she was able to appreciate some of the machine's features which were not obvious to the rest of us.

On the whole, she was very impressed with its performance. It's apparently very easy to operate and even the most hamfisted operator ought to have no trouble with it. In contrast to some semi-automatic sewing machines, threading and bobbin loading are child's play, which is a distinct advantage in a machine designed primarily for decorative work where colours need to be changed frequently.

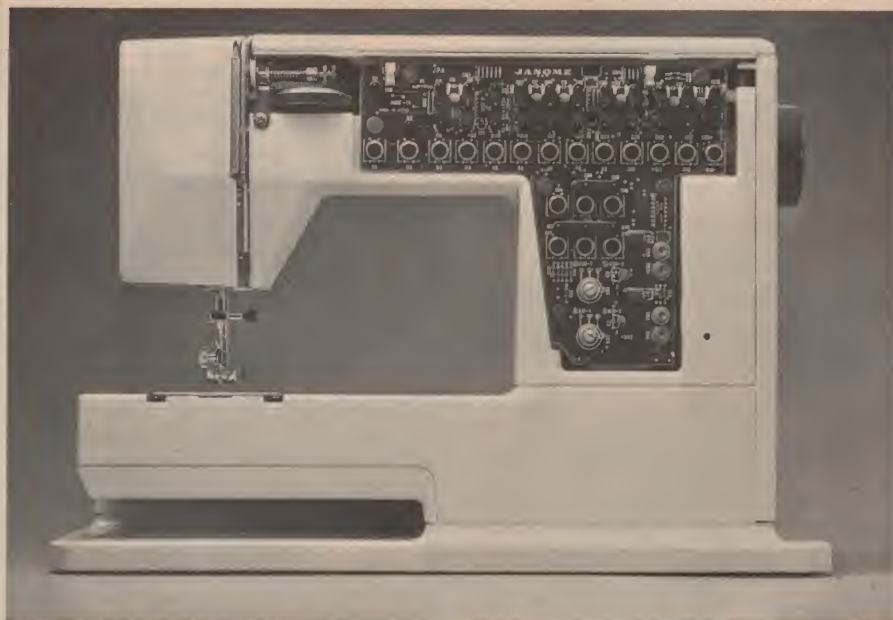The automatic tension on the machine Elaine tested worked absolutely perfectly on a variety of different fabrics, with no trace of 'pulling' or



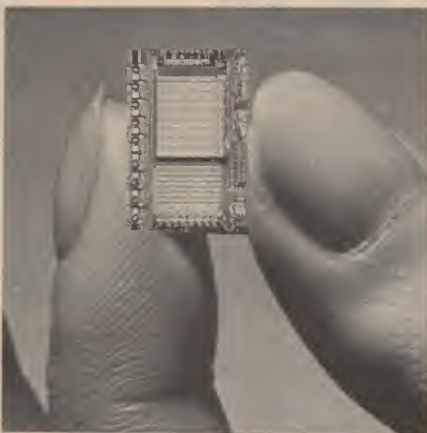Behind the side panel is an array of LEDs to show which stitches have been selected.




One of the memory chips where the stitch patterns are stored.

'spitting' caused by over or under-tensioning. She was also pleased with the number of 'stretch stitch' options in the range of stitch patterns. These are stitches that can be used for straight-forward sewing of stretch fabrics to give a seam that will stretch along with the fabric.

In fact the only practical criticism of the Memory 7 is that it has no 'gathering foot' to automatically gather up a cuff (for example) while sewing a trimming onto it. However, given the general range and versatility of the machine, this is hardly a serious drawback.

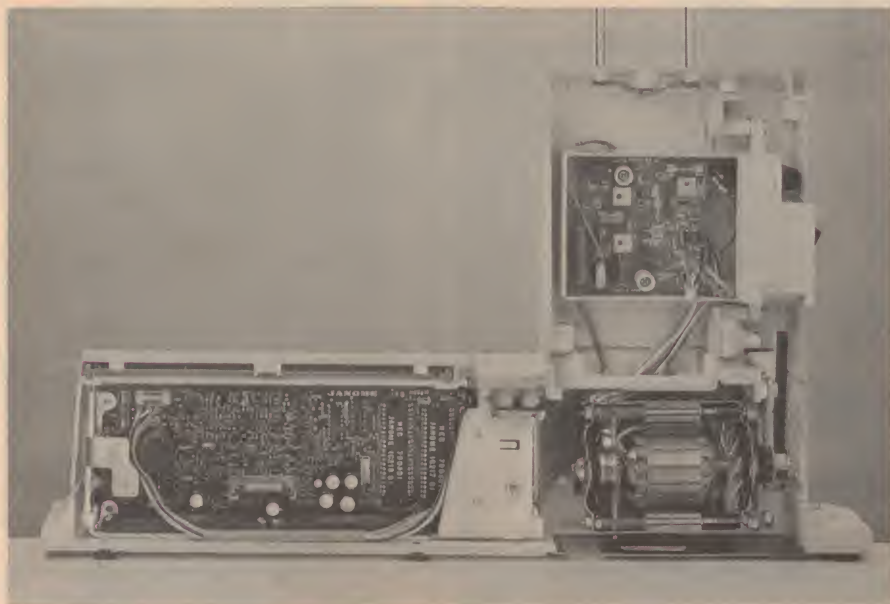The Memory 7 will cost around \$900 and is available from major retail stores and sewing centres.



Cutaway view showing the stepping motor and some of the control circuitry.

### Sewing machines — a brief history

Around 1830 Barthelemy Thimonnier built about 80 wooden sewing machines with hooked needles (steel, we hope!) to make uniforms for the French army, but they were all wrecked by rioting tailors who feared they would destroy their livelihoods.

An American, Walter Hunt, invented the eye-pointed needle in 1832 but failed to patent it. Another American, Elias Howe, incorporated it in the first lockstitch sewing machine, which he patented in 1846. This used a curved needle which carried the thread through to the underside of the fabric where it interlocked with a second thread carried by a reciprocating shuttle. Howe's machine did not have an automatic fabric feed — this was perfected in the 1850s by A.R. Wilson.

Isaac M. Singer, who invented the foot treadle and the presser foot, brought together the ideas of several of his predecessors in a machine which became the industry standard when it went into full scale production in the 1860s. In doing so, he infringed some of Howe's patents, but after a long legal wrangle Howe and Singer agreed to share their patents and both made fortunes.

The zigzag machine was developed in Japan in the 1950s and that nation is now the world's largest sewing machine manufacturer.

# ELECTRONICS COURSES

FULL OR PART TIME

- Post Trade
- Technician
- Certificate of Technology
- Computer Service

COLOUR TV  
AMATEUR - HOBBY  
RADIO  
COMPUTERS  
COMMUNICATIONS  
INDUSTRIAL CONTROL  
MICROPROCESSORS  
MOTOR SPEED CONTROL  
DIGITAL



991 Whitehorse Rd  
Box Hill 88 0691

# IMPORT COMPANY FOR SALE

WELL ESTABLISHED  
IN ELECTRONICS  
FOR 20 YEARS  
GOOD SCOPE FOR  
EXPANSION

Tel (02) 36-4401, A.H. (02) 36-1147.

# MICRO MINIATURE FANS



24 - 72 mm  
DIAMETER,  
SWISS  
PRECISION  
MAKE.

MICRONEL

P.O. Box 108, Double Bay, NSW 2028

Tel (02) 36-4401, A.H. (02) 36-1147.

# LOOPY VIDEO

Shop: 418 Bridge Road, Richmond, Vic.  
Mail: PO Box 347, Richmond, 3121, Vic.  
Second hand video recorders and tapes,  
cheap. Also new.

## OSI HARDWARE FOR OHIO COMPUTERS

Superboard II .....\$367 (inc. tax)  
Sil Covers/VDU Stands.....\$18.95  
RF Modulators 5/9V.....\$19.95  
4K RAM Kits.....cheap

## OSI SOFTWARE FOR OHIO COMPUTERS

Almost 100 varieties for C1P/SIL.  
Less available for C2/4P; enquire.  
Categories are: Games, Education, Business, Text,  
Instructions (Modifications), and utilities.  
C.1. Catalogue. Brief descriptions of all programs,  
free hints on programming and use of OSI comput-  
ers.....\$2.95  
Example of titles:  
G.25 Alien Invaders.....\$9.95  
G.30 Air-Sea Battle.....\$9.95  
G.33 Grand Prix.....\$9.95  
G.28 Death Ship (2 tapes).....\$18.95  
U.16 Filename (tape).....\$8.95  
U.19 Cursor/Editor C2/4.....\$11.95  
U.20 Mini-Assembler.....\$9.95  
U.21 Single Key Basic.....\$9.95  
T.1 (was I.6) The First Book of OSI.....\$16.95  
T.2 Aardvark Journal (6 issues).....\$10.95  
I.23 Light Pen (Instructions).....\$6.00  
I.16 G T Conversion.....\$2.95

Mail Orders allow postage e.g. OSI Software 1 or 2  
\$1.00, 3-5 \$1.50, 6-9 \$2.00, 10 or more items \$2.50.

All prices INCLUDE sales tax.  
Prices subject to change without notice.

## AIM-65 ENCLOSURE

For a professional appear-  
ance. Space for one addi-  
tional expansion card.

\$59.00

## VISIBLE MEMORY FOR AIM, SYM

High resolution 320 x 200  
bit mapped pixel display  
matrix. 8K byte dual  
ported dynamic RAM.

\$249.00



• **GRAPHICS/TEXT S/W** gives point plotting, line drawing,  
character generation \$29.00 • **AIM PRINT S/W** superb exten-  
sions for AIM printer. Allows graphics and text as 10 rows of  
up to 127 characters per row \$29.00 • **VIDEO PLUS MC6845**,  
2K RAM expansion to 6K, two 6522 S/W on cassette \$293.00  
A&T. • **DRAM PLUS** 16K expansion to 32K 4116's, 16K  
Eprom space EPROM Programmer. 50 x 70 mm WW area,  
S/W on cassette. \$353.00 A&T. • **PROTO PLUS** space for 40  
x 14/16, 4 x 24/40, 3 x VR \$48.00 • **MOTHER PLUS** buffered  
and decoded, 5 addit. boards \$98.00 A&T. • **CARD CAGE**  
**PLUS** compatible with Mother Plus, anodised aluminium.  
\$28.00 • **MUSIC SYNTHESIZER** four simultaneous voices,  
D/A, filter, amplifier. \$55.00 A&T. • **Music Synthesizer S/W**  
for AIM or SYM on cassette \$25.00  
P&P \$3.50. Prices plus sales tax if applicable.

**energy CONTROL**

PO BOX 31, GOODNA 4300.  
PHONE (07) 288-2757.

Prices subject to change without notice.

SAE for  
Datasheet

## SORCERER OWNERS!

Upgrade your existing 8K Basic with the new Software  
Source Mod 1.01. Makes your Basic into a Superbasic  
with capabilities that outstrip even some Disc Basics.

- Full input checking to eliminate unseen syntax errors and line  
overflows.
- Redo from start if type mismatch in input statements.
- Save numeric arrays with confidence.
- Full line editing on input — change part of line without retyping  
it all.
- Full selective renumbering — move your subroutines around;  
make a hole to insert more text.
- Delete any block of lines.
- Full recovery of program after accidental reset.

Available only for Exidy Standard Basic version 1.0.  
Basic Mod 1.01 (include Rompac with order) \$125.00  
Available as kit with full instructions .....\$100.00

## OTHER SOFTWARE AVAILABLE

String Saver: save Exidy Basic string arrays .....\$37.50  
Eddit: merge/renumber/edit Basic programs .....\$35.00  
Moneychart: chart cashflow of any business.....\$58.00  
Management Report: see where & how money is spent.....\$53.00  
Supercalc: Sorcerer becomes a 'supercalculator'.....\$12.50  
Util 3: Use your development pac efficiently .....\$24.50  
Life: play Conway's game superfast.....\$8.50  
Biorhythm: Plot your biorhythms fast.....\$8.50  
CP/M programmes: (available in lifeboat or exidy formats on  
Micropolis 5 1/4 quad density disks. Specify when ordering).  
Q: Sorted CP/M directory .....\$17.50  
Compare: Compare two disk files.....\$17.50  
Fix: View/alter any byte on the disk .....\$17.50

## SPECIAL INTRODUCTORY OFFER

C.10 Digital Cassette Tapes, box of 10, \$8.85.  
16 Sector 5 1/4 Diskettes, box of 10, Single Density  
\$40.00, Quad Density (box of 10 plus free library case)  
\$60.00

Send cheque/money order to:

SOFTWARE SOURCE,  
PO Box 364, Edgecliff, NSW 2027.

All prices inclusive. For free catalogue send SAE.  
Need specialised software? — call us, we can help.

**SOFTWARE SOURCE**

Phone (02) 33-4536

## PROGRAMMERS

**Wanted:** Free-lance  
programmers familiar with  
TRS-80 Level II BASIC to  
write customized software  
packages for dynamic  
electronics retailer.

If you are a University student,  
tutor, lecturer, doctor, lawyer,  
computer programmer or  
microcomputer buff and if you  
own a TRS-80/SYSTEM 80  
and/or enjoy programming in  
BASIC, why not take this  
opportunity to make some  
extra money in your leisure  
time by writing various  
software programmes for us?  
Give me a call — you have  
nothing to lose but plenty to  
gain.

Please direct enquiries to:



**MARK SIM  
DICK SMITH  
ELECTRONICS**  
Phone (02) 888 3200

# 26 MEGABYTES

## \$5250

+ SALES TAX

# DRIVE A HARD BARGAIN!

Suddenly, S-100 microcomputer systems can easily handle 100 million bytes. Because Morrow Designs™ now offers the first 26 megabyte hard disk memory for S-100 systems — the DISCUS M26™ Hard Disk System.

It has 26 megabytes of useable memory (29 megabytes unformatted). And it's expandable to 104 megabytes.

The DISCUS M26™ system is delivered complete — a 26 megabyte hard disk drive, controller, cables and operating system — for just \$5,250. Up to three additional drives can be added.

The DISCUS M26™ system features the Shugart SA4008 Winchester-type sealed media hard disk drive, in a handsome metal cabinet with fan and power supply.

The single-board S-100 controller incorporates intelligence to supervise all data transfers, communicating with the CPU via three I/O ports (command, status, and data). The controller has the ability to generate interrupts at the completion of each command to increase system throughput. There is a 512 byte sector buffer onboard. And each sector can be individually write-protected for data base security.

The operating system furnished with DISCUS M26™ systems is the widely accepted CP/M\* 2.2.

\*CP/M is a trademark of Digital Research.

See the biggest, most cost-efficient memory ever introduced for S-100 systems, on demonstration now at



## MICROCOMPUTER PRODUCTS



MORROW DESIGNS™

My Road, Guildford, NSW 2161. Phone (02) 632-6301, 632-4966. Telex AA25958.

# WHY IS THIS AUSTRALIA'S FASTEST SELLING COMPUTER?



**Simple. It is far and away the best value computer available in Australia**

We admit it! Australia's fastest selling computer was the TRS-80. Was. It has now been well and truly beaten by the remarkable System 80 from Dick Smith Electronics. It has TRS-80 compatible level II BASIC as standard. So most\* of the huge range of software written for the TRS-80 is compatible with the System 80! Not only that, the System 80 has S-100 bus expansion capability...

\* A small number of TRS-80 programs will not run properly on the System 80 without minor modification.

- **Level II compatible BASIC as standard**  
(Tandy charge extra for level II)
- **Industry standard S-100 bus expansion**  
(They use their own non-standard system)
- **RF output: uses any TV set as a monitor**  
(You have to buy a true video monitor with theirs)
- **Two motor controlled cassette interfaces**  
(Theirs only has one)
- **Inbuilt cassette deck (no inter-connections necessary)**  
(Their cassette deck is completely separate)
- **Inbuilt power supply (no inter-connections)**  
(Tandy power supply must be connected up)
- **AND THE BEST PART OF ALL: IT IS MUCH CHEAPER THAN THE TANDY EQUIVALENT!**

**Send for our FREE Computer Comparison Chart**

## DICK SMITH SYSTEM 80

**4K RAM WITH LEVEL II BASIC \$695<sup>00</sup>**  
Cat X-4003

**16K RAM WITH LEVEL II BASIC \$750<sup>00</sup>**  
Cat X-4005

Terms available to approved applicants

## DICK SMITH ELECTRONICS

**NSW**  
126 York Street,  
147 Hume Hwy,  
182 Pacific Highway,  
30 Grosse Street,  
813 Princes Hwy,  
818 George Street,  
531 Pittwater Road,  
283 Kairs Street,

**SYDNEY**  
CHULLORA  
GORE HILL  
PARRAMATTA  
BLAKEHURST  
SYDNEY  
BROOKVALE  
WOLLONGONG

**VIC**  
  
  
**QLD**  
**ACT**  
**SA**  
**WA**

388 Lonsdale Street,  
858 Bridge Road,  
Dandenong & Springvale Rds,  
188 Logan Road,  
842 Gympie Road,  
96 Gladstone Street,  
60 Wright Street,  
414 William Street,

**MELBOURNE**  
**RICHMOND**  
**SPRINGVALE**  
**BURANDA**  
**CHEMERSIDE**  
**FYSHWICK**  
**ADELAIDE**  
**PERTH**

Ph 87 8834  
Ph 428 1814  
Ph 87 8834  
Ph 381 8233  
Ph 68 8266  
Ph 88 4844  
Ph 212 1882  
Ph 328 8844



**SHOPS OPEN 9AM to 5.30PM**  
(Saturday: 9am till 12 noon)  
**BRISBANE:** Half hour earlier.  
ANY TERMS OFFERED ARE TO  
APPROVED APPLICANTS ONLY  
RE-SELLERS OF DICK SMITH  
PRODUCTS IN MOST AREAS OF AUST



**MAIL ORDER CENTRE:** PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.

# Print-out

## Hand held computers

Portable computer terminals and completely portable microcomputer systems are just coming onto the American market.

**Although their makers would dearly love to succeed with their new products in the mass consumer market, business users are the most promising prospect so far.**

As one company president put it, "We're going to see hand held computers used more and more by big companies with a large sales force. A salesman with access to his company's computer could sit at a customer's facility and get things like the exact status of an order, inventory situation, or price quotes."

So far there are no standard approaches to portable computers, with each company going its own way and aiming at a different market sector. Commodore have been displaying prototypes of their

'Minipet', which uses the same 6502 microprocessor as their well-known PET. Its hand held keyboard/processor unit has the letters arranged in typewriter fashion, with separate number keys, and interfaces with a normal TV screen to display monochrome images.

Production models of the Minipet are expected to retail for about US\$200 when they are introduced, or 50% more for a version which will display in colour. These prices are so far only estimates and the final price will depend on the amount of memory included and whether a liquid crystal display is added to the TV facility. Commodore are also planning to produce a US\$500 system with cassette mass storage and a printer included.



Tandy's TRS-80 Pocket Computer has only just been released here. It features resident BASIC and 1.9K of RAM. Priced at \$249, a cassette interface and recorder are also available.

National Panasonic and Quasar have systems with hand held Keyboard/CPU's and peripherals housed in an attache case. These systems are also able to communicate with remote computers via optional modems and acoustic couplers.

They are aimed more up-market, with higher prices justified by their larger memory capacity and greater speed. Panasonic's system has 73 kilobytes of RAM and 40K of ROM.

Sinclair's ZX80 has been selling for less than Aus\$200 in the UK for the last six months and was introduced to the USA at the Chicago Consumer Electronics Show in June. It's basically designed for the hobbyist (you can get it at 20% discount in kit form) and is a Z80 based CPU/keyboard module that interfaces with any cassette recorder and TV monitor. No doubt there'll be lots of interest in this when it's released here (due this month!).

## Are PETs good for business ?

**Properly trained Commodore PETs could be the small businessman's best friend.**

That's what Sydney entrepreneur John Guidice believes and he's acted on his convictions in establishing the Microcomputer House to market PETs with business software packages.

He first became interested in the possibilities of these microcomputers when he bought one for his own personal use. Being a DP professional, he soon became dissatisfied with the limitations of its standard operating system and the simple BASIC programming capability, so he set out to de-

velop his own software. While he was doing this, he also started a users' association and began editing a magazine and newsletter for it.

Guidice aims to lease PETs for around \$140 per month, with software developed by Data soft, Hanimex and himself, including a word processing package.

More information from The Microcomputer House Pty. Ltd., 19 William St, Alexandria, NSW 2015. Phone (02) 699-4334.

# Print-out



## Integrated business software

**IMS Computer Systems, the Melbourne based software house, has released two integrated packages which form the base of a totally integrated business system.**

The systems released are General Ledger 2.1 and Creditors Ledger 2.1. The packages can operate in either a stand alone application, or the General Ledger can access all purchase analysis information on the Creditors Ledger to provide the integrated function.

In addition to the integration programs, the packages include additional features over General Ledger V1.0 and Creditors V1.3, the previous release.

The General Ledger contains budgets for twelve months, providing profit and loss MTD and YTD actual, budget and variation, printouts of budgeted amounts, balance sheet, trial balance, transaction print etc. It is suitable for companies, partnerships and sole traders. The 500 accounts in the chart can be manipulated to suit the user's need.

The features of the Creditors Ledger, apart from general ledger account integration, include: purchase analysis by supplier MTD and YTD, and discount received MTD, YTD, purchase analysis by product

group, cheque printing, listings of invoices, credit notes, and cash payments, remittance advices, aged trial balance etc.

The packages also include enhancements to speed up processing. The debtors and integrated order entry invoicing system is currently being upgraded to provide a totally integrated business system. This is due for release in the fourth quarter 1980.

The packages are designed to run on CP/M systems such as the Micro Star, Superbrain, Croemco etc and support twelve brands of VDUs. The packages utilize the latest release of CBASIC2 (2.06) which has been designed for CP/M version 2.

The prices, which include manual and system diskette, are \$500 for the General Ledger and \$400 for the Creditors. For users of previous IMS systems, there is a 50 percent upgrade charge.

Further information can be obtained from IMS head office 825 St Kilda Rd, Melbourne 3004. (03) 51-9156.

## Disk drives for the HP-85

**Hewlett-Packard are bringing out a set of disk drives for their HP-85 personal / professional computer.**

The new HP 82900 Series drives read double-sided double-density minifloppies. The dual master drive allows 540K of on-line storage, which can be doubled if necessary with a dual add-on drive.

Users who want the speed and convenience of disk but don't need so much capacity can opt for a single master drive to get 270K of storage, which can be doubled if necessary with a single add-on drive.

The interface between the disk drives and the computer is the HP-85 Mass Storage ROM. With this plugged into the HP-85 the disk operating system is ready to go as soon as power is turned on and no bootstrapping is necessary.

Included on the ROM are a set of thirty additional BASIC commands that allow the user to take advantage of the mass storage capabilities without learning a new language.

Other features of the ROM include a TRANSLATE command which automatically upgrades previously-written tape based programs for use on the disk drives and the ability to store and retrieve the CRT graphics display quickly.

First deliveries of the drives and the ROM are expected on September 1st. Further details are available from Hewlett-Packard Australia Pty. Ltd., 31-41 Joseph St, Blackburn, Vic 3130. (03) 89-6351.



## Contrec cuts development costs

**A new development system for the Intel MCS-48 range of microcomputers is said to be priced well below comparable systems.**

The makers, Contrec Systems, don't actually tell us the price though. They do tell us the system is based on the Cromenco Z-2D computer and that it will run all the standard software packages including BASIC, Fortran, Pascal, wordprocessing and accounting systems.

All the usual features like assembly, emulation and file storage are standard and an auxiliary MCS-48 Computer Unit

allows testing and debugging of programs in a stand alone mode or with prototype hardware.

The system also provides assemblers and simulators for 8085 and Z80 software development and full emulation facilities for the 8085 are expected to be announced later this year.

Further information from Contrec Systems Pty Ltd at 55, Dundas Place, Albert Park, Vic 3206. (03) 690-6905.

## Dick Smith Sounds Off

**Australia's best-known electronics retailer/wholesaler is distributing several types of sound synthesis units.**

To begin with, there's the low cost sound effects and music package for his own System 80 microcomputer. This is known as 'Sound Off' and is also compatible with the TRS 80 Level 11 machine. It consists of a battery powered amplifier which connects to the computer via the normal external cassette recorder cable, and a cassette tape with the software recorded on it. It is said to achieve a wide range of pitch, duration and dynamic characteristics.

Much more elaborate is an S-100 card called the SBI Music Synthesiser, which comes either in kit form or ready assembled. It's programmable

over a nine octave range from 15Hz to 25kHz, with fifteen possible output levels and waveforms definable in 32 bytes of memory. Attack and duration are also programmable.

For the Exidy Sorcerer, there's a speech analyser/synthesiser unit known as Cognivox, which plugs directly into the computer and uses the latter's power supply.

Software support enables the device to 'learn' to recognise up to 32 spoken words with an accuracy of 98%, to make spoken responses, to play two different voice operated video games or to function as a talking calculator.

## Twelve volt impact printer

**The latest miniature printer from Daneva Control is designed for 12 V battery operation.**

A single board microprocessor controller generates the characters, manages the buffer store and drives the hammers of the Duoprint II.

The complete upper and lower case ASCII 7 x 5 dot matrix character set is standard. Reversed lines, inverted, double width and bold characters can all be selected by ASCII non-

printed commands.

The printer measures 110 mm x 175 mm and accepts 55 mm wide paper. It is expected to be used in point of sale terminals, data loggers, ticket issuing machines and label printers.

More info from Daneva Control Pty. Ltd., 66 Bay Road, Sandringham, Vic 3191. (03) 598-5622.

## Swiss matrix printer

**Wenger Datentechnik of Switzerland announce a microprocessor controlled dot matrix printer for professional data processing applications.**

Controlled by an Intel 8080, the Swiss Print Matrix is fully programmable with up to 4K of user program space. A 1K buffer is standard but there is an option for 2K.

The machine can cope with up to six character fonts and will also operate in a graphics mode to print images with a resolution better than 1000 dots per square centimetre.

Standard features on the printer include a fault alarm, parallel and serial interface, vertical and horizontal tabs and

form feed. The paper feed tractors are adjustable and are said to have exceptionally fast slewing rates.

For those not directly concerned with the printer but obliged to work near it the Swiss Print Matrix's most welcome feature is its relative quietness. Sound output is claimed to be typically 3 dB less than comparable machines.

More details from the distributors Datatel Pty Ltd, 3 Raglan St, South Melbourne, Vic 3205. (03) 690-4000.




## 32 Character 5 x 7 dot matrix LCD display

**Liquid Xtal Displays Operation, a part of General Electric Company's Electronic Components Division, has released a 32 character 5 x 7 dot matrix LCD display, configured for conductive, elastomeric connection.**

The GE-LXD reflective display consists of two rows of 16 characters 7.5 mm high. Overall dimensions of the display are 33 x 122 mm. This new display (designated 95E) expands the GE-LXD product line, which include 8- and 16- character dot

matrix displays, and a complete series of 7-segment two to eight character LCDs.

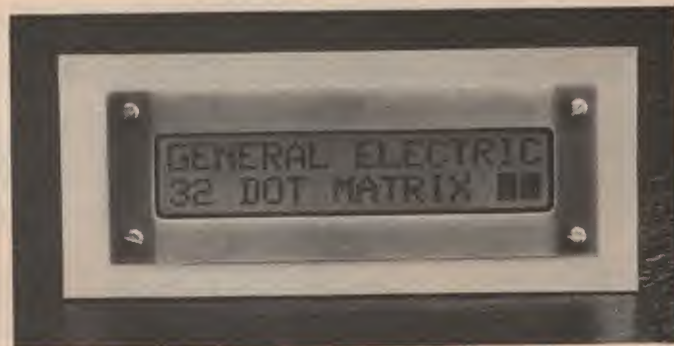In other areas, LXD is committed to growing with new developments, and the company anticipates significant market growth in the future.



# HARDWARE & SOFTWARE

## From DICK SMITH



### PROFESSIONAL DAISY WHEEL PRINTER FOR WORD PROCESSOR SYSTEMS

This superb unit is a self-contained printer with in-built asynchronous serial interface conforming to the established RS-232C standard. It prints on business stationery up to 380mm wide at the rate of 45-65 characters per second - three times faster than golf-ball typewriters. Top quality office systems printer that is below competition prices.

**\$3,390.00**

Cat. X-3260

### EXIDY S-100 BUS EXPANSION UNIT

The way to go if you want extra versatility from your Sorcerer.

**\$575**

Cat. X-3010

● Allows up to 6 plug-in cards ● Connects directly to Sorcerer's 50-way expansion socket via supplied cable ● All S-100 lines fully buffered ● Separate 2.000MHz crystal clock provided for S-100 cards which cannot use the 01 and 02 clock signals derived from the Sorcerer's 2.106MHz clock ● Provision for mounting up to six 25 pin "D" connectors for additional I/O ports, etc.



### THE SORCERER

Cat. X-3001  
SORCERER  
Cat. X-1196  
MONITOR

The Sorcerer is the expandable Z-80 based microcomputer that allows you to add peripherals to take it from basic computing through to advanced office business systems.

● 16K RAM expandable to 48K (on board) ● Serial I/O and Parallel I/O ● S-100 BUS compatible ● Cassette I/O for two recorders at speeds of 300 or 1200 baud ● Video I/O - 1920 characters full screen ● Full ASCII 128 characters (64 defined characters and 64 undefined characters) ● Graphic resolution 122,880 pixels ● Includes 8K BASIC plug-in ROM PAC™ in MICROSOFT™ ● Dimensions 490 x 330 x 100mm ● Weight 6 kilograms.

(Ask for our FREE comparison chart between the Sorcerer and other well known computer brands).

Dust cover to suit  
Cat. X-3005 **\$5.95**

**\$1,395.00**

### VIDEO MONITOR

This is a superb 30cm black and white video monitor that can be used on AC and DC. Simple connection to your computer. Features jitter free and distortion free characters. Can be used with most computers on the market.

Cat. X-1196

**\$149.50**

### WORD PROCESSOR PAC

Remove the plug-in BASIC PAC™ and replace it with the powerful WORD PROCESSOR PAC™ and you will have the basis of an office computer system.

Features: ● Automatic text wrap ● Automatic checking of drastic commands ● Powerful search function ● Auto commands ● Macro programming - all this plus extensive user instructions.

Cat. X-3085

**\$275.00**

### WOW! SOUND EFFECTS FROM YOUR SYSTEM 80!

(Also suitable for TRS-80 Level 11)

## SOUND OFF!



Yes! At last there is an add-on sound effects generator for your System 80 or TRS-80 level II computer. It will give you exciting music synthesis and sound effects facilities that you haven't had before!

Here's what you get

● Battery powered amplifier unit which connects to your computer via the normal external cassette recorder cable ● Software - cassette with demonstration program plus a 'patch' program ● A comprehensive 8 page user's manual

HURRY! LIMITED STOCKS AVAILABLE AT PRESENT!

Cat. X-3648

**'SOUND-OFF' PACKAGE:**  
Includes amplifier module, software cassette and very comprehensive user manual:  
**ONLY \$19.50**

**SEE THE OTHER DICK SMITH ADVERTISEMENTS IN THIS PUBLICATION FOR STORE ADDRESSES AND PHONE NUMBERS**

### LIGHT PEN FOR SYSTEM 80

**\$9.95**

Cat. X-3645



Fantastic light pen for use with your TRS-80 or System 80 computer. Uses ALSO FOR TRS-80 your cassette player as a preamp. Complete with plug & battery snap. Use with program tapes below.

### NOUGHTS & CROSSES

Just insert this program cassette into your computer cassette player and enjoy playing the game with your light pen.

Cat. X-3647

**\$11.95**

### MICROPOLIS™ QUAD DENSITY DISC DRIVE

The Micropolis mod 2 drive with controller enables you to store 315,000 bytes on just 1 disc. By adding the mod 2 add-on drive (up to 3) you can obtain up to a maximum of 1.26 Megabytes! Complete with all software to enable you to be up and running in a very short time.

Model 1043/mod 2 with controller.

Cat. X-3205 **\$1,350**

Model 1023/mod 2 add-on

Cat. X-3208 **\$750**



### SOFTWARE FOR SYSTEM 80 and also the TRS-80

#### TIME TREK

Hunt the Klingons through space and fight an intergalactic war. Has nine levels of play. (4K level I and II).

Cat. X-3650

**\$17.95**

#### STIMULATING SIMULATIONS

10 games on one cassette from monster chase to nautical navigation and lost treasure. (4K level I and II).

Cat. X-3652

**\$17.95**

#### ELECTRIC PAINTBRUSH

Create dazzling real time graphics. Commands let you draw lines, turn corners, change white to black, repeat previous steps or call other programs. (4K level I and II).

Cat. X-3654

**\$17.95**

#### BLOCKADE

Many variations whereby you and your opponent try and make each other collide with a wall. (4K level I and II).

Cat. X-3659

**\$17.95**

#### BRIDGE CHALLENGER

Practice and improve your game of Bridge. (16K level II).

Cat. X-3656

**\$17.95**

#### MICRO CHESS

The computer is programmed to beat you at chess and you are trying to beat it - absorbing & educational.

Cat. X-3658

**\$22.50**

#### SIMUTEK I

Contains 5 games that would normally cost \$19.50 each! Great fun for all the family and friends. (4K level I and II).

Cat. X-3685

**\$17.95**

### C.I.T.H. BRAND DOT MATRIX PRINTER



The model 8300P dot matrix printer is a no-nonsense unit that can churn out the full 96 character ASCII at a brisk 125 characters per second on standard fan-fold paper. Character spacing of 80, 40 or 132 columns which are software selectable. A quality unit that costs less than \$1,000!!

Cat. X-3255

**\$970.00**

### JABEL COMPUTER MAINS FILTER

Having trouble with memory crashes? Then the answer is the Jabel Mains Filter - it will remove those annoying spikes from the 240V mains and thereby protect your memory!

Cat. M-9850

**\$75.00**

### C10 COMPUTER CASSETTE

Dick Smith special grade cassette tape with 5 minutes per side and 36K capacity per side.

Cat. X-3500

**\$1.95**

### SKETCH 80

For the System 80 and TRS-80  
A program tape that allows you to sketch on your VDU - the light pen becomes a real writing tool!!  
SEE LIGHT PEN ABOVE

Cat. X-3646

**\$17.95**

### NEW NEW NEW DUE IN SHORTLY

**COGNIVOX™**  
VOICE INPUT & OUTPUT FOR THE SORCERER

★ Recognizes up to 16 words.  
★ 16 word voice response vocabulary  
★ Easy two pass training  
★ Up to 98% recognition accuracy  
★ Generates music & sound effects  
★ Excellent software support  
★ Connects directly to Sorcerer

Cat. X-3150

**\$199**

# MICRO-80 PRODUCTS FOR TRS-80 AND SYSTEM '80 MICROCOMPUTERS

## 77 TRACK DISK DRIVES DOUBLE YOUR CAPACITY

**DD-7S** ... .. \$775  
Micropolis Floppy Disk, 77 Track, 100% larger capacity than most mini-floppy drives, complete with cable, power supply, chassis, and includes NEWDOS '80.

**DD-7** ... .. \$649  
Same as above but no cable or Newdos '80.

**DC-4** ... .. \$45  
4 drive connector cable.

## ★ ★ SPECIAL ★ ★ MPI DISK DRIVES ONLY \$339!!

40 track bare drive for TRS-80. Only requires readily available 5 volt 0.7 amp and 12 volt 1 amp power supply to be up and running. Can be mounted in simple cabinet or used bare.

## DISKETTES FOR TRS-80

**GREENCORP** ... .. \$4.50 ea  
**VERBATIM 77 TRACK** ... .. \$7.99 ea  
Minimum Order 10

## EXATRON STRINGY FLOPPY

**\$352.50 incl p&p**

15 times faster than cassette, infinitely more reliable. Completely under computer control, the stringy floppy is easier to use than disks and is a very much cheaper alternative. Will save and load any L2/16K software. Special software also available.

**Wafers for Stringy Floppy**  
**\$3.50 ea. Any Size**

## MICRO-80 MAGAZINE

**ANNUAL SUBSCRIPTION** ... .. \$24.00  
Monthly Magazine dedicated to TRS-80 and System '80 users. Every issue contains at least 6 new programs, plus problem solving columns, hardware articles, readers' letters, hints, etc., etc.

## FREE SOFTWARE OFFER

**\$40 WORTH OF SOFTWARE FOR TRS-80 AND SYSTEM '80 WITH EVERY NEW SUBSCRIPTION TO MICRO-80!**  
Every new subscriber will receive on cassette, ready to load, 3 x Level I and 3 x Level II programs (includes our fabulous household budget program), with a regular retail value of at least \$40.

## 16K MEMORY EXPANSION KIT ONLY \$97 incl. p&p

These are prime, branded, 200 ns (yes, 200 ns!) chips. You will pay much more elsewhere for slow, 350 ns. chips. Ours are guaranteed for 12 months. A pair of DIP shunts is also required to upgrade the CPU memory — these cost an additional \$4.00. All kits come complete with full, step-by-step instructions, no soldering is required. You don't have to be an electronic type to instal them.

## THE FABULOUS NEWDOS 80 IN STOCK NOW!

**ND-80** ... .. \$149  
The disk operating system that gives:

- New basic commands that support variable record lengths up to 4095 bytes long.
- Mix or match disk drives — supports any number of tracks from 18 to 80. Use 35, 40 or 77 track 5" mini disk drives or 8" disk drives, or any combination.
- A security boot-up for basic or machine code programs. User never sees "Dos-ready" or "Ready" and cannot "break" clear screen or issue any direct basic statement including "List" ... .. and much, much more

**ND-35+** ... .. \$99  
Newdos+ for 35 track drives

**ND-40+** ... .. \$110  
Newdos+ for 40 track drives

## BOOKS

### LEVEL II ROM REFERENCE MANUAL \$24.95 plus \$1.20 p&p

Produced in Australia by MICRO-80, this book is a must for the machine language programmer or for the BASIC programmer who wants to understand how the BASIC interpreter works. Over 70 pages packed full of useful information and sample programs. Applies to both TRS-80 and SYSTEM 80.

### TRS-80 DISK AND OTHER MYSTERIES \$24.95 plus \$1.20 p&p

The hottest selling TRS-80 book in the USA. Disk file structures revealed, DOS's compared and explained, how to recover lost files, how to rebuild crashed directories — this is a MUST for the serious Disk user.

### INTRODUCTION TO T-BUG

**\$12.50 plus \$1.20 p&p**  
Describes in detail how to use Tandy's T-bug. Each command explained and discussed in detail with examples. A must for the T-Bug user.

## AUSTRALIAN SOFTWARE

**BMON (L2/16K) \$19.95 plus 50c p&p**  
The ultimate program to assist BASIC programmers.

**TOUCHTYPE (L2/4K) \$19.95 plus 50c p&p**  
22 lessons to teach you to type on your own keyboard and screen!

**RPN CALCULATOR (L2/16K & 32K) \$14.95 plus 50c p&p**  
Turns your computer into a \$600 calculator. Ideal for Architects, Surveyors, Engineers, Teachers, Scientists, etc.

**U-BOAT (L2/16K) \$7.50 plus 50c p&p**  
You're the Commander, read all the guages, fire the torpedoes, crash dive, get the enemy before his depth charges get you!!

**MMM-1 GAMES PACK (L2/4K) \$7.50 plus 50c p&p**  
3 fast moving games — INDY 500, SUB-HUNT, KNIEVEL

**MMM-2 GAMES PACK (L2/4K) \$7.50 plus 50c p&p**  
3 more games with fast moving graphics — TANK, THIEF, SHOOTOUT

## PROGRAMS BY

**MICROSOFT**

**BASIC COMPILER** ... .. \$210  
Converts Level II basic programs to machine code, automatically. A compiled program runs, on average, 3-10 times faster than the original basic program.  
(Requires 48K One Disk)

### DISK EDITOR ASSEMBLER

**Save \$30** ... .. **ONLY \$109**  
Supports macros, linking loader, editor, cross reference.  
(Requires 32K One Disk)

**ADVENTURE ON DISK** ... .. \$37.15  
This game fills an entire diskette. Endless variety and challenge as you seek to rise to the level of Grand Master (until you gain skill, there are whole areas of the cave that you cannot enter).  
(Requires 32K One Disk)

**EDITOR ASSEMBLER-PLUS** ... .. \$41.15  
A much improved editor assembler and debug/monitor for L2/16K machines. Assembles directly into memory, supports macros and conditional assembly, includes new commands — substitute, move, copy and extend.

**LEVEL III BASIC** ... .. \$59.95  
Loads on top of Level II Basic and gives advanced graphics, automatic renumbering, single stroke instructions (shift-key entries), keyboard debounce. Suitable for L2/16K and up. (Not Disk Basic).

## SCOTCH BRAND

### PERSONAL COMPUTING CASSETTES

C-10 pack of 10 ... .. \$26.00 incl. p&p  
C-30 pack of 10 ... .. \$28.00 incl. p&p

### TO: MICRO-80

PO Box 213, Goodwood, SA 5034

284 Goodwood Rd, Clarence Park,

SA 5034 Phone (08) 272-0966

Please rush me the items checked below:

- ☐ 12 month subscription to MICRO-80 and my free software cassette ... .. \$24.00
- ☐ 12 month subscription to MICRO-80 and the cassette edition, plus my free software cassette ... .. \$60.00
- ☐ The latest issue of MICRO-80 ... .. \$2.50


### PLUS THE ITEMS LISTED BELOW

DESCRIPTION	PRICE
TOTAL ENCLOSED	

Name .....

Address .....

Post Code .....

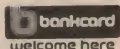 No .....  
welcome here

Please debit my Bankcard \$ .....

Expiry date .....

Signature .....

ETI



## New family of low cost plotters

**Five new models have been added to the successful HI-PLOT range of digital plotters aimed at both the OEM and end user markets.**

Anderson Digital Equipment say this new family of UL listed digital plotters are designed to make hard copy output affordable and practical for the small system user in business, science, drafting, architecture, numerical control, mapping, education, personal computing and many other applications.

The DMP family of plotters now comprises six models; two standard and four "intelligent". Both are available with plotting sizes of both 8½" x 11" (DIN A4) and 11" x 17" (DIN A3).

The DMP-2 is a basic A4-size plotter with a built-in RS-232C and parallel interface, it has a pen speed of 2.4"/sec. (61 mm/sec.) and can plot at either 100 or 200 increments per inch (about 40 or 80 increments per cm).

The DMP-5, like the DMP-2, is a "basic" plotter. It suits A3-size and has a built-in RS-232C and parallel interface. The DMP-5 is plug compatible with the DMP-2

and can utilise software developed for the DMP-2.

The DMP-3 is an 'intelligent' A4-size plotter with a built-in microprocessor and features a pen speed of 75 mm per second. Use of Houston Instrument's DM/PL (Digital Micro/Plotter Language) permits minimum software burden on the host computer. For example: a simple print "H" will move the pen to the lower left hand corner, a print "U" instruction will raise the pen. Self-test and pen positioning are easily accomplished via a computer or terminal keyboard. The DMP-3 comes with an RS-232C or Centronics compatible interface.

The DMP-6 is an A3-size version of the DMP-3 and features a built-in microprocessor, easy remote pen positioning and pen speed of 2.4 inches per second (61 mm/sec.).

The DMP-4 (A4-size) and the DMP-7 (A3-size) represent the top of the DMP line. Electronic

## Electronic fund transfer

**There is an enormous interest at the present time in systems for the electronic transfer of funds to eliminate cheque books for many transactions and to obviate much of the paper work which takes up so much time in banks, credit companies etc and numerous retail organisations.**

It is confidentially anticipated that highly reliable data terminals will be installed at increasing numbers of establishments such as banks, shops, petrol filling stations, hotels and similar establishments.

Electronic fund transfer will undoubtedly have a major impact on the retail world and its international growth potential is extremely large. Eventually it could affect almost everyone who makes a purchase, pays for a service or who uses a bank.

Racal-Transcom Ltd, of Salisbury in England, is to concentrate on the development of electronic fund transfer systems which they believe will revolutionise the banking system in the 1980s.


An important feature of their system is security of information and the equipment will incorporate vital cryptographic circuitry necessary to prevent unauthorised interception or alteration of information. The user will also be provided with a permanent printed record of every transaction.

When a customer wishes to

make a purchase in a busy supermarket, he or she will be given a small handheld keyboard and will enter his or her personal code number. The equipment will first check that this corresponds to the account number on the banker's card which the shop assistant has placed in the point-of-sale terminal.

The equipment will then be able to automatically debit the bank account of the customer and at the same time automatically credit the bank account of the supermarket with the amount of the goods purchased.

Although the supermarkets and organisations providing the equipment will have to meet its cost, they will have the advantage that they will receive the money into their accounts immediately the goods are sold with absolute security and this will help to offset the cost of the equipment. In addition, it is claimed the use of this equipment will save much time both for the customer and for the shop assistant.

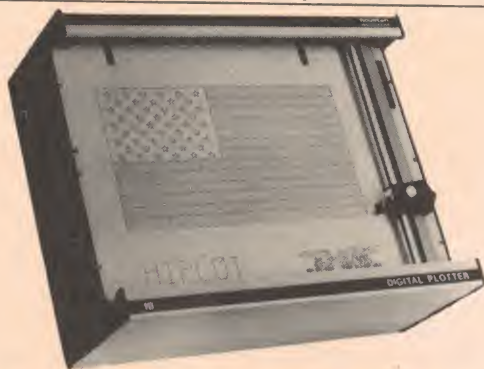

controls facilitate position of the X and Y axes. Self-diagnostics are activated by means of pushing dual buttons on the convenient front panel controls. Through use of the DM/PL instructions, the need for software is minimised.

Prices for the DMP Series

plotters start at \$1595. Metric versions of all models are available. For complete information and descriptive literature contact: Anderson Digital Equipment Pty Ltd, P.O. Box 322, Mt. Waverley Vic, (03)543-2077; or P.O. Box 341, Pennant Hills NSW, (02)848-8533.

**Normally, an S-100 computer costs hundreds of dollars more.**



**Ours costs hundreds of dollars less!**

This is the Tandy TRS-80 level II computer complete with monitor. With its own non-standard expansion interface, & RS-232C interface, it sells for

**\$1787<sup>95</sup>**

(Price as per Tandy 1981 catalogue)



This is the Dick Smith System 80 level II computer, complete with monitor. With an industry standard S-100 bus expansion interface\*, it sells for

**\$1398<sup>50</sup>**

\*Due in stock shortly.

**Both computers run with virtually the same software...**

**WHICH COMPUTER WOULD YOU CHOOSE?**

**STOP PRESS**

**SYSTEM 80 S-100  
EXPANSION INTERFACE  
DUE IN SHORTLY!**

- ★ 3 slot S-100 card cage.
- ★ Inbuilt power supply.
- ★ Mother board.
- ★ 2 vacant S-100 sockets for further expansion.
- ★ Supplied with single S-100 card providing complete floppy disc control.

Specifically designed for the System 80 to expand the basic concept into the world of floppy disc drives, Centronics type parallel printers, serial printers, expansion of the System 80 to 48K of RAM and RS-232C communications facilities—expand your System 80 for added benefits.

**ONLY  
\$499<sup>00</sup>**

Cat. X-4010


P&P \$5.50

**DON'T NEED A FULL S-100 INTERFACE?**

If you don't want to run an S-100 expansion but would like to use a parallel printer such as the Dick Smith Cat. X-3255 ITOH 8300P @ \$970, then you can with this parallel interface. Simply connects between your System 80 and the printer.

**SYSTEM 80  
PARALLEL  
PRINTER  
INTERFACE**

**\$89<sup>50</sup>**

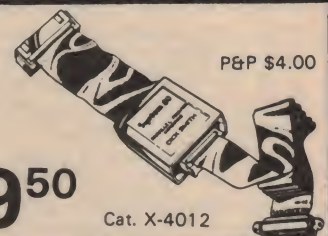

P&P \$4.00

Cat. X-4012

**DICK SMITH ELECTRONICS**



SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



# MENSA COMPUTERS PTY. LTD.

Suite 3, 454 St. Kilda Road, Melbourne, 3004. Telephone: (03) 26-5683, 26-6150.

## FINDEX — The Real Computer



### THE WORLD'S FIRST PORTABLE MICROCOMPUTER Battery or mains operated

RAM 48K to 2 megabytes, bubble memory to 2MB, gas plasma display, optional audio, printer, mass storage mini floppys to 800K bytes, hard disk to 195 megabytes, acoustic coupler, S-100 bus, battery optional, CPU with real time clock. For dynamic businessmen on the move. Ideal for real estate agents, insurance brokers and accountants.

## SUPERBRAIN™ SERIES

## BUSINESS SYSTEMS

Priced competitively from as low as \$45.00 p.w. lease cost including sales tax and software.



Powerful, multi-purpose microcomputer systems.

## TYPICAL APPLICATIONS

Debtors ledger and statements, creditors ledger and remittances, general ledger and trial balance, order entry/invoicing, sales analysis, payroll/wages, enquiry, word processing, mailing, record keeping, ledger card, doctors office, real estate, agency accounting, hotel/motel accounting, branch office accounting.

Facilities management consulting.

Software and computer sales.

Computer data preparation.

## OPAL 1000

The OPAL 1000 is an 8 slot S-100 system conforming to the new IEEE standards. A Delta Products Z80a 4 MHz CPU card, with 2 RS232c serial and 3x8 bit parallel ports, is used in conjunction with the Delta Products Disk Controller. Memory is provided by a 4MHz 64k dynamic RAM Board by Measurement Systems and Control. The memory board is fully bank selectable and is designed for upgrading to a multi-user system. Disk drives are 2x8" Shugart SA801R running at double density (480k/disk) and fitted with our exclusive Disk Saver which prolongs the life of the drives and floppy disks by turning off the AC power to the drives 14 seconds after the last drive select and thus reduces routine maintenance. The Disk Saver also reduces the risk of data loss due to power failures. The software is CP/M version 2.2 with Delta Product's utilities which include DTEST (for testing drives and floppy disks) and M2 (a comprehensive memory test program). The Delta PROM monitor enables fault finding to be carried out independently of the Disk Drives. The system is mounted in an attractive pressed Aluminium housing with a cast front panel fitted with reset button and key operated on/off switch.

Dealers for Opal in Victoria.

Sole Distributor for Findex, Victoria and NSW.

## SUPPLIERS FOR NDKS S-4000

### MATHEMATICS

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{\text{avg}}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{\text{avg}}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{\text{avg}}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{\text{avg}}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

# Print-out

16 or 32K RAM Addressable in 4K segments

REGULATORS

Prototyping area with separate connector space.

8 to 16K EPROM (Eprom not included).

Two 6522 VIA I/O CHIPS

EPROM PROGRAMMER (2716 or 2732)

## Peripherals for AIM65 and SYM-1 owners

**A range of peripherals to suit the AIM65 and SYM-1 micros are stocked and distributed here by Energy Control of Queensland.**

Distributorships are held for 'The Enclosure Group's' moulded AIM65 enclosures, the 'Computerist' range of intelligent video, memory and mother boards from Massachusetts, and the 'Microtechnology Unlimited' graphics boards.

The Computerist has recently

released a new memory board called the Dram Plus. This provides up to 32K of 4116 dynamic memory and up to 16K of EPROM space on board together with an EPROM programmer for 2716/2516 and 2732/2532 type EPROMs and a 50 mm x 70 mm wire wrap

area. Memory test and EPROM programming software is also available on cassette.

Microtechnology Unlimited of New Hampshire has a high resolution graphics board featuring a 320 x 200 bit mapped pixel display matrix together with AIM65 software which allows graphics printing on the

AIM65 on-board printer. You can print up to 10 rows with up to 127 characters per row. A multi-harmonic, four-voice music synthesiser is also available.

Details available from Energy Control, 73 Eric St, Goodna (P.O. Box 31) QLD 4300. (07)288-2757.

## S-100 hard disk drive

**A hard disk drive system just released in this country can expand the memory of S-100 systems beyond 100 Megabytes.**

The DISCUS M26 system from Morrow Designs of the US has a basic 26 megabyte hard disk drive with a controller and operating system which can cope with up to three additional drives of the same kind.

The single board S-100 controller communicates with the CPU via three I/O ports (for

command, status and data) and can generate interrupts at the completion of each command. Each sector can be individually write protected and there is a 512 byte on-board sector buffer.

Further details are available from the distributors, A.E.D., 123 Military Rd, Guildford, NSW 2161. Phone (02) 632-6301.



# Attention all computer users

Electro Medical Engineering Pty. Ltd. proudly announce the release of their exciting new Sendata 700 Series acoustic modems. This low cost acoustic coupler is modular in design, easy to operate, and offers unsurpassed performance even when both ends of the connection are acoustically coupled.



## **700 Originate Only**

Operates at up to 300 BPS Full Duplex and up to 1200 BPS Half Duplex.  
Powered via the terminal interface or from 9v plug pack.  
CCITT V24 (RS232) compatible.  
Suits most telephone handsets.



## **Use 700 Originate Only for portable terminal applications.**

Plug compatible with Teletype 43, Digital LA34, and new GEC Terminet 2030.  
Available with switch selectable answer/originate option.  
Use 700 Answer/Originate to establish your own message exchange service.  
Optional carry case available for above terminals ideal for portable applications.



## **700 Originate/Answer suits most home computers.**

Suits all home computers with RS232 output  
Communicate with other users using 700 Answer/Originate.  
Exchange your programs over the telephone network.  
Establish your own data base service.

The 700 Series is available in 1200 Half Duplex form or with split baud rates of 1200/75BPS.

**Electromeds eight years experience in the design and manufacture of a range of acoustic couplers ensures highest possible performance.**

### **REPRESENTED BY:**

**VIC.** Anderson Digital Equipment Pty.Ltd. 543 2077. The Logic Shop Pty.Ltd. 51 1950. **NSW.** Anderson Digital Equipment Pty.Ltd. 848 8533. The Logic Shop Pty.Ltd. 699 4910. **ACT.** Anderson Digital Equipment (ACT) Pty.Ltd. 58 1811. **QLD.** Anderson Digital Equipment Pty.Ltd. 350 2611. **SA.** Applied Data Control Pty.Ltd. 79 9211. **WA.** W.J. Moncrieff Pty.Ltd. 325 5722. **TAS.** Management Technology. 34 4522. **NZ.** Anderson Digital Electronics (NZ) Ltd. 64 4585.

## **ELECTRO-MED**

**ELECTRO-MEDICAL ENGINEERING P/L.**

**69 SUTHERLAND ROAD, ARMADALE, VICTORIA, 3143. AUSTRALIA.**

**TELEPHONE: (03) 509 5844**

**TELEX: AA36384**

## Voice recogniser for TRS80

**A speech recognition unit designed for use with the TRS80 microcomputer is claimed to have an accuracy of 98% on a 40 word vocabulary.**

The VET-2, from Scott Instruments of the USA, has a four kilobyte operating system housed on a 133 mm disk that also stores up to seventeen 40 word memory templates. Response time with a single 40 word memory is said to be 200 ms but may be slower with more extended vocabulary.

The system will only respond to particular speakers, which is clearly an advantage in some applications and a disadvantage in others. Each operator must repeat the desired vocabulary words several times to register the voice pattern templates in memory. When the operator subsequently speaks to the machine, it compares his or her speech to the template patterns and makes its recognition decision.

VET-2 uses two new software techniques to improve speed and accuracy. In the first of these, the system analyses the

number of syllables in a sentence before making any comparisons with the templates. This automatically eliminates from consideration those words in the vocabulary that do not contain the correct number of syllables — anything from a third to a half of the vocabulary.

The second software technique, known as variance weighting, divides the vocabulary into two parts — those words that are commonly pronounced in much the same way by different speakers or at different times and those whose pronunciation varies more from person to person and time to time. In some cases, the makers claim, this technique allows the VET-2 to be operated by two different people using the same set of templates.

More information from Scott Instruments, 815 North Elm, Denton, Texas 76201, USA.

## NMOS micros unveiled

**Seven new single-chip micros using N-channel MOS construction have been unveiled by American Microsystems Inc.**

Designated the S2200 series, the new devices feature on-board memory ranging from 512 bytes to 2048 bytes. Three members of the family also have 8-bit a-to-d or d-to-a conversion capability.

The California company also took the wraps off its new micro-

processor development station, Phoenix-1, at the giant Wescom/80 electronics show last month. The Phoenix-1 supports the company's new S2200 family as well as Motorola's 6800 and Texas Instruments' 990 micro-processors.

## Microsoft Z80 for Apple

**A "Z80 Softcard" that allows the Apple to run software written for Z80-based computers has just been announced by Computerland.**

The Z80 Softcard is a plug-in peripheral that actually contains a Z80 microprocessor and you can use it with the Apple II or Apple II Plus, but you'll need 48K of memory.

Each Softcard comes with Version 2.0 Microsoft BASIC, Version 5.0 Conversion Utilities

complete documentation plus two disks, each containing CP/M — you get one 13-sector disk for use with DOS 3.2 and one 16-sector disk for use with DOS 3.3 or Language Card.

Enquiries to Computerland, 555 Collins St, Melbourne Vic 3000. (03)62-5581, 62-6737.

## For Sorcerer Apprentices

**Being the proud owner of a Home Computer can not only bring hours of joy but a certain amount of frustration as well. Most non-computing people would not know the difference between a bit and a byte, and probably still think a buss is something to get you from here to there. We hope this column might help shorten some of those sleepless nights.**

This column is intended for the non-professional Home Computer Owner — specifically the growing number of Exidy Sorcerer users. Over the next few months, this column will present hints and tips for Sorcerer users and also provide a forum where any problems or hints you have can be aired. We invite readers to forward any queries or other material to this column care of Roger Harrison, Editor ETI, 15 Boundary St, Rushcutters Bay, NSW 2011.

### Hint:

There is a way to switch your printer on and off from a BASIC program, and that is to poke the CENDRV address into the SEND vector of the Monitor to switch it on and to poke VIDEO into the vector to switch it off. Here is how you do it:

Include the following lines at the beginning of your program:

```
0 VE=PEEK(-4095)*256+PEEK(-4096)-47
1 IF VE>32767 THEN VE=VE-65536
```

Then, to switch printer on, simply use:

```
POKE VE,147
```

and to switch it off:

```
POKE VE,240
```

Simple, isn't it?

### Hint:

Ever wondered how to make your cursor flash? Here is how it is done:

Choose a convenient part of memory that is not being used for anything else. (0 to FF can sometimes be convenient in a BASIC programme). Enter following code from the Monitor (BYE from Basic):

```
0000: 06 18 CD 18 E0 10 10 CD D6 E9 3E 5F BE F5 C4 CC
0010: E9 F1 CC E8 E9 18 E9 28 E9 C9
```

Now, all there is to do is to set your input vector to the start address of the routine using the Monitor command:

```
SE I=xxxx
```

Of course, our example has been entered from 0 to 19, but your version could run elsewhere. The above code needs no modification to run anywhere in memory.

### Question:

I am trying to write a small BASIC program and I'm having trouble clearing the screen. Is there a neat way of doing this?

### Answer:

Certainly. Simply include in your programme the statement PRINT CHR\$(12). This will effectively clear the screen and put the cursor in the top left position (HOME).

### Question:

I have heard that it is possible to RESTORE data halfway through a program. Is this correct?

### Answer:

Yes. One of the un-documented functions in Exidy BASIC is its ability to RESTORE to a line number. Thus the statement RESTORE 100 will restore the data pointer to line 100. The next data will be read from line 100 onwards, and any data before line 100 will be ignored.

A.P.F. Fry

# Computer Country Pty. Ltd.

## "THE MICROCOMPUTER PROFESSIONALS"

Thinking of purchasing a microcomputer system or adding to the one you already have? Make a good investment — invest a little bit of time to talk to the professionals at Computer Country. Remember the quality of the after-sales hardware service and continual after-sales software and hardware advice you get is just as important as the price of the system you buy. Come and have a chat with the professionals of Computer Country just once and you'll realise how much help we can be in enabling you to get the most out of your microcomputer system.

Computer Country stocks a wide range of microcomputer hardware including the Apple, Northstar, Commodore, Texas Instruments, NEC, Impact Data and many more. We carry a wide range of software for many systems including the TRS-80. We can also help you in customising software for your specific application.

Our service department not only completely backs up all hardware purchased from us, but invites enquiries from those who have purchased elsewhere and have hard-to-fix problems.

**MAKE A SMART MOVE  
— COME TO**

**COMPUTER COUNTRY  
338 QUEEN STREET,  
MELBOURNE, VIC 3000**

Note: Computer Country is now expanding nationwide. Franchise opportunities are available in N.S.W., Qld., W.A., N.T., Tas. and S.A. Contact the Managing Director NOW before your area is taken.

# C70MGP

General Instrument's  
*NEW!* Thinking Cap  
Keyboard



General Instrument's Keyboard Division has combined state-of-the-art microprocessor technology with the reliability and simplicity of capacitive keys to create a highly flexible, low cost keyboard for OEM's and hobby projects.


The C70-MGP is chock full of features like 4 level ASCII encoding, serial and parallel outputs, N-Key rollover, provision for RS232 and 20MA loop connection, cursor control and user definable keys and programmable baud rates, all for around \$150, plus tax. At a dealer near you.

AUTHORISED DEALERS: **Sydney** (02) E. & M. Electronics 51-5880. A.E.D. 632-6301. Applied Technology 487-2711. G.E.S. 439-2488. **Melbourne** (03) Sontron Instruments 568-4022. Cottage Computers 481-1975. Ellistronics 602-3282. Stewart Electronics 543-3733. **Brisbane** (07) Baltec Systems 36-5183. Zero One Electronics 371-6707. **ACT** (062) Ortex 82-4995. **Adelaide** Rogers Electronics (08) 42-6666. **Perth** (09) Micro Controls 325-2444. **New Zealand** Southmark (9) 798-078.



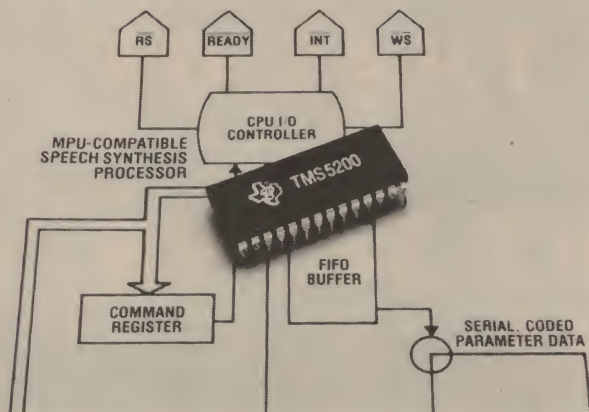**daneva control pty. ltd.**

66 Bay Road, Sandringham, Vic., 3191. Ph: 598-5622 Telex: AA34439



## Texas gets another voice

**The family of Texas Instruments speech synthesis chips has a new baby called TMS5200.**

His most interesting feature is that he contains an onboard buffer organised on a first in first out (FIFO) basis, 16-bit parallel in and serial out. This buffer frees the CPU for the 50 milliseconds that it takes to exhaust itself and allows speech data to be stored in PROM, RAM or any other random access storage medium.

Like his elder brother TM5100, the new chip is P-channel MOS and uses an encoding method called Linear Predictive Coding. Texas ex-

plain this as 'a technique of analysing and synthesising human speech by determining from original speech a description of a time varying digital filter modelling the vocal tract.

"This filter is then excited by either periodic or random inputs. An on-chip 8-bit digital-to-analogue converter transforms digital information passed through the filter into synthetic speech." So now you know!

Enquiries to Texas Instruments Asia Ltd, Serangoon Rd, P.O.138, Singapore 9132.

## 'SABER' data repeater

**A single integrated circuit device which can physically extend a common buss between close-coupled or remote digital data processing or communications equipment and repeat and retransmit signals without signal degradation has been introduced by Signetics.**

The new integrated circuit is the 8X41, otherwise known as the Signetics Asynchronous Bi-directional Bus Extender and Repeater (SABER).

In contrast to more complex retransmission schemes which may involve six or more separate integrated circuits, the eight-channel 8X41 SABER can transfer data between up to either pairs of elements in a data processing or communications system without external logic.

By inserting the 8X41 in series with a properly termi-

nated open collector buss, the signals passing through the buss in either direction can be repeated without degrading buss drive capability or signal rise and fall time.

The SABER's eight data channels are controlled by the lines which determine whether the direction of transmission or whether the device is to simply repeat the data on either buss.

Potential use of the chip would be any application where data is exchanged over a

## Support for the Z8000

**Support and development hardware for the Z8000 sixteen bit microprocessor is arriving thick and fast.**

First of all, Zilog has released news of an intelligent microprocessor emulator subsystem called ZSCAN 8000 which they say represents a new modular approach to development systems.

Previous systems have combined the software development capability with the emulator in a single unit, which meant that the system was restricted to a single microprocessor.

ZSCAN 8000 interfaces to Zilog's PDS 8000 development systems for use with both versions of the Z8000, but it can also be used easily with other microcomputers, minicomputers and mainframes — in fact any host with a standard RS232C interface.

Priced at around \$4500, ZSCAN 8000 will be available here in about three months.

Next there's the Z8010 Memory Management Unit, which offers dynamic segment relocation and memory protection for each of the Z8001's address spaces. It's designed to give the memory space a logical rather than a physical structure and to protect the user from inadvertent errors and the operating system from unexpected access by the user.

Each Memory Management Unit has 64 randomly accessible segments ranging in size from 256 bytes to 64 kilobytes

and these can be mapped into a total physical address space of 16 megabytes. Introductory price is \$187 each for ten or more.

The Z8000 MPU is the first of a new series of microcomputer boards based on the Z8001 processor. It can function either as a stand-alone single board microcomputer or as the master in a set of several peripheral boards. There are 32K bytes of onboard RAM with parity protection and 8K bytes of additional ROM space. Priced at \$2295 it's available now.

A new system-level backplane buss structure can be used with all three of Zilog's micros, the Z8, Z80 and Z8000. Its 32 address/data lines and 28 control lines mean that it will also be able to accommodate future 32 bit micros.

Complete information on all of Zilog's family of microcomputer components is contained in their new 'Microcomputer Components Data Book', a 254 page catalogue which provides technical data consisting of functional descriptions, architecture and programming information, pin descriptions and electrical specifications.

More info on all Zilog products from the distributors, Zap Systems Pty Ltd, 51-53 Chandos St, St Leonards, NSW 2065. Phone (02) 438-4533.

common parallel buss, especially where direct memory access (DMA) is required. This would include EDP, CPU and peripheral equipment, multi-processor distributed networks and systems, as well as automatic test and measurement systems.

The high output drive of the 8X41 can sink up to 70 milliamps of current and drive a buss on which up to several hundred peripheral devices are connected. Input current

requirement is only 100 microamps!

The 8X41 has a maximum delay time of 30 nanoseconds, is TTL compatible, has open collector outputs and operates from a single 5 V power source.

The SABER is available in 24-pin plastic dual in-line package. Detailed specifications, delivery and pricing are available from Philips Electronic Components and Materials, 67 Mars Road, Lane Cove NSW 2066. (02)427-0888.

**WITH THE PRICE OF OUR  
DISK DRIVES ONLY  
ABOUT HALF THAT OF  
TANDY'S,  
PEOPLE MIGHT THINK  
THEY MUST BE  
INFERIOR.**

**HERE'S WHAT A REVIEWER HAS TO  
SAY IN THE "TANDY & SYSTEM 80"  
NEWSLETTER.**

AUGUST ISSUE, VOL. 11 PAGE 3

*"DICK SMITH DRIVES" are in reality a Pertec 40 track drive they have a 20ms track to track seek and are generally quieter in their running. They have separate power supply allowing the unit to run cooler and because of their 40 tracks they store 102.4K bytes. Both sides of the diskettes can be used without modification.*

*"TANDY DRIVES" have been made by 2 suppliers, the earlier drives were Shugart, whereas the later models are Teac. Both these drives are 35 track units and have a track to track of 40ms. The total storage is 89.6K bytes and because of an inbuilt power supply they run quite hot and in enclosed spaces are prone to motor speed errors!! Only one side of the diskette can be utilized. Slightly noisier than the Pertec.*


*As the all up cost of 4 DICK SMITH drives is about \$1000.00 cheaper than the TANDY unit, the DICK SMITH drives seem a far better buy.'*

**PERHAPS WE  
SHOULD HAVE  
MADE THEM  
\$100 DEARER!**

**SEE THE OTHER DICK SMITH  
ADS IN THIS MAGAZINE  
FOR STORE ADDRESSES**



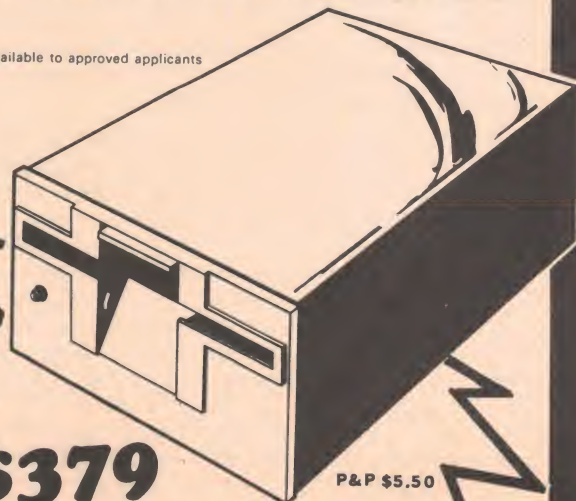Credit terms available to approved applicants



**\$379**

Cat. X-3230

Power supply to suit 2 drives  
Cat. X-3234

**\$60.00**

P&P \$5.50

**ETI READER OFFER**

**computer users —**

# FANTASTIC OFFER ON FLOPPY DISKS



## SPECIAL PRICES

	10-19	20-49	50-99	100+
133 mm (SS, SD)	\$4.95	\$4.39	\$3.99	\$3.29
200 mm (SS, SD)	\$5.95	\$4.86	\$4.25	\$3.95

**Both sizes can be mixed to qualify for the quantity discount.**

## Packing and delivery

10-19	\$1.50
20-49	\$2.00
50-99	\$2.50
100+	\$3.00

Floppy disks are the highly convenient magnetic media used for mass storage with minicomputer systems. Dindy Marketing (Aust.) Pty Ltd has made available a quantity of 133 mm (5") diskettes and 200 mm (8") floppy disks for ETI readers at special prices. These single-sided, single-density disks are manufactured in the USA and are identical to those marketed here by two large well-known electronics retailers.

Each precision coated disk is enclosed in a PVC jacket with a protective liner. This material has low frictional properties and resists mechanical shock and heat. Minute foreign particles are absorbed by the liner, leaving the disk 'clean' for optimum recording performance. The disk itself consists of oriented polyester coated with a uniquely formulated gamma-ferric oxide, encapsulated in a wear resistant binder providing minimum friction with maximum durability. The smooth, polished surface results in low head and pad wear and gives long performance life.

All stages of manufacture of these disks are carried out in environmentally 'clean' rooms and each stage is continuously monitored to ensure accuracy in accordance with rigid industry standards. Before being consumer packed, the specially coated material is tested for signal levels, modulation and resolution, and the disk certified free of errors.

**NOTE: Offer closes 13 November**

**Money back guarantee:** Dindy offer to refund the purchase price in full if you are not completely satisfied and provided you return the goods within 14 days of receipt.

**Mail this coupon now and ensure delivery of your order before Christmas. Make out your cheque or money order to 'Dindy Disk Offer', don't forget to include post and delivery charges.**

NOTE: This offer is made by Dindy Marketing (Aust.) Pty Ltd and ETI is acting as a clearing house only. Cheques or money orders should be made payable to 'DINDY DISK OFFER' and sent, together with the coupon (or a photostat or clear, hand-written copy of same), to Disk Offer, ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011. We will then process your order and pass it on to Dindy who will send you the goods. Please allow up to four weeks for delivery.

**Send coupon to:  
Dindy Disk Offer**

**ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011**

**Please supply:**

Quantity ..... 133 mm ..... \$ .....  
..... 200 mm ..... \$ .....

Packing and delivery: ..... \$ .....

**TOTAL: \$ .....**

(Disks may be mixed for quantity discounts)

Name .....

Address .....

..... Postcode .....

Cheque or money order .....

Or use your Bankcard 

4	9	6																	
---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

 Expiry Date .../.../...

Signature .....

# COMP-SOFT

## MICROCOMPUTER SERVICES

### OHIO SCIENTIFIC (OSI) COMPUTERS

- Superboard and software    ● HP-85 (16K RAM, 16K ROM)
- C1P    ● C4P    ● C4PMF    ● 5" (16x32) VDU, 5" printer
- C8P    ● C8PDF    ● 60CPS, RS232

### TRADING HOURS

Monday to Thursday:  
9.30 am-5.30 pm  
Friday: 4.30 pm-8.30 pm  
Saturday: 9.00 am-12.30 pm

235 SWAN STREET, RICHMOND. PHONE (03) 428-5269.

## SWITCHING POWER SUPPLIES


The California DC range of switching regulated power supplies is now available in Australia. The LR Series of open frame supplies provide size and weight savings over linear, series regulated supplies. Conservatively rated for long life, the LR Series was designed for use in computers, computer peripherals and industrial controls. They provide power for floppies; tape drives, memories and microprocessors. The range includes versions with up to four independent output voltages.


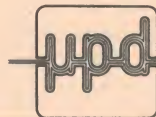
#### Standard features include:

- Plus/Minus 20 percent line tolerance
- Inrush limiting on turn-on
- Individual output regulation of 1 percent
- Individual output current limiting with foldback
- Thermal protection
- 50 millivolt P-P output ripple and noise
- 0-40 degrees C convection cooling without derating
- 70 percent minimum efficiency at full load

The power supplies range in price from \$170 to \$330.



**MicroPro Design Pty. Ltd.**

PO Box 153, North Sydney, NSW 2060. Phone (02) 438-1220.

## EXCITING NEW POCKET SIZE DIGITAL MULTIMETERS

'SANSEI' 2200A DIGITAL MULTIMETER, with a 3½ digit LCD display. This new Multimeter has now been released, with an accuracy of 0.3% for under \$100. Other features include auto polarity, low battery and overrange indication. Supplied with Test Leads, spare fuse and battery.

#### RANGES

DC . . . . 2, 20, 200 and 1000 V  
AC . . . . 2, 20, 200 and 600 V  
OHMS .2K, 20K, 200K, 2M, 20M  
DCA . . . . . 2mA, 20mA, 200mA, 500mA

ONLY  
**\$95**

+\$14.25 S.T.

#### Diode Test range

This is a 0.3% basic instrument with 200 hour continuous operation from a single battery.

**SEND TO:**



'SANSEI' 2000A DIGITAL MULTIMETER, with a 3½ digit LCD display. We are now able to offer an AUTO RANGING D.M.M. for the price of a normal D.M.M. It has an accuracy of 0.3% and features low battery warning, and overrange indication. Test leads, spare fuse and battery supplied.

#### RANGES

DC . . . . 2, 20, 200 and 1000 V  
AC . . . . 2, 20, 200 and 700 V  
OHMS . . . . 2K, 20K, 200K, 2M  
DCA . . . . . 200mA

ONLY  
**\$138**

+\$20.70 S.T.

This is a 0.3% Basic Instrument with 30 hours continuous operation.

**MONEY BACK GUARANTEE**  
Packing and delivery \$2.00



**CHRISTIE RAND PTY. LTD.**


P.O. BOX 48, EPPING, NSW, 2121. PHONE: (02) 477-5494.

# \$399 COMPLETE COMPUTER KIT

ATZ 80  
OWNERS  
MANUAL

Z80  
PROGRAMMING  
COURSE

KEYBOARD

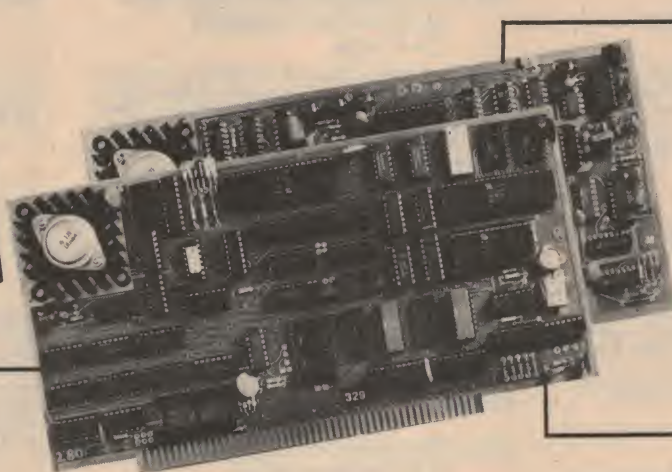

CASSETTE  
INTERFACE

**LEARN AS YOU BUILD THIS POWERFUL S100/Z80 MODULAR MICROCOMPUTER. YOUR ATZ80 KIT INCLUDES -**

- \* DGZ80 AUSTRALIA'S MOST POPULAR SINGLE S100 BOARD MICROCOMPUTER.
- \* DG640 S100 VIDEO DISPLAY UNIT.
- \* POWER SUPPLY, MOTHER BOARD, CASSETTE INTERFACE, HEX KEYPAD.
- ALSO -**
- \* DETAILED CONSTRUCTION MANUAL
- \* EXCLUSIVE Z80 PROGRAMMING COURSE.
- \* SAMPLE PROGRAMS TO RUN.
- \* EXPERIMENTS TO CARRY OUT ...  
COMPUTER CONTROLLED BURGLAR ALARM,  
ROBOT, MUSIC GENERATOR, TIME CLOCK,  
VIDEO GAMES ETC.
- \* FULL TECHNICAL BACKUP AND SUPPORT SERVICE.

Now you can build your own S100/Z80 based micro computer and learn this exciting new technology as you go. Based on the DGZ80 (ETI November 1978), you are assured of a proven versatile design. Hundreds have already been sold to hobbyists in Australia, New Zealand, Hong Kong and to Government Departments such as C.S.I.R.O. Defence, Transport and to industry such as I.B.M., Rothmans, Leeton Steel Works etc.

The ATZ80 is a complete computer. You just add a tape recorder and a modified T.V. and you have a system equal to those costing \$1,000 or

more. Because it is already based on the S100 system you can readily expand your system adding extra memory boards, I/O boards and peripheral such as printer and floppy disks. Full program support is available, BASIC, EDITOR, ASSEMBLER etc. now readily available. Your Z80 is supplied with detailed construction manual and an exclusive step by step programming course that seems so lacking in other kits.

You can add options as required such as the CLARE C70 keyboard (\$165.00) and extra memory 16K S100 Static memory card (\$259.00), Card frame (\$49.50), 19 slot Mother board (\$49.50).

With the ATZ80 you have a complete, self contained microprocessor which you can apply immediately or expand to equal computers sold for \$20,000 or more.

Call into our Showroom for a personal demonstration or order by mail. (Return as received within 14 days for a full refund if not completely satisfied).

Please send for our free comparison chart.

All prices include Sales Tax.




**APPLIED  
TECHNOLOGY  
PTY. LTD.**

MAIL ORDERS TO:  
PO Box 311, Hornsby 2077.

Please add \$2.00 per order  
towards cost of post and packing.

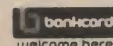OFFICE/SHOWROOM  
1a Pattison Avenue, Waitara 2077.  
Hours: 9-5 Monday to Saturday  
Telephone: 487 2711



# Radio & Electronics Books

**BERNARD BABANI (publishing) LTD**

**160: COIL DESIGN & CONSTRUCTION MANUAL**  
**B.B. Babani**

• Complete book on how to design and make RF, IF, audio and power coils, chokes and transformers. Every type is discussed and calculations given. Covers AM and FM radio and TV.

**96 pages**

**Price \$2.75**

**202: HANDBOOK OF ICs EQUIVALENTS AND SUBSTITUTES.**  
**B.B. Babani**

• One of the most complete IC equivalent and substitute guides yet published. Full data on over 9500 ICs. Covers digital and linear of all types from UK, USA, Japan, Germany, France, Czechoslovakia etc.

**128 pages**

**Price \$3.70**

**221: 28 TESTED TRANSISTOR PROJECTS**  
**R. Torrens**

• Some circuits are completely new — others are more familiar designs. The projects can be split into simple building blocks to enable readers to combine circuits for specialised needs.

**96 pages**

**Price \$4.60**

**224: 50 CMOS IC PROJECTS**  
**R.A. Penfold**

• CMOS ICs are suitable for an extraordinarily wide range of applications, are cheap and easy to obtain. Here are a number of interesting and useful projects in four general categories: (1) Multivibrators, (2) Amplifiers and oscillators, (3) Trigger devices, (4) Special devices.

**112 pages**

**Price \$3.50**

**225: PRACTICAL INTRO TO DIGITAL ICs**  
**D.W. Easterling**

• This book introduces the reader to digital ICs (mainly TTL 7400 series). Besides a number of simple projects, contents include details of a Logic Test Set which enables constructors to identify and test digital ICs. Also includes digital counter-timer.

**80 pages**

**Price \$4.60**

**227: BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS**  
**R.A. Penfold**

• Enables total beginners to tackle practical electronic so he or she can confidently build electronics projects such as published in ETI and other magazines and books. Subjects include component identification, tools, soldering, various building methods, cases, legends etc. Practical basic projects are also included.

**112 pages**

**Price \$4.60**

**BP1: 1ST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES**  
**B.B. Babani**

• Complete transistor equivalents guide. More than 25 000 transistors with alternatives and equivalents. Covers devices made in UK, USA, Japan, Germany, France, Europe, Hong Kong etc. See also BP 14 (below).

**80 pages**

**Price \$2.25**

**BP 14: 2ND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES**  
**B.B. Babani**

• The second book contains data on devices not included in the first. This book supplements BP1, no data is duplicated.

**208 pages**

**Price \$4.05**

**BP 24: 52 PROJECTS USING IC 741**  
**Rudi & Uwe Redmer**

• Originally published in German, this book achieved huge European sales. Now translated into English with copious notes, data and circuits, this book is a must for those interested in any way in this inexpensive and most versatile IC.

**80 pages**

**Price \$3.50**

**BP 33: ELECTRONIC CALCULATOR USERS HANDBOOK**  
**M.H. Babani**

• An invaluable book for all calculator users. Presents formulae, data, methods of calculation, conversion factors etc, often with examples. Includes way to use simple four-function calculator for Trig functions (sin, cos, tan); Hyperbolic functions (sinh, cosh, tanh), Logs, Square Roots & Powers.

Comprehensive conversion factors incorporated, including length, area, volume & weight through specialised conversions such as viscosity, illumination, cargo shipping measures etc. Also formulae for discounts and mark-up, currency conversions, interest, solutions of equations, binary and octal numbers, areas and volumes, stats and maths etc.

**208 pages**

**Price \$3.50**

**BP 36: 50 CIRCUITS USING GERMANIUM, SILICON, ZENER DIODES**  
**R.N. Soar**

• Contains 50 interesting and useful circuits and applications in many different branches of electronics.

**64 pages**

**Price \$2.75**

**BP 37: 50 PROJECTS USING RELAYS, SCRs & TRIACS**  
**F.G. Rayer**

• Relays, SCRs and Triacs have a wide range of applications — from motor speed control, dimming, heating, timers, light-sensitive circuits, warning devices, light modulators, priority indicators, circuit breakers etc. Book gives tried and proven circuits which will tolerate wide latitude of components and values allowing easy modification to suit special needs.

**112 Pages**

**Price \$4.60**

**BP 39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS**  
**F.G. Rayer**

• Field effect transistors are used in many circuits. The projects here include amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, plus miscellaneous devices. The FET used is not critical and many other types will work as well. This book will be of interest to all enthusiasts, shortwave listener, radio amateur, hi-fi buff or general electronics experimenter.

**112 pages**



**Price \$4.60**

**BP 40: DIGITAL ICs AND PIN CONNECTIONS**  
**Adrian Michaels**

• Equivalents and pin connections of a popular user-orientated selection of digital ICs. Shows details of packaging, families, functions, manufacturer and country of origin. Includes devices by Fairchild, Ferranti, Harris, ITT, Motorola, National, Philips, RCA, Signetics, Sencocem, SGS-Ates, Siemens, SSSI, Stewart Warner, AEG-Telefunken, Texas, Teledyne. Companion volume to BP 41 — Linear ICs.

**320 pages**

**Price \$9.00**

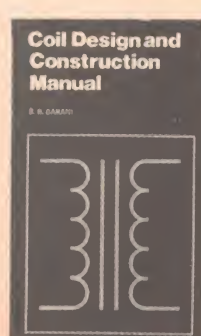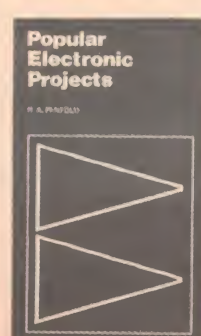

**BP 41: LINEAR IC EQUIVALENTS  
AND PIN CONNECTIONS**  
**Adrian Michaels**

• Essentially similar in concept to above but deals with linear integrated circuits.  
**320 pages** **Price \$10.00**

**BP 42: 50 SIMPLE LED CIRCUITS**  
**R.N.Soar**

• 50 interesting and useful circuits and applications using LEDs. A useful book for beginner and advanced enthusiast alike.  
**64 pages** **Price \$3.50**

**BP 44: IC 555 PROJECTS**  
**E.A.Parr**

• Every so often a device is made that is so useful one wonders how life went on before it! The 555 IC is one such. First made by Signetics it is now manufactured by almost everyone in the business. It is very cheap and readily obtainable.  
Included in this book are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus a section on the subsequent 556, 558 and 559 devices.  
**160 pages** **Price \$6.45**

**BP 45: PROJECTS IN  
OPTO-ELECTRONICS**  
**R.A.Penfold**

• Opto-electronic projects of interest to all electronics enthusiasts. Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra-red transmitters and receivers, modulated light transmission and photographic projects.  
**112 pages** **Price \$4.95**

**BP 47: MOBILE DISCO HANDBOOK**  
**Colin Carson**

• Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.  
**128 pages** **Price \$4.95**

**BP 48: ELECTRONIC PROJECTS FOR  
BEGINNERS**  
**F.G.Rayer**

• This book gives the newcomer to electronics a wide range of easily built projects. Actual component and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.  
**128 pages** **Price \$4.95**

**BP 49: POPULAR ELECTRONIC  
PROJECTS**  
**R.A.Penfold**

• A collection of the most popular types of circuits and projects covering radio, audio, household and test equipment.  
**144 pages** **Price \$5.35**

**BP 51: ELECTRONIC MUSIC AND  
CREATIVE TAPE RECORDING**  
**M.K.Berry**

• This book shows how electronic music can be made at home with simple and inexpensive equipment. It describes how sounds are created and recorded to build up a final composition. It shows how to build a small studio including mixer and various sound effects units.  
**96 pages** **Price \$4.60**

**BP 53: PRACTICAL ELECTRONIC  
CALCULATIONS AND FORMULAE**  
**F.A.Wilson**

• This book is for the practical person's workshop bench. It bridges the gap between technical theory and cut-and-ried methods which may work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths has been avoided where possible. Many tables are included. This one's a beauty!  
**256 pages** **Price \$8.25**

**BP 56: ELECTRONIC SECURITY  
DEVICES**  
**R.A.Penfold**

• Simple and more sophisticated burglar alarms using light, infra-red and ultrasonics; also other types of alarm such as gas and smoke detectors, flood alarms, doorphone and baby alarms etc.  
**112 pages** **Price \$5.35**

**ELEMENTS OF ELECTRONICS**  
**F.A.Wilson**

**BP 62 — Book 1**

**BP 63 — Book 2**

**BP 64 — Book 3**

• This series provides an inexpensive intro to modern electronics. Although written for readers with no more than basic arithmetic skills, the use of maths is not avoided — all the maths is taught as the reader progresses.

The course concentrates on the understanding of concepts central to electronics rather than continually digressing over the whole field — on the basis that once the fundamentals are mastered, the workings of most other things are soon revealed. The author anticipates where the difficulties lie and guides the reader through them.

Book 1 . . . All the fundamental theory necessary to a full understanding of simple electronic circuits and main components.

Book 2 . . . Alternating current theory.

Book 3 . . . Semiconductor technology leading to transistors and ICs.

These three books constitute a complete, inexpensive electronics theory course of inestimable value in either hobby or career.

**224 pages** **Price \$8.25 (each volume)**

**BP 65: SINGLE IC PROJECTS**  
**R.A.Penfold**

• All projects in this book are simple to build and are based on a single IC. A few projects use one or two transistors in addition. A strip board layout is provided for each project together with special constructional points and setting up info. The five chapters are: Low level audio, Audio power amps, Timers, Op-amps, Miscellaneous circuits.

**128 pages** **Price \$5.50**

**BP 66: BEGINNERS GUIDE TO  
MICROPROCESSORS AND  
COMPUTING**  
**E.F.Scott**

• An introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. The only prior knowledge assumed is very basic arithmetic and an understanding of indices.

**128 pages** **Price \$6.45**

**BABANI BOOKS — MAIL ORDER, DIRECT FROM ETI !**

Please send me:

Book	Qty.	
160	...	BP41 . . .
202	...	BP42 . . .
221	...	BP44 . . .
224	...	BP45 . . .
225	...	BP47 . . .
227	...	BP48 . . .
BP1	...	BP49 . . .
BP14	...	BP51 . . .
BP24	...	BP53 . . .
BP33	...	BP56 . . .
BP36	...	BP62 . . .
BP37	...	BP63 . . .
BP39	...	BP64 . . .
BP40	...	BP65 . . .
		BP66 . . .

Post & handling:

1 - 4 books: \$1.35

5 - 10 books: \$2.70

11 - 20 books: \$3.50

over 20 books: \$5.00

I enclose \$ . . . . . (inc. p & h.)

Note: Prices are effective until Jan. 1st 1981.

Name . . . . .

Address . . . . .

. . . . . postcode . . . . .

Send to: ETI 'Book Sales', 3rd Floor,  
15 Boundary St, Rushcutters Bay NSW 2011.  
Please allow 4 - 5 weeks for delivery.

WE REGRET WE CANNOT SUPPLY NEW ZEALAND READERS



# CISA

## The one-stop Microcomputer Shop for total service to TRS-80\* users

\*TRS-80 is a registered Trademark of Tandy Radio-Shack

### NOW AVAILABLE CISA DISK PASCAL

Executes up to 60 times faster than DISK BASIC.  
HAS FULL DISK I/O FEATURES and many facilities not available on languages costing many hundreds of dollars.  
DO NOT CONFUSE WITH CHEAP CASSETTE-BASED 'TINY' PASCALS.

Systems overlays and developments will be available to registered users at a nominal charge.

Includes the fastest and most powerful screen editor we have seen.

Will edit PENCIL, SCRIPSIT and ASCII files.

PASCAL is much easier to manipulate than ASSEMBLY, and is practically as efficient as it compiles into a true-optimized machine-code.

More efficient than currently available BASIC COMPILERS selling for twice the price.

We honestly believe that this Australian written PASCAL to be the fastest, most sophisticated and powerful high-level language available anywhere in the world for the TRS-80 Model I.

## RELEASE 1.0 \$99.00

(numbered copies to registered single-users only)

### CISA HARDWARE AND MODS

#### HEAVY DUTY POWER LINE FILTER

Essential in most domestic situations .....\$65.00

CISA LIGHT PEN (again in stock)  
Includes full documentation and sample program.....\$19.95

CISA DATA DIGITIZER  
Use this with HISPED program and you really have a business system in LEVEL 2. Requires no system modifications.....\$57.50

AUTOMATIC TELEPHONE DIALLER  
Easy attachment to TRS-80. Requires no hardware mods. Complete with softwares and documentation.....\$57.50

16K UPGRADE KITS  
KEYBOARD KIT .....\$85.00

INTERFACE KIT (yes there is a difference)\$105.00  
We fit — \$20.00 plus carriage \$5.00 overnight return.

DISK DATA SEPARATOR  
These are the components that TANDY forgot. Virtually eliminates all disk I/O errors. Absolutely essential for 77 track users. We fit.....\$49.95 (sorry no kits)

GREEN PHOSPHOR TUBES  
Not a cheap plastic overlay. We fit a genuine professional standard VDU tube with 1/4" armoured low reflective front panel. (no kits) .....\$99.00 (fits old and new type Tandy VDU and current Disk Smith monitor)

CISA RS232 PRINTER-DRIVER  
Operate any RS232 or 20MA serial printer with this Australian made unit. Includes software ..\$54.75

LOWER CASE MODIFICATION  
Get video lower-case for BOTH Scrpsit and Electric Pencil. Fitted.....\$49.95

VIDEO STABILISER CRYSTAL  
Totally removes shimmer and wobble on your video. Highly recommended for Green Tube.

Kit.....\$19.95  
Fitted.....\$39.95  
DUMMY PRINTER  
Plug this into the parallel port of the interface and avoid system lockups. If you accidentally type LLIST or LPRINT .....\$14.95

### TRS-80 SOFTWARE

AIR TRAFFIC CONTROLLER L2/16K  
Supervise a large area of air-space in real time.....\$9.95

SPACE GAMES L2/16K  
Five brilliant games in the classic space series .....\$14.50

STRATEGY GAMES L2/16K  
Four fascinating games to test your judgement and logic .....\$14.50

ADVENTURE SERIES L2/16K  
Adventure-1, The Count, Voodoo Castle. Each.....\$14.95

Z-CHESS  
A fast and exacting opponent. 6 levels of play. L2/16K.....\$19.95

Disk 32K.....\$24.95  
DISASSEMBLER in BASIC L2/16K only

Disassembles ROM and high memory machine language routines .....\$9.95

TAPECHECK L2 16K plus  
Checks and verifies every millimetre of a cassette tape. Also useful as cassette I/O diagnostic\$9.95

RS232 DIAGNOSTIC 32K/DISK  
Interrogates, tests and reports on EVERY feature of Tandy RS232 board.....\$19.95

FLOPPY DOCTOR 32K/DISK  
This is the most comprehensive and exacting series of memory and disk I/O tests we have seen.

From Micro-Clinic, USA.....\$29.95  
SIMUTEK 7 separate packages

These seven packages are excellent value for any TRS-80 owner.....\$14.95 ea.  
Plus many, many more.

### "HISPED" TAPE OPERATION

2K Baud PLUS for the TRS-80\*

- Save, verify and load programs up to 4 times faster than normal
- Save, verify and load array data up to 30 times faster than PRINT
- User variable hardcopy formatting (3 output routines work with most printers)

- "HISPED" is a machine language program (not a hardware add-on)

- 2 copies plus a free basic test program supplied on high quality cassette — for level 2, 16K, 32K or 48K.\*

MAKES STRINGY FLOPPIES REDUNDANT.

## \$24.95

Available only from Cisa and authorised agents.

### MICROPOLIS DRIVES FOR THE TRS-80\*

For the enthusiast: 192K bytes per drive.

SINGLE 77 TRACK .....\$699.00

A professional disk drive for the business user:

TWIN 77 TRACK 385K.....\$1499.00

Both complete with heavy-duty case and inbuilt power supply and free despatch to TRSDOS.

Requires cables — 2 drive \$30, 3 drive \$40, 4 drive \$50.

MIX 'N MATCH with any 35 or 40 track drive.

SHOP WHERE YOU CAN BE SURE OF SERVICE  
BACK-UP AND YOUR WARRANTIES HONOURED.

### SOFTWARE FROM RACET

INFINITE BASIC \$49.95 L2 and DISK

Add 30 BASIC commands plus full MATRIX MANIPULATION.

Add 50 STRING functions, including high-speed sorts.

BUSINESS BASIC (requires INFINITE BASIC).....\$29.95

Another 20 functions including set printer parameters, 127 digit mathematical functions, binary array searches and hash code generator.

COMPROC Command Processor for Disk .....\$19.95

Auto your system to any sequence of DOS, machine-language or BASIC routines. Includes screen-print, auto debounce and lower-case software driver.

DSM Disk Sort and Merge Min 32K and Disk.....\$75.00

Sorts 85K diskette in less than 3 minutes.  
Sorts 190K diskette in less than 6 minutes.

COPYSYS for cassette systems.....\$14.95

Copy and verify virtually any machine-language program.

GSF 32K and 32K DISK .....\$34.95

18 high-speed machine-language routines including high-speed in-memory sorts.

Sorts a 1,000 element string array in 6 seconds.

### PHONE OR CALL AND BROWSE. TRADE ENQUIRIES INVITED

Trading Hours: 9am to 6pm Monday-Friday, 9am to 12.30pm Saturday.

All the above fine products are available at or can be ordered from:

SOFTWARE-80, Shop 11/198 Moggill Road, Taringa, Brisbane, QLD 4000. Phone: (07) 371-6996.

SOUTH COAST COMPUTING SERVICES, 90 Warrigee Street, Nowra, NSW, 2540. Phone: (044) 24967.

THE BYTE SHOP, Colbee Court, Phillip, ACT, 2606. Phone: (062) 81-5011.

H.S. ELECTRONICS, 104 Charles Street, Launceston, TAS 7520. Phone: (003) 31-8942.


## CISA MICROCOMPUTING PTY. LTD.

159 KENT STREET, SYDNEY, NSW 2000. PHONE: (02) 241-1813.

Orders under \$100 add \$2.00 p and p. Over \$100 post free. For repairs and mods to systems — send by carrier — you pay, we pay return carriage.

# 'THE S100 BUS STOP'™

## SBC200

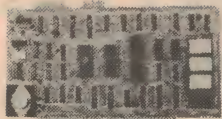

Z80 single board computer, 4MHz, 16K EPROM, 1K RAM, 16K EPROM, 1 serial port, 1 input & 1 output parallel port, power on jump, 2K monitor, 2716 4 channel counter/timer, software controlled baud rate generator, modem look alike, vectored interrupt

KIT \$360.00 ASS & TESTED \$440.00

## MPB100



Z80 CPU board, switchable 2 or 4 MHz operation, power on jump to any 4K boundary, on board 2716 PROM socket, optional front panel provision, wait state generator, 2K monitor available, will suit dynamic RAMs.

KIT \$260.00 ASS & TESTED \$310.00

## 16K STATIC RAM



2114 low power RAM chips, 4K address boundary, standard bank select (40H) 4 MHz operation with no wait state required when using our chips, wait state generator for above 4MHz plated thru holes, solder resist, optional 300NS RAMS available.

KIT \$315.00 ASS & TESTED \$380.00

## 32-64K DYNAMIC RAM



Bank select, 200 nS chips standard up to 4MHz speed, will accept 64K RAMs to give 256K per board, switch selectable boundaries, invisible refresh, phantom output disable, standard S100, plated thru holes, solder resist, components overlay.

KIT 32K-\$525 48K-\$670 64K-\$815  
A&T 32K-\$605 48K-\$750 64K-\$895

## 2708 EPROM



Switch selectable as 8 or 16K card 8K address boundary, wait state gen, suites industry standard 2708's standard S100, plated thru holes, solder resist.

KIT \$98.00  
ASS & TESTED \$125.00

## SERIAL-PARALLEL I/O PORT



Dual serial ports with RS232 & TTY outputs, nine programmable parallel ports, wire wrap cross link area for parallel I/O, switch selected baud rates, 9600-75 baud, 4 byte address decoding for I/O, switch selected, plated thru holes, solder resist.

KIT \$189.00 ASS & TESTED \$225.00

## SINGLE DENSITY DISK CONTROLLER



IBM 3740 soft sectored, operates standard 8" or 5" drives, single or double sided drives, utilizes FD1771 controller chip, runs CP/M disk opp software, operates with Z80, 8085 & 8080 CPU, CP/M, BIOS & diagnostic prompts to suit are available.

KIT \$258.00 ASS & TESTED \$308.00

## SINGLE/DOUBLE DEN. DISK CONTROLLER



Operates with single & double den. single & double sided drives & 8" or 5" drives in any combination of 4 drives simultaneously, phase lock loop data recovery, with SDOS operating system you can run all CP/M and CDOS programmes.

KIT \$360.00 ASS & TESTED \$420.00

## 80 x 24 VIDEO



On board Z80, 80 char. x 24 lines, 7 x 10 matrix, keyboard interface, 96 up & lower character, 32 special characters, optional 128 extra char composite video, for/rev scrolling, XY address cur, blinking underline reverse video & field protect.

KIT \$380.00 ASS & TESTED \$450.00

## EPROM PROGRAMMER



2708, 2758, 2716, 2516, 2732 EPROMS switch selected, 26V generator, ZIF socket, CP/M driver program, max. time 100 sec for 16K bit EPROMS mod. available for TMS 2716 EPROMS, optional PROM based driver routines STD S100, plated thru holes.

KIT \$205.00 ASS & TESTED \$255.00


## EXTENDER/TERMINATOR



True active termination, fuse protect supply rails to extension socket, numbered test points, reset line (75) not terminated, solder resist, plated thru holes, standard S100 D.I.L. resistor packs, this board is a must for reliable operation.

KIT \$85.00 ASS & TESTED \$105.00

## WIRE WRAP PROTOTYPING BOARD

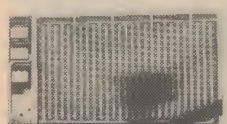

Now with plated thru holes, GND & supply rails on both sides, +5V +12V & -12V regulator provision. Hole array is 1" x .3" to suit all IC package sizes, provision for filter bypass caps, 5V reg is T03.

BOARD ONLY \$38.50

## TVI-912B TERMINAL



80 x 24 intelligent terminal, 2 page screen, printer port, dual intensity upper/lower case, 110-9600 baud, numeric pad, cursor control, XY curs block mode, self test, micro based learn siegler ADM31 look alike, full editing capabilities.

\$1295.00


## LA34 34 DECwriter



30 CPS, 128 char set 110-300 baud 9 x 7 dot matrix, adjustable line and character spacing, opt. numeric keypad, light weight (13Ks), STD RS 232 serial com., opt. tractor feed, & paper roll holder, comes with friction feed as standard.

STANDARD VERSION \$1595.00


## Z80 STARTER KIT

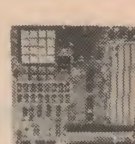

Onboard keyboard & HEX display, Kansas City cassette, PROM programmer S100 interface, 2K RAM, 4K PROM, 2K optional, 2K monitor, CTC timer, interrupts, 2x8 bit ports, wire wrap area, 120 page manual, single 5V supply, single step, breakpoints.

KIT \$350.00 ASS & TESTED \$420.00

## S-100 & 6800 CHASSIS

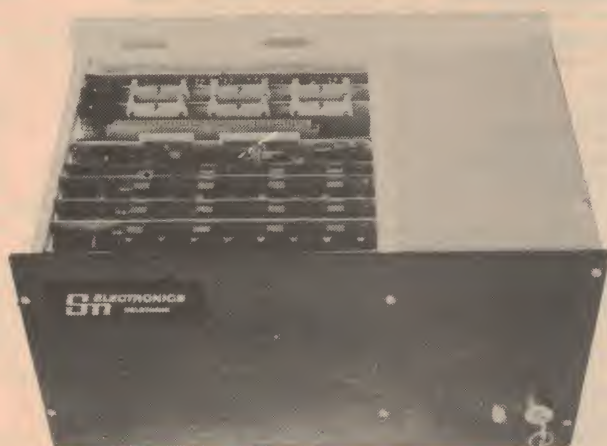

11 slot backplane, fully card guided, 15 amp power supply, fan, key switch, bench mount, rack mount, anodised aluminium, 5 edge connectors standard. S-100 Bench Kit \$345, S-100 Rack Kit \$306, 6800 Bench Kit \$370.00, 6800 Rack Kit \$330. Assembled prices add \$100.

## PMS100

Introducing the PMS100 by SME Systems, an all new package microcomputer based on a Z80 CPU. This system will suit all users ranging from computer technicians, programmers and small to medium company accounting requirements.



Technical specifications are as follows:

4 Mhz Z80 CPU, 64K Dynamic memory with bank select to allow up to 8 pages of 64K each, and up to 256K of RAM on a single board, RS232 serial port and 8 bit parallel ports. Up to 16K EPROM which can be switched out after power up to allow a full 64K of user RAM per bank. Dual QUME 8" d/sided drives running at single or double density. Density selection is automatically chosen by the use of double or single density formatted disks. External Mini drives can also be interfaced to the controller. The DOS supplied is compatible with standard CP/M and CDOS to allow a wide selection of software to be used, such as MBASIC, CBASIC, COBOL, ALGOL, PASCAL, FORTRAN, ASSEMBLY LANGUAGE, WORD PROCESSING, MULTITASKER, AND ACCOUNTING PACKAGES. All of which can be supplied from SME Systems.

The PMS100 is AUSTRALIAN designed and built and can be supplied as a basic system or as a complete turnkey system including terminal, printer and software.

**SME ELECTRONICS**  
MELBOURNE  
Ph (03) 842-3666  
Trading hours: 10am-6pm Mon to Fri.  
1096 Doncaster Rd, Doncaster East, Vic 3109.  
PO Box 19, Doncaster East, 3109, Telex AA37213.  
DEALER Canberra — 81-5011, Sydney — 661-9237.

Send 66c in stamps for HARDWARE CATALOGUE.  
CP — M user group software 43 volumes.  
CATALOGUE \$4.00

ALL PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST).  
DEALER ENQUIRIES WELCOME.  
Prices and specs. subject to change without notice.  
All prices tax free, for retail prices add 15 per cent.

**bankcard**  
welcome here

**SME**  
SYSTEMS

Give name, number, expiry date and signature for mail order sales.



# HI-ENERGY CASSETTES

## SPECIAL READER OFFER

### AT LOW, LOW PRICES

Tape	1-19	20-99	100 +
C46	\$1.29	\$0.99	\$0.86
C60 + 6	\$1.79	\$1.59	\$1.39
C90 + 6	\$2.09	\$1.99	\$1.79



#### CLOSING DATE:

13 November

— order now in time  
for Christmas !

#### BONUS:

For orders over \$60.00 we will  
include a can of Tape Head  
Clean Spray valued at \$2.25.

### Dindy Hi-Energy Cassettes

- low noise/high output
- Cassette case screwed together, not glued
- Five year unconditional replacement guarantee
- Bonus taping time on C60 and C90

NOTE: This offer is made by Dindy Marketing (Aust.) Pty Ltd and this publication is acting as a clearing house only. Cheques or money orders should be made payable to 'Dindy Cassette Offer', and sent to ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011. We will then process your order and pass it on to Dindy, who will send you the goods. Please allow up to four weeks for delivery.

#### Dindy Cassette Offer

Please supply: Quantity ..... C46 ..... \$ .....  
 ..... C60 ..... \$ .....  
 ..... C90 ..... \$ .....  
 Packing & delivery — under 99: \$2.50  
 over 100: \$4.00 \$ .....

(Tapes may be mixed for discount)

TOTAL: .....

NAME .....

ADDRESS .....

Postcode .....

Cheque or money order .....

Or use your Bankcard 

4	9	6																	
---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

 Expiry Date ... / ... / ...

Signature .....

#### CHARACTERISTICS

DINDY 'HI-ENERGY' — NORMAL Eq: 3180us + 120us Bias: Normal  
 Physical Properties Unit C60 C90 C120

Base Material			Tensitized Polyester	
Width	mm	3.81	3.81	3.81
Length	m	90	135	180
Base Thickness	um	11.5	7.5	6.0
Coating Thickness	um	3.8	3.8	3.0
Total Thickness	um	15.3	11.3	9.0
Colour		Brown	Brown	Brown

#### Magnetic Properties

Coercivity (Hc)	Oe	320	320	320
Retentivity (Br)	Gauss	1100	1100	1100
Max. Inductance Bm	Gauss	1350	1350	1350
Squareness	Ratio	0.82	0.82	0.82

#### Electro-

#### magnetic properties

Bias Setting at 6.3 kHz	dB+	+4.0	+4.0	+4.0
Relative Sensitivity (333 Hz)	dB	+3.5	+3.5	+3.5
Variation of Sensitivity	dB	+/-1.0	+/-1.0	+/-1.0
MOL 333 Hz/3% THD	dB	+4.0	+4.0	+4.0
10 kHz/3% THD	dB	-9.0	-9.0	-9.0
Signal/noise ratio (NAB)	dB	58	58	58
Signal/noise ratio (MOL/NAB)	db	64.5	64.5	64.5
Print through	dB	-59	-59	-59
Third Harmonic Distortion				
250 nwb/m	%	0.8	0.8	0.8
160 nwb/m	%	0.2	0.2	0.2




# eSOUND

**FEATURE: ● CONSUMER ELECTRONICS SHOWS  
— A TALE**

**REVIEWS: ● NAKAMICHI 482 CASSETTE DECK  
● ACCUPHASE C7 MC HEADAMP**

**122  
110  
135**
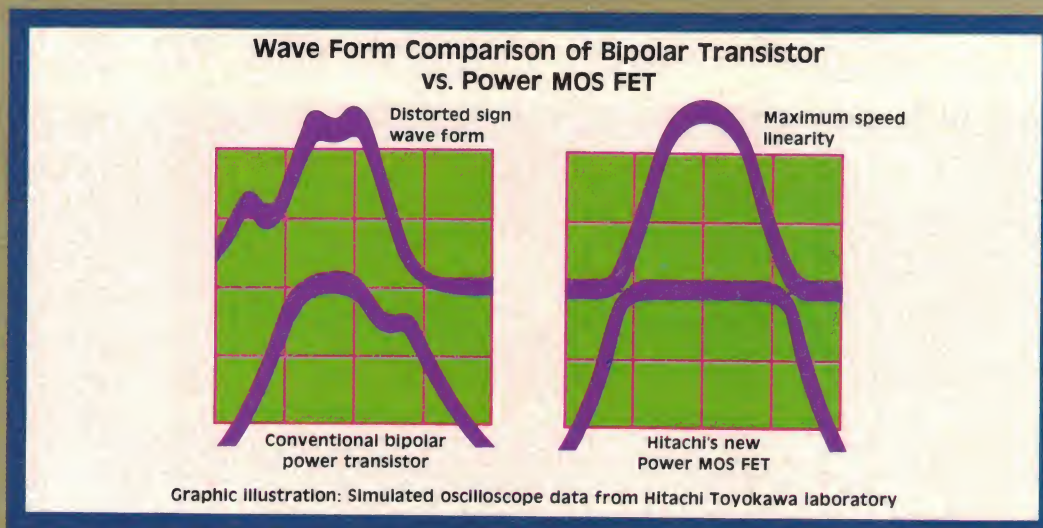
# The world's fastest integrated amplifier



## Hitachi Power MOS FET

The HA-7700 Stereo Integrated Amplifier brings you stunning sound reproduction. The Hitachi Power MOS FET offers ultra-high switching speed for dramatically reduced distortion and outstanding transient response. It features the same incredible technology that went into our renowned HMA-7500 Stereo Power Amplifier and HA-8700 Stereo Integrated Amplifier.

Power output is 70 watts per channel with no more than 0.008% total harmonic distortion from 20 to 20,000 Hz. And all stages are direct coupled, so you get the purest waveform reproduction fidelity from input to output.

The RIAA phono equalizer is a top-precision design employing only the highest-quality components for low-distortion and true-to-life disc playback. There's a full complement of control and convenience features for maximum system flexibility.

The HA-7700. True purity in waveform reproduction is here.



HA-7700



Hitachi Sales Australia Pty. Ltd., 153 Keys Road, Moorabbin, Victoria 3189 Tel: 95 8722

# Owners of Nikon, Pentax, Olympus, Minolta, Canon, Leica... improve your images.



Kodak Elite 35 Prints set a new standard of excellence in color reproduction for 35mm camera owners.

1. Kodak Elite 35 Prints measure 15cm x 10cm (6" x 4") have a finely-textured matt finish, and square corners.
2. Kodak Elite 35 Prints are processed from negatives individually assessed by computer.
3. Kodak Elite 35 Prints are subject to extremely strict quality controls.

4. Kodak Elite 35 Prints are returned to you with the negatives in special plastic sleeves for complete protection.

Kodak Elite 35 Prints take slightly longer to process and cost a little extra, but that's what you'd expect for wanting the best.


Kodak Elite 35 Prints are available from all C41 compatible 35mm color negative film.

KODAK (Australasia) PTY. LTD.



KO/6163/Y/KSB

## TEAC offers dbx !

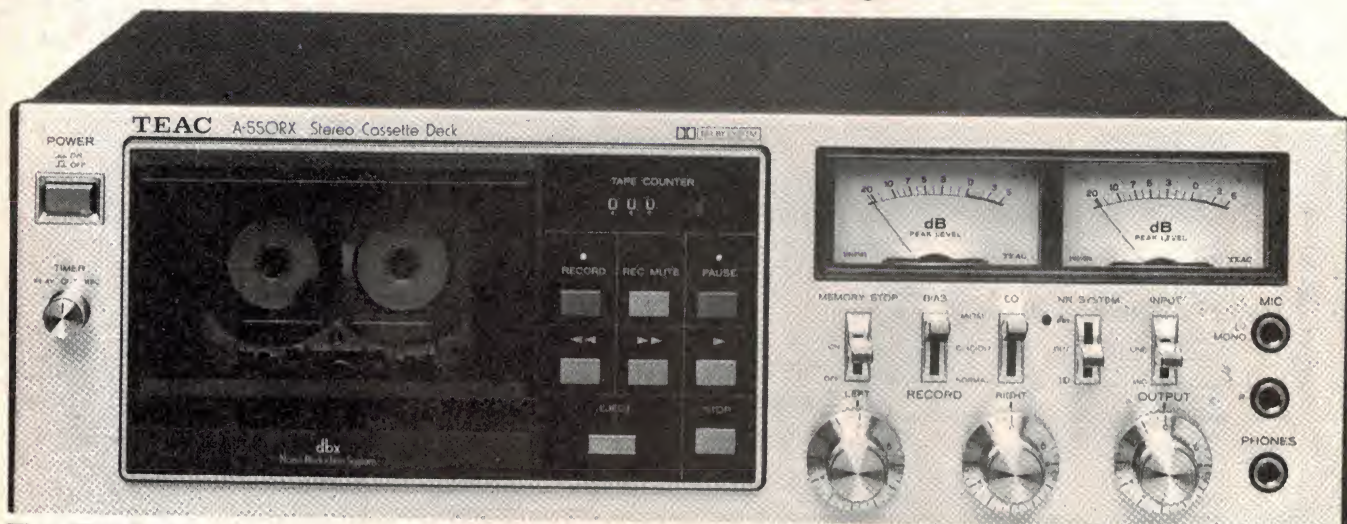

The TEAC corporation are now offering dbx noise reduction units to support their range of cassette and open reel tape recorders.

**The dbx system of logarithmic compression before recording and expansion before playback was explained in last month's ETI review of the dbx 3BX dynamic range enhancer.**

It can give an improvement in dynamic range of more than 30 dB, compared to the 10 dB or so that is possible with Dolby systems.

TEAC's A-550RX cassette deck has built-in dbx circuitry and is also provided with Dolby

circuits for playing back Dolbyised recordings or recording tapes that will be played back on other machines (e.g. in the car) which do not have dbx. Like all new high quality cassette decks these days it's compatible with metal tape.

Other TEAC decks can also be upgraded to dbx standards of noise suppression. The RX-8 is a dbx unit designed to com-

plement the C Series cassette decks, the DX-2A model is for use with the X-10 and X-10R open reel decks and the RX-9 is made to match the A-3440 multitrack open reel recorder.

TEAC have an interesting array of new equipment for 1980/81, which they released at a function in Melbourne during August. We've more 'goodies' to tell you about in later issues.

## Pioneer play it safe

**DC or not DC? That is the question currently plaguing amplifier designers. Pioneer's answer is — neither!**

Their SA-710 integrated amplifier and SX-D5000 receiver released at July's C.E. Show, both feature what they call 'DC with a difference'.

The difference is that they have retained the input capacitors.

This way they reckon to avoid the risks of overload inherent in amplifiers that are entirely direct coupled, while still eliminating the disturbing effects of capacitor-induced phase shifts in the negative feedback loops.

The power amp section of the SX-5000 receiver uses an unusual (but not unique) principle, which seems set to become very fashionable. It's a form of class

AB operation. Neither of the paired output transistors on each channel is ever cut off, but unlike class A, the bias current is not held constant. Instead, a 'Vari-bias' circuit monitors the incoming signal level and adjusts the bias current accordingly, feeding less bias current to the transistors during

low signal periods.

This cuts down thermal losses and hence improves efficiency. Pioneer claim the circuitry involved is so simple that it does not limit the transient response at all.

The same company also released three new capacitor-coupled amplifiers at the

C.E. Show, SA-610, SA-510 and SA-410 with outputs of 45 W, 30 W and 20 W per channel respectively. The most interesting feature of these three is that their tone control networks are incorporated in the negative feedback loops of the power amplifier section, not the preamp.





## Sound safe.

Agfa SUPERFERRO—the sound safe—will record and store your music safe in sound, ready for when you want it. And we mean all the music. The outstanding performance of Agfa SUPERFERRO is achieved through the use of a particular form of ferric oxide particle that is uniform in shape and size. The second factor is an Agfa technique that enables more particles to be deposited per sq. mm of tape, with each particle separated and in line to eliminate cross-over interference.

The advanced technology of the SUPERFERRO tape results in five big improvements:

1. Reduced background noise.
2. Better maximum output level.
3. Improved dynamic range.
4. Improved high frequency output level.

5. Reduced harmonic distortion. In addition, Agfa SUPERFERRO cassettes feature a special mechanism for improved running properties.

Agfa SUPERFERRO—the sound safe you can bank on for outstanding performance.



\*Registered trademark  
of AGFA-GEVAERT  
Antwerp/Leverkusen.

## All-in-one audio test kit

**Neal-Ferrograph of the UK have produced a single instrument which performs a variety of useful audio measurements.**

Their RTS 2 combines an audio oscillator, a millivoltmeter, a distortion-measuring filter and a wow and flutter meter in a small unit that weighs less than six kilos. Pushbutton switches are used to select the different functions.

Only one input and output lead is connected to the equipment under test, which is one reason why the instrument is claimed to reduce testing time by up to 30%. Another is that the readout is expressed directly in dB or percentage terms, which saves the time otherwise spent on arithmetic (and avoids errors too).

The oscillator covers the frequency range from 15 Hz to 150 kHz and has a maximum output of 3 V.

THD from 0.1% to 100% can be measured by the distortion section of the instrument, which has an output for connecting an oscilloscope or additional filters.

The millivoltmeter can be switched to read voltages either at the output of the oscillator or at the high impedance input. It can be used to read drift, distortion, wow and flutter or voltages from 1 mV to 100 V in eleven ranges.

There are three ranges of measurement for wow and flut-

ter, with full scale deflections of 0.1%, 0.3% and 1% respectively. Variations in mean speed of up to 2% either way are within the scope of the instrument.

The RTS 2 also includes an external 40 dB attenuator and a test tape for checking azimuth

alignment and replay characteristics of tape recorders.

A separate Auxiliary Test Unit is available, which enables the RTS 2's oscillator and meter sections to be used either simultaneously or separately for a variety of weighting and mon-

itoring test on equipment of professional standard.

Further information can be obtained by writing to Neal-Ferrograph, North East Audio Ltd, Simonside Works, South Shields, Tyne and Wear NE34 9NX, England.



## Bouquet for Philips

**Philips' unique feedback-controlled belt-drive turntables have won them a coveted Hi-Fi Grand Prix citation for turntable technology from the American magazine 'Audio Video International'.**

Such citations are awarded as a result of a ballot of over 1500 hi-fi retailers in all parts of the United States.

The 'Direct Control' turntable design aims to provide the same accuracy as direct-drive turntables without the expensive constructional techniques they involve.

The platter is belt driven by a dc motor and has a tachometer built under it. The output of the

tachometer is converted into a dc voltage proportional to the turntable speed and this voltage is continuously compared to a stable dc reference voltage. The difference voltage is fed back to regulate the motor speed.

According to Philips, turntables using this system can achieve wow and flutter figures of less than 0.03% (WRMS) and rumble lower than -70 dB.




**Sansui**

Only hi-fi, everything hi-fi.



# Non-compromise computerized

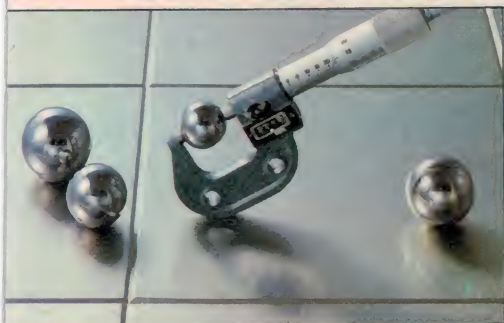

Fully computerized operations have many powerful advantages. Flawless decisions, meticulous monitoring, foolproof functions, record protection and the desirable convenience of random band selection are only a few.

But some audiophiles have had reservations about such systems and their reasons are not mysterious. Until now, you had to accept the one particular cartridge that came with the system.

From now, with Sansui's new XR-Q11, you can freely select whichever cartridge you like. This important

freedom is possible because Sansui engineers have perfected a dual sensor system which is independent of the cartridge.

Until now, the specs and performance of band selector turntables were usually not the very best. The XR-Q11 now changes the sound picture. Speed is better than 99.99% perfect! Wow and flutter is under 0.015%. And performance is peerless thanks to the direct-drive quartz-servo motor. Speed monitoring is exceptionally fast and accurate with Sansui's dual-heads that read the 960 magnetic "marks" coating the platter's inside rim.

Carefully examine the unique, straight D-O-B tonearm. Using basic principles of physics in a new configuration, this tonearm radically reduces all kinds of spurious vibrations, including feedback from the stylus. Combined with the BMC super-dense cabinet and PAT. PEND. floating sub-base, mechanical interferences of the most overt and subtle types have been virtually

eliminated for superb reproduction of even the most difficult dynamic musical qualities.

The facts are clear. The XR-Q11 is one of the world's finest turntables by any standard. And it is the only turntable in its class with the sophisticated convenience of computerized operation including Sansui's Computerized Track Sequence Selection (CTSS).

The new XR-Q11 CTSS turntable: when you want to approach the ultimate.

## SANSUI XR-Q11

**SANSUI ELECTRIC CO., LTD.**

14-1 Izumi 2-chome, Suginami-ku, Tokyo 168, Japan

**VANFI (AUST.) PTY. LTD.**

297, City Road, South Melbourne, Victoria 3205,

Australia Tel: 690-6200

283 Alfred Street, North Sydney, N.S.W. 2060,

Australia Tel: 929-0293

It's a better system, at a better price, and it's Sony. In Sony's new TC-K81 three head cassette tape deck, each head

The new TC-K81 also has microcomputer control and feature-touch operation, and LED Peak Programme Meter,

# Sony's 3 head system. It's 3 ways better.

has its own individual casing and suspension system.

You get precise azimuth alignment,\* equal record and playback head-to-tape pressure, and reduced magnetic leakage flux.

It's a unique three-head system, with two-motor, closed-loop dual capstan drive with metal tape compatibility.

bias and record level calibration system, and Dolby\*\* NR.

It's an exceptional new system, at an excellent price. And it's Sony.

So in three-head technology, we're three-ways better.

## SONY®

\*Factory aligned.

\*\*Dolby is a registered trademark of Dolby Laboratories.



## High power amp from Jaycar

Jaycar's model 3002 power amp gives 300 watts per channel into four ohms and is ruggedly designed for sound reinforcement applications.




It's a modified version of one of our own designs, the ETI-466 amp featured in last February's issue. One of these amps is used for each channel of the 3002, with a separate power supply for each to allow maximum power output with both channels driven and to minimise crosstalk.

Multiple protection circuits enable the 3002 to stand up to the abuses which any amp used "on the road" has to face sooner or later. Loadline protection allows the full power to be delivered into either four or eight ohm resistive and reactive loads and the amplifier will withstand

almost any load condition, including short circuits at reduced power.

A relay network protects loudspeakers in case of faults in the amp, which are indicated by a LED on the front panel and there's an inbuilt turn-on delay to protect speakers against switching transients.

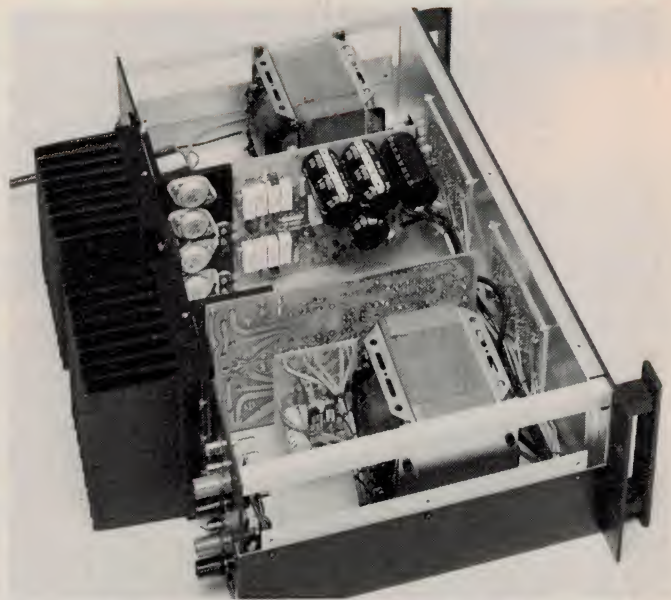The twin, peak reading level meters are also an ETI design — they're the ETI 438 meters which first appeared in the December 1975 issue and are reprinted in our 'Test Gear' and '30 Audio Projects' books. These meters have a fast attack time of less than one mil-



lisecond to detect very short transients and a relatively slow release time of half a second for good indication of average levels.

The whole amplifier fits a standard 19 inch rack (430 mm) and is less than 133 mm high. Input connections are by RCA socket (two per channel paralleled to avoid looping to other amps) and speaker out-

puts are via heavy duty binding posts.

Visitors to the ETI stand at the recent Consumer Electronics Show in Sydney will have heard the Jaycar 3002 doing a splendid job of driving our demonstration Series 4000 speakers.

More information from Jaycar Pty Ltd at P.O. Box K39, Haymarket, NSW 2000. Phone (02) 264-6688.

## You can't believe your ears !

Engineers at Rank Wharfedale's factory in the UK have conducted a series of tests showing that hi-fi systems can often outperform listeners' ears.

They deliberately 'clipped' the signals fed to loudspeakers and found that the extent to which listeners noticed the distortion depended on the kind of music that was playing. Disco music could be clipped as much as 5% of the time before people noticed anything was wrong. (At least one member of ETI's staff thinks disco would sound much better clipped down to zero 100% of the time, but that's another story!)

Classical music, especially piano, is much more sensitive. Listeners began to notice something was wrong even when clipping occurred less than one per cent of the time.

When the music was played loud, the results were even less encouraging for audiophiles. At high volume as much as 15%

clipping on pop music and 5% on classical pieces passes unnoticed. This is because the human ear introduces its own distortion at these levels, which masks the clipping.

Similar results were obtained when Wharfedale's testers experimented with the subjective effects of speaker coloration. They mixed a controlled amount of synthetic coloration with a clean sound and found that the degree to which this was noticed also depended on the type of music.

With some pieces of music coloration was scarcely noticeable; on others it was glaringly obvious. And some people can tell the difference between a coloured and a flat response, but actually prefer the coloration!

## Single-chip FM receiver


An experimental 3.5 mm square chip contains virtually all the components of a complete frequency modulated broadcast receiver.

Engineers at Philips Laboratories in Holland have achieved this remarkable miniaturisation by reducing the intermediate frequency from 10.7 MHz down to only 70 kHz. This means that the critically tuned L-C or ceramic filters usually used can be replaced by simple low-Q R-C networks which are much easier to incorporate into integrated circuits.

FM broadcast stations use a maximum of 75 kHz deviation which would lead to audio distortion in a normal receiver with a 70 kHz intermediate frequency. To avoid this, the Philips chip has frequency feedback circuitry which 'compresses' the modulation to  $\pm 15$  kHz, resulting in virtually no harmonic distortion.

The chip also includes a new kind of muting system, which depends on the correlation between the IF signal and an inverted, delayed version of itself. These two signals should be identical if the receiver is properly tuned, in which case the correlation is high and the muting circuitry switches the demodulated audio signal to the audio output. When the receiver is detuned, the correlation between the two signals is small and the audio signal is suppressed.

The receiver uses standard bipolar technology and comprises about 280 circuit elements. Supply voltage range is 3 to 18 volts, with a current consumption of 9 milliamps at 6 volts.

A photograph of a woman from the waist down, wearing a white short-sleeved shirt tied in a knot at the waist and blue denim shorts. A pack of Drum cigarettes is tucked into her waistband. She is holding a lit cigarette in her right hand. The background is a soft-focus outdoor scene.

# WHO SAID 'MEN SMOKE DRUM'?

The natural  
satisfaction of  
full flavoured,  
imported Drum.  
It's the most  
enjoyed ready-  
rubbed cigarette  
tobacco in  
Australia.





## Remember how great she looked last summer.

National Colour Video Camera and Portable VHS lets you keep those moments and relive them over and over.

It's so simple. Point the camera, shoot... instant result. No processing is required with automatic viewing on TV, through your National Portable VHS recorder. Light to carry and will operate under low light conditions.

*Other features include:*

- Power zoom control
- Brilliant colour reproduction
- Pause control
- Electronic viewfinder
- Built-in microphone
- Low power consumption.

**Because time doesn't stand still...**



**VHS**



**National**  
Instant Home Video

Net 100



## Nakamichi 482 discrete head cassette recorder

"Impeccable . . . the best performance we have seen from any cassette deck to date."

WITH SO MUCH talk about digital techniques, one could be forgiven for thinking that conventional reel to reel and cassette tape recorders were about to be eclipsed. Actually, nothing could be further from the truth. Both of these tape recording systems are well established in their respective fields and will continue to be so for some time.

The cassette recorder, which now dominates the consumer market, has undergone remarkable technical development, particularly in the last five years, which has resulted in truly outstanding improvements in performance. They are now able to satisfy discriminating buyers who are looking for frequency linearity, wide dynamic range, acceptable wow and flutter and low distortion.

Five years ago few machines could do better than a 13 kHz bandwidth, very few had a significant output below 50 Hz and most produced distortion

greater than 1% at -6 VU. The almost universal adoption of Dolby systems had achieved reasonable signal-to-noise ratios for the majority of machines but wow and flutter figures were generally so inferior to those of reel to reel recorders that very few serious amateurs really considered using cassette recorders at home.

The original Nakamichi 1000 and 700 series of recorders changed the opinions of most amateurs (and quite a few professionals as well), but they were large, expensive and complicated. The Nakamichi 482 is much smaller, designed to stack on top of other pieces of equipment and costs a fraction of the price of its illustrious forebears. In fact, after allowing for inflation, we believe the real cost of today's 482 is about one-fifth the cost of the 1000 when it was first released, and the 482 is a superior machine.


Nakamichi's products are now re-

garded as being in the forefront of cassette recorder development. Their reputation has generally been enhanced by each new model they have released and the 482, which is the latest in the line, is no exception. It attains a level of performance which even Nakamichi will find it hard to improve on. At \$599 the 482 costs about \$200 more than its predecessor the 480, mainly because it incorporates three crystal permalloy heads (which are basically the same as those on the 582 model).

### The unit close up

Externally the 482 looks very similar to the 480 series, with the same black brushed aluminium escutcheon and large pneumatically damped cassette well. (A satin-finish model is also available). On the right are a pair of peak reading VU meters covering the range from -40 dB to +7 dB, and beneath them are two slide recording level

Louis A. Challis  
& Associates Pty Ltd.

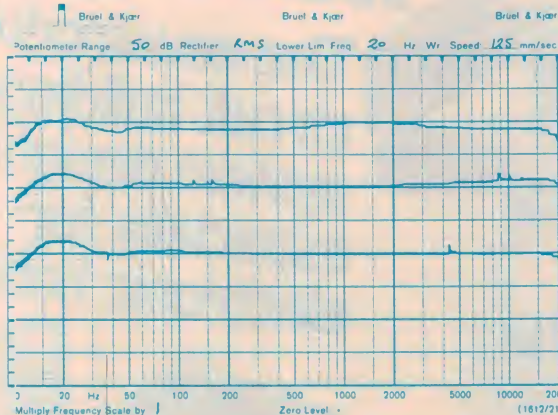

attenuator controls. While these two controls look good, we were critical of their ergonomic design in the 480 series and are still critical of them in the 482.

There are three interlocked push-buttons for selecting EX, SX, and ZX tapes, which is shorthand for low noise gammaferric oxide tapes (EX), chromium dioxide or chromium equivalent tapes (SX) and metal alloy tape (ZX). An equalisation switch selects equalisation time constants of 70 or 120 microseconds. At the rear are two pairs of coaxial sockets for input and output and a 5 pin DIN type socket for connecting a remote control unit.

The most prominent feature inside the machine is a large and beautifully fabricated printed circuit board installed in an inverted position. All the components are on the underside of the board so that when the cover is removed one finds oneself face to face with the circuit designations and probe points, which is just the kind of layout that service engineers need for troubleshooting.

We removed the bottom to look at the components and found that they told us only a little more about the unit than the printed circuit board did with components on the top. Dolby circuitry is in the form of parallel dual in line ICs for the encoding and decoding circuits. A double Dolby facility allows Dolbyized material to be directly monitored through the decoding Dolby circuitry while it is being recorded. Nakamichi have gone to a lot of trouble to select their chips so that the encoding and decoding characteristics are very closely matched, avoiding thereby some problems that other manufacturers have experienced because of imprecise matching of randomly selected chips.

The integrated circuits are mounted in sockets to simplify installation and replacement. Like other Japanese manufacturers, Nakamichi try hard to avoid unnecessary wiring operations, so the majority of connections on this board are direct to ancillary circuitry. The board incorporates one plug-in socket and most other terminations are

made by wire wrapped connections for harnesses leading to the motor drive, recording heads and front panel switches.


The cassette drive mechanism appears to be the same as that previously seen in the 480 version and features solid plastic mouldings combined with aluminium plates to achieve what appears to be an extremely rugged and stable drive mechanism, which is obviously stronger than the previous generation of drives.

## On test


The first area where this deck outperforms its predecessors is the replay frequency response. Here it gives the best performance we have seen from any cassette deck to date. On the Maxell UDXL-1 the response is better than 10 Hz to 20 kHz, on TDK SA it is every bit as good and even flatter and on TDK MA-R60 it is 10 Hz to 14.5 kHz and only 6 dB down at 20 kHz. The flatness of these responses equals that of many high quality reel to reel recorders.

— turn to p.116 ►

Louis A. Challis  
& Associates Pty Ltd.


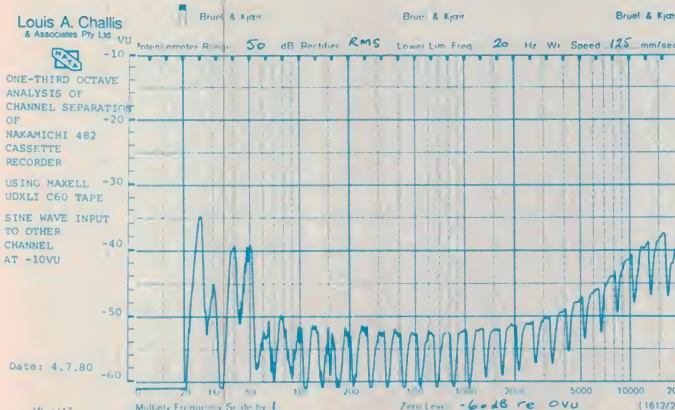


Louis A. Challis  
& Associates Pty Ltd.

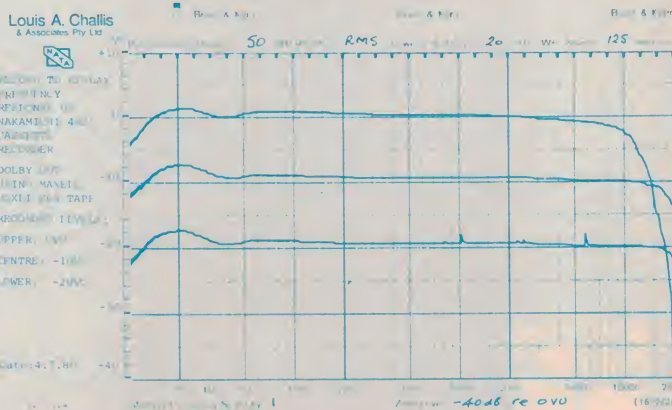
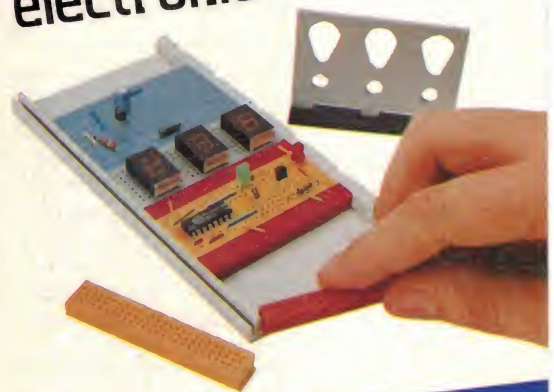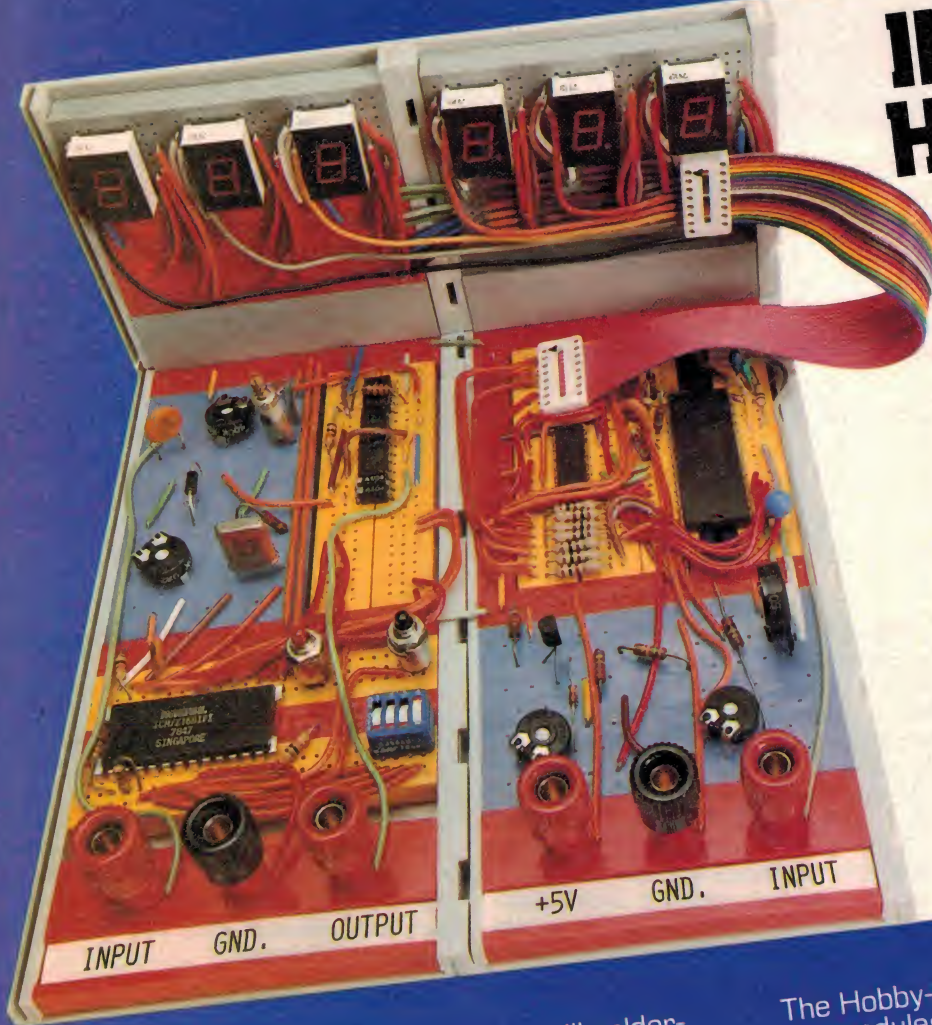
# INTRODUCING HOBBY-BLOX™

The new modular  
circuit building  
system designed  
especially for  
electronic hobbyists.



Until now, you had to buy "professional" solderless breadboards for your projects and pay "professional" prices. Now there's Hobby-Blox, a totally new circuit-building system that's not only economically priced but offers many more advantages to the hobbyist.

At the core of the system are two expandable starter packs, one for discrete component projects, the other for integrated circuit projects. Each comes with a number of Hobby-Blox modules that fit into a tray and an illustrated project booklet. In addition, the system includes 14 separate component packs you can purchase individually — terminal, distribution and bus strips, speaker panels, binding posts, etc.

The Hobby-Blox system is easy to use because the modules are color-keyed and letter/number indexed. It's time-saving, because they're solderless. It's compatible with DIP's of all sizes and a wide variety of discrete components. And you save money, because the parts can be reused again and again.

How far can you go with the Hobby-Blox system? Take a look at the example above. Then you'll know why we say, "your only limit is your own imagination!"

Patents Pending  
© A P PRODUCTS INCORPORATED 1980




A P PRODUCTS INCORPORATED  
1359 West Jackson Street  
Painesville, Ohio 44077  
(216) 354-2101

**For a free catalog,  
contact your local  
HOBBY-BLOX™ dealer:**


N.E.T. PTY. LTD.  
92 Woodfield Boulevard  
Caringbah, N.S.W. 2229  
TEL: 525-6090

RIFA PTY. LTD.  
P.O. Box 485  
Cross House, 2 Cross Street  
Hurstville, N.S.W. 2220  
TEL: 570-8122

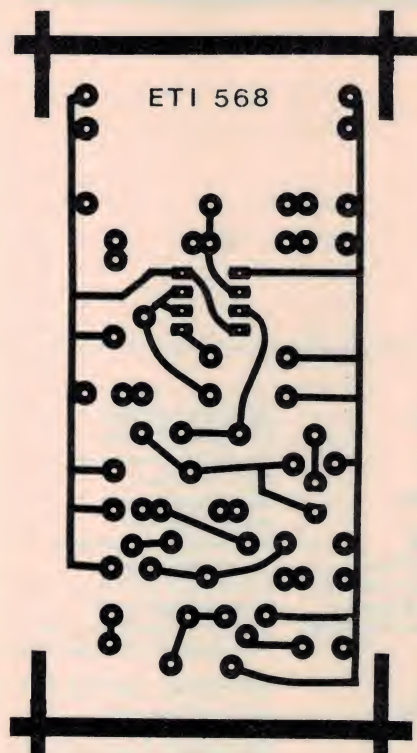RIFA PTY. LTD.  
P.O. Box 95  
202 Bell Street  
Preston, Victoria 3072  
TEL: (03) 480-1211



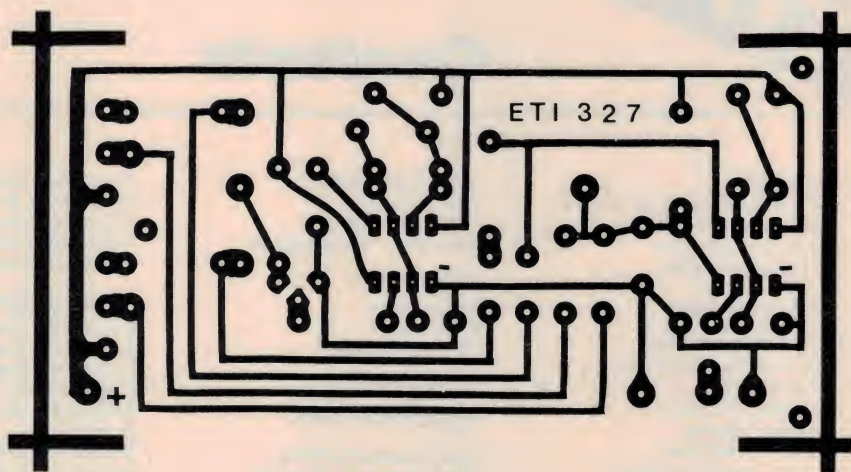Instructions on how to make your own pc boards using the Scotchcal method and exposing through this page may be found on page 113 of the March '80 issue.



Here is the pc board for last month's Quality AM Tuner, as promised.



# Number Two ETI CIRCUITS

## Contents

### ALARMS

Comprehensive Burglar Alarm  
SCR Alarms  
Car Radio Protector  
Fire Alarm, Simple

### AMPLIFIERS & PREAMPLIFIERS

Non-Inverting Amplifier  
AC Amplifier  
AC Amplifier, Simple  
Voltage Follower  
Flexible Response  
Hi Z, Hi Gain Amplifier  
Voltage Controlled Amplifier  
Recording Pickup  
Direct Coupled Power  
CMOS Power Booster  
Photocell Amplifiers  
12 Volt PA System  
Class A Amplifier  
Clipper Preamp  
Headphone Amplifier  
Op-Amp Circuits, Standard

### SIGNAL PROCESSORS

Track and Hold Circuit  
Track and Hold, Simple  
ADSR Envelope Shaper  
Frequency Doubler  
Frequency to Voltage Converter  
Frequency Meter, Analogue  
Digital to Analogue Converter  
Schmitt Trigger, Without Hysteresis  
Schmitt Trigger, Simple  
Pulse Lengthener, Optical

### SIGNAL GENERATORS

Square Wave, Low Frequency  
Square Wave Generator  
Monostable Multivibrator  
Triangular Waveform Generator  
Marker Generator  
Voltage and Frequency Calibrator  
VCO, Simple  
Voltage Controlled Oscillator  
Sine Wave Oscillator  
Tone Burst Generator  
Thermistor Oscillator  
Theremin  
Exponential Waveform Generator

### FILTERS

Loudness Control  
Rumble Filter, Switchable  
VCF, Cheap  
CMOS Filters  
Voltage Controlled Filter  
Tone Control, Active  
Tone Control Circuit

### SPECIAL EFFECTS

Organ, Simple  
Warbling Alarm

Guitar Synthesiser  
Guitar Fuzz  
Drum Simulating  
Fishcaller, Transistorised

### MIXERS

Audio Mixer  
Basic Mixer  
Switched Mixer

### DETECTORS & COMPARATORS

Low Battery Warning  
Battery Voltage Monitor  
Recording Level Meter  
Comparator Voltmeter  
Voltage Comparator  
True RMS Detector  
Positive Peak Detector  
True RMS Converter  
Temperature Sensor, Differential  
Schmitt, 555

### INDICATORS

Temperature Sensor, Remote  
Warmth Indicator  
Warning Flasher  
Transistorised Flasher  
Blown Fuse Indicator  
Neon Indicators  
Neon Tube Flasher

### SWITCHING

Stereo Input Selector  
Stereo Switch, Simple  
Logic Touch Switch  
Stereo Only  
Input Selector, Sequencing  
Audio Switch  
Touch Switch, Thermo  
LED Changeover Circuit  
OR Gate, SCR  
AND Gate, SCR  
4016 DPDT Switch  
Beam Splitter, Oscilloscope  
Twilight Switch, Automatic

### SEQUENCE & TIMING

Time Delay Switch  
Snooze Delay Unit  
Timer, 1-12 Minutes  
Code Switch  
Timing Circuit  
Combination Lock  
Flexible Timer

### POWER CONTROL

Impulse Power  
Half-Wave Control  
Improved Half-Wave  
Zero Switching  
Triac Lamp Flasher

Triac Slave Controller  
Light Show, Simple  
DC Lamp intensity  
Train Speed Control  
Temperature Controller

### POWER SUPPLIES

Current Source, Drift Free  
Constant Current, High Voltage  
Output Voltage, Adjustment  
High Voltage, Variable Regulator  
Switched Output  
Dual PSU  
Mobile Power Supply  
Converting Single to Dual  
Op-Amp Supply  
Low Ripple PSU  
Zener Assistance  
Crowbar, Simple  
Low Voltage, Short Protection  
Low Ripple at Low Current  
30 Volt Regulators  
Standard Configurations

### TEST

FET Testing, Static  
Diode Tester  
Ammeter, Wide Range  
Millivoltmeter, Audio  
DC Probe, 100 000 Megohm  
Measuring RMS with a DVM  
Logic Indicator, Audible  
Transformer-Inductor Tester  
Pulse Catcher Probe  
JFET Test, Quick

### DIGITAL

Data Selector, Two Way  
7 Segment Improvement  
3 Chip Die  
Hex to 7 Segment  
Binary Calculator  
TTL Keyer  
ASCII Keyboard  
Counter-Display Module  
Clock Generator, Multiphase  
Windicator  
Self-Clear  
LED Counter

### AUTOMOBILE

Fuel Gauge, Digital  
Immobilisation, Automobile

### MISCELLANEA

Emergency Lights  
Digital Thermometer  
SCR One Shot  
SCR Multivibrator  
Meter Amplifier  
Night Light, Automatic  
Telephone Circuit  
Headphone Adaptor  
Rising Edge Trigger  
Position Transducer, Digital  
Temperature Stabilized Relay

### CRYSTAL OSCILLATORS

LF-VHF, Various

### SPEAKER CROSSOVERS

Computer Aided Design

### BATTERIES

Characteristics and Composition

### CONVERSION TABLES

Hex-Decimal-Hex  
Decimal-Hex-Octal-Binary

### LOGIC DATA

CMOS-TTL Comparison  
TTL Functions  
CMOS Functions  
Truth Tables, Logic  
Boolean Algebra, Laws  
CMOS Pinouts  
TTL Pinouts  
MPU Glossary

### MISCELLANEOUS DATA

Transistor Characteristics  
FET Characteristics  
Diode Characteristics  
Semiconductor Packages  
Problems?  
Colour Codes  
Component Codes  
Preferred Values

*Please note: the Circuits Books are intended as 'ideas directories' — they are not meant for the beginner.*

**\$2.95\* ON SALE NOW**  
direct from Electronics Today  
International, 15 Boundary Street, Rushcutters Bay,  
NSW 2011 — at \$3.40 incl. postage.  
(\* recommended retail price only).

# DENON AUDIO SYSTEM 70

Some hi-fi systems tend to be over-endowed with cosmetic design features.

In selecting a system, we feel that the most important consideration is its ability to faithfully reproduce an original sound.

We rely on the following components to do just that.

● **PMA-530 Preamplifier:**

combined equalizer/power amplifier using direct DC servo system.

60W — 60W output.

● **TU-530 AM/FM Stereo Tuner;**

linear phase ceramic filters.

Built-in servo lock.

MPX circuits with pilot cancellers.

● **DR-230 Metal Tape Compatible Stereo Cassette Deck;**

double gap ferrite erasing head.

IC full-logic circuit controls.

Capstan servo motor.

● **SC-101 Speakers;**

compact, yet peak input power 80W.

● **DP-30L D/Drive Turntable;**

non contact record end sensor.

Excellent vibration damping

by high density compound cabinet.

Servo controlled arm lifter.

For the location of your nearest DENON dealer please contact:

*Hi-Fi Audio Equipment*

**AMALGAMATED WIRELESS (AUSTRALASIA) LIMITED**

554 Parramatta Road, Ashfield, NSW 2131 Phone 797 5757

Canberra  
80 5200

Adelaide  
272 2366

Melbourne  
560 4533

Perth  
271 0888

Launceston  
44 5155

Townsville  
79 6155

Hobart  
72 4366

Brisbane  
44 1631



## IT'S WHAT IS INSIDE THAT MATTERS



— from page 111.



Louis A Challis and Associates Pty Ltd

## MEASURED PERFORMANCE OF NAKAMICHI 482

SERIAL NO. A114 04415

### RECORD TO REPLAY FREQUENCY RESPONSE AT -20VU:

Tape	Dolby	Lower -3dB Point	Max Point and Frequency	Upper -3dB Point
Maxell UDXLI C60	OUT	10Hz	+ 2dB @ 20Hz	>20kHz
Maxell UDXLI C60	IN	12Hz	+ 0.5dB @ 21Hz	20kHz
Maxell UDXLII C60	OUT	<10Hz	+ 2dB @ 20Hz	>20kHz
Sony Metallic 46	OUT	<10Hz	+ 2dB @ 20Hz	20kHz

SPEED ACCURACY: 0.1%

### WOW AND FLUTTER:

WOW: Average 0.1% P-P  
FLUTTER: Uweighted 0.13% RMS  
Weighted 0.06% RMS

### HARMONIC DISTORTION:

Tape: Maxell UDXLI C60

		100Hz	1kHz	6.3kHz
OVU:	2nd	-	-	-
	3rd	-56.7dB	-42.9dB	-34.1
	4th	-	-	-
	5th	-56.1dB	-56.5dB	-
	THD	0.21%	0.73%	1.97%
-6VU	2nd	-	-	-
	3rd	-53.8dB	-58dB	-43.7dB
	4th	-	-	-
	5th	-	-	-
	THD	0.20%	0.13%	0.65%

### MAXIMUM INPUT LEVEL:

(for 3% third harmonic distortion at 1kHz)

Tape: Maxell UDXLI C60 +6VU

### DYNAMIC RANGE:

Tape: Maxell UDXLI C60

Dolby Out	51dB(1in)	55.5dB(A)
Dolby In	58dB(1in)	64.5dB(A)

### ERASURE RATIO:

(for 1kHz signal recorded at +6VU: 3% third harmonic distortion)

Tape: Maxell UDXLI C60 >83dB

## A TOTAL DEPARTURE




## CHADWICK EXECUTIVE MONITOR ME 12

### SPECIFICATION


ENCLOSURE	: Bass reflex.
FREQUENCY RES	: 25 Hz — 22 kHz.
IMPEDANCE	: 8 ohms.
SENSITIVITY	: 91 dB.
POWER RATING	: 120 Watts RMS.
CROSSOVER	: 480Hz, 3.5kHz, 10kHz.
DIMENSIONS	: 816 x 400 x 430 mm.
WEIGHT	: 35 kg.

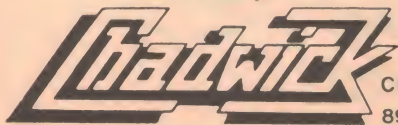WHEN LISTENING BECOMES PARAMOUNT. HEAR THE EXCEPTIONAL CLARITY AND DETAIL OF THE EXECUTIVE MONITOR ME.12.



CHADWICK AUDIO FURNISHINGS PTY. LTD.

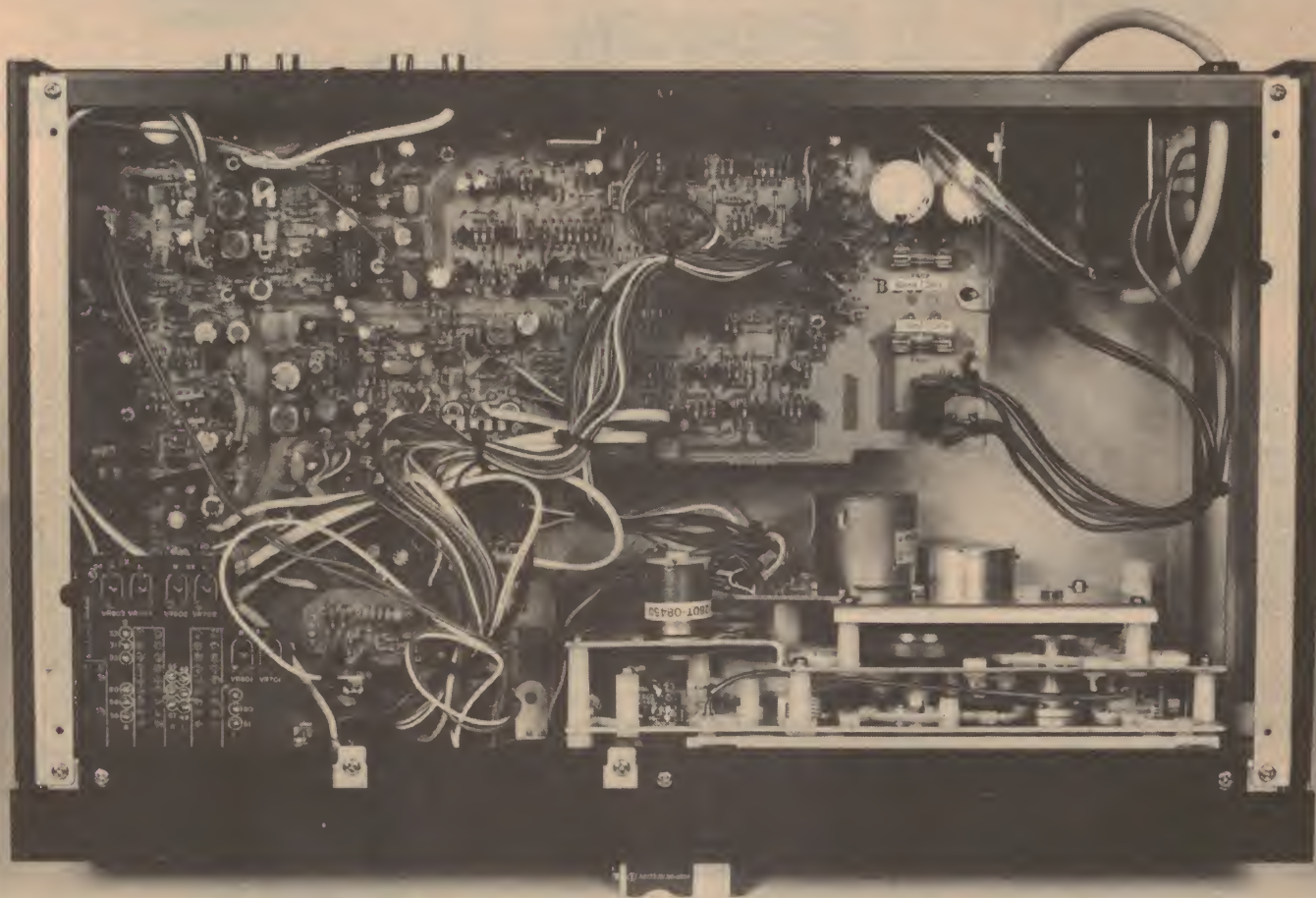89 CARNARVON ST. SILVERWATER, 2141 PH. (02) 647-1103



If the replay response is impressive, the record to replay response is even more so. On Maxell UDXL-1, Maxell UDXL-2 and Sony metallic tape the response extends well beyond the normal specification limits of 10 Hz to 20 kHz, with a flatness of response which is truly exemplary. Anybody who would complain about this frequency response (or ask for more) needs his head examined. Having said this, we still don't doubt that Nakamichi themselves are working right now on refinements to improve this performance!

The noise figures are likewise impeccable. With the Dolby in, the dynamic range is 58 dB unweighted and 64.5 dB A-weighted; without Dolby, the figures are 51 dB unweighted and 55 dB A-weighted. The distortion figures are in many respects even more impressive with total harmonic distortions of 0.21% at 100 Hz, 0.73% at 1 kHz and 2% at 6.3 kHz at 0VU. At -6VU these figures

have dropped to 0.2%, 0.13% and 0.65% respectively.

Wow and flutter performance is particularly good for a cassette recorder, although it is slightly inferior to that of the model 480. The erasure ratio is also slightly down, being 83 dB, compared to the 94 dB achieved by the 480. The channel separation is also not quite as good, but is nonetheless fully acceptable or consumer use.

Our subjective evaluation of this machine was also particularly pleasing. We used a number of prerecorded cassettes, including metal alloy tapes brought back from Japan, as well as other demonstration tapes. While they were all good, none of them developed all the performance that this machine can provide. The record to replay performance was outstanding and the very low distortion, coupled with the low wow and flutter made it particularly difficult to detect the difference between source and tape in an A-B test.

## Conclusion

The Nakamichi 482 outshines the 480 in a number of important areas, justifying the \$200 price differential. The 482 is an outstanding machine and we would confidently recommend it to anybody who wants above average performance and an unsurpassed frequency linearity. ▶

### NAKAMICHI 482 DISCRETE THREE-HEAD STEREO CASSETTE RECORDER

*Dimensions:* 450 mm wide x 135 mm high x 289 mm deep.

*Weight:* 6.4 kg

*Price:* \$599 rrp

*Manufactured by Nakamichi Corporation, Tokyo, Japan.*

*Serial No:* A114

Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.

## ATTENTION CONNOISSEURS OF HI-FI



Woodland Audio introduces a Turntable Base that effectively improves the performance of the renowned Connoisseur BD1 Turntable Kit. Advantages of selecting the Woodland Audio Turntable Base:

- Helps eliminate Feedback
- Produces a tight, clean, and detailed sound
- Enhances stereo image and separation
- Increases Dynamic range
- Is aesthetic in appearance

The Woodland Audio Turntable Base can be installed in minutes as a replacement for your present base or as an excellent choice of base for a new Connoisseur BD1 Kit.

The base is manufactured from high density materials and laminates to ensure a rigid, no-compromise turntable platform that successfully dampens vibration. It has been designed for the audiophile who requires maximum musical satisfaction from the BD1 Kit.

The Woodland Audio Turntable Base is available in three tasteful veneered finishes either direct from the manufacturer or in Brisbane from Stereo Supplies, Roma Street, City.

Pictured above is the Woodland Audio Turntable Base with the Connoisseur BD1 Kit, Grace G707 Tonearm, EEI MC 555 Moving Coil Cartridge and Micro Shock Absorbing Feet.

### TO BUY DIRECT FROM THE MANUFACTURER:

- simply select the required veneer finish.  
☐ Knotty Pine ☐ Teak ☐ Matt Black
- send details of tonearm to be used
- enclose cheque or postal order for \$96 (add \$5 freight)


MAIL TO:

*Woodland Audio*

50 Sherbrooke Road,  
Acacia Ridge, 4110,  
Brisbane.

TRADE ENQUIRIES WELCOME

## PHILIPS HI-FI SPEAKER KITS

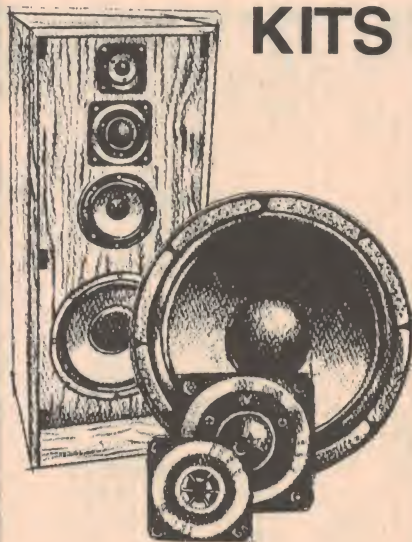

**FREIGHT FREE**  
**SA, VIC, NSW, NT**  
(nearest bus/rail station)

PHILIPS ETI 4000/1 4 way 100w speakers and C/O \$459.00  
PHILIPS ETI 4000/2 3 way 100w speakers and C/O \$350.00  
12K12 12" 3 way 40w complete kit veneered boxes, lining, C/O speakers \$299.00

140T8 Tweeter	\$12.00 ea. ....
162T8 Tweeter	\$13.50 ea. ....
1610T8 Tweeter	\$16.00 ea. ....
5060sq8 Midrange	\$22.00 ea. ....
210sq8 Midrange	\$32.00 ea. ....
2160sq8 Midrange	\$33.00 ea. ....
12650/W8 Woofer 60w	\$54.00 ea. ....
12100/W8 Woofer 40w	\$55.00 ea. ....
12200/W8 Woofer 80w	\$73.00 ea. ....
12250/W8 Woofer 100w	\$78.00 ea. ....
80652/W8 8" Woofer 50w	\$26.00 ea. ....
70601/W8 7" Woofer 30w	\$20.00 ea. ....
4060/W8 4" Woofer	\$19.00 ea. ....
ADF3000 Crossover	\$12.00 ea. ....
ADF500/4500/8" Crossover	\$21.00 ea. ....
ADF600/4000/8" Crossover	\$32.50 ea. ....
ETI4000/1	\$85.00 ea. ....
ETI4000/2	\$55.00 ea. ....

Goods sent at purchaser's risk. Insurance extra \$5.00.

**WORLD IMPORTS**  
232 RUNDLE STREET, ADELAIDE, S.A.  
5000. Phone (08) 223-6539.

Name .....

Address .....

.....P/Code.....

or debit my Bankcard.

Signature .....



## Mail Order KEF Drivers & Kits

CERTIFIED MAIL  
DELIVERY THROUGHOUT  
AUSTRALIA  
& NEW ZEALAND  
Bankcard accepted

**KEF**  
**B139**

Superb 30 x 21cm bass driver, with solid flat diaphragm of unique construction, acting as a perfect rigid piston, to give clean, distortion-free bass over the frequency range 20-1,000Hz. The KEF range also includes mid range and high frequency units, with dividing networks designed to link them into compatible systems.



*the no-compromise approach  
to uncoloured sound*

For full information, write to:  
AUDIOKITS  
PO BOX 553  
BROOKVALE NSW 2100





**You can't take your home stereo with you in the car, but now you can take its sound.**


### **Introducing Bose® Direct/Reflecting® car stereo.**

Bose introduces the Model 1401™ Direct/Reflecting® car stereo.

Which means that now you can listen to the same quality sound when you're sitting in a traffic jam or cruising down the highway, that you hear when you're home with your stereo system.

Two Direct/Reflecting® speakers with adjustable vanes let you reflect the sound off the rear window or other solid surfaces of the car. And reflect sound the way it is reflected in a concert hall.

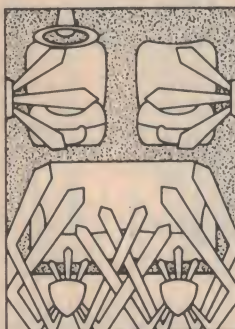And two accessory speakers can be mounted in the doors to bring even greater dimension and fullness. And all speakers are



full-range speakers based on the famous Bose 901® system.

The Bose 1401 system comes with a Booster/Equalizer that boosts the power to 100 watts total when all four speakers are used. At .09% THD. And it all fits under the dash.

The system also features a Spatial Control™ to shape the sound to the acoustics of your car; active equalization for flat power radiation in the car environment; and a low frequency control.

Come in for a demonstration and drive home listening to the same quality sound you'll hear when you get there.

**BOSE®**

Australasian Distributors: Bose Australia, 11 Muriel Avenue, Rydalmere 2116, Sydney NSW. Phone 648-1022.

Covered by patent rights issued and pending.

**fact:**  
there's a Shure  
microphone  
that's right for your  
application  
& equipment...



**SM81**

First of the new breed of high-performance, studio-quality unidirectional condensers—technically state-of-the-art, exceptionally rugged and superb sound.



**SM59**

You've seen it on TV musical shows where sound quality is a must. Unidirectional, dynamic with *exceptionally* flat response, extremely low handling noise; mellow, smooth, and accurate sound.




**SM58**

The most widely used "on-stage" hand-held dynamic cardioid microphone—the world standard noted for its distinctive, crisp sound.



**UNIDYNE® III**

The world-famous UNIDYNE® III family offers top value per dollar. Uniform cardioid pattern helps control off-axis coloration, background noise, and feedback.

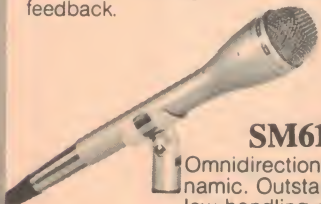

**SM61**

Omnidirectional dynamic. Outstanding low handling noise. Handsome, smooth looks with new VERAFLX® dent-resistant grille—a favorite on-camera mic with soundmen and entertainers.

**fact:**  
the microphone  
is your link  
with your  
audience



Eddie Rabbitt

Marilyn McCoo and  
Billy Davis, Jr.

Buddy Rich

Mick Jagger

### Take it from the Professionals...

A top-quality microphone makes a measurable difference in upgrading the sound of any system—and Shure microphones are universally recognized as the world's standard of quality. Wherever sound quality, reliability, uniformity, and intelligibility are prerequisites, you'll find that professionals choose, and use, Shure. You'll find more Shure microphones than any other single brand in applications as diverse as live entertainment, radio and TV, hotel and auditorium sound reinforcement, churches and temples, Congress, legislatures and the White House, and public safety—anywhere that sound excellence is a prime consideration. They are the reliable, professional connection between you and the people you're trying to reach. Send for complete literature. Please let us know your microphone application.

### The Sound of the Professionals



**AUDIO ENGINEERS P/L**  
342 Kent Street,  
SYDNEY 2000 N.S.W.

**AUDIO ENGINEERS (Vic.)**  
2A Hill Street,  
THORNBURY 3071 Vic.

**AUDIO ENGINEERS (Qld.)**  
51A Castlemaine Street,  
MILTON 4064 Qld.

**ATHOL M. HILL P/L**  
33 Wittenoom Street,  
EAST PERTH 6000 W.A.

# "The 4000/2... a superb loudspeaker system you can afford."



The 4000/2 system is the second in a series of loudspeaker systems designed by ETI and developed in co-operation with Philips Elcoma. Each unit incorporates the latest Philips loudspeakers from Europe. The result is a superb system that rivals many commercial units in quality and performance at the right price.

Because the 4000/2 system is also available in kit form for home construction, you can make impressive savings and still have a high performance system that looks like it has been put together by a professional.

A 100 watt RMS system.

The total kit includes:

- 300mm high performance woofer
- 50mm textile dome – mid range

- 25mm textile dome – tweeter
- 14 element cross over network.

See your Philips dealer today or send for complete details including a free reprint of the original construction article. Further information on Philips loudspeakers; a list of Philips dealers and a free 4-speed stroboscope card for checking the speed accuracy of your turntable.

## Philips Electronic Components and Materials

P.O. Box 50  
LANE COVE. N.S.W. 2066

Please send me complete information on the Series 4000/2 loudspeaker system plus my free 4-speed stroboscope card and further information on loudspeakers.

NAME \_\_\_\_\_

Please Print

ADDRESS \_\_\_\_\_

STATE \_\_\_\_\_

P'CODE \_\_\_\_\_



**Electronic  
Components  
and Materials**

# PHILIPS


AHEARN EL 35

ETI October 1980 – 121

# Consumer electronics shows — a tale of two cities

East-West rivalry contributed not a little to the success of this year's Perth and Sydney electronics shows.

**Dennis Lingane**

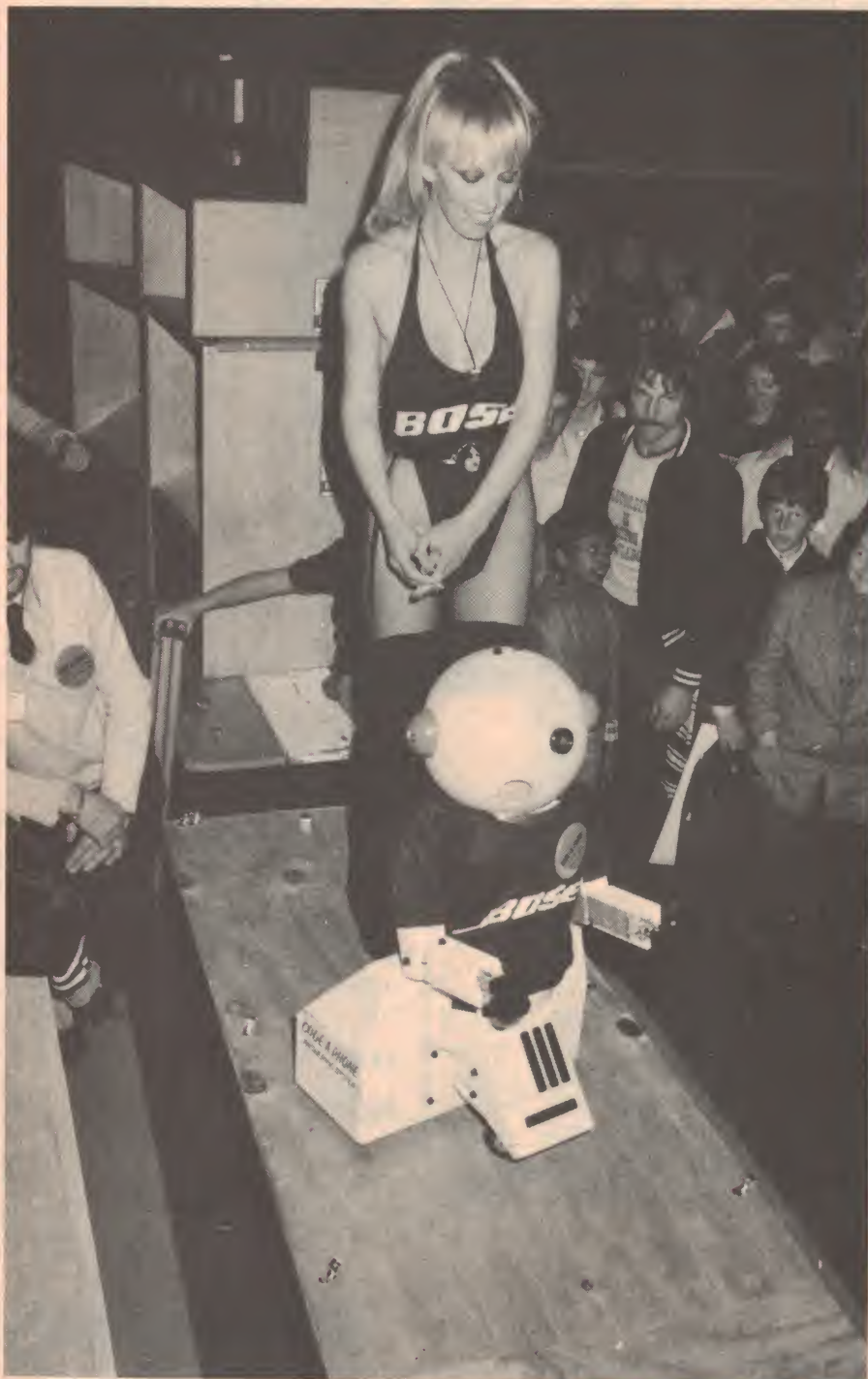

A small robot steals the limelight from the Bose disco dancer at Sydney's show.

THE Perth Electronics Show is now firmly established, but its success has not been well received by big brother in Sydney.

The national body that stages the Sydney Consumer Electronics Show gave the Perth industry committee an ultimatum this year — "Change your name or we will organise an industry boycott". Since the members of the Perth committee are only the State minions of the Sydney bosses they were not in a very good position to refuse.

To get the show on they had to accept the ultimatum of the Easterners and change the name to the Perth Electronics Show, dropping the previous Consumer Electronics title.

Why is the national committee so uptight about the Perth show? Because they are afraid, it would appear, that Perth may take the national show away from Sydney.

Last year when Perth staged its electronics show for the first time it pulled an attendance of over 20 000, even though it had been pre-empted three weeks earlier by a very large and successful hi-fi show run by the local hi-fi tycoon Hal Wallis and a number of manufacturers.

At that time, the Sydney national committee had tried to stop the Perth organisers calling their show the Consumer Electronics Show, but couldn't, because the name hadn't been registered in Perth by the national body. When they tried to register it they found the WA Hi-Fi Industries Association had jumped in ahead of them.

However, they weren't really worried because it was generally believed that the Perth show would be a second-rate affair. They were in for a shock, because interstate representatives who attended the Perth show came back wide-eyed!

Sydney's 1979 C.E.S. put through little more than 20 000. Perth, with a quarter of the population, put through the same number of people in four days as Sydney did in seven. The venue, the Perth Entertainment Centre, is top quality and was bathed in stage light-

ing with theatrical effects throughout the show.

Members of the national association must have begun to realise that a well organised show in the right venue in Perth could be more attractive than Sydney to the national retailers who are the main target for the national show. Apathetic dealers who can't be bothered to attend the Sydney show might be more interested in flying to Perth with their wives for a tax-deductible holiday.

Products shipped from Japan could be off-loaded at the Fremantle docks, where dockers are far less inclined to strike than their Sydney brothers. And a "suitable venue" might just be the arrival and departure terminals at the Fremantle Harbour, which is a massive two-floor barn type building stretching for hundreds of metres. This would mean the industry could off-load from the ships straight into the terminal.

So the pressure was really on the organisers of the Sydney show to produce the goods in 1980 — or else!

The national body followed the Perth lead and allowed electrical appliances and white goods into this year's show, doubled the advertising budget to \$80 000, booked four pavilions in the Sydney showgrounds, crossed their fingers and prayed.

The result was a terrific success story. Over 50 000 people attended the show, and for the first time it had plenty of exposure on the TV news, radio news and newspapers, thanks to major attractions like a swag of robots, and a first-class PR company.

With a sense of relief the national committee met after the show and elected the same committee stalwarts to run the industry and the show again for 1981.

## Sydney highlights

While the Perth show is consumer oriented, the Sydney show is mainly for the trade with the public being allowed in to help pay for the cost of running it. But although the signing of order books may be the main criterion for the success or failure of the Sydney show it is in fact only one of the benefits it offers the industry.

The comradeship, fun, involvement, camaraderie, brotherhood and everything else the show creates amongst the manufacturers, wholesalers and retailers, are a priceless investment.

With characteristic one-up-manship, John McTavish from Bose stole most of the limelight by offering a free T-shirt to anyone putting it on and wearing it around the show. Thousands were given away and everyone seeing the Bose T-shirt asked "Where do you get it?". One girl even stripped off on the stand to don



Model, Linda Ferguson gazes admiringly at Marantz's two-speed cassette decks.



Penthouse Pet Tracey Wallace demonstrating the Bose car stereo at Sydney's show.

# LIGHTING FOR ENTERTAINMENT



## BULLET BEAM

The Bullet Beam uses the seal beam, cool running Par 36 Ultra narrow spot lamp. It is particularly effective for display purposes, club and restaurant high lighting, and also illuminating Mirror Balls.

- Ideal for mobile disco.
- Positive location for colour frames and colour wheels.
- Available in colour of your choice.

## SPECIAL

**BULLET BEAMS — ONLY \$40.00 EACH**

(plus S/T if applicable)

With Par 36-4416 lamp. Gives out rectangle shape — great for dance floors.  
(Offer to 30/11/80 only)



## MIRROR BALLS

Large range of shapes and sizes.

16" (40cm)


24" (60cm)

36" (90cm)

16 x 24" (40 x 60cm)

Motor Drives are also available.

## MIRROR MAGIC

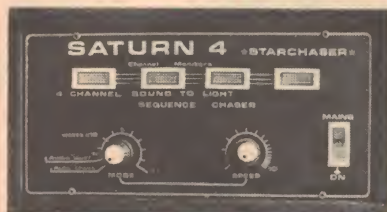

## SATURN 4

The Starchaser Controller is designed to control Snakelights and other lamps. It is a four channel unit using the latest in electronic technology to provide low cost, high quality performance.

The Snakelights plug straight into the rear panel via a flexible lead to socket.

Auto Chase is adjusted by the speed control from one change per 7 seconds, to 30 per second. By switching to Audio Level and again varying the Speed Control a wide range of effects can be achieved such as pumping, whizzing, bouncing and auto reversing sound to light sequencing can be achieved. During music breaks it will "pause-hold" on the last channel the music was picked up. Pattern indication is given by four easy to see large indicators.



## PAR 56 SCANNER

- All steel construction.
  - Built in colour frame (never needs replacing).
  - All black wrinkle finish, or colour of your choice (red, blue, purple, etc.).
  - Fully portable.
  - Par 56 300W lamps.
- Powerful beam scanning across the dance floor. Best effect can be obtained by connecting this fitting to a Lighting Controller in order to achieve a pulsating rhythm etc.

Ideal for mobile discos, bands, clubs etc.



## THE QUAD LIGHT

The Quad Light is a versatile lighting fixture accepting 4 spot lamps (each 75 or 100 watts), and can incorporate an adjustable bracket.

The Unit is of rugged steel construction with a durable wrinkle finish. (Colours again available).

The Quad Light can be used free-standing or wall or ceiling mounted and the integral swivel bracket gives precise positioning of the lighting. This fitting is an effective, low cost lighting unit, suitable for many applications. When four different coloured globes are used, unusual multi-coloured shadows are produced. This is particularly effective for display lighting.

For Discolighting, the Quad Light is the ideal unit to use, especially with a sound to light controller.

Also available — Tri Light, Duo Light and Uni Light.



## PAR 56

- All steel construction.
- Par 56 300W lamps.
- Barn Door if required.
- Colour Wheel.
- All black wrinkle finish (or colours).
- Ideal for mobile disco, bands, clubs etc.
- Built in Colour Frame (never needs replacing).

## ACCESSORIES

- Roscolene, Supergel, Lee Filters.
  - Cables, plugs, stands.
  - Lamps, — Philips, Osram, Tungsram.
  - SA Dealer of Nashua Gaffa Tape.
- To be released soon — PAR 64's.

ALL TRADE ENQUIRIES WELCOME

# SPECTRUM LIGHTING COMPANY

18 THOMAS STREET, CAVAN, SA, 5094

PHONE (08) 260-2500, A.H. (08) 263-8665

THE PROFESSIONAL LIGHTING EQUIPMENT



The robots fascinated kids and adults alike . . . er, the small one in the clearing is the robot.



Marantz made sure they couldn't be missed. This structure was great with the kids — as a slide !

her shirt and brought the whole pavilion to a standstill!

Blondie the disco dancer achieved a magic double act with Huggy the US robot who became a star of the show. Les Black, the chairman of the show committee, still talks about the morning when the half-metre dictator rolled out of the Boulevard Hotel lift in Sydney's William Street, went straight up to the bell captain and said: "Would you please call me a taxi!"

Nightly, the exhausted executives went on the town and the Bourbon and Beefsteak Restaurant, Rogues Nightclub and many other night spots became the scene for industry interchange and show anecdotes.

Like the man who rolled a wad of bills out of his pocket and tried to buy the ETI series 4000 four-way loudspeakers right off their stand because "they were the best things he'd heard anywhere!"

Another moment of excitement for ETI was the kidnapping of its R1D1 robot, who disappeared overnight and was later found lurking amongst the rubbish cans behind one of the show's fast food stands.

## The West strikes back

Once the formalities of the Sydney show were over, all eyes turned to Perth, where Leo Overington, who heads the committee, has almost single-handedly pulled the show through its various crises.

Would he be able to match the Sydney attendance? Not possible, said everyone. There was no chance that in only four days the Perth show could even approach the 50 000 attendance of the seven day Sydney effort.

By lunchtime on the Saturday (30 August), with the afternoon and evening, plus all of Sunday to go, Perth passed its 1979 figure. The atmosphere in the massive Perth Entertainment Centre, which housed the show on two floors, was electric.

Penthouse Pet, Tracey Wallace, flown over by John McTavish as part of his Bose circus, had sold out of Penthouse magazines and the crowds queued to sign a petition to elect her as Penthouse Pet of the Year.

Overhead, a laser show went through its 'Star Wars' act every hour on the

hour. The Atari electronic games stand, manned by W.A. Futuretronics rep Jeff Krasnostein, collapsed three times under the pressure of the hundreds of kids and adults.

Bob Purvis established a recording studio where children were allowed to sit at a professional 24-channel desk and mix down musical instruments off an 8-track tape. Bob was demonstrating harmonisers and voice pitch control gadgets so energetically that even his well-trained tonsils gave out.

Lowry and Technics fought out an electronic organ battle only yards from each other, and mesmerised members of the public sat for hours in the W.A. Astronautical Society exhibition watching movies on the NASA and European space research programmes.

After Saturday lunchtime the attendance figures were kept deadly secret and a sweepstake was organised. Through the noise and the excitement the question kept being asked: "What do you think the number is now?"

The final figure of 40 000, announced at the after-show party, brought the house down. "That will shove it up those



Aiwa's extraordinary slide-out turntable from their minis.



Pioneer launched their 'domestic' video disc player at the Sydney show.

# STAGE & EFFECTS LIGHTING

## ALL YOUR REQUIREMENTS AUSTRALIA WIDE

### PAR 36 PENCIL BEAMS

The great Hotspot and Solo sale!



We are overstocked on Par 36 Pencil Beams. The incredible pinbeam spots used in discos, clubs, by bands — for rainlite curtains, mirrorballs — effects — everything. So buy now at the old prices.

**HOTSPOTS:** Complete pencil beam lantern to accept the PAR 36 display lamp 25w, 5.5V.

**RRP only \$49.00** (This time last year Hotspots sold at \$56.00, so you are saving even more).

**SOLO'S:** PAR 36 lamp housing without transformer — great where huge numbers of PAR 36 lamps are needed for giant effects. Complete with colour filter clip.

**RRP only \$19.99** (Last year — \$25.00 — save).

**PAR 36 DISPLAY LAMPS:** The long life PAR 36 lamp — 5.5V, 25w.

**RRP only \$9.70** (Last year \$12.00).

#### OTHER PAR 36 PRODUCTS AVAILABLE

**RAINFIGHT:** The high powered version, 50w, 12V Quartz lamp.

**SPACEBEACONS:** 4, 8 or 16 rotating PAR 36 lamps.

**SPINNERS AND SCANNERS:** Single rotating or scanning PAR 36 lamp.

### NEW THE LATEST IN LIGHTING EQUIPMENT FROM CEITEX



The ultimate multiple controller for installations or mobile work.

- 4 channel dimmer
- audio chaser
- colour organ
- auto dimmer

The Colourgram 4 is a selectable controller offering either dimmer or effect functions with dimmable background levels. The Colourgram 4 will handle inductive loads like Hotspots and Rainlights without problems up to 20 amps max. load.

### REMOTE LIGHTING SWITCHBOARD



- 12 channel system — 2000w per channel
- electronic switching — no interference
- 4 preset switchdesk with flash buttons and chaser
- complete on-stage rack

Call the professionals for the whole lot in stage lighting. Hire and Sales.

(Not all Barratt Lighting agents stock all lines at once — call and check first).

**SYDNEY:** Ceitex 2/33 College St, Gladesville (02) 896-2900

**WOLLONGONG:** Trilogy Electronics 40 Princes Hwy, Fairy Meadow (042) 83-1219

**NEWCASTLE:** Your Move Lighting 37a Beaumont St, Hamilton (049) 69-3560

**BRISBANE:** Harvey Theatrical Lighting 21 Crosby Rd, Albion (07) 262-4622

**GOLD COAST:** Rave Audio Visual 2388 Gold Coast Hwy, Mermaid Beach (075) 38-3331

**MELBOURNE:** Clearlight Shows 17 Alex Ave, Moorabbin (03) 553-1446

**MELBOURNE:** Lighting Corporation 131 Brighton St, Richmond (03) 429-5122

**ADELAIDE:** Hiwatt Lighting 37 Angus St, Nth Adelaide 5006 (08) 212-2033

**ADELAIDE:** Optical Acoustics 22 Finnis St, Nth Adelaide 5006 (08) 267-2049

**ACT:** Topstage Productions 12/4 Ipswich St, Fyshwick ACT 2609 (082) 80-6940

**PERTH:** Stagecraft 1142 Hay St, West Perth 6005 (09) 321-9363.

**PERTH:** Kosmic Sound 1074 Albany Hwy, Bentley (09) 361-8981

**HOBART:** Good Oil Sound 310 Liverpool St, Hobart (002) 23-5151

Also available Australia-wide at Strand Rank Electronic outlets.

New Brisbane outlet: **RAVE LIGHT & SOUND** 95 Bridge Rd, Fortitude Valley. Phone (07) 52-3310.

Distributed nationally by

Telex AA25298

**BARRATT LIGHTING PTY. LTD.**


140 Myrtle Street, Chippendale, NSW 2008.

NOW OPEN: New One-Stop Lighting Shop Showroom. All products ex-stock.

New Phone No. (02) 698-8499



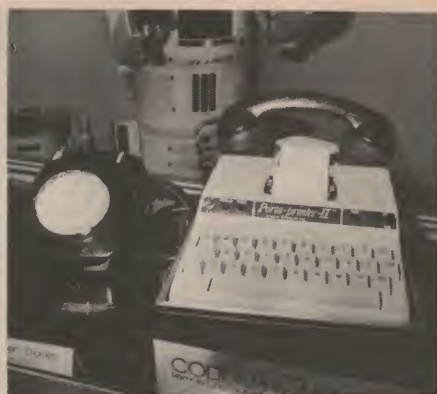The KLH analogue bass control unit attracted some attention.



The Porta-printer II data terminal — a new product this year.

b...s in the East." was the jubilant reaction.

But the animosity that now exists between the two shows should never have happened, and can be directly attributed to the pressure the Sydney people brought on the W.A. show.

### Seriously

But seriously folks, industry politics and show antics apart, what did this year's Sydney CES have to offer?

Pioneer and Philips both showed their video disc systems and the hot rumour now is that we will see the launch of the PAL video disc system before the end of 1981. Philips is due to complete a factory in Belgium this year and will start making the players by the beginning of 1981. Meanwhile a software factory is due to be completed in the UK by the beginning of 1981 and will be in production by mid-1981.

Philip's Ron Ward says that his company has now developed a new video disc software production system using a photographic technique which will reduce the complexity and expense of manufacturing the discs. Pioneer's Les Black says that as soon as PAL software is available in Australia he will launch the Pioneer video disc here. Meanwhile, the two companies appear to be manoeuvring for the kudos of being "first off the rank in Australia".

Philips also showed their eight hour

flip-over video system which won't be released until the end of this year. However, Grundig, who are their partners in this venture have already started shipping in stocks and there appears little doubt that Australia is once more to become a three-format market.

Not that it is important now. With the video disc about to be launched the software is going to become less important in the video cassette market and the only point of interest will be the recording ability of the cassette.

On the hi-fi side there were no takers for the Thorens \$13,000 turntable, but plenty of interest in the unique new Aiwa slide-out turntable. Ian Woodehouse of Aiwa says that the orders he received at the show are treble the initial order he placed with Japan. "People have freaked out over the new turntable," he says. "It's different, and at \$430 is priced right."

Aiwa and several other companies increased their mini hi-fi range and are still expecting this market to do well in coming years as Australians switch from "big is beautiful" to "small is nicer" because it takes up less room.

Sansui's colour display 'fading' sound system created a lot of interest. Instead of switching from phono to tuner, to tape, you fade from one to the other and at the half way stage can actually run both inputs together. A colourful screen ▶



Philips' remarkable eight hour flip-over video cassette recorder.

# WHEN IT COMES TO SOUND . . .

*We've been hiring, for the last 5 years, sound systems to many local, interstate & international groups & artists. Now our expertise in equipment knowledge goes into selling the right sound equipment to you! Talk to us first, we'll get your act together!*

**RIGHT FROM THE:**  
MICROPHONES (BEYER/SHURE)  
STANDS/CABLES  
MIXERS (JANDS)  
MXR GRAPHIC EQUALIZERS  
DBX COMPRESSOR/LIMITERS  
CROSSOVER (JANDS)  
POWER AMPS (JANDS)  
JBL SPEAKERS  
'W' BINS  
MID CABINETS  
JBL HORNS  
JBL TWEETERS

**MISCELLANEOUS:-**  
CANNONS  
PIEZOS  
GAFF  
DI BOXES  
SESSIONS  
CATCHES/CORNERS  
MUFFIN FANS  
MODIFICATIONS  
RACK/ROAD CASES  
ETC. ETC.

**SALES & HIRE  
DROP IN OR GIVE US A CALL!**

**DSA CONCERT SYSTEMS**  
156 GIVEN TCE, PADDINGTON 4064  
PHONE (07) 36 6367

# A professional mic at a really good price

## Numark

MODEL No. UC965

A thoroughly dependable, well-finished professional quality microphone at a surprisingly keen price — look for the name: Numark.

### SPECIFICATIONS:

Type — Black electret IC.  
Frequency Response —  
20-20,000Hz plus or minus  
3.5dB.  
Z — 600 Balanced.  
Polar response — Cardioid.  
Battery — 1.5V penlight.  
Complete with 6m mic lead,  
case and holder.

R.R.P.

# \$60

TRADE ENQUIRIES WELCOME

## Freedman Electronics


91a Liverpool Road,  
Summer Hill, NSW 2130.  
Phone (02) 797-9941.
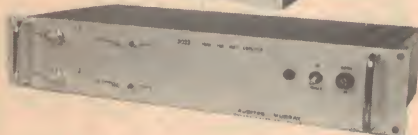
# The Auditec P.A. Amplifier Range

~Australian designed, Australian manufactured



**K104, K105**  
Free standing 120  
watt amplifiers with  
either 2 or 4 input  
channels.



**2033, 1034**  
Rack mounting 2 x  
100 watt and 200 watt  
studio monitoring  
amplifiers. Where  
reference amplifier  
quality is required.



**1009, 1027, 2009**  
Rack mounting 120 and 250  
watt amplifiers with optional  
preamplifiers and VU meters.



**A-SERIES**  
For mounting into a case or  
cabinet. In 2 x 60 watt, 120  
watt, 250 watt, 2 x 120 watt.

There are three reasons why you should install an Auditec instead of an imported amplifier: **QUALITY, RELIABILITY and PRICE.**

**AUDITEC MAJOR STOCKISTS:** VIC: ZEPHYR PRODUCTS, 70 Batesford Road, Chadstone, 3148. Phone (03) 568-2922. QLD: DELSOUND PTY. LTD., 1 Wickham Terrace, Brisbane, 4000. Phone (07) 229-6155. SA: NEIL MULLER PTY. LTD., 8 Arthur Street, Unley, 5061. Phone (08) 272-8011. WA: WILLIS ELECTRONICS, 993 Hay Street, Perth, 6000. Phone (092) 321-7609. ACT: MUSIQUE BOUTIQUE, 29-31 Colbee Court, Phillip, 2606. Phone (062) 81-5255. NT: DARWIN COMMUNICATIONS SYSTEMS, 2420 Scriven Street, Casuarina, 5792. Phone (089) 85-3184. FARMER & DAVIES ELECTRONICS, Weber Sales Bld., Fogarty Street, Alice Springs, 5750. Phone (011) 52-2967. TAS: Stage Systems, 52 Mollie Street, Hobart, 7000. Phone (002) 34-4009.

**OTHER AGENTS:** NSW: RAY WALSH SOUND SYSTEMS, 448 Swift Street, Albury, 2640. Phone (060) 21-1502. W.M.R. ELECTRONICS, "Wirra-Willra", Belmont Road, Glenfield, 2167. Phone (02) 605-1203. DAWES SOUND SYSTEMS, 7 Mitchell's Pass, Blaxland, 2774. Phone (047) 39-4421. D.R. HI-FI & ELECTRONICS, 657 Pittwater Road, Dee Why, 2099. Phone (02) 982-7500. LANDERS MUSIC CENTRE PTY. LTD., 302 Summer Street, Orange, 2800. Phone (063) 62-6515. TRILOGY WHOLESALE ELECTRONICS, 40 Princes Highway, Fairy Meadow, 2519. Phone (042) 83-1219. R. ARCHER & SON, 107 Bungaree Road, Wentworthville, 2145. Phone (02) 631-4538. QLD: BUNDABERG HI-FI, 244 George Street, Bundaberg, 4670. Phone (071) 71-3176. KELLER ELECTRONICS, 94 Elena Street, Maryborough, 4650. Phone (071) 21-4559.

For full details of these amplifiers  
phone, write or call at ...

## AUDITEC AUSTRALIA PTY. LTD.

10 Waitara Avenue, Waitara, NSW 2077  
(Adjacent to Pacific Highway)  
Phone (02) 48-4116

# SONICS

The Australian music magazine dedicated to the art and craft of sound

\$1.95\* N.Z. \$2.15  
OCT.-DEC. 1980

**GARY NUMAN**  
Techniques of the Machman

**GUITAR SYNTHS**  
The pleasures of infinite sustain



**Available early Sept.**

**A.M.T.A.  
Trade  
Fair Guide**

the Australian  
magazine  
dedicated to  
the art and  
craft of sound

Sonics is a magazine for everyone who has an interest or involvement in music or musical electronics. Published quarterly, in March, June, September and December, each issue contains features, equipment reviews, constructional projects, distributor and brand indexes and much, much more.

#### Sonics October 1980 line-up:

**FEATURE** — Fairlight C.M.I.: Australian digital synthesis goes world-wide

**RIGS** — Country music with Bose under the 'Big Top'

**SOUNDPROOF** — Paradise Studio: prime facilities in a lavish atmosphere

**PROFILE** — Ian Moss, Cold Chisel's guitarist

**HARDWARE** — Teac's 144 Portastudio and Crown's PSA-2 amplifier

**SHOP** — Billy Hyde Drum Clinic

**SHINE ON** — Latest products and news in the lighting game

**LEFTY CLEF** — The saga begins...

**PLUS** — extra features, a B.I.Y. project, and all the news, views and happenings in electric music and musical electronics. Rendezvous with Sonics in October.

Also available..... Sonics 1980 Yearbook is Australia's first comprehensive directory of electronic musical equipment, featuring articles on keyboards, guitars and pick-ups, amplifiers, speaker systems and microphones. The Yearbook is still available from most newsagents, or direct from Sonics, 4th Floor, 15 Boundary St, Rushcutters Bay, NSW 2011 — Price \$4.35 plus 75 cents post and packaging.



AR's High Tech speakers attracted a lot of attention at Perth.



Philips' laser video disc player.

changes colours as the inputs change.

Yamaha showed their PX2 turntable, and the new T7 tuner. Both the turntable and tuner are lower-priced versions of the expensive prototypes shown last year. The T7 tuner replaces the T1, with better specs and a lower price and the PX2 is only \$1000 compared to the PX1 price of \$6000.

Pioneer launched 35 new products including two tuner systems for the launch of FM commercial radio, and a new digital display, electronic-tune car radio cassette unit. Their new car music director speakers also raised a lot of interest.

The Bose car stereo created interest with its 100 watt amplifier and four-way speaker system.

National showed its new rear pro-

jection 1140 mm (45-inch) TV on a retailer's stand (they declined to take part in the show this year), and with a price of approx. \$3000 it is expected to be a big seller. National did exhibit in Perth, and showed the much-awaited model 7000 video recorder that is National's answer to Sony's infra-red remote control market leader.

Wharfedale, AR and KLH released new speakers. The KLH speakers are 'computer bass boosted' and this really appealed to the public's love of gimmicks while Arthur Muldoon of AR spent hours trying to explain to one customer that the new AR Hi-Tech speakers are not wireless units with their own receivers.

Last year Arthur put all the speaker wires through a garden hose to keep

them neat and one customer afterwards commented that he loved the fluid-cooled AR speakers, but was there any other way of getting the fluid to the speakers because his wife wouldn't tolerate a garden hose in the lounge!

Sharp showed their new card-operated computerised microwave oven. The inclusion of this kind of item helped to attract more wives to this year's Sydney show, giving them something to take an interest in while Dad drools over the hi-fi and video and the kids inspect the computers and electronic games.

Hi-fi still retains its star rating in the show and so far this year hi-fi sales are up 50% nationally, proving that exhibiting with the rest of the industry hasn't harmed the business. ●



REF: VE-2

RRP \$27.45

It is a fact that a video recorder's ability to record and reproduce clean sharp images diminishes with continued use. For optimum performance tape heads, tape guides and pinch rollers must be cleaned about every 20 hours of running time. Airborne contaminants combined with room humidity and oxide particles create residues on all these parts. Simple routine maintenance with the Bib Video Maintenance Kit will prevent this, and at the same time reduce undue wear on the critical tape contact points.

The kit is supplied with a comprehensive instruction manual.

**Bib®**

*Videophile Edition*

A new range of video maintenance products from the world's leading specialists in audio/video maintenance since 1954.

#### BIB VIDEO MAINTENANCE KIT

● Five special purpose cleaning tools ● Special formula head cleaning fluid ● Can of patented dust-away air blast ● Inspection mirror ● Anti-static cleaning cloth. All these items are packed in a strong storage container. In difficulty send direct plus \$1.00 post and packing.

#### BIB HI-FI AUSTRALIA

43 Birmingham Street, Alexandria, NSW 2015.  
Phone (02) 667-2750, 669-3892.

HAS THE TASTE STOPPED  
GETTING THROUGH?



If your present tobacco just doesn't deliver the  
satisfaction you want, then roll a Cannon.


A rich new blend of medium dark cigarette  
tobacco that's just a little bit stronger.

Cannon, for the taste you're missing out on now.

**CANNON.**  
**SLIGHTLY STRONGER.**



# \$2 buys a lot of Sydney.

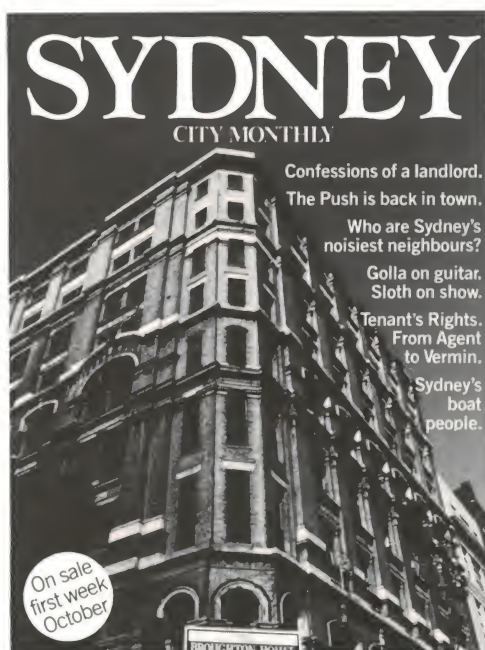

What goes on in this town would fill a magazine. And that's what Sydney City Monthly is all about.

Every month you can check out what's on; galleries, the theatre, conferences, opera, dance, rock, jazz, classical.

Every month Sydney City Monthly reveals and reviews; restaurants, exhibitions, movies, books, wine, art.

And every month you meet the people who make this town buzz with fashion, gossip, politics, money, fun.

Sydney City Monthly has become just about as popular as Sydney itself.

## The Push is back in town.

The Money.  
The Gentry.  
The Speculator.

Here they come. Back from St. Ives. Up from Moss Vale. Down from Palm Beach. Not to work. But to live. In Liverpool Street, Clarence Street, even George Street.

## How to tell a William & Mary from a George & Anne.

Unless you know your antiques you may be better off with Danish modern. You can be duped. Even dealers can be duped. An investigation into where to buy and what to buy.

From Paddo to Lane Cove, from auction to markets.

## Tenant's Rights. From Agent to Vermin.

Everything you need to know about renting. From Pets and Privacy to Late Rent and Eviction. And the names of ten organisations who will make sure your rights are protected.

## Who are Sydney's noisiest neighbours?

- A. Stereo freaks?
  - B. Party givers?
  - C. Dog lovers?
- And who can you call to dob them in?
1. The police?
  2. The council?
  3. The Noise Pollution Control Commission?

## Confessions of a landlord.

Let a furnished flat (with no t.v.) on a short lease to a middle-aged, middle grade (unmusical) public servant.

Then up the rent every 6 months.



## Golla on guitar. Sloth on show.

Sunday at the museum is anything but dead. It can mean a concert in the fossil hall with George Golla.

Or a look at life under water in the marine hall. Or a 10 minute trek through the desert at night.



## Sydney's boat people.

There are just 4 houseboats left on Sydney harbour. Soon there may only be 3.

Who's on board and why? And who's left them high and dry?



Sydney City Monthly. At your newsagent. \$2.

Consult the experts with  
over 25 years in the field.  
**WE HAVE WHAT YOU WANT  
LOOK!**

Sydney's widest range of UHF — VHF  
amplifiers 40-840 Mhz.

1. 75.D16 dB gain 1. Outlet
2. 75.T12 12 dB gain 2. Outlets
3. 75.T10 10 dB gain 3. Outlets
4. 75.T10 10 dB gain 4. Outlets
- 1.75.D25 25 dB gain 1. Outlet
- 2.75.D21 2dB gain 1. Outlet
- 16-100 16 dB gain 1. Outlet
- 27-100 27 dB gain 1. Outlet
- 42-100 42 dB gain 1. Outlet
- 40-100WN 40 dB gain 1. Outlet
- 40-100HL 40 dB gain 1. Outlet
- 27-500 dB gain 1. Outlet


COMPLETE RANGE of Kingray and Hills  
Mast head and Line Amplifiers.  
Largest range of Line and Single Outlet  
Plates and Sockets.

SPLITTERS: 2.75.T/S — 3.75T/S, 4.75T/S —  
5.75T/S, 6.75T/S to 8.75T/S.

Outside splitters: 2.75T/S0 — 4.75.T/S0.  
Waterproof housing.

**If you don't see it  
listed, ask for it.**

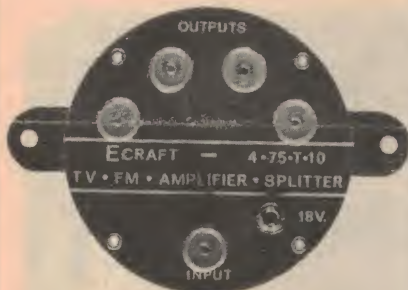REMEMBER: THE WIDEST RANGE OF  
UHF-VHF SPLITTERS — PLATES —  
AMPLIFIERS IN SYDNEY TODAY.



**NOTICE TO INSTALLERS/WHOLE-  
SALEERS:** Save dollars on coaxial cable.  
Ring now for the best prices and  
cable in Australia.

**FREE ADVICE GIVEN.  
ELECTRO-CRAFT  
MFG P/L**

68 Whiting Street, Artarmon, NSW  
2064. PO Box 398.  
Phone now (02) 438-4308 ext 6.  
Hours: Mon-Fri 8am to 5pm.

# Follow the dotted line and win a Commodore.



At 9.32 am  
on Monday 26th  
May Evan Green of  
GMH and Matt  
Whelan of

Wheels magazine  
left Melbourne for a bit of a spin.  
Around Australia.

If you can answer three  
questions about their drive you  
could win a brand new Holden  
Commodore.


The questions you'll need  
to answer are in the September,  
October and November issues  
of Wheels magazine.

And the clues to the  
answers are in a report  
written by Matt Whelan  
in September Wheels.

It's not an  
easy contest.  
But it's a lot  
easier than a  
non-stop drive  
around Australia.



## The Digital Age has begun . . .

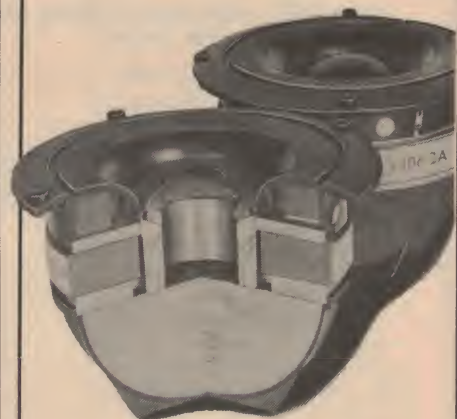

The answer that some eminent  
manufacturers have to the  
introduction of directly cut and  
digitally mastered discs with their  
60-70dB dynamic range  
capability is the fitting of  
protection devices to so-called  
state of the art loudspeaker  
systems.

**DYNAUDIO** components and  
systems will replay this dynamic  
range without compression and  
also the demanding 90dB plus  
capability of the coming digitally  
encoded discs. Realistic  
reproduction has advanced a  
step forward.

**DYNAUDIO** high fidelity drivers  
use hexagonal wire, ferrofluidics  
and dynamic transient linearity  
system (DTL) for fast rise time  
and low IM distortion.

**Sole Distributors in Australia:**  
**Dynaudio (Aust) Pty Ltd**  
PO Box 2 Hawthorn Vic 3122  
Phone: 818 2647.

**Available from:**  
VIC: Soundcraftsmen: 66 Kooyong Rd  
Caulfield Vic 3161, Phone: 509 2444  
Tivoli Hi-Fi: 654 Glenferrie Rd  
Hawthorn 3122, Phone: 818 8637

NSW: Leisuresound: 401 Pacific Hwy  
Artarmon NSW 2064, Phone: 438 4166  
38 York St Sydney NSW 2000,  
Phone: 29 1364

# BOOKS

Just some of the books from the biggest range of radio and electronics books in Australia. If the book you require is not listed below, it can be ordered from us.

**NEW - NEW - NEW** Latest editions of some of the most popular books on the subject:

The Master IC Cookbook (Clayton L. Hallmark)	\$12.50
IC Array Cookbook (Walter G. Jung)	\$10.00
Amateur Operator's Handbook (Revised Dec. 78)	\$3.60
(Postal & Telecommunications Dept.)	
ARRL Handbook 1980	\$14.95
R.S.G.B. Handbook — Volume 1	\$21.95
R.S.G.B. Handbook — Volume 2	\$18.90
The World In My Ears (Cushen)	\$13.35
Radio Handbook — 21st Edition (New edition) (William Orr)	\$27.75

## ADAM OSBORNE BOOKS:

An Introduction to Microcomputers — Volume 0 —	
The Beginner's Book	\$10.40
An Introduction to Microcomputers — Volume 1 —	
Basic Concepts	\$16.20
An Introduction to Microcomputers — Volume 2 —	
Some Real Microprocessors	\$29.00
An Introduction to Microcomputers — Volume 3 —	
Some Real Support Devices	\$19.00
Some Common Basic Programs	\$16.20
Accounts Payable and Accounts Receivable	\$18.60
Payroll with Cost Accounting In Basic	\$18.60
General Ledger	\$24.50
Z80 Assembly Language Programming	\$16.20
Z80 Programming for Logic Design	\$13.50
8080A/8085 Assembly Language Programming	\$16.20
6800 Programming for Logic Design	\$13.50
6800 Assembly Language Programming	\$13.50
8080 Programming for Logic Design	\$13.50
6502 Assembly Language Programming	\$16.20

## AMERICAN RADIO RELAY LEAGUE PUBLICATIONS:

All New A.R.R.L. Code Kit	\$14.50
Hints and Kinks for the Radio Amateur	\$7.20
The Radio Amateur's VHF Manual	\$7.20
Understanding Amateur Radio	\$8.80
The Radio Amateur's License Manual	\$7.20
A Course in Radio Fundamentals	\$7.20
Specialized Communications Techniques for the Radio Amateur	\$7.20
FM & Repeaters for the Radio Amateur	\$8.80
Single Sideband for the Radio Amateur	\$7.20
Ham Radio Operating Guide	\$7.20
Electronics Data Book	\$7.20
Solid State Design for the Radio Amateur	\$12.80

## MICROCOMPUTERS/MICROPROCESSORS BOOKS:

Programming the Z80 (Rodney Zaks)	\$19.00
Z80 Microprocessor Programming and Interfacing	
Book 1 (Nichols/Nichols/Rony)	\$14.75
Z80 Microprocessor Programming and Interfacing	
Book 2 (Nichols/Nichols/Rony)	\$17.50
Best of Interface Age, Volume 1	
Software in Basic (Ed. Carl D. Warren)	\$17.80
Best of Interface Age, Volume 2	
General Purpose Software (Ed. Interface Age)	\$12.70
The A to Z Book of Computer Games (Thomas C. McIntire)	\$9.95
6502 Software Gourmet Guide & Cookbook (Scelbi)	\$16.80
How to Build Your Own Working Robot Pet (Frank DaCosta)	\$8.50
The Complete Handbook of Robotics (Edward L. Safford, Jr.)	\$9.95
Programming Microprocessors (M.W. McMullan)	\$9.25
Microcomputer Primer (Waite & Pardee)	\$10.75
How to Buy and Use Minicomputers and Microcomputers (W. Barden, Jr.)	\$13.50
Z80 Microcomputer Handbook (Barden)	\$11.95
Microcomputers for Business Applications (Barden)	\$11.95
Scelbi "8080" Software Gourmet Guide & Cookbook	
Reduced from \$10.00 to	\$4.99

## OTHER TITLES:

Music and the Synthesiser (Bruce Graham)	\$15.00
The S-100 and other Micro buses	
(Elmer C. Poe & James C. Goodwin)	\$7.95
Microprocessor Cookbook (Michael Hordeski)	\$7.50
TV Antennas and Signal Distribution Systems (M.J. Salvati)	\$13.50
Building Hi-Fi Speaker Systems (Philips)	\$10.75
Master Handbook of 1001 Practical Electronic	
Circuits (Ed. Kendal Webster Sessions)	\$15.95
The Complete Handbook of Public Address Sound Systems (F. Alton Everest)	\$9.95
Getting Acquainted with the IC (Rufus P. Turner)	\$6.75
Practical Antennas for the Radio Amateur (Scelbi)	\$15.40
IC OP-AMP Cookbook (Walter Jung)	\$17.50
TTL Cookbook (Lancaster)	\$12.95
TV Typewriter Cookbook (Lancaster)	\$13.50
CMOS Cookbook (Lancaster) 1st Edition 1977	\$14.25
Active Filter Cookbook (Lancaster)	\$19.95
IC Timer Cookbook (Jung)	\$13.50
The Cheap Video Cookbook (Lancaster)	\$7.95
Electronics Pocket Book — 3rd Edition (P.J. McGoldrick)	\$10.50
Computers in Action — How Computers Work 2nd Edition (Donald D. Spencer)	\$8.00

For mail orders please add: \$1.40 Local \$1.75 Interstate

**McGILL'S AUTHORISED NEWSAGENCY PTY. LTD.**

187 Elizabeth Street, Melbourne. Phone: 60-1475-6-7

Prices Subject to Alteration

# LIGHTING AS FLEXIBLE AS YOUR THINKING...

... that's what Sevlén Lighting offers you. The most portable, economical and adaptable low priced lighting system ever invented, a must for clubs, displays, windows and dance venues.

Connected via a new advanced locking mains line socket to a four channel STARCHASER controller, an amazing sequence is produced all within a tube. No complicated connections, no wiring, no messy installation problems, just plug on — take it anywhere, anytime. Bend it, shape it, hang it overhead, on stairs or ceilings.

If you need more, just connect another snakelight on to the other end — (each \*snakelight is 10 metres long). Up to 300 metres of scintillating, pulsating chase.

The new connectors introduced are locked together when plugged in and cannot be accidentally separated while in use. The special miniature lamps have a unique continuity link which ensures that even if one lamp fails, the whole circuit continues to work without interruption

\*12 different colours available.



## SEVLEN LIGHTING PTY. LTD.

### MANUFACTURERS OF LIGHTING CONTROL SYSTEMS

Office: 4 Weldon Street, Burwood, 2134, NSW  
Telephone (02) 74-8905

# here's what the laboratory says about audio technica

"The Audio Technica AT-12E, although very modestly priced, features one of the flattest responses provided by any of the cartridges we have reviewed over the last 15 years . . . this cartridge performed as well as many cartridges selling at five times the price . . ."

Reproduced from a review in ETI Feb. 1980, by Louis A. Challis & Associates Pty. Ltd.

AT-12E




AT-11



AT-11E



AT-10

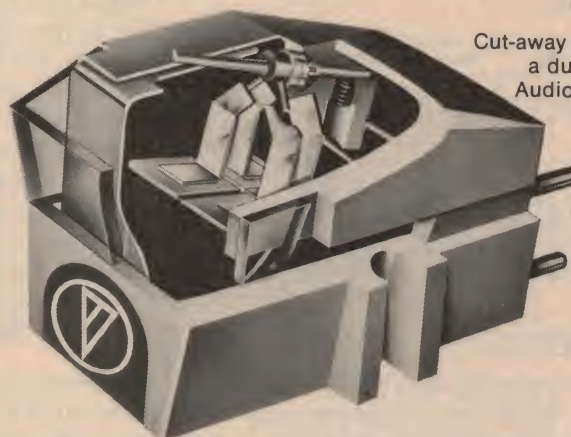

Cut-away section of a dual magnet Audio Technica cartridge.

To obtain top performance you must look for a cartridge with a dual magnet system, as perfected by Audio Technica.

## AT 12E

Value leader among elliptical stylus models. Employs finely-crafted 0.4 x 0.7 mil bonded diamond mounted to thin-wall cantilever. Dual Magnet design assures flat response and excellent stereo separation. For all modern record changers and turntables.

### •AT-12E technical data

Frequency Response: 15 ~ 26,000 Hz  
Tracking Force: 1.0 ~ 2.0 g (Optimal Force 1.5 g)  
Output Voltage: 4.2 mV (1 kHz 5 cm/sec)  
Channel Separation: Minimum 23 dB (1 kHz)  
Static Compliance:  $25 \times 10^{-4}$  cm/dyne  
Load Resistance: 47 k $\Omega$

Replacement Stylus ATS-12

## AT 11

Flat response and remarkable tracking ability distinguish this Dual Magnet cartridge. Spherical bonded tip is best for use with older or budget record changers. High output matches moderately-priced systems.

### •AT-11 technical data

Frequency Response: 15 ~ 22,000 Hz  
Tracking Force: 1.5 ~ 2.5 g (Optimal Force 2.0 g)  
Output Voltage: 4.8 mV (1 kHz 5 cm/sec)  
Channel Separation: Minimum 21 dB (1 kHz)  
Static Compliance:  $22 \times 10^{-4}$  cm/dyne  
Load Resistance: 47 k $\Omega$

Replacement Stylus ATS-11

## AT 11E

Our lowest cost elliptical stylus cartridge yet built to high Audio Technica standards. Bonded 0.4 x 0.7 mil elliptical tip and thin-wall cantilever combine to offer unusual high frequency tracking ability in this price category. Excellent replacement for older cartridges to improve your system.

### •AT-11E technical data

Frequency Response: 15 ~ 25,000 Hz  
Tracking Force: 1.5 ~ 2.5 g (Optimal Force 2.0 g)  
Output Voltage: 4.8 mV (1 kHz 5 cm/sec)  
Channel Separation: Minimum 21 dB (1 kHz)  
Static Compliance:  $22 \times 10^{-4}$  cm/dyne  
Load Resistance: 47 k $\Omega$

Replacement Stylus: ATS-11E

## AT 10

Almost identical to the AT-11, the AT-10's flat response and remarkable tracking ability enables high quality stereo sound reproduction. Uses bonded spherical stylus. Has same characteristics that fit moderately priced systems so well.

### •AT-10 technical data

Frequency Response: 20 ~ 20,000 Hz  
Tracking Force: 2.0 ~ 3.0 g (Optimal Force 2.5 g)  
Output Voltage: 4.8 mV (1 kHz 5 cm/sec)  
Channel Separation: Minimum 20 dB (1 kHz)  
Static Compliance:  $20 \times 10^{-4}$  cm/dyne  
Load Resistance: 47 k $\Omega$

Replacement Stylus ATS-10

# audio technica

available at all quality hi fi dealers

If you have any supply problems however, please contact the nearest Maurice Chapman outlet to ascertain your closest supply source.

**THE MAURICE CHAPMAN GROUP PTY. LIMITED**


44 Dickson Ave, Artarmon, NSW. 2064. Phone 438-3111 • 150 Burwood Rd, Hawthorn, Vic. 3122. Phone 818-1730.

• Perth 446-5679 • Brisbane 44-7566 • Adelaide 272-8011

# The new BASF high precision cassette.
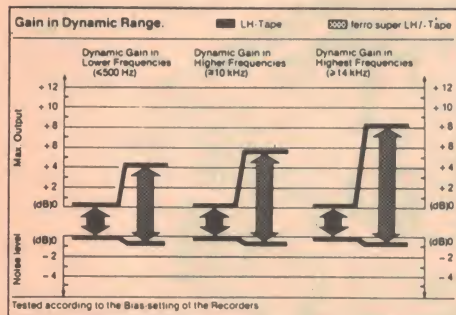
## An unbeatable case for buying The Green One.

Dubbed The Green One for ease of identification, the new BASF ferro super LH I displays high precision and performance throughout.



In the mechanics of the cassette, BASF has achieved new standards of azimuth precision, taking full advantage of the outstanding LH I quality.

A dense coating of super-fine


ferric oxide particles has produced a mirror-finish tape with extremely strong magnetic direction preference.

The end result—true Hi-Fi in the normal bias position I (Ironoxide or Fe 120  $\mu$ s EQ). Plus higher volume levels with minimised distortion.


One common cassette fault. Deviation in vertical position of the pins diminishes high-frequency output, which results in loss of sound brilliancy. Minimum tolerances ensure that no fault can occur with the new BASF ferro super LH I.

In the tough, screw-together polystyrene, precision moulded shell, slip sheets eliminate tape edge damage. A mu-metal shield blocks stray magnetic fields.

A felt pressure pad on a phosphor

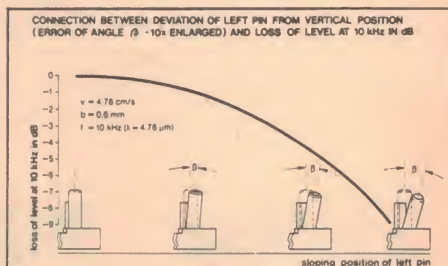

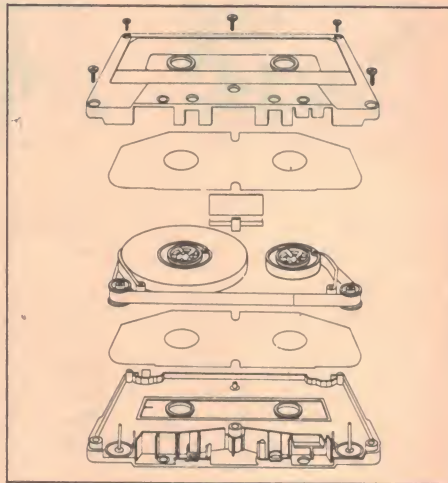bronze spring ensures precise head contact on any deck. Flanged roller guides on lubricated stainless steel pins provide precise tape feed and azimuth alignment.



The patented BASF Security Mechanism (SM) prevents scrambling of tape and guides the tape smoothly within the cassette. A large strong window gives clear visibility to the best BASF ferro super I tape yet.

So spend a little more, and get more for your money.

**Go for The Green One.**  
**Step up to Hi-Fi precision.**



**BASF**



**Quality across the range.**

## Accuphase C-7 moving coil cartridge head amplifier

Louis Challis found this unit so sensitive and accommodating he could hardly bear to part with it!

THE BEST moving coil cartridges have a clarity and transparency which is exciting to say the least. So it's not surprising that more and more manufacturers are adding at least one moving coil model to their range of moving magnet types.

This must be disconcerting for many audiophiles, because moving coil cartridges need an amplifier with a higher input sensitivity and signal-to-noise ratio than most conventional amplifiers or receivers can achieve at present. It's true that some amplifier makers do now provide a moving coil input stage, but this is usually only on their newest and most expensive models. If you already have a good amplifier you obviously don't want to replace it just so you can try out a different kind of cartridge, so you have to look for an alternative.

Some moving coil manufacturers offer a solution with a step-up transformer designed for their own particular cartridges, but many others do not. The Accuphase C-7 Head Amplifier is designed to fill this gap by providing an active preamplifier with a frequency response which is flat from 20 Hz to 20 kHz and only 0.5 dB down at 5 Hz and 100 kHz.

### Description


It's a simple unit, housed in a long, thin box with coaxial input and output sockets and a mains lead for 250 volt, 50 Hz operation. The metallic case is

sprayed in the same Hammertone colour as other Accuphase equipment and features an additional grounding wire to be connected to the main

amplifier to minimise earth loop problems.

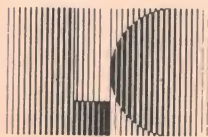The manufacturers provide very little detail or data with the unit, except a ►





Louis A Challis and Associates Pty Ltd

## MEASURED PERFORMANCE OF ACCUPHASE C-7 M/C HEAD AMPLIFIER

### FREQUENCY RESPONSE:

(-3dB)	Left	2.2 Hz to > 100kHz
	Right	2.3 Hz to > 100kHz

### SENSITIVITY:

(for 1 Watt in 8Ω)	Phono Pass	Left	0	Right	0 dB
	Phono Gain		25.4		25.7dB
	Overload M/C		20 mV		19 mV

### INPUT IMPEDANCE:

	Left	Right
Phono M/C	100	100 Ω

### OUTPUT IMPEDANCE:

Left	110 Ω
Right	110 Ω

### HARMONIC DISTORTION (M/C):

	100Hz	1kHz	6.3kHz
(Input of 5mV)			
2nd	-84.2	-88	-85.5 dB
3rd	-85.3	-96	-94.2 dB
4th	-95.2	-	- dB
5th	-	-	- dB
THD	0.007	0.0043	0.0044 %

### TRANSIENT INTERMODULATION DISTORTION: < 0.01 %

(3.15kHz square wave and  
15kHz sine wave mixed 4:1)

### NOISE & HUM LEVELS:

(re 1 Watt into 8Ω)	Phono Pass	-64 dB(Lin)	-82 dB(A)
(with volume control set for 1 watt output with:	Phono M/C	-67 dB(Lin)	-76 dB(A)
5mV input (Phono Pass)	(figures are degraded by high hum content)		
0.5mV input (Phono M/C )			

### MAXIMUM OUTPUT M/C:

260mV VRMS



## PHILIPS LOUDSPEAKERS

### PROFESSIONALLY DESIGNED SPEAKER KITS

If you are in the market for a \$2000 set of speakers with only a few hundred dollars in your pocket, we could have just what you want. The ETI 4000 Series Speakers — using Philips Drivers — compare very favourably with speakers costing twice to three times as much. If you are on a really tight budget you could consider the Philips AD12K12 kit — a 70 watts r.m.s. per channel 12" 3-way system — which you assemble completely in about 2 hours. A steal at under \$300 per pair. You can buy all components with or without boxes, any way you like. We have both the ETI 4000-I and II on display, as well as other Philips Kits. Come in for an audition, or write for further information.



# northpoint hi-fi

**WAGNER** ELECTRONICS  
SALES & SERVICE

100 Miller St, North Sydney.  
Ph 922-7780.

305 Liverpool Rd, Ashfield.  
Ph 798-9147.

warning that, because of the 100 dB gain that is possible from the input of this preamplifier to the output of the main amplifier, it is desirable to minimise unwanted electrical pickup. For this reason, they say the unit should be located as far as possible away from the amplifier, record player, cassette deck or any other equipment which radiates spurious and unwanted magnetic fields. They also take special care to point out the need to take the normal safety precaution of turning down the volume control of the main amplifier when making any connections on the head amplifier.

Accuphase claim that the fixed input impedance of 100 ohms provided by the C-7 matches the output impedance of every available moving coil cartridge, from the two or three ohms of some Ortofon models up to the 40 ohms of the EMT cartridges.

To make sure that you do not copy their design, they go to the trouble of encapsulating the 26 transistors, nine FETs, two integrated circuits and eight diodes in thermal epoxy. Frankly we do not believe the claim in the data sheet that this has been done to achieve a greater immunity to hum pickup. Without X-raying the encapsulated circuitry we could find out precious little about what it contains. The only other control provided is a bypass switch to disconnect the head amp from the rest of the amplification chain.

## In the lab

Objective testing of this unit proved to be more complex and difficult than we expected. In the first place, most of the manufacturer's claims were readily

substantiated in the first phase of our testing program. Frequency response was almost perfectly flat from dc to 20 kHz. The distortion figures, while they were excellent, were a shade higher than those claimed by Accuphase, although we did note afterwards that their performance figures were obtained at a lower input level than we used. The amplifier gain was 25.4 dB for the left channel and 25.7 dB for the right, which is a little different from the precise 26 dB claimed by the manufacturer. However, these differences are probably of only academic interest in the overall assessment.

We initially experienced considerable difficulty in the laboratory in achieving the order of hum and noise rejection that Accuphase claim — 72 dB A-weighted with respect to an input level of 0.1 millivolts. In fact we wasted many hours before recording our final figures of 67 dB unweighted and 76 dB A-weighted. We simply had no idea there were such high ac magnetic field strengths within our laboratory and spent a lot of time finding the right spot in which to perform the measurements.

Even so, these figures are quite commendable and we were also particularly impressed by the 19 millivolt overload point recorded for the input. In real terms I was unable to fault the objective performance of the unit.

## Subjectively

I was even more impressed by the C-7's performance with a series of moving coil cartridges which I used for my own subjective evaluation. The first of these cartridges was an Audio Technica AT30E with which I have been evaluating the unit for three months.

So satisfied was I with its performance that I must admit I was in no hurry to finish the review! Truthfully, my subjective assessment of this unit took far longer than any I have previously carried out. I played hundreds of records, including a wide range of new 'direct to disc' records, ten digitally recorded discs from Telarc and Sony CBS, a range of Sheffield records and many of my other favourites. On all of these the amplifier performed impeccably.

## Conclusion

The Accuphase C-7 Head Amplifier performs its function exceptionally well and provides a performance that neither subtracts from, nor adds unwanted effects to the performance of quality moving coil cartridges. These are now a force to be reckoned with in the latest generation of record players and the C-7 head amp is a convenient and very effective way of expanding the amplifier chain to accommodate them. ●

### ACCUPHASE C-7 MOVING COIL CARTRIDGE HEAD AMPLIFIER

#### Dimensions:



102 mm wide x 61 mm high x 350 mm deep

Weight: 2.5 kg


Price: \$530 rrp

Manufactured by Kenosonic Laboratory Inc., Yokohama, Japan.

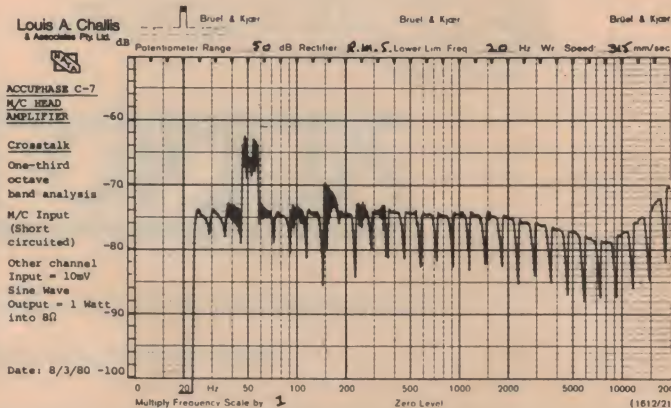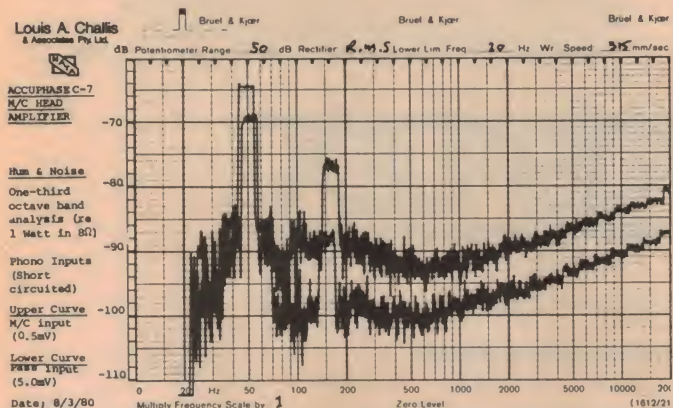Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.



# All audiophiles weren't created equal!

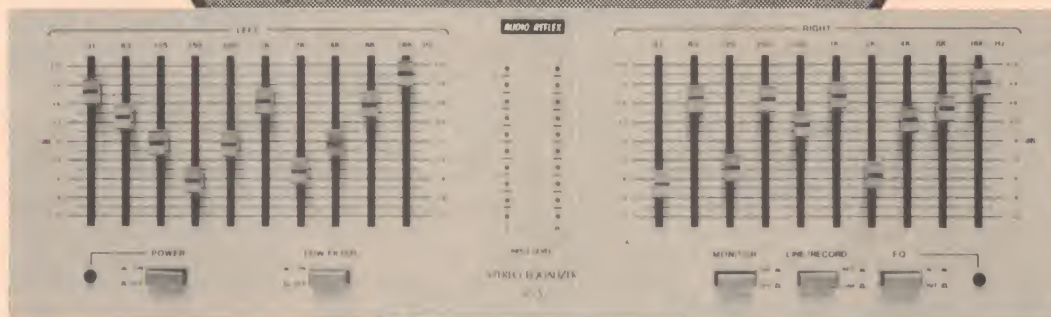

## Computer- balanced in your own home\*

No two listening rooms are the same. When you buy an Audio Reflex Equaliser, our technician uses a special computer to analyse your room and your stereo system. Then he makes the necessary adjustments to give you sound that's as close as possible to the way the recording engineer heard it in the studio. ONLY computer-analysis can accurately measure system response and room acoustics. ONLY Audio Reflex offers this service.

\*Capital cities only



## Be your own recording engineer

With an Audio Reflex Equaliser, you can emphasise your favourite instruments — subdue others. The Audio Reflex technician gives you a chart which allows you to return your equaliser to the correct settings at any time. He'll also show you how to adjust for variations such as big parties in your home.

## 5 Year Warranty

Audio Reflex warranty includes all parts and labour for 5 years from date of purchase. Full details of warranty protection are printed on the warranty card.

# AUDIO REFLEX

You'll hear more from us. Clearly.

7 Orchard Road, Brookvale 2100, NSW Telephone: 938 4188. Telex: AA20160

Hear more at your local Audio Reflex dealer.

28131

# Introducing a totally new concept in stereophones.

The new Koss HV/X high velocity stereophone represents a remarkable breakthrough in hear-thru stereophone design and performance. For the first time, Koss engineers have been able to create a lightweight, hear-thru stereophone that combines the transparency of high velocity phones with the superior bass performance of closed-type phones. The result is a breathtaking musical experience.

## CONTOURED VARIABLE-DENSITY EARCUSHIONS

While most lightweight, hear-thru stereophones have earcushions that fit against the ear, the new Koss HV/X features a unique, contoured, variable-density cushion that fits around the ear. Not only does this unique earcushion design create a far more comfortable stereo-  
phone but it has also allowed Koss engineers to create a dramatically better element



design as well.

These new variable-density earcushions are made up of a very porous material that is acoustically transparent at the perimeter of the earcushion yet compressed toward the center region. This varies the pattern of acoustic resistance over portions of the earcushions creating the proper seal for specific bass frequencies while al-

lowing the flow of middle and high frequencies at the perimeter of the earcushions.



## LIGHTWEIGHT ELEMENT

The uniqueness of the new variable-density earcushions made it possible

for Koss engineers to design a lightweight element that reproduces a Sound of Koss you have to hear to believe. Incredibly, even though the overall weight of the element was reduced, Koss engineers were able to develop a magnet with enough magnetic density to drive an extra large diaphragm. With a response range of 15 to 35,000 Hz, the new Koss HV/X will drive you into ecstasy and our competitors nuts.

## HEARING IS BELIEVING.

Slip into the new Koss HV/X or HV/XLC with volume/balance controls at your audio dealer soon. You'll like the best of both worlds: the open, airy, up-front sound of hear-thru stereophones and the deep, rich bass performance of closed-type stereophones.

*For more information on the HV/X, our full line of stereophones and loudspeakers or our new Koss K/4DS digital delay system, write to*



**ELECTRO-VOICE AUSTRALIA PTY. LTD.**

© 1980 Koss Corp

**KOSS® stereophones/loudspeakers**  
**hearing is believing™**

ELECTRO-VOICE AUSTRALIA PTY. LTD. 174 Taren Point Road, Taren Point, NSW, 2229. Phone (02) 525-8588.

**A ONCE-ONLY OFFER!**



# SUPERB REEL TO REEL TAPES

Dindy Marketing have a limited quantity of these EMI tapes available, **only for the duration of this offer** (unless sold out before the offer expires) so rush your order now. These tapes will not be offered again as EMI is ceasing production.

*NOTE: This offer is made by Dindy Marketing (Aust.) Pty Ltd and ETI is acting as a clearing house only. Cheques or money orders should be made payable to 'EMITAPE OFFER' and sent, together with the coupon (or a photostat or clear, handwritten copy of same), to Emitape Offer, ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011. We will then process your order and pass it on to Dindy who will send you the goods. Please allow up to four weeks for delivery.*

## Send coupon to: EMITAPE OFFER

ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011

Quantity .....	900 x 5/825 .....	\$ .....
.....	1800 x 7/825 .....	\$ .....
.....	2400 x 10 1/2/816 .....	\$ .....
.....	10 1/2" NAB reels .....	\$ .....
1 - 9 tapes	\$2.50	Packing & delivery: .. \$ .....
10 - 29 tapes	\$3.50	
30+ tapes	\$4.00	TOTAL: \$ .....

(Tapes can be mixed for quantity discounts)

Name .....

Address .....

..... Postcode .....

Cheque or money order .....

Or use your Bankcard 

4	9	6																	
---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

 Expiry Date ... / ... / ...

Signature : .....

## EMITAPE 816 MATT BACKED PROFESSIONAL AUDIO TAPE

The advantages of back-coated tapes — such as high spooling speeds and uniform wind under adverse conditions, together with the reduced risk of edge-damage — are already widely recognised. These advantages are frequently obtained, however, at the expense of other, no less important characteristics. The most significant adverse effects are deterioration in amplitude modulation noise, caused by imprint effect from the backing on to the oxide during storage, and a higher degree of head and guide wear.

The development of **EMITAPE 816** has been concentrated on eliminating these disadvantages while combining the benefits of matt backing with the stringent audio performance. **EMITAPE 816** is a standard play professional audio tape, its polyester base having a specially treated back coating.

**EMITAPE 816** is not recommended for use on recorders using pressure pads.

### AUDIO PERFORMANCE SPECIFICATION 38.1 cm/sec (15in/sec)

<b>REFERENCE BIAS</b>	1 dB over bias at 1 kHz (this condition is that with increase of bias current the 1 kHz output level has fallen by 1 dB from its maximum value).	
1. Sensitivity at	1 kHz	0 dB
	4 kHz	+1.5 dB
	10 kHz	+2.5 dB
	16 kHz	+4 dB
2. Bias current ratio at 1 dB over bias (at a frequency of 1 kHz)		0.87
3. Maximum Output Level for 3% third harmonic distortion at 1 kHz (Ref. 1)		+6 dB
4. Maximum Output Level for saturation at 10 kHz (Ref. 1)		+5.25 dB
7. The ratio of the 1 kHz Maximum Output Level to Bias Noise		74.5 dB full track (6.25 mm tape width)
8. The ratio of the 1 kHz. Maximum Output Level to Bias Noise		66 dB full track (6.25 mm tape width)
9. The ratio of the 1 kHz Maximum Output Level to print first pre-echo after storage for 72 hours at +20° C.		58 dB
Ref. 1	Relative to an RMS flux of 320 nWb/m tape width (32 mMx./mm.) at a frequency of 1 kHz.	
Ref. 2	Measured in accordance with the paper by E.G. Trendell entitled "The Measurement and Subjective Assessment of Modulation Noise in Magnetic Recording". Journal of the Audio Engineering Society, December 1969, Volume 17, Number 6.	

## Tapes available

EMITAPE 825 900ft (274 m) on 5" (133 mm) reels (quantity: 800)

EMITAPE 825 1800ft (549 m) on 7" (178 mm) reels (quantity: 4500)

EMITAPE 816 2400ft (732 m) on 10½" (267 mm) metal reels with NAB hub (quantity: 1100)

Metal Reels — 10½" (267 mm) with NAB hubs; boxed.

Tapes can be mixed for quantity discounts.

These prices are around half what the tapes were selling for originally.

## OFFER PRICES

	1 - 9	10 - 29	30+
900 x 5, 825 tape	\$3.99	\$3.69	\$2.98
1800 x 7, 825 tape	\$6.99	\$6.28	\$5.88
2400 x 10½, 816 tape	\$16.99	\$15.27	\$13.85
10½" Metal Reel —	\$9.97, any quantity.		

**Order now and ensure delivery before Christmas !**

**Offer closes 13 November**

## EMITAPE 825. LOW NOISE LONG PLAY PROFESSIONAL AUDIO TAPE

EMITAPE 825 is a low noise long play audio tape which was specially developed for professional studio mastering and broadcasting. This tape has an excellent signal to print ratio and a specially treated coating which gives extremely low head wear and low modulation noise. The wide frequency response obtainable from this tape ensures an excellent high fidelity performance when used in conjunction with any good quality tape recorder.

### AUDIO PERFORMANCE SPECIFICATION

	19.05 cm/sec (7½in/sec)	9.53 cm/sec (3¾in/sec)
Recommended Bias	1 dB overbias at 1 kHz (the value of bias used by the majority of professional recording and broadcast engineers)	The value of bias current required to record a 333 Hz signal which when reproduced gives an output level of +3 dB (Ref. 1a) with a third harmonic distortion content of 5%
Frequency Response (when compared with EMI Standard Tape S.4)	Within +/– 2 dB from below 31.5 Hz to 16 kHz	Within +/– 2 dB from below 31.5 Hz to 16 kHz
Maximum Output Level	+3 dB (for 3% Third Harmonic Distortion at 1 kHz (Ref.1))	+3 dB (for 5% Third Harmonic Distortion at 333 Hz (Ref.1a))
Maximum Output Level (for Saturation at 10 kHz)	–1 dB (Ref.1)	–7 dB (Ref. 1a)
Maximum Output Level (for Saturation at 10 kHz)	–1 dB (Ref. 1)	–7 dB (Ref. 1a)
Signal to Noise Ratio (a) Weighted in accordance with IEC 123A, BS3489-1962 (A Curve) and ASA Standard S1-4-1961 (A curve) using a measuring instrument with the same dynamic characteristic as a Standard Volume Indicator (BS3489-1962 and ASA Standard C16-5-1961)	66 dB (Ref. 2)	58 dB (Ref. 2a)
(b) Weighted using a filter and a quasi peak measuring instrument in accordance with DIN45405	57 dB (Ref. 2)	51.5 dB (Ref. 2a)
Ref. 1	Relative to an RMS flux of 320nWb/m tape width (32mMx/mm) at a frequency of 1 kHz.	
Ref. 1a	Relative to an RMS flux of 250nWb/m tape width (25mMx/mm) at a frequency of 333 Hz.	
Ref. 2	The ratio of the 1 kHz Maximum Output Level to Bias Noise.	
Ref. 2a	The ratio of the 333 Hz Maximum Output Level to Bias Noise.	
Note	The figures quoted are mean values and subject to manufacturer's tolerances.	


# B&W DM12

## THE UNOBTRUSIVE REVOLUTIONARY

We could have built something smaller, but we were determined to build a miniature speaker that rises way above the limitations hitherto imposed by a small enclosure. In particular, we wanted to achieve wider response and more realistic sound levels in the low frequency range. We also wanted safe power-handling capacity. Thanks to our unique resources in computer and laser technology and the sheer creativity of our design team, DM12 achieves all this and more.



## B&W LOUDSPEAKERS

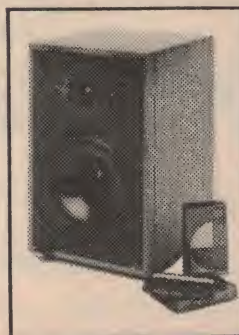

### It's certainly small.

Just 355mm (14 in) high x 220mm (8¾ in) wide x 270mm (10½ in) deep.

### 106dB.

That's the surprising peak sound pressure level DM12 produces from its 12 litre enclosure.

### Monitor standard.

Frequency linearity + 2 dB 85 Hz to 20kHz.

### APOC-protected.

B & W's exclusive audio-powered overload circuit protects against accidental damage or overload.

For further information see your B & W dealer or contact  
Convoy International Pty Ltd  
4 Dowling Street Woolloomooloo NSW 2011  
Telephone (02) 3582088

# MASTER CHECK

## VOLTAGE ANALYSER

Voltage indicated:  
6, 12, 24, 50, 110,  
240, 415 V  $\approx$



**NEW**  
**\$24** Plus 15%  
sales tax  
P & P \$2.00

### MASTER CHECK

- Cannot be over ranged.
- Indicates AC or DC Voltage.
- Automatic Voltage indication.
- Read off polarity at a glance.
- Designed for Australian conditions.
- 7 Voltage indication steps by L.E.D.'s
- Robust lightweight plastic construction.
- AC or DC Voltage Check from 6 to 415 Volts.
- Useable on battery operated devices to three phase AC.
- Available from Electrical Wholesalers throughout Australia.

**ALSO AVAILABLE** Multi-Check — Handy solid state continuity checker.  
Will check AC or DC Voltages from 4.5 to 415 Volts.

**BELL**

**BELL INSTRUMENTS PTY. LIMITED**

Garema Circuit, Kingsgrove 2208 NSW.  
PO Box 154. Tel (02) 750-6000.

74 Raglan Street, Preston 3072 Vic.  
Tel (03) 44-5021.

**Special offer \$26**  
PLUS \$2.00 POSTAGE/HANDLING

## Mini Alarm Car Clock



The new Omron Quartz Travel Alarm will fit in your brief-case, pocket or purse, and even stick on your bathroom mirror. As a digital car clock, it's superb. Special mounting tape is supplied to stick it to your dashboard. It's small, and because it's small it fits anywhere.

The Mini Alarm Car Clock measures only 62 (W) x 43 (D) x 9 (H) mm and has a small magic fastener, easel support on the back. Just set the alarm and the electronic beep will wake you up. The clock movement is totally solid state, and is a unique product of the latest Quartz technology. It is accurate to within twenty seconds per month (at normal temperature). It costs only \$26.00 plus \$2.00 postage/handling — a special price to our readers. Simply fill in the coupon below and mail today.

.....  
Complete the coupon and mail together with your payment to this magazine's Mini Alarm Car Clock Offer, G.P.O. C102, Sydney 2000. Make your cheque payable to Murray/Modern Magazines and endorse with your name and address.

Name ..... Address .....  
(Please Print)

State ..... Postcode ..... Please send me ..... (number of clocks)

I enclose my cheque/money order for \$ ..... (\$26 plus \$2.00 postage/handling) or please debit my

Bankcard No. .... Signature .....

ETI 98010

# PROFESSIONAL AUDIO EQUIPMENT

## MODEL 3002 — 2 CHANNEL POWER AMPLIFIER



### FEATURES

- 300 Watts per channel.
- Massive rear mounted heatsinks.
- Multiple speaker protection circuits.
- Peak output power meters.
- Constructed to withstand the tortures of 'On the road' use.
- Standard 19" rack mounting.
- Separate power supplies for each channel.
- Dual RCA input sockets to allow bridging to other amplifiers.
- Equally suited to Hi Fi use or P.A./Disco situations.

### BRIEF SPECIFICATIONS

Output Power — 300 watts/channel into 8 ohms.  
 200 watts/channel into 4 ohms.  
 Frequency Response — 20Hz to 20kHz  $\pm 0.5$ dB.  
 Hum and Noise — 105dB below rated output.  
 Harmonic Distortion — Less than 0.05% to 80 watts.  
 Less than 0.15% at rated power.  
 Input Sensitivity — 1.0 volts for rated output.  
 Dimensions — 482mm x 133mm x 340mm.  
 Weight — 20 kgs.

**\$452.00 plus freight.**



## MODEL 2801 — 1/3 OCTAVE EQUALISER

The 2801 is a single channel graphic equaliser that divides the audio spectrum into twenty-eight one third octave bands. Each frequency segment is controlled by a slider that provides up to  $\pm 10$  dB of adjustment in standard ISO steps.

The 2810 was designed primarily to compensate for any deficiencies in the linearity of speaker systems, acoustic peculiarities of the hall or listening room, and inadequacies of program source quality. In P.A. application the equaliser may be used to improve sound quality and increase intelligibility by attenuating problem frequencies that cause ringing, boominess, or other disruptive resonances that occur in acoustically difficult rooms. The 2801 allows sound systems to be "tuned" according to the special acoustics of a room, to maximise output and minimise feedback. As a creative tool in sound recording or re-recording the 2801 allows complete freedom in contouring response over the complete audio spectrum from 31.5 Hz to 16 KHz.

**\$198.00 plus \$3.00 freight.**



## MODEL 2010 — 2 CHANNEL EQUALISER

The 2010 is a two channel graphic equaliser featuring ten adjustable controls on octave centre frequencies (independent for each channel). Each control provides up to  $\pm 14$ dB of adjustment. Each channel is also equipped with a level match control giving an overall gain of adjustment of  $\pm 14$ dB.

The functional versatility of the 2010 equaliser is unsurpassed. Eight modes of operation are available from the push button switches on the front panel.

Included amongst these are the ability to equalise both recording and playback when dubbing tapes.

The 2010 has been designed to be compatible with all commercially available equipment and is ideal for use in a Hi Fi system or P.A. system.

**\$162.00 plus \$3.00 freight.**

*For further information, please send a 35c stamp  
 for full specification sheets, or call at our showroom for a demonstration.*

**jaycar**  
 PTY LTD

**380 SUSSEX STREET, SYDNEY, NSW**  
**P.O. BOX K39, HAYMARKET 2000**  
**TEL: (02) 264-6688**

# Your last chance. . .

## our 'win a trip to Hong Kong' contest closes this month. Get your entry in now!

### HERE'S HOW IT WORKS:

We want to know what you the amateurs want from your hobby so that we, as a company, can serve you and Australia better. So we're asking you to tell us, in fifty words or less, 'The best way that Dick Smith Electronics can promote the fantastic hobby of Amateur Radio to the benefit of Australia'.

Entry to the competition is only open to purchasers of any Yaesu equipment from Dick Smith stores or authorised Dick Smith Yaesu resellers, between 1/8/80 and 1/11/80 - enter and you could win and be on your way to Hong Kong.

Entries will be judged initially by a panel from Dick Smith Electronics to produce five finalists: these will be judged by Neville Williams, MIREE, Editor-in-chief of Electronics Australia magazine.

The winner will be notified by Dick Smith, and will be announced in Electronics Australia and Electronics Today International.

So if you're thinking about buying Yaesu, why not buy it in the next few weeks: of course, only from Dick Smith Electronics or authorised Dick Smith Yaesu re-seller!

### RULES AND CONDITIONS

Entries will only be accepted on the official entry form, which is available only with the purchase of any item from the Yaesu range from a Dick Smith store or Dick Smith authorised re-seller.

All entries must show the model number and serial number of the item purchased, (if applicable), and be signed by the store manager or authorised person.

In the space on the entry form, write in one paragraph of not more than 50 words.

'The best way that Dick Smith Electronics can promote the fantastic hobby of Amateur Radio to the benefit of Australia'.

Post your entry to: Amateur Radio Contest

Dick Smith Electronics

PO Box 321,

North Ryde NSW 2113.

Entries close at 5pm on Monday, 3rd November, 1980. Entries received after this date will not be considered. Final judging will take place on 10th November, 1980. The judge's decision will be final and no correspondence will be entered into.

The winners flight departs from, and returns to Sydney, the winner must travel to Sydney at his/her own expense. All entries become the absolute property of Dick Smith Electronics Pty. Ltd who may use such entries as they see fit.



## YES, we have the incomparable Yaesu FT107M/DMS

**ALL THIS FOR ONLY**


**\$1278<sup>00</sup>**

Cat. D-2871

The FT107M/DMS is the rig you've been waiting for. Advanced engineering plus rugged design enables this rig to have the 'edge' on the opposition. Features include variable IF bandwidth, audio peak and notch filters, RF speech processor, full coverage from 160 through 10 metres, plus WWV/JJY on receive. It is also fitted with the new WARC frequencies. The AC power supply comes as a plug-in module and is ready fitted in the case. The FT107M/DMS also comes with memory. These plus other outstanding features place the FT107M/DMS in the forefront of what the serious amateur requires from his hobby.

### THE NEW YAESU

Cat. D-2887

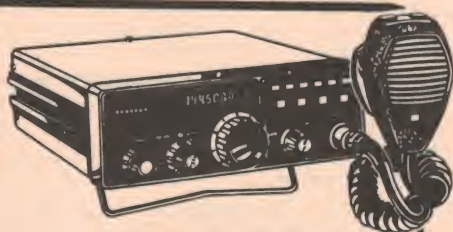

The FT480R is coming — the all new FT480R has sophisticated microprocessor control circuitry to bring new dimensions in flexibility to you — today's 2 metre operator.

At the time of going to press, these units were on the high seas, check with our stores NOW — they could very well be in stock.

**Priced at only \$543<sup>00</sup>**

### TERMS AVAILABLE

**FROM \$138 DEPOSIT & \$38.32 OVER 48 MONTHS**

**SPECIAL NOTE:** Finance company regulations restrict finance to 'approved personal customers' only. However, if you wish to 'pay off' a Yaesu and cannot call into one of our stores, you can always ring us and order your Yaesu by Bankcard. All you do is quote your Bankcard number, name and address, and we charge your Bankcard account. What is more, we'll send your new Yaesu anywhere in Australia for only \$6.00 road freight: that's below what it costs us!

# NOW, more than ever, it pays to buy Yaesu from Dick Smith





## Heard Island expedition gets up steam

**The Heard Island DX Association is making steady progress towards its aim of reactivating the uninhabited subantarctic island and is now confident of success in early 1981.**

As we reported in the July ETI, the idea is to mount a full scale DX-pedition and spend a minimum of fourteen days actually on the island. It is intended to offer a place on the expedition to a professional scientist who will be able to assist the DXers with his experience of Antarctic conditions as well as pursuing his own research.

The Australian government have advised that "...there is no objection in principle..." to the activation of Heard although they have stipulated a number of conditions that must be met to ensure the safety of personnel and the protection of the native fauna and flora.

Negotiations are underway to charter a vessel for the voyage,

which is expected to take about ten days each way and will be the main expense the expedition has to meet.

Donations so far received amount to about \$800, roughly what was anticipated following the initial low-key announcements of the project. Now that the mission is 'all systems go', the organisers expect the flow of funds to increase.

If you would like more information, or can help with cash or equipment, please write to:

**Jim Smith,  
Heard Island DX  
Association,  
P.O. Box 2053,  
Konedobu,  
Papua New Guinea.**

## Amateur radio weekend

**The Blue Mountains of NSW will be the delightful springtime setting for an amateur radio weekend scheduled for the 17th to 19th of October.**

The function, which will include courses in theory, regulations and Morse code, has been specially designed to help people studying for the November novice examination, but the organisers emphasise that anyone with an interest in amateur radio will be welcome.

An amateur radio station will be continually in operation, so that scouts and guides will have a chance to participate in the world-wide jamboree-on-the-air.

The all-in charge for food and accommodation is \$22 for

adults, \$18 for full time students and instructors, \$7.50 for children two to four years old and \$2.00 for the under-tuos.

The exact location is Camp Carey, which is about one and a half kilometres walk from Wentworth Falls railway station. All those interested in attending, instructing or supervising are invited to write to:

**Amateur Radio Weekend,  
Craig Robinson VK2PDF,  
P.O. Box 35,  
Croydon, NSW 2132.**

Phone (02) 74-0316.



## High power combiners

**Five high power band II TV/FM combiners have been built for Telecom by Antenna Engineering Australia.**

The picture above shows the unit which will be installed in Bunbury, Western Australia, where it will enable the two 20 kW transmitters of TV channels 3 and 5 to be combined with a 10 kW FM transmitter

to a common antenna.

Design features include a channel separation of 800 kHz, which together with the modular design allows for future system expansion with minimal disturbance to existing services.

## Club News from SA

**The Naracoorte district of South Australia now has its own amateur radio club whose callsign is VK5ARN.**

The organisation, which has an active membership of about twenty at present, is officially known as 'Naracoorte Amateur Radio Club' and its address is P.O. Box 45, Naracoorte, SA 5271.

Meetings are held on the

fourth Friday of the month at 8.00 pm CST and the venue is usually the Department of Further Education buildings in Naracoorte, but it's advisable to check this with the DFE on (087)62-2199, or Rob Smith VK5NRR, on (087)62-2134.

## ... and Brisbane

The Brisbane Amateur Radio Club informs us that they now meet at S.E.S. — 'C' Group Headquarters, on the corner of School and Ipswich Roads, Yeronga, on the second and fourth Fridays of each month at 1930 EAST.

## Audio impulse noise limiter

THIS CIRCUIT is particularly intended for those interested in DXing, that is, listening for distant radio stations. However, the same circuit has other uses such as reducing the scratch level on very old records (Note that this is not the normal type of scratch filter circuit normally associated with hi-fi equipment). It also has uses in PA equipment where it can limit the input to the final stages and prevent overload distortion; distortion will still be present when an overload occurs but it is not as objectionable as that usually produced.


The circuit is designed to take almost any audio input but the output will have all peaks above a certain level (which can be adjusted) eliminated.

Anyone who has listened to a really weak radio signal will know the limitations imposed by the noise. At any one time there are literally thousands of thunderstorms taking place somewhere in the world and sensitive receivers will hear lightning a considerable distance away. Often, the level of noise is much higher than that of the radio signal that is wanted.

Apart from lightning, there is more local interference such as that produced by poorly suppressed motor cars or electric motors. With a powerful radio signal these are just not noticeable since the noise level is well below that of the radio signal, but on distant stations the noise level all but buries the signal.

The circuit can either be wired into a receiver circuit or directly from a headphones socket in which case the headphones are wired to this unit instead. If wired into a circuit permanently, RV1 should take the place of the normal volume control and the output (RV2) should be control slider. An extra control plus a switch will also have to be mounted on the receiver front panel. The circuit can either be left in permanently, as at most settings it will not affect the signal, or it can be switched out.

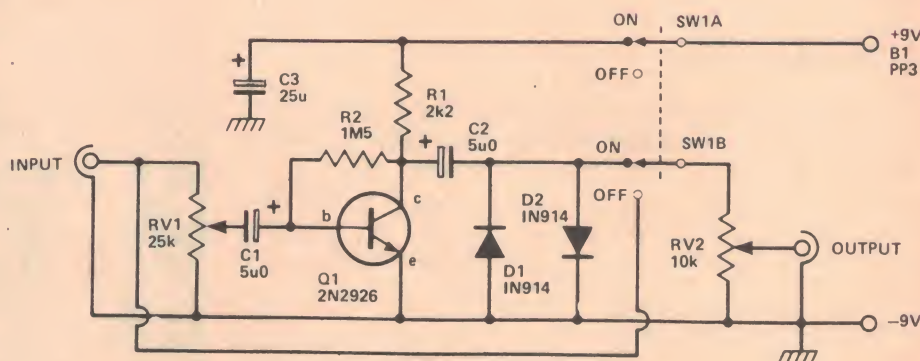The output of the receiver, which, as we have said, can be from the volume control or the headphone socket, is



taken to the input and amplified by Q1 which is connected in the common emitter mode. This transistor will considerably increase the audio level and this is applied via a dc blocking capacitor, C2, to the two silicon diodes D1 and D2.

In the normal way these diodes will not have any bias voltage applied across them and so they will present a high resistance, and will not affect the output in any way. However, as soon as the output from the amplifier exceeds about 0.6 V the diodes will conduct and short the output to the line. Two common (0V) diodes are needed, connected 'back-to-back' so that both positive and negative going peaks are shorted out.

The idea of the amplifier is to make sure that whatever the input level across RV1, it can be amplified so that at least 0.6 V can be applied across the diodes. Since RV1 is adjusted so that the level is always the same, a volume control has been included in the circuit so that the output level can be controlled in the usual way; this is accomplished by RV2.

To limit the noise, the input level is increased until the audio signal that is wanted is just distorting and then backed off slightly so that no distortion is heard on peaks above that level. 'Spikes' will hardly be heard in the output as they will be clipped by the diodes above the preset limit. RV2 is

then used as a volume control.

If RV1 is adjusted well below the limiting level and RV2 is adjusted for normal listening levels, the circuit has no effect. However, it is a simple matter to include SW1 which will bypass the circuit. The supply voltage can be taken from a battery as shown in the circuit, the current drain being very small, or from the receiver's supply. If this is transistor operated with 9 V then there will be no difficulty but if the receiver is a valve type or uses a supply potential higher than 9 V then a suitable dropping resistor from the HT supply rail will have to be included. The value will depend on the supply voltage but for 250 V a resistor in the order of 150k ohms will be about right; this should be connected between the HT line and the slider of SW1a.

The effect of the noise limiter is quite remarkable and by switching the circuit in and out it is possible to compare the results. The noise will still be there but not at an annoying level and the signal will be very, very much clearer. ●

SHORT CIRCUITS is a feature that lies somewhere between Ideas for Experimenters and complete Projects. Generally, the items published in Short Circuits will involve tried circuits that have not necessarily been fully developed, but fairly complete details are included as a guide to readers. Unfortunately, owing to the nature of these items, we cannot give further details other than what is provided in the article. Contributions for Short Circuits are always welcome.

## TRY THIS EXCITING HOBBY!

Build your own Organ, at half the cost of a ready-built Organ.

### WITH WERSI ORGAN KITS

Wide range of models:  
COMBO to large CHURCH ORGANS



Also

- STRING ORCHESTRA
- BASS SYNTHESIZER
- ELECTRIC PIANO
- and the famous WERSIVOICE ROTATION SOUND

All available from:

**CLEFTRONICS PTY. LTD.**

9 Florence St., Burwood, Vic. 3125


Phone: (03) 288-7899

Catalogue 104 pages in colour — \$3.00 (incl. postage).  
Klaus Wunderlich Demonstration Record, music only with jacket notes — \$7.00 (incl. postage).

# 35 years young

and still on top

## NEW CRYSTAL MARKER OSCILLATOR

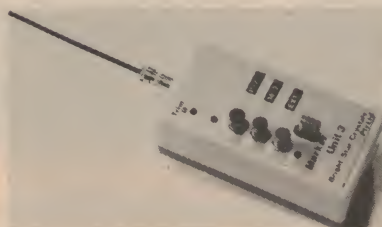

Marker frequency from 2MHz to 20MHz

Manufacturers of

**PIEZO ELECTRIC CRYSTALS**  
Contractors to Federal and State Government Departments.

**REPRESENTATIVES:**

**NSW:** J. E. Waters,  
11 Salisbury St, Botany. 2019.  
Ph 666-8144.

**SA:** Rogers Electronics,  
65 Magill Rd, Stepney. 5069.  
Ph (08) 42-6666.

**QLD:** Fred Hoe & Sons P/L,  
246 Evans Rd, Salisbury North.  
Brisbane. Ph 277-4311.

**WA:** Westest Electronics,  
71 Jean St, Hamilton Hill. 6161.  
(Mail only) Ph (09) 337-6393.

**TAS:** Dilmond Instruments,  
PO Box 219, Bellerive. Hobart.  
Ph 479-47-9077

Send SAE for new catalogue or quote for your requirements.







## Bright Star Crystals Pty Ltd

PO Box 42, Springvale.  
Ph (03) 546-5076 Telex AA36004
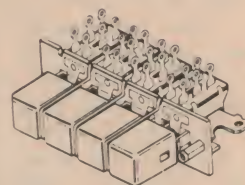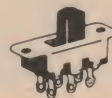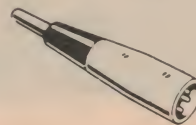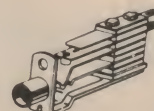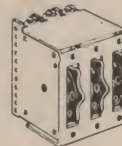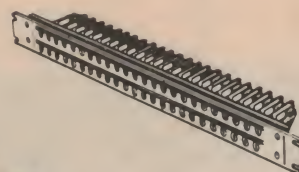
## SWITCHCRAFT

CONNECTORS & ELECTRONIC COMPONENTS

Superb quality and reliability from one of the oldest and most experienced manufacturers in the U.S.A.



**AUSTRALIAN DISTRIBUTORS**

**AUDIO TELEX COMMUNICATIONS PTY. LTD.**

**SYDNEY**  
1 Little Street,  
Parramatta, 2150  
Tel: 633 4344

**MELBOURNE**  
7 Essex Road,  
Mt. Waverley, 3149  
Tel: 277 5311

**BRISBANE**  
394 Montague Road,  
West End, 4101  
Tel: 44 6328

## SX-200 VHF UHF / HF RECEIVER

AM and FM

\$479



### Breakthrough in Scanning Receiver Technology.

The new SX-200 represents the latest STATE-OF-THE-ART technology in the development of Scanning Monitor Receivers. It has many features that previous have not been available on receivers of its type.

For example the tremendous frequency coverage, which encompass all of the following bands:— HF & UHF CB, 27 & 155MHz MARINE, Australian LOW BAND, AIRCRAFT band, VHF SATELLITE band, 10Mx, 6Mx, 2Mx and 70Mx AMATEUR, VHF HIGH BAND and UHF TWO-WAY band. Other features include Automatic detection of am or fm on all bands. Squelch Circuitry that can be used to LOCK OUT carrier only and spurious signals. Fine Tuning control for off channel stations. 240 VAC plus 12VDC operation. Squelch Operated Output that may be used to trigger a tape recorder or channel occupancy counter and accurate Quartz Clock.

Write for a brochure or drop in for a demonstration of this remarkable receiver.

**G.F.S. ELECTRONIC IMPORTS**  
15 McKEON ROAD, MITCHAM, 3132.  
(03) 873 3939

A unique individual —

# Radio astronomy's original pioneer — Grote Reber

by Roger Harrison VK2ZTB

I was surprised to learn last year that Grote Reber, virtually the 'founder' of the science of radio astronomy, lived and worked in Tasmania. I had the rare opportunity to meet him in June and to talk about his work.



THE SCIENCE of radio astronomy is not fifty years old, yet it has had a more profound influence on our knowledge of the universe and the fundamental physics of nature than has Galileo's invention of the optical telescope.

In the late 1920s, a young engineer from Bell Telephone Laboratories, Karl Jansky, was set the task of investigating the cause of interferences on transoceanic telephone links. Between 1929 and 1932, with his "merry-go-round" antenna, he made a series of observations. Along the way he detected a source of noise that appeared to be fixed in space and which came from the centre of our galaxy. Upon the completion of his research and the publication of a scientific paper, Karl Jansky was transferred to other work. He did not pursue the matter further and the significance of his discoveries was not realised by the astronomers of his day.

Some years later Grote Reber was looking for something "a little more exciting" to extend his hobby of amateur radio. He had come to know Karl Jansky, who suggested to the 22 year old Reber that he "look to the heavens".

Reber designed and built the world's first 'radio telescope', a 10m diameter

parabolic dish, constructed of wood and galvanised iron sheeting. He designed and prefabricated every part prior to assembling the dish in his back garden. That dish is preserved in the Smithsonian Institute's museum in the US.

Grote Reber first attempted observations near 3000 MHz but results were inconclusive, largely owing to the limitations of the technology of the time. He subsequently modified his equipment for use on 900 MHz and later 160 MHz, eventually succeeding in making what was the first 'map' of the sky ever to be completed using radiation other than that of the visible spectrum. He also detected and described radio emissions from the sun.

The science of radio astronomy was born.

Reber's observations were taken up and extended by others following publication of his results, but work was interrupted by World War II. Following the war, interest in radio astronomy burgeoned, propelled by the explosion in technology as a result of the war effort. Whilst most workers in the young science headed for higher and higher frequencies, Grote Reber thought he might go in the other direction. In the late 1940s and early 50s, it was thought

that the lowest possible observation frequency was about 10 MHz, a limit set by the 'opacity' of the ionosphere — the region of ionised gases extending from about 100 km to about 800 km that encircles the earth and refracts radio waves, permitting communications over long distances on the 'shortwave' bands between 1 MHz and 30 MHz.

Reber was interested in what the sky 'looked like' at frequencies below 3 MHz, but many of the "... experts of the day, self-appointed and otherwise ..." said it would be "impossible" to make observations at these frequencies. Firstly, the ionosphere 'got in the way' like an invisible curtain or shroud, and secondly interference from man-made signals, along with atmospheric noise, would mask even strong cosmic signals.

Fortunately, Reber, having a determined nature (a "cussed streak", as he puts it) took no notice of "... these Cassandras ..." and set out to thoroughly research the problems of making observations below 3 MHz.

He sought to find a 'window' through the ionosphere, where the vertical incidence critical frequency (that frequency where a signal beamed directly overhead will pass through the ionosphere)

dropped below 1 MHz on occasions. He made a search of the available ionospheric data (ionospheric research was then itself still a fledgling science) and found several regions around the world where the ionosphere behaved as required. However, there were a few restraints. He had to choose an area that was remote, to be away from sources of man-made noise and interference, but in a 'civilised' country so that he could avoid any political problems and build a suitable antenna without incurring large transport and construction costs. Climate was another factor in Reber's choice.

He chose the highlands of Tasmania.

## Meeting the man

I was introduced to Grote Reber on a cold, windswept afternoon last June. It was the shortest day of the year and I had driven from Launceston with a friend of Grote, Jim Davis, VK7NOW, and Jim's friend Bill Carter, VK7AK, who knew the mountain roads like the back of his weatherbeaten hands.

We arrived at the house Grote rents from a neighbour to find him sawing timber for the 'solar house' he's working on — of which more later. We discussed the project briefly and then drove to the radio astronomy installation just a handful of kilometres away. The casual observer, if he noticed at all, would no doubt be mildly curious about the lines of stark, grey poles set up some distance from the road on an expansive tract of flat land but there is little to give away their purpose. The entrance to the 'observatory' is unprepossessing and unmarked — just another paddock gate. A 3 km long dirt road, broken by several cattle grids, leads to the small hut located in the 'centre' of the antenna array. An ingenious sign at the first cattle grid says "Warning: Radio Astronomy". Grote says it's quite effective in "...keeping out the idly curious".

At the hut, Grote Reber gave us a description of his work and the equipment he uses and has used. He talks in a clear, well-reasoned manner and his mid-west American accent is still strong. It's a fascinating story that he tells.

## What and how

Reber came to Australia in the early '50s and searched out a suitable site for his antenna. This was to be an array covering some 400 acres, consisting of 128 dipoles centred on a frequency near 2 MHz!

Construction commenced in 1953 and Reber began observations the following year. The whole structure, supported on a series of locally-felled eucalypt hard-



Current receiving equipment is all solid state. The antenna feedline can be seen to the right, chart recorder on the left.

wood poles each some 20m high, was erected on a level area on a farm located in a natural depression in the mountains east of Lake St. Clair.

The entire array was constructed on a "shoe string" budget, on money obtained from a research grant, with the assistance of local people. A great deal of effort was made to ensure that the structure would last 20 years or more. The poles are clearly still in good condition and should exceed the design life by a wide margin.

The 128-dipole antenna array is an 'aperture synthesis' type and has a beamwidth of 7°! In its original configuration the beam pattern could be 'steered' electronically by changing the phasing on the network of antenna feeders. While it sounds simple enough, the job had to be done by physically moving a series of clip-on shorting straps on the open-wire feedlines. This task takes two men about half a day!

The array could be set to 'view' a particular sector of the sky, the rotation of the earth 'sweeping' the beam across the selected path. The beam can be steered in elevation from near the northern horizon, through the zenith ('straight up') and almost to the southern horizon.

Each dipole in the array has been constructed to cover the range between about 1800 kHz and 2000 kHz. This is done using a cunning technique involving the antenna length and a specially-constructed tuned matching transformer that provides a response similar to a double-tuned circuit.

Each dipole is cut a little 'short' for the desired operating frequency and its feedpoint exhibits a capacitive reactance along with the antenna's characteristic radiation resistance. The dipole feedpoint is tapped onto a large, high-Q inductor that resonates near 2 MHz with its own self-capacitance and the capacitive reactance of the

antenna. Inside this coil, and thus tightly coupled to it, is another which is tuned by a variable capacitor. The open-wire feedline to the rest of the system is tapped onto this coil to provide the desired impedance match. The whole assembly forms an over-coupled transformer which exhibits the classic 'double-humped' wideband response. Grote carefully designed this transformer arrangement to have minimum loss (about 0.5 dB) and an acceptably 'flat' response (2 dB, or less, variation) across the band of interest.

128 of these assemblies were constructed, each housed in a weatherproof box made of galvanised iron sheet with ceramic feedthrough insulators for the feedline connections. Most were disassembled from the antenna system and stored some years ago.

Grote Reber has a self-confessed "obsession with measuring things". After all, isn't that what radio astronomy's all about? True to form, he *measured* the variation in ground resistance beneath his antenna array, plotted equal-resistance contours and calculated the overall ground resistance.

The receiver and recording system are housed in a small hut located near the centre of the large array. Power is obtained from batteries, which was some problem with the original receiver system as it used valves! About 18 years ago Grote constructed a solid-state receiver which is still in use. It is considerably smaller than the old valve 'monster' which took up the whole of the small table provided for the purpose. The receiver is tunable so that an observation frequency can be selected which is clear of ground wave propagated (and some ionospherically propagated) signals. The receiver only has four stages (plus an audio stage for headphone use) and includes several selectable bandwidths and integration times on the detector output. Hooked ▶

# Don't let modern technology pass you by!



## Learn Microprocessor Programming and Application Techniques

If you're involved in scientific or electronic pursuits, microprocessors are becoming a way of life and a dominant factor in your success or failure. The EE-3401/ET-3400 self-learning program and accompanying computer trainer is the easy, effective way to learn about these powerful devices. The program uses Heath's proven self-instructional techniques including programmed instructions and audio-visual aids to teach computer programming, microprocessor operation, interfacing and related topics.

**This self-instruction program covers microprocessor basics, computer arithmetic, programming, interfacing and much more. It assumes a knowledge of electronics equivalent to Heath's Digital Techniques Program.**

Using Heath's proven self-instruction techniques the EE-3401 guides you, step by step, through the complexities and power of machine language programming, hardware I/O interfacing and microprocessor theory and design applications.

The microprocessor course is organised into 10 learning units as follows: 1: Number Systems & Codes, 2: Microcomputer Basics, 3: Computer Arithmetic, 4: Introduction to Programming, 5: The 6800 Microprocessor—Part 1, 6: The 6800 Microprocessor—Part 2, 7: Interfacing—Part 1, 8: Interfacing—Part 2, 9: Programming Experiments, 10: Interfacing Experiments. Each unit is complete with introduction, unit objectives, activity guide, experiment, examination and examination answers.

The EE-3401 is complete with 62 electronic components required to complete the experiments. These components include two 2112 256 x 4-bit RAM's, 6820 PIA interface chip, 1406 d/a converter, 741 and 301 op amps and a variety of other microprocessor-oriented devices. The ET-3400 Computer Trainer is required for the experiments in the Microprocessor Course.

Course EE-3401

\$155.00

## Keep up to date with Microprocessor Self-Instruction Program

### Microprocessor Trainer for EE-3401 Program



Functioning as a miniature digital computer, the ET-3400 Microprocessor Trainer is essential for the experiments in the EE-3401 self-instruction program. After completing the program, the ET-3400 is ideal for breadboarding, prototyping and system design.

The ET-3400 features a built-in 1K ROM monitor program for controlling unit operation; 6-digit hexadecimal 7-segment LED display for address and data readout; 17-key hexadecimal keyboard for entering programs and data. Has 256 bytes of random access memory (RAM) built-in, expandable to 512 bytes with the RAM's supplied in the EE-3401 program. Also has 8 buffered binary LED's for display of breadboard logic states, 8 SPST DIP switches for binary input to breadboard circuits, a breadboarding socket for prototyping, interfacing and memory circuits.

All microprocessor address, control and data busses are buffered and terminated on the front panel for ease of connection to prototype circuits. There's also provision for a 40-pin external connector to extend memory and I/O capacity. Built-in +5, +12 and -12 volt power supplies.

Kit ET-3400

\$347.00

### Microprocessor Trainer Accessory

The ETA-3400 gives you the additional I/O and memory you need to turn your ET-3400 Microprocessor Trainer into a complete, personal computer system. It provides an audio cassette interface so you can store programs on convenient cassettes. It also provides an additional 1K bytes of memory so you can run longer and more sophisticated programs through the ET-3400. The memory can be expanded to 4K bytes with the optional 3K chip set (ETA-3400-1). A serial I/O with EIA 20mA loop format provided in the ETA-3400 accessory lets you hookup a video terminal such as the H9. The new ROM monitor-debugger program provided with the accessory lets you implement the standard trainer monitor functions through the external terminal. Memory locations can be examined or changed, break points can be initiated, and program debugging can be accomplished with a single instruction step feature. A tiny BASIC interpreter is provided in ROM to let you do actual programming using the BASIC language. 11" W x 3" H x 12" D (279 x 76 x 305mm).

Kit ETA-3400

\$270.00

ETA-3400-1, Optional 3K Chip Set

\$ 86.00

NOTE: a terminal such as the H9 is required to operate in BASIC or with the new monitor.

## ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for \$..... is enclosed plus \$7.00 for package and post.

Name .....

Address ..... P/Code .....

- ☐ Course EE-3401    ☐ Kit ET-3400    ☐ Kit ETA-3400  
☐ ETA-3400-1    ☐ Please send me free catalog.

Send to: W. F. Heathkit Centre  
 220 Park St., South Melb. 3205. Phone 699 4999.

WF716/80

onto the output is a simple spring-driven chart recorder used to collect the data. Grote also uses an outboard BFO to detect the presence of weak signals that may interfere with his measurements.

If you tune around 2 MHz of an evening you'll find the region 'alive' with signals. How does Grote Reber hear the stars? It works like this: When the critical frequency of the ionosphere above his antenna dips below 2 MHz, all those signals that usually 'bounce' off the ionosphere no longer have any ionosphere in the region to 'bounce' off. The ionospheric curtain 'withdraws', all those interfering signals head off into space and the cosmic noise 'comes in'. It sounds like the 'hiss' of a radio receiver not tuned to any signals. Grote Reber estimates the cosmic noise to be around 20 microvolts at the antenna terminals of his receiver.

The ionosphere will only 'open up' at certain times, however. These times are greatly influenced by the diurnal (daily), and seasonal cycles of ionospheric activity and the longer term influence of the solar activity cycle which has 'peaks' and 'troughs' roughly spaced at 11 year intervals.

During a trough, or minimum, in solar activity, the ionospheric critical frequencies are much lower than during a peak, or maximum. As a consequence, Grote Reber can only make his observations during a solar minimum and suitable conditions generally last only 18 months or less. To make matters worse, the critical frequencies are only low enough during the winter months and at night — generally between 11 p.m. and 3 a.m. or so!

Grote made his first observations during the winter of 1954, a solar minimum year. He then had to wait until 1963-64 for the next solar minimum! From data compiled during those observing years, he built up a 'map' of the sky at a wavelength of 150 metres — quite an achievement, since the longest wavelength observations to date had been at a wavelength around 10 metres (about 30 MHz). His results were published in *The Journal of the Franklin Institute (USA)* in 1968. He last made observations during the solar minimum of 1975-76 and he's currently waiting for the next solar minimum (due around 1986 or so).

In the meantime, a curious limitation has arisen. It seems that long term solar activity is reducing the period over which he can make observations and the number of days during that period when the critical frequencies are low enough. The 'smoothed sunspot number' (a statistical measure of solar activity) during the 1954 minimum was as low as



The 'solar house' Grote Reber is constructing in Tasmania. He designed and prefabricated the complete framework from oregon he bought direct from a mill in Oregon, USA, and imported here.

two but during the minimum just past it was greater than 10, with a consequent general increase in the ionospheric critical frequencies.

Quite undaunted, having proved the "Cassandras" conclusively *wrong*, Grote is preparing for the next minimum and another series of observations during those long, cold Tasmanian winter nights.

### Other projects

The radio astronomy observations at 150 metres wavelength don't occupy all of Grote's time. He is employed part of the time by a local division of the CSIRO in a field quite removed from radio astronomy. He's also engaged in constructing and researching an electric car — this project is currently in America undergoing wind tunnel trials; he spends part of his time each year in the US. Apart from that, he is currently engaged in constructing a 'solar-powered' house which was partly completed when we saw it on our visit. This project is typical of his thorough, carefully thought-out approach to everything he does. The frame is timber and was completely designed and prefabricated prior to erection. He sought a local supply of oregon for the frame but found the timber offered of too poor a quality. On a trip to America last year he bought a container load of oregon and had it shipped to his Tasmanian address! Not only did he get the quality of timber he wanted, but he saved a considerable amount of money in the process.

The house is a two-storey structure with a slanted roof and the largest external wall facing due north. This wall is made up of 102 'cells'. About 12 are used for windows; the rest collect heat from the sun, raising the temperature of the air in the cell. This heated air is drawn by fans down into a deep basement which takes up the entire area

under the house. This basement is to be filled with rocks, each about the size of an egg. The heat will be stored in these rocks during the day and during the night, heat will be obtained from the rocks by drawing air from the basement and circulating it through the house.

The eaves overhang the front of the house so that it is shaded during the middle of the day in summer, preventing the house from becoming overheated.

The outer cladding and the roof are of aluminium siding with internal reflective insulating sheet and asbestos batts. Grote has designed his house so that there will be no need for any heating or cooling system fuelled by that precious and increasingly expensive commodity — petroleum oil. Light and power will be obtained from the Tasmanian SEC grid — as it's hydro-electric power (and thus, ultimately, solar-derived) he figures that's fair enough.

The windows, though smaller than are fashionable, are designed to provide adequate natural lighting while minimising heat loss.

At a stage in life when most people have either retired or are rapidly approaching the end of an active working life, Grote Reber's pioneer attitude is as strong as ever and he continues to march forward, with well thought-out and carefully executed strides, where others merely 'dabble their toes' or turn away seeking easier paths. ●

### Epilogue

It was at the suggestion of Jim Davis that I took the opportunity to meet Grote Reber who, I must confess, was one of the heroes of my youth. Jim arranged the meeting at very short notice and he and Bill Carter proved able navigators. I am indebted to both gentlemen.

For those interested in further reading on radio astronomy, 'Radio Astronomy for Amateurs' by Hey, obtainable from some technical bookshops makes good reading. The author wrote a series on 'Radio Astronomy for Amateurs' published in ETI between December 1971 and April 1973.

# Radio Australia gets Darwin go-ahead

The Federal Government recently approved reconstruction plans for the Radio Australia transmitter complex on Cox Peninsula, across Darwin harbour. If all goes to plan, the transmitters of Radio Australia on Cox Peninsula should be fully active by Nov 1982.

**Radio Australia operated three powerful shortwave transmitters, each of 250 kilowatts, at Cox Peninsula until Christmas Day in 1974 when cyclone Tracy wrecked the antenna arrays and cut off the power supply to the peninsula.**

Submarine power cables across to Cox Peninsula will need to be repaired before regular broadcasts can recommence, although some irregular test broadcasts have been made in the past year by using an emergency power generator at the transmitter site.

Main costs in reactivating the Cox Peninsula transmitters will be the installation of the submarine cables across Port Darwin, and the installation of a new antenna system.

New curtain antenna arrays are to be installed, which could be lowered to ground level to

avoid damage from any future cyclones. These antennas are of a type similar to those installed at Radio Australia's Carnarvon (West Australia) transmitter site, which have proved very successful during cyclonic conditions.

Amazingly, the transmitters themselves suffered little or no damage from cyclone Tracy. However, the buildings housing the transmitters are to be cyclone-strengthened for added security.

An earlier proposal to re-site the Radio Australia Darwin station at Humpty Doo, 60 km south east of Darwin was rejected. Although the Humpty Doo site would be less prone to cyclone damage, the re-siting of the transmitters would have entailed greater costs and further delays in re-activating what will be Radio Australia's most important transmitting station.

## World Radio Television Handbook 1981

**This publication is an essential reference book for all those even slightly interested in radio, be it shortwave, medium-wave or FM.**

The Australian Radio DX Club will again be co-ordinating orders for the upcoming 1981 edition. The 1981 edition should cover well over 500 pages listing shortwave, mediumwave and television stations throughout the world together with station addresses, personnel and policy towards reception reports.

For further information about ordering your copy of the 1981 World Radio and Television Handbook, please send a stamped, self-addressed envelope to the address in this

column. The edition should be published around early February 1981.

**NOTE!** All times are given in Greenwich mean time (GMT). To convert to Australian Eastern Standard Time, add 10 hours (11 hours during Daylight Saving Time, November to February). To convert to Central Standard Time, add 9.5 hours and Western Time add 8 hours.

All frequencies are given in kHz.

These notes are compiled by Peter Bunn on behalf of the Australian Radio DX Club (ARDXC). Further information on DXing or the activities of the ARDXC may be obtained from P.O. Box 79, Narrabeen, NSW 2101, for a 22¢ stamp.



## New service from Ecuador

**Station HCJB, the Voice of the Andes in Quito, has recently introduced a new service for Australia in Spanish. This has meant a cut in the English language Australia service of 30 minutes.**

HCJB has replaced the last half hour of the 0700-1100 English broadcast with a Spanish programme especially for Australian listeners. The programme is heard on the same channels as the English service, that is: on 6130, 9745 and 11 900.

HCJB is also not pleased with

the performance of their 11 900 frequency, realising that it suffers quite a deal of interference from jamming on the adjacent 11 905.

The station would be glad to receive recommendations from Australian listeners for alternative frequencies to 11 900, within the 25 metre band.

## Change brings Iceland within reach

**Iceland has for some years operated a 7.5 kilowatt short-wave transmitter on 12 175 with a daily broadcast for local seamen from 1200-1300. This time period made reception of Iceland almost out of the question here in east Australia.**

However, a time change for this daily broadcast means Iceland is now within the bounds of possibility for Aussie DXers.

Iceland now broadcasts the daily programme between 1855 and 2000, still using 12 175, and this transmission should propagate into east Australia. However, due to heavy utility activity on 12 175, Reykjavik makes a difficult catch.

Reports from DXers in south Asia indicate that the signal has made it to that region so we can hold out hope that should the utility transmitters clear 12 175, we in Australia will also be able to log this very rare country.

## Colombia returns

**After an absence of well over 18 months, Radio Super de Cali in Colombia has returned to shortwave, and on a new frequency.**

Radio Super de Cali is now heard on 6085, and gives best reception between 0730 and 0930 in Melbourne. Cali previously used 6120 when on shortwave when last heard in 1978.

That frequency often varied to

6125 and the station was never known for regularity in their broadcasting schedule.

Meanwhile, the other Radio Super currently well heard is Radio Super de Bogota, on 6065, best signals being between 0700 and 1000.

# The Philips Super-M Hi-Fi pick-up cartridges give you brilliant high-fidelity reproduction



## GP 412 II

A masterpiece of engineering that brings out the best in any music. The titanium stylus shaft contributes to super low playing weights (0.75 — 1.5g), giving extra long life to your records.

**\$118.88\*** Code 251 17031



## GP 401 II

It's a tiny magnet of high-energy Super-M magnet steel that gives this cartridge high sensitivity and an excellent smooth response right from 20 to 20,000 Hz. Ideal for high quality automatic turntables where you can safely use an elliptical stylus.

**\$59.52\*** Code 251 17034



## GP 422 II

The stereo plus discrete 4-channel cartridge that will delight the enthusiast. Features a shaftless stylus, excellent trackability, and a frequency spectrum well in excess of 50kHz. Just about the best that money can buy.

**\$137.94\***

Code 251 17032



## Other Popular Philips Service Products



### Stereo Headphones N6309/02

Soft Cushioned, light and comfortable, these phones give beautiful clarity right through a wide range.

**\$45.11\***

Code 242 47018



### Stereo Headphones N6308/02

Big 3" speakers produce a big sound, with slider volume controls and adjustable headband. Great value at just

**\$17.17\***

Code 242 47008



### Stereo Headphones N6306/02

Equipped with two volume controls for adjustment of the spatial sound, giving great separation.

**\$13.95\***

Code 242 47014



### 0° Freeze Type 815/FRS Pressure Pack

Makes it quick and easy to locate faults and check settings in thermal components.

**\$3.88\***

Code 389 50088



### V.C.R. Cleaning Cassette

Removes deposits around video heads and tape guides. Use every 30 hours for maximum results.

**\$19.20\***

Code 395 90102



### Disco Combi Set

Uses a special fluid to gently clean the grooves. Stylus brush included.

**\$3.89\***

Code 395 90157



### Degreaser/Cleaner type 815/DCS Pressure Pack

Ensures reliability of switches in all types of electrical equipment.

**\$4.89\***

Code 390 87003

All Philips audio and video service products are available through your nearest Philips Service Centre.

**SYDNEY:** 443 Concord Road, Rhodes. N.S.W. 2138 Telephone (02) 73 0231. The Philips Building, 15 Blue Street, North Sydney, 2060. Telephone (02) 922 0181. **NEWCASTLE:** 190 Parry Street, Newcastle West, 2302. Telephone: (049) 61 1631. **CANBERRA:** 86 Wentworth Avenue, Kingston, A.C.T. Telephone (062) 95 0321. **MELBOURNE:** Cnr. Miles & Dodds Street, South Melbourne, 3205. Telephone (03) 699 2711. **HOBART:** 2A Pierce Street, Moonah, Tasmania, 7009. Telephone: (002) 28 0121. **BRISBANE:** 55 Forbes Street, West End, Brisbane, 4101. Telephone: (07) 44 8121. **TOWNSVILLE:** 38 Punari Street, Currajong, 4812. Telephone: (077) 79 7422. **ADELAIDE:** 81-97 Flinders Street, Adelaide, 5000. Telephone (08) 223 2999. **PERTH:** 875 Wellington Street, West Perth, 6005. Telephone: (09) 321 5131.

\* Recommended retail price

# PHILIPS

# ServiceServiceService



AHEARN PS3

# PREDICTIONS

NOVEMBER 1980

Covering 3 to 40 MHz, these predictions show the times radio contact is possible between the areas designated beneath each graph, as well as the possible 'mode' and reliability. Vertical columns indicate time — commencing at 0000 UT on the left, to 2300 UT at right. For reliable predictions follow the times and frequencies indicated by the F character.

Complete information on using these predictions can be obtained by sending a stamped, self-addressed envelope to:-

ETI — Predictions  
3rd floor 15 Boundary St  
RUSHCUTTERS BAY NSW 2011.




These GRAFEX style computer generated predictions are provided courtesy of the Australian Ionospheric Prediction Service.

## KEY TO SYMBOLS

- A blank area means no normal propagation is possible.
- % ..... path open 50 - 90% of days in month.
- F ..... path open at least 90% of days in month.
- B ..... propagation possible via E and F layers over 90% of days. Overrides 'F'.
- M ..... propagation possible by both 1st and 2nd F-layer modes. Expect strong fading.
- S ..... propagation possible by 2nd mode (also 3rd and mixed E and F modes). Expect strong fading, weak signals.
- A ..... High absorption indicated. Expect weak signals.

40 ..XZ.....	40 ..XZ.....	40 ..XZ.....	40 ..XZ.....	40 ..XZ.....	40 ..XZ.....
39 ..XZ.....	39 ..XZ.....	39 ..XZ.....	39 ..XZ.....	39 ..XZ.....	39 ..XZ.....
38 ..XZ.....	38 ..XZ.....	38 ..XZ.....	38 ..XZ.....	38 ..XZ.....	38 ..XZ.....
37 ..XZ.....	37 ..XZ.....	37 ..XZ.....	37 ..XZ.....	37 ..XZ.....	37 ..XZ.....
36 ..XZ.....	36 ..XZ.....	36 ..XZ.....	36 ..XZ.....	36 ..XZ.....	36 ..XZ.....
35 ..XZ.....	35 ..XZ.....	35 ..XZ.....	35 ..XZ.....	35 ..XZ.....	35 ..XZ.....
34 ..XZ.....	34 ..XZ.....	34 ..XZ.....	34 ..XZ.....	34 ..XZ.....	34 ..XZ.....
33 ..XZ.....	33 ..XZ.....	33 ..XZ.....	33 ..XZ.....	33 ..XZ.....	33 ..XZ.....
32 ..XZ.....	32 ..XZ.....	32 ..XZ.....	32 ..XZ.....	32 ..XZ.....	32 ..XZ.....
31 ..XZ.....	31 ..XZ.....	31 ..XZ.....	31 ..XZ.....	31 ..XZ.....	31 ..XZ.....
30 ..XZ.....	30 ..XZ.....	30 ..XZ.....	30 ..XZ.....	30 ..XZ.....	30 ..XZ.....
29 ..XZ.....	29 ..XZ.....	29 ..XZ.....	29 ..XZ.....	29 ..XZ.....	29 ..XZ.....
28 ..XZ.....	28 ..XZ.....	28 ..XZ.....	28 ..XZ.....	28 ..XZ.....	28 ..XZ.....
27 ..XZ.....	27 ..XZ.....	27 ..XZ.....	27 ..XZ.....	27 ..XZ.....	27 ..XZ.....
26 ..XZ.....	26 ..XZ.....	26 ..XZ.....	26 ..XZ.....	26 ..XZ.....	26 ..XZ.....
25 ..XZ.....	25 ..XZ.....	25 ..XZ.....	25 ..XZ.....	25 ..XZ.....	25 ..XZ.....
24 ..XZ.....	24 ..XZ.....	24 ..XZ.....	24 ..XZ.....	24 ..XZ.....	24 ..XZ.....
23 ..XZ.....	23 ..XZ.....	23 ..XZ.....	23 ..XZ.....	23 ..XZ.....	23 ..XZ.....
22 ..XZ.....	22 ..XZ.....	22 ..XZ.....	22 ..XZ.....	22 ..XZ.....	22 ..XZ.....
21 ..XZ.....	21 ..XZ.....	21 ..XZ.....	21 ..XZ.....	21 ..XZ.....	21 ..XZ.....
20 ..XZ.....	20 ..XZ.....	20 ..XZ.....	20 ..XZ.....	20 ..XZ.....	20 ..XZ.....
19 ..XZ.....	19 ..XZ.....	19 ..XZ.....	19 ..XZ.....	19 ..XZ.....	19 ..XZ.....
18 ..XZ.....	18 ..XZ.....	18 ..XZ.....	18 ..XZ.....	18 ..XZ.....	18 ..XZ.....
17 ..XZ.....	17 ..XZ.....	17 ..XZ.....	17 ..XZ.....	17 ..XZ.....	17 ..XZ.....
16 ..XZ.....	16 ..XZ.....	16 ..XZ.....	16 ..XZ.....	16 ..XZ.....	16 ..XZ.....
15 ..XZ.....	15 ..XZ.....	15 ..XZ.....	15 ..XZ.....	15 ..XZ.....	15 ..XZ.....
14 ..XZ.....	14 ..XZ.....	14 ..XZ.....	14 ..XZ.....	14 ..XZ.....	14 ..XZ.....
13 ..XZ.....	13 ..XZ.....	13 ..XZ.....	13 ..XZ.....	13 ..XZ.....	13 ..XZ.....
12 ..XZ.....	12 ..XZ.....	12 ..XZ.....	12 ..XZ.....	12 ..XZ.....	12 ..XZ.....
11 ..XZ.....	11 ..XZ.....	11 ..XZ.....	11 ..XZ.....	11 ..XZ.....	11 ..XZ.....
10 ..XZ.....	10 ..XZ.....	10 ..XZ.....	10 ..XZ.....	10 ..XZ.....	10 ..XZ.....
9 ..XZ.....	9 ..XZ.....	9 ..XZ.....	9 ..XZ.....	9 ..XZ.....	9 ..XZ.....
8 ..XZ.....	8 ..XZ.....	8 ..XZ.....	8 ..XZ.....	8 ..XZ.....	8 ..XZ.....
7 ..XZ.....	7 ..XZ.....	7 ..XZ.....	7 ..XZ.....	7 ..XZ.....	7 ..XZ.....
6 ..XZ.....	6 ..XZ.....	6 ..XZ.....	6 ..XZ.....	6 ..XZ.....	6 ..XZ.....
5 ..XZ.....	5 ..XZ.....	5 ..XZ.....	5 ..XZ.....	5 ..XZ.....	5 ..XZ.....
4 ..XZ.....	4 ..XZ.....	4 ..XZ.....	4 ..XZ.....	4 ..XZ.....	4 ..XZ.....
3 ..XZ.....	3 ..XZ.....	3 ..XZ.....	3 ..XZ.....	3 ..XZ.....	3 ..XZ.....

# TNT AUSTRALIA COURIER WIDE SATCHEL.

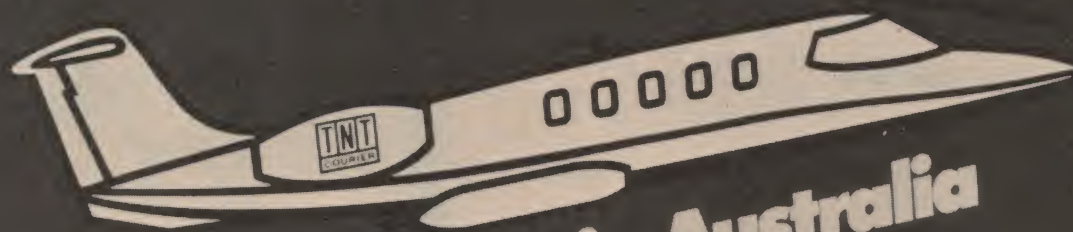

**\*anywhere in Australia  
overnight.**

*\*Anything which fits inside this satchel may be sent almost anywhere in Australia, overnight.*



## Now your newsagent can solve your urgent parcel problems.

This TNT Courier Overnight Satchel has just turned your friendly newsagent into an air freight depot. For \$8.75 you can send anything that fits inside to almost anywhere in Australia. Overnight. You don't have to wrap a thing. The bag is tough, waterproof and tear resistant.

You can buy TNT Satchels at most newsagents throughout Australia. (At present in N.S.W., they are

available only in Sydney, Newcastle, Wollongong, Gosford and A.C.T.). Just address the satchel and leave it with your newsagent. TNT Courier collect it, air freight it overnight and deliver the next morning.

The TNT Courier Suburban Satchel is for overnight local deliveries in all mainland capitals (and soon Hobart) for just \$5.00.

**TNT Courier Overnight Satchels. \*Anything, anywhere, overnight.**

A Speedy Communications product. \*Anything which fits inside the satchel may be sent almost anywhere in Australia, overnight.



# AT LAST!

## DICK SMITH'S FUN WAY INTO ELECTRONICS VOL 2


- Twenty exciting and useful projects to build
- Learn how to make your own printed circuit boards
- How to use a multimeter
- How to solder

Yes – the long awaited 'Fun Way into Electronics, Volume 2' is due in stock in September.

The follow-up to the incredibly popular 'Fun Way 1' this book contains another twenty projects which are all useful devices: everything from electronic jewellery to a home and car burglar alarm!

They're all built on printed circuit boards – so we'll not only give you step-by-step instructions, we'll also show you how to solder! And there are attractive cut-out labels in the back of the book to give your projects a really professional appearance.

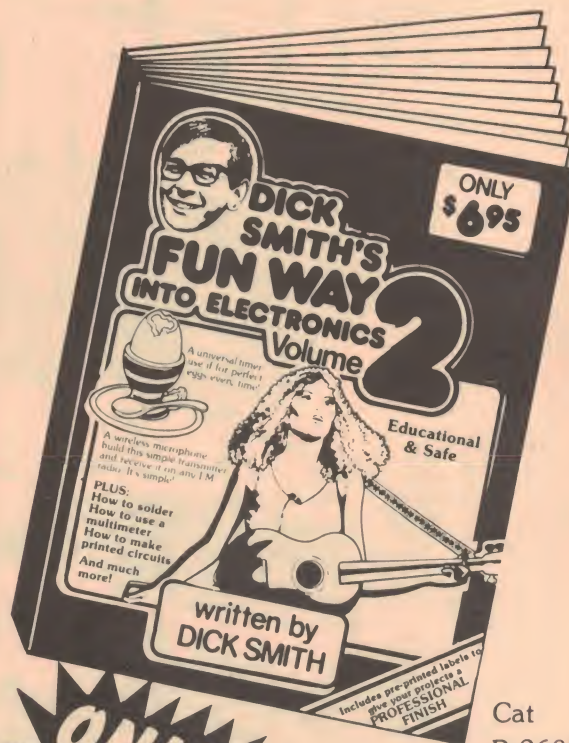Dick Smith's Fun Way into Electronics, volume 2: it's a great gift idea, and it will be available from your nearest Dick Smith store or re-seller almost immediately, and from most good bookstores and newsagents shortly.



**ONLY \$6.95**

Cat  
B-2605

**Schools, re-sellers,  
etc: ask about our  
incredible bulk  
discounts!**

**SPECIAL 7 DAY NO-RISK TRIAL OFFER:** We'll send you a copy of 'Fun Way Volume 2' by return mail for just \$6.95 – that's pack and post FREE! If you're not completely happy with it, return it to us in original condition and we'll send you a refund. What could be simpler? (7-day offer also available from all Dick Smith company-owned stores. Book must be returned to point of purchase within 7 days, and in original condition, to qualify for refund).

### KITS OF PARTS FOR FUN WAY II PROJECTS:

Full kits of parts for all projects in 'Fun Way 2' will be available with the release of the book. These kits include all components required, the printed circuit board, solder and wire etc. For details of the projects, the kit prices, etc, please refer to the 1980 Dick Smith catalogue, page 25.

# DICK SMITH ELECTRONICS



SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS

# MINI-MART

## Where readers can advertise — For Sale/Wanted/Swap/Join.

• We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — **please** — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable.

• **Conditions:** Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:  
**ETI Mini-Mart, Modern Magazines**  
15 Boundary St,  
Rushcutters Bay NSW 2011

**WANTED:** Controller, disc drives, software and documentation for 8080/S100 based system, any condition. Phone Bill Bencke (062) 31-6935 reverse charges.

**NORTH COAST** persons interested in computers contact Ray Evans to share NSW Uni correspondence courses in BASIC and microprocessors. P.O. Box 36, Iluka, NSW 2460. Phone (066) 46-6173.

**8K static S-100 RAM board** low power 450ns memory assembled and tested, \$115. Brian Ald (047) 21-5333.

**SELL:** Dream 6800, assembled and tested \$200, power supply extra \$50. Phone (08) 31-1222.

**OMEGA (OSI Microcomputer Enthusiasts Group Australia)** has details on software and hardware mods for your OSI C1, C2 or C4. It is only \$5 per year, including the newsletter (bimonthly). Contact Geoff Cohen, 72 Spofforth St., Holt, ACT 2615. Phone (062) 49-2688 b.h., (062) 54-7608 a.h.

**SORCERER USERS** — software group and program interchange. Join forces to solve the software shortage. Contact J. Stephenson, 4 Melinga Pl., Tarooma, Hobart, Tas 7006. Phone (002) 27-8770.

**WANTED:** SS50 or SWTPC 6800 computer printer, terminal, disk drive, boards, etc. Ray Evans, P.O. Box 36 Iluka, NSW 2460. Phone (066) 46-6173.

**FOR SALE:** 3 S100 WW pcbs \$30; 16K x 1 dynamic memory (4116) chips \$8 ea, plus other items. Write to F. Macri, 7 Winifred Av., Carlingbah, NSW 2229.

### MISCELLANEOUS

**SPECTRUM Analyser Meguro-MAT 142** dual trace, audio frequency tracer, as new. Hewlett-Packard 120B rack mounted, from \$350. Phone (02) 46-5451.

**150 in 1 Dick Smith experimenters kit** exc. cond. \$25. Phone Leon (062) 54-2662 a.h.

**APPRECIATE** circuit diagrams and pcb patterns for Road Race TV game using AY-3-8603 IC or Warfare TV game using AY-3-8605 IC. D. Stafford, 20 Rigby St., Annerley, Qld 4103. Phone (07) 48-2378.

**WANTED:** Old Astor super delux 6 valve or (5) short wave (any condition). G. Bracey, P.O. Exeter West, Tamar, Tas 7251. Phone 94-4126.

**CASIO FX-502P** owners; anyone interested in forming users group to sell/swap programs? Send s.a.e. suggestions to Clive Conway, 80 Third Ave., Joslin, SA 5070.

**WANTED:** Oscilloscope, single or dual trace depending on price, prefer B.W.D. brand, to suit serious hobbyist. Phone (03) 232-5725 a.h.

### AUDIO

**LUXMAN L2 amp & T2 tuner** \$225 each. YAMAHA TC800D cassette deck \$200 all exc. cond. phone Leon (062) 542662 a.h.

**RECEIVER,** Realistic DX-160, in perfect condition. Bargain at \$100 plus free set of headphones. Phone (02) 46-1848.

**TRANSMISSION LINE** loudspeakers PRO 9TL. Salter, 33 Belvedere Way, Lynwood, WA 6155. Phone (09) 350-7254 b.h.

**SELL:** ETI 4000 amp with toroidal transformer \$220; Hitachi TRQ 262D cassette deck \$90; Echo-sound AM/FM Tuner \$45. I. Hawke, 44 Enfield Ave., North Richmond, NSW 2754. Phone (045) 73-2068.

**LUXMAN L3 D.C. 50W/CM amp, B.E.S. V60** Geo-static speakers, Technics SL1300 direct drive turntable, Top Pickering mag cartridge. All in immaculate condition, cost over \$1500, sell \$1200 o.n.o. Alan Calleja, 48 Elgin St., Morwell, Vic 3840.

### COMMUNICATIONS

**SELL:** Icom IC701, inc mic, as new \$950. RM3 remote control suit 701/211 \$100. Kenwood TL 120 linear as new \$195. Daiwa RF 660 speech processor \$80. Phone (02) 57-4648.

**BUY:** Barlow Wadley or synthesised receiver. SSB amateur mobile transceiver (Swan, Drake, Alda). Cheap. ZL4BT care N. McMillan, 25 Daphne Ave., Bankstown, NSW 2200.

**AUSTRALIAN Radio DX Club** for shortwave, mediumwave Dxers. For a sample copy send one 22c stamp to P.O. Box 79, Narrabeen, NSW 2101, mentioning this ad.

**LINEAR HF amplifier, 1 - 30 MHz, Yaesu** Musen FL-2100B, uses two Eimac 572Bs, as new, purchased March 1980. 1.2 kilowatt DC input, maximum ham power all bands and overlap for new bands, \$395 sacrifice. John Berry, 40 Grosvenor St, Woollahra, NSW 2028. Phone (02) 389-6455 b.h.

### COMPUTERS

**TRS-80** green screens, 1/8" perspex with adhesive pads for easy mounting. \$12 incl. postage. D. Silver, Flat 1, 'Kenley Close', Leonard St., Parkville, Vic 3052.

**SELL:** Computer system. KT9500 2650 computer, 14K RAM; 5V/10A, +/-12V power supply; VDU includes Honeywell keyboard, EME-1; TV monitor; cassette recorder/interface; software. (Parts cost \$1600) \$1400 o.n.o. David (02) 663-2559.

**OLIVETTI I/O** electric typewriter, u/case and i/case characters, suit word processor and computer applications. \$225. Long, 46 Gloucester St., Sydney, NSW 2000. (02) 27-2982 a.h.

**Computer power supply.** IN3209 15 amp rectifiers, 3 x 37,500 uF condensers, voltage stabilised type. Transformer 24, 5, 40 V output, 240 V input, \$40. R. Long, (02) 27-2982 a.h.

**OHIO C2-4P** computer. 8K RAM, 8K BASIC, all documentation, lots of software, as new. \$600. M. Finn 16 Inga St., East Burwood, Vic. (03) 288-5116.

**MICRO 2650 (KT9500), 16K RAM, 110/300 baud,** keyboard, EME VDU, cassette interface, 10 amp p/s, BASIC, considerable software, full documentation. \$400. Phone Mick (03) 288-5116.

**WANTED:** Dead or damaged EPROMS — will reimburse postage. Send to Mark Berndt, 213 Cape St., Heidelberg, Vic 3084.

**COPYRIGHT:** The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

**LIABILITY:** Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid. The Publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.



## Because it's hard enough getting a home together, we've put all this cover together.

Six insurance covers in one.

It's called the AGC Insurance Executive policy for homeowners and householders.

And it saves you dealing with six different insurance companies and worrying about six different policies.

You get one simple policy.

Up to six kinds of cover.

It's a policy that's never been beaten.

### **Your home itself.**

AGC provides insurance cover for your home. Even garages, out buildings and swimming pools.

And we also offer you the New Rebuilding Cover alternative.

These days there is generally a big difference between the current value of your home and what it would cost if you had to rebuild.

AGC's Rebuilding Insurance protects you automatically against inflation. And the increased cost of building materials.

### **The contents of your home.**

We'll cover household goods and personal effects of every description.

No depreciation on goods or articles less than 5 years old. (Excluding linen and clothing.)

### **Specified personal property anywhere in Australia**

We'll also cover the special things you value.

Very valuable objects such as furs, jewellery, paintings and the like.

### **Other essential protection.**

Your AGC Executive policy can also give you cover against Personal Legal Liability

Death of nominated person by accident.

And, if you employ domestic help, workers' compensation (not applicable in Queensland).

With AGC's Executive policy you're not only covered by up to six different types of insurance.

You're covered by a big name – **AGC Insurances.**

Sydney: Phillip & Hunter Streets.

Melbourne: 31 Spring Street.

Brisbane: Tank Street & North Quay.

Adelaide: 10 Pulteney Street.

Perth: 165 Adelaide Terrace.

Hobart: 161 Collins Street, and offices throughout Australia.

AGC (Insurances) Limited. A division of Australian Guarantee Corporation Limited in which the Bank of New South Wales is the major shareholder.

AGC 994 FCB

# How to crack a highly paid job as an electronics technician.



We'll give you excellent training - as good as you'll get anywhere in Australia.

We'll give you free medical, dental and hospital treatment.

We'll provide plenty of good tucker and a comfortable place to stay.

We'll give you substantial leave, and on top of all that, we'll pay you well while you're training.

On your side, you'll give us a period of hard, but interesting and rewarding work. And, when eventually you leave us, you'll find yourself a fully qualified and experienced Electronics Technician. Not a bad thing to be, these days.

So, if electronics is your idea of a great career and you are (at time of entry) approx. 15 to 17 for apprenticeship

and over 17 for an Adult Trainee, join the Navy, Army or Air Force.

Phone us at:

Adelaide 223 2891. Brisbane 226 2626.

Canberra 822 333 Hobart 34 7077.


Melbourne 61 3731. Perth 325 6222.

Sydney 212 1011.

Write to either the Navy, Army or Air Force Electronics Technician Counsellor, GPO Box XYZ in your nearest State Capital City (please

include your date of birth).

**Learn  
Electronics  
with us.**

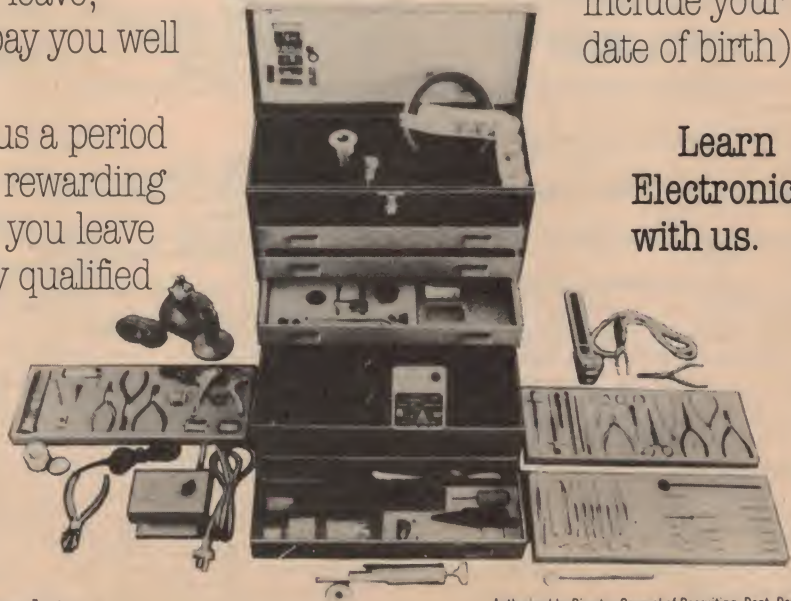

Authorised by Director-General of Recruiting, Dept. Defence.  
TSAP15.FP.48

# KITS for projects

WE GET MANY enquiries from readers wanting to know where they can get kits for the projects we publish. This list is a guide to suppliers of kits and components for ETI projects.

We have listed here most of the projects published over the last few years which are either available as kits or can still be made up by shopping around for components. Suppliers listed against a particular project will either stock it as a kit or stock the pc board plus the other components.

## Printed circuit boards

Those suppliers listed against specific projects here are able to supply pc boards for those projects. Printed circuit boards for every project ever published in ETI are available through the following companies (to the best of our knowledge):

RCS Radio      Radio Despatch Service  
651 Forest Rd    869 George St  
Bexley NSW      Sydney NSW 2000

For current projects and a more comprehensive list of pc board suppliers refer to the Shoparound page in this and previous issues. This list will be updated roughly every four months.

## Key to Companies

- A Applied Technology Pty Ltd, 1A Paterson Avenue, Waitara, NSW 2077. Ph. (02) 487-2711.
- B Bill Edge Electronic Agencies, 115 Parramatta Road, Concord (PO Box 1005, Burwood North 2134). Ph. (02) 747-6472.
- C J.R. Components, PO Box 128, Eastwood, NSW 2122. Ph. (02) 85-3385.
- D Dick Smith Electronics P/L, Cnr Waterloo & Lane Cove Roads, North Ryde, 2113. Ph. (02) 888-3200.
- E All Electronic Components, 118 Lonsdale Street, Melbourne, Vic 3000. Ph. (03) 662-3506.
- F Tasman Electronics, 12 Victoria Street, Coburg, Vic 3058. Ph. (03) 354-5062.
- J Jaycar Pty Ltd, PO Box K39, Haymarket, NSW 2000. Ph. (02) 211-5077.
- K S M Electronics, 10 Stafford Court, Doncaster East, Vic 3109. Ph. (03) 842-3950.
- L Ellistronics, 289 Latrobe Street, Melbourne, Vic 3000. Ph. (03) 602-3282.
- M Mode Electronics, PO Box 365, Mascot, NSW 2020. Ph. (02) 666-6324.
- N Nebula Electronics Pty Ltd, 15 Boundary Street, Rushcutters Bay, NSW 2011. Ph. (02) 33-5850.
- O Orbit Electronics, PO Box 7176, Auckland, New Zealand.
- P Pre-Pak Electronics, 718 Parramatta Road, Croydon, NSW 2132. Ph. (02) 797-6144.
- R Rod Irving, PO Box 135, Northcote, Vic 3070. Ph. (03) 489-8131.
- V Silicon Valley, 23 Chandos Street, St. Leonards, NSW 2065. Ph. (02) 439-4655.
- W Willis Electronics, 993 Hay Street, Perth, WA 6000. Ph. (09) 321-7609.
- Y Trilogy, 40 Princes Highway, Fairy Meadow, NSW 2519.

## Project Electronics

- 041 Continuity Tester ..... W,R,D,B,Y,L
- 042 Soil Moisture Indicator ..... R,B
- 043 Heads or Tails Circuit (Oct 76) ..... W,R,D,E,A,F,B,Y,L
- 044 Two Tone Door Bell (Oct 76) ..... W,R,D,E,O,A,F,B,Y,L
- 045 500 Second Timer ..... W,D,E,A,B,Y,L
- 047 Morse Practice Set ..... W,D,O,A,B,Y,L
- 048 Buzz Board ..... W,D,A,B,Y,L
- 061 Simple Amplifier (Oct 76) ..... W,R,D,E,A,B,Y,L
- 062 Simple AM Tuner (Mar 77) ..... W,D,E,B,Y
- 063 Electronic Bongos ..... R,D,A,B,Y,L
- 064 Simple Intercom (Nov 76) ..... W,A
- 065 Electronic Siren ..... W,R,D,E,O,A,B,Y,L
- 066 Temperature Alarm (Dec 76) ..... W,D,E,A,B,Y,L
- 067 Singing Moisture Meter ..... D,B,Y
- 068 LED Dice Circuit (Oct 76) ..... W,R,D,E,A,B,L
- 070 Electronic Tie Breaker (Jan 77)
- 071 Tape Noise Limiter (Jun 78) ..... R,E,F
- 072 Two-Octave Organ (Jun 78) ..... W,D,B,Y
- 081 Tachometer (Mar 77) ..... W,E,O
- 082/
- 528 Intruder Alarm ..... W,R,E,A
- 083 Train Controller ..... W,R,E,L
- 084 Car Alarm ..... W,R,D,E,A,B,Y,L
- 085 Over-rev Alarm ..... W
- 086 FM Antenna ..... W
- 087 Over-LED ..... W,E
- 088 Hi-Fi Speaker ..... W

## Test Equipment

- 132 Experimenter's Power Supply (Feb 77) ..... E,O
- 133 Phase Meter (Apr 77) ..... E
- 134 True RMS Voltmeter (Aug 77) ..... E
- 135 Digital Panel Meter (Oct 77) ..... E
- 136 Linear Scale Capacitance Meter (Mar 78)
- 137 Audio Oscillator (May 78) ..... W,D,E
- 138 Audio Wattmeter (Nov 78) ..... E,B
- 139 SWR/Power Meter (May 78)
- 140 1GHz Frequency Meter-timer (Mar 78)
- 141 Logic Trigger (Jan 79) ..... E
- 142 High Current Power Supply (Feb 79) ..... W,E
- 143 Curve Tracer (Jan 79) ..... W
- 144 Expanded-scale RMS Voltmeter (Jun 79) ..... E
- 148 Versatile Logic Test Probe (Jul 79) ..... E,L

## Simple Projects

- 243 Bip Beacon (Apr 77)
- 244 Alarm Alarm (Feb 77) ..... F
- 245 White Line Follower (Nov 77) ..... F
- 246 Rain Alarm (Apr 78) ..... F
- 248 Simple 12V to 22V Converter (Jul 78) ..... W
- 249 Electronic Combination Lock (Apr 79) ..... E
- 252 The Passionmeter (Aug 79)
- 253 Electronic Grenade (Hot Potato) (May 79)
- 254 Egg Timer (Jun 79) ..... W

## Motorists' Projects

- 316 Transistor Assisted Ignition (May 77) ..... W,E,O,K
- 317 Rev. Monitor Counter (Jul 77) ..... E
- 318 Digital Car Tacho (Jul 78) ..... W,E,K
- 319 Variwiper MK II (Sep 78) ..... W,E,O
- 320 Battery Condition Indicator (Apr 79) ..... E,L

## Audio Projects

- 448 Disco Mixer (Nov 76) ..... W
- 449 Balanced Microphone Amp (Nov 76) ..... W,D,E,J,F,Y
- 450 Bucket Brigade Audio Delay Line (Dec 77) ..... W,E
- 451 Hum Filter (Jul 79) ..... D,E,F
- 470 60 W Amp Module (May 79) ..... W,R,E,F,B,P,L,A,V
- 471 High Performance Stereo Preamplifier Unit (Jun 79) ..... W,R,E,F,B,P,A,V,L
- 472 Power Supply — the Series 4000 Stereo Amp (Jul 79) ..... W,R,E,F,B,V,L
- 473 Series 4000 Moving-coil Cartridge Preamplifier ..... F,J
- 480 50-100 Watt Amp Modules (Dec 76) ..... A,W,R,D,E,J,O,Y,L
- 481 12V 100 Watt Audio Amp (May 77) ..... R,E
- 481 High Power PA/Guitar Amp (Jun 77) ..... W
- 482 Stereo Amp (Jan 77) ..... O,E
- 482 Stereo Amp Part 2 (Feb 77) ..... O,E
- 483 Sound Level Meter (Feb 78) ..... E
- 484 Simple Compressor Expander (Jul 77) ..... A,E
- 485 Graphic Equaliser (Jun 77) ..... W,E,J,O
- 486 Howl-round Stabiliser (Nov 77) ..... J
- 487 Audio Spectrum Analyser (Feb 78) ..... E
- 489 Audio Spectrum Analyser 2 (Apr 78) ..... E,J
- 490 Audio Compressor (Dec 78)
- 491 Simple Graphic Equaliser (Mar 79) ..... W,E
- 495 Transmission Line Speakers (Aug 77)

## Miscellaneous

- 546 GSR Monitor (Mar 77) ..... W,E
- 547 Telephone Bell Extender (Jun 77) ..... E
- 548 Photographic Strobe (May 77) ..... W,E
- 549 Induction Balance Metal Detector (May 77) ..... W,D,E,L
- 550 Digital Dial (Aug 78) ..... E,O
- 551 Light Chaser (Sep 78) ..... W,E,O
- 552 LED Pendant (Sep 78) ..... A
- 553 Tape/Slide Synchroniser (Oct 78) ..... E
- 556 Wind Speed/Direction Indicator (Dec 78)
- 557 Reaction Timer (Feb 79) ..... E
- 558 Mast-head Strobe (Feb 79) ..... E
- 559 Cable Tester (Mar 79)
- 575 Portable Fluorescent Light Wand for Car, Camping (Aug 79) ..... W
- 577 General Purpose Power Supply ..... J
- 581 Dual Power Supply (Jan 77) ..... W,E,Y
- 582 House Alarm (Jul 77) ..... W,E,O,A
- House Alarm — Installation Instructions (Aug 77) ..... W
- 583 Marine Gas Alarm (Aug 77) ..... D,E,M
- 585 Ultrasonic Switch (Sep 77) ..... R,D,E,O,F
- 586 Shutter Speed Timer (Oct 77) ..... E
- 587 UFO Detector (May 78)
- 588 Theatrical Lighting Controller (Nov & Dec 77 Jan & Mar 78) ..... N
- 589 Digital Temperature Meter (PCB135) (Dec 77) ..... E
- 590 LCD Stopwatch (Oct 78) ..... O,N
- 591 Up/Down Presettable Counter (Jul 78) ..... D,E
- 592 Light Show Controller (Aug 78) ..... E
- 593 Colour Sequencer (Dec 78)
- 594 Development Timer (Apr 79) ..... E
- 595 Aquarium Lamp Controller (May 79)

## Electronic Music

- 602 Mini Organ (Aug 76) ..... W,D,E,A
- 603 Sequencer (Aug 77) ..... W
- 604 Accentuated Beat Metronome (Sep 77) ..... E
- 605 Temp Stabilized Log-exponential Converter (Sep 78)

## Computer Projects

- 630 Hex Display (Dec 76) ..... E,A
- 631 ASCII Keyboard (Dec 76) ..... W,E,O,A
- 631 Keyboard Encoder (Apr 77) ..... W,E,O,A
- 632 Video Display Unit (Jan 77) ..... A,E,O
- 633 TV Sync Generator (Jan 77) ..... A,E
- 634 8080 Educational/Prototyping Interface (Jul, Aug 78)
- 635 Microcomputer Power Supply (Sep 77) ..... O
- 637 Cuts Cassette Interface (Jun 78) ..... V,E,A
- 638 Eprom Programmer (Jul 78) ..... W,E,A
- 639 Computerised Musical Doorbell (Mar 78) ..... A
- 640 S100 VDU (Apr, May, Jun 78) ..... W,O,A,V
- 641 S100 Printer (Sep 78) ..... O
- 642 16k S100 RAM Card (Feb 79) ..... K
- 650 STAC Timer (Nov 78) ..... A,E,L
- 651 Binary to Hex Number Converter (Jun 79) ..... E

## Radio Projects

- 712 CB Power Supply (Jun 77) ..... W,E
- 713 Add-on FM Tuner (Sep 77)
- 714 VHF-Log-Periodic Antenna (Feb, Mar 78)
- 715 VHF Power Amplifiers (Nov 77)
- 716 VHF Power Amplifiers (Jan, Feb 78)
- 717 Crosshatch Generator (May 78) ..... W,D,E,A,Y
- 718 SW Radio (Oct 78) ..... E
- 719 RF Field Strength Indicator (Nov 78)
- 720 2m VMOs Power Amp (Jan 79)
- 721 Aircraft Band Converter (Mar 79) ..... W,E
- 722 Antenna for Aircraft Band Converter (May 79)
- 724 Microwave Oven Leak Detector (Jul 79) ..... D,E,B
- 725 Simple SSB Generator employs Polyphase Network using Standard Components (Aug 79) ..... E,L
- 730 Get Going on Radioteletype (Aug 79) ..... E,L

## Electronic Games

- 804 Selectagame (Nov 76) ..... O
- 804 Selectagame (Rifle Project) (Mar 77) ..... O
- 805 Puzzle of the Drunken Sailor (Oct 77)
- 806 Skeet (Jan 78) ..... O
- 810 Stunt Cycle TV Game (Jun 78) ..... D,O
- 811 TV Tank Game (Oct 78) ..... O
- 812 Wheel of Fortune (Dec 78)
- 813 Race Track Game (Jan 79) ..... O
- 814 The 'Dinky-Die' (Aug 79)

## Editor

**Roger Harrison VK2ZTB**

## Technical Editor

**David Tilbrook VK2YMI**

## Project Manager

**Phil Wait VK2DKN**

## Editorial Staff

**William Fisher B.Sc. (Hons)**

**John Pollard M.A., Ph.D.**

**J.B. Scott B.Sc./B.E. (Hons)**  
**VK2YBN**

**Jan Vernon B.A.**

Art Direction and  
technical photography  
**Ivy Hansen**

## Layout

**Bill Crump**

## Reader Services

**Jan Collins**

## Managing Editor

**Collyn Rivers**

## Acoustical Consultants

**Louis Challis & Associates**

## Editorial and Sales Office

**4th Floor, 15 Boundary St  
Rushcutters Bay NSW 2011**

**Ph: 33-4282; Tlx: 27243**

Sales Manager: **Bob Taylor**

Sales Admin: **Jan Collins**  
(address as above)

## Melbourne

**Tom Bray**  
150 Lonsdale St  
Melbourne Vic 3000  
Ph: 662-1222; Tlx AA34543

## New Zealand

**Geoff Collins**  
P.O. Box 39163  
Tel: (9)760-150  
Auckland NZ

## United Kingdom

**Australian Consolidated Press**  
Ludgate House  
107 Fleet St  
London EC4A 2AL  
Ph: 353-1040; Tlx: 267163

## Adelaide

**Admedia Group**  
24 Kensington Rd  
Rose Park SA 5067  
Ph: 332-8144; Tlx AA82182

## Japan

**Genzo Uchida**  
Bancho Media Services  
15 Sanyocho  
Shinjuku-Ku  
Tokyo 160  
Ph: 359-8866  
Cable: Elbanchorito

## Brisbane

**Geoff Horne Agencies**  
60 Montanus Drive  
Bellbowrie QLD 4070  
Ph: 202-6229

## USA

**Peter Samuel**  
Australian Consolidated Press  
444 Madison Avenue  
New York NY 10022  
Ph: 751-3383; Tlx: 620892

## Perth

**Aubrey Barker**  
133 St Georges Terrace  
Perth WA 6000  
Ph: 322-3184; Tlx: AA93810

Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St, Rushcutters Bay, NSW 2011. It is printed (in 1980) by Wilke & Co, Browns Rd, Clayton, Victoria and distributed by Gordon and Gotch. Recommended retail price only.

## Reader Enquiries

**By Mail:** There is no charge for replies but a foolscap-size stamped addressed envelope **must** be enclosed. Queries relating to projects can **only** be answered if related to the item as published. We cannot advise on modifications to projects, other than errata or addenda, nor if a project has been modified or if components are otherwise than specified. We try to answer letters as soon as possible. Difficult questions may take time to answer.

**By phone:** We can only answer readers' technical enquiries by telephone **after 4.30 pm**. In enquiring by telephone about back issues or photostats, please ask for the "Subscriptions Department". **33-4282**

## ORDER FORM

I enclose \$ . . . . . for (tick appropriate box/es):

NAME . . . . .

ADDRESS . . . . .

. . . . . POSTCODE . . . . .

- ☐ Subscriptions \$21.50 per year within Australia \$ . . . . .  
\$27.00 overseas (surface mail) \$ . . . . .  
Airmail rates on application.
- ☐ Back issues (\$2.50 from April 1977 on)
- ☐ or photocopies (\$2.50 per article per issue)

Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .  
Project No. . . . . Month . . . . . Year . . . . . \$ . . . . .

\* Please attach a list if more than four required.

- ☐ Binders No. . . . . @ \$6.10 each in NSW \$ . . . . .  
No. . . . . @ \$7.50 each other states \$ . . . . .

## ALL PRICES INCLUDE POSTAGE

Send orders to: **ETI, 4th Floor, 15 Boundary St,  
RUSHCUTTERS BAY NSW 2011 Phone: (02)33-4282**

DREGS' junior correspondent likes to go dancing in clubs where the bands play fast and loud, and he likes to be right in front of the stage where the sound levels are only just below the threshold of pain. In these conditions it's very difficult to hold any kind of conversation — you have to shout at the top of your voice and repeat yourself several times to convey the simplest message.

He was more or less resigned to this until the other day when he caught

sight of our September 1978 issue, whose cover features the LED pendant project. This was intended simply as a novelty item, but our little rager realised its possibilities as a communications device. The level of ambient light in the average rock club is quite low enough to allow a LED display to stand out clearly and a small keypad mounted on the wrist would allow simple messages to be conveyed.

Eventually our minion intends to produce a sophisticated version with

an eight character display on which real words can be shown, but for the time being he's making a number of simple one-digit versions. The idea is to use some kind of code, along the lines of the ten-codes used by CBers. Common questions and answers could be assigned a conventional number code, so for example to convey the message, "Hi, you were here last night weren't you?", you might flash 6 followed by 8 and "This band are boring, let's go back to my place" might be indicated by a 4 followed by a 9.

Coding is still a bit of a problem because the code has to be understood by half-wits and those who may be a little 'off the planet' (Dregs' junior won't say in which category he belongs), but the range of conversation in rock clubs is never very wide and most people should have no difficulty memorising the codes for the few phrases they habitually use.

## The Great Dregs Awful Puns Competition

Well, well...since kicking off the competition on this page in the July issue we've seen some great examples of awful puns! First off the mark was H. Meallin, VK3ATK, of South Oakleigh in Victoria, with "Your sample pun Hertz". Maybe so, maybe so but Managing Editor, Collyn Rivers, didn't agree! Then Trevor Bartlett of Nurioopta in South Australia came up with several. His best/worst was: "Are integrated circuits used in Antarctica known as IC(e) chips?". Hmm. One reader had a very obscure story about dynamic ROMs but the one that takes the prize in this first round came from 17 year old Evan Troup of Frankston in Victoria. It reads: "The reason that no one will ever be able to program a computer to compose music is that their Bach is worse than their byte"! Your copy of Computers & Computing is on its way, Evan.

Right-oh folks, keep those awful entries coming. Send to: The Great Dregs Awful Puns Competition, ETI Magazine, 3rd floor, 15 Boundary St, Rushcutters Bay NSW 2011.



# REAL HI-FI

## AND IT'S ALL IN OUR COLOUR CATALOGUE

The truth is, JVC have always produced real hi-fi components and we believe this current range represents JVC's finest range ever. Here are some real innovations and performance features to whet your appetite:— Quartz locked turntables with uncanny accuracy; Receivers/Amplifiers, some with built-in SEA Graphic Equaliser and DC, class A/B amplification; Cassette deck with JVC automatic computerised tape tuning; Computer designed

speaker systems; Separate but matching JVC components designed to compliment one another, perfectly. And all this real hi-fi know-how is yours ...merely for the asking.



**If you think they look different,  
wait till you've heard them!**

### FREE OFFER COLOUR HI-FI CATALOGUE

Just fill out this coupon and we'll fill you in on what's available and new in terms of JVC hi-fi entertainment...and it's all FREE!

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_ Postcode \_\_\_\_\_

WT1323/ETI/79

I am especially interested in...

- ☐ Cassette Decks
- ☐ Matching Systems ☐ Amplifiers
- ☐ Speakers
- ☐ Turntables
- ☐ Receivers

Just address your  
envelope to...  
JVC Hi-Fi Advisory  
Service,  
Post Office Box 307,  
North Ryde,  
N.S.W. 2113

# JVC

**the right choice**

# The revolutionary Honeycomb Disc Speaker System!




Another Technics  
'first' that brings...

*Sounds Alive*



Cross Sectional View of the SB-10

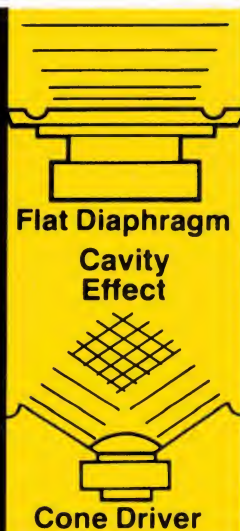

The most obvious difference... between the new Technics honeycomb disc speaker system and conventional speaker systems is that the speaker units are flat instead of conical. This flat sound radiating surface at last puts an end to all of the distortions inherent in the traditional cone-shaped design. Cone shaped drivers suffer from something called the 'cavity effect' which causes peaks and dips in the upper end of the driver's frequency range.

But cone shaped drivers do have their advantages, namely a combination of low mass and high rigidity which contributes to pisonic motion. In designing this new Technics honeycomb speaker system we were faced with the problem of retaining or improving upon the cone-shaped speaker's low-mass, high-rigidity characteristics while developing a flat speaker surface. We found the answer in the 'axially symmetric honeycomb diaphragm.' It is well known that honeycomb structures are very light and strong, which is why they are extensively used in aircraft construction. In spite of the honeycomb's low mass, it is very rigid and difficult to bend.

## Technics